

Lecture 14


DC Motors and driving them

Agenda

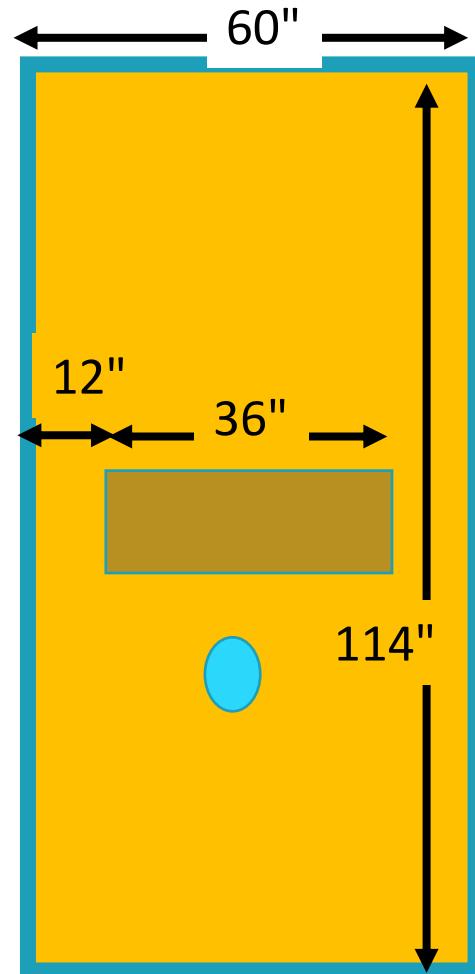- 00. Review Lab 4: Mobility
- 01. MOSFETS/BJT recap
- 02. DC Motors + Solenoids
- 03. Driving DC motors

Lab 4

- Circle the center wall 3 times.
- 1st trial remote controlled from home through the internet
 - There will be lag in control
- 2nd trial autonomous mode
- Drop off your mobile base at GM lab.
 - Your TA/coach is your pit crew.



Lab 4 Constraints

- You may use Teensy or ESP32 for controlling vehicle
 - You must use ESP32 for WiFi interface. (note using one processor is easier than two).
 - Your vehicle can be up to 12" x 12" x 12"
-
- You may use any motor or servo you wish.
 - You are encouraged to purchase items for this lab from your allocation

Purchasing Allocation

- Each student may purchase upto **\$75** worth of items from the following:
- Digikey.com: Electronics
- Mcmaster.com: Mechanical
- Adafruit: DIY electronics
- Sparkfun: DIY electronics
- Polulu: Motors, hubs
- Amazon.com: Everything



Purchasing Allocation



- You can have items shipped to your home.
- Track the costs of things you purchase (you will submit your purchases in the final report)
 - Include cost of item
 - Ignore shipping costs in your cost estimation
- Details in *Purchasing for MEAM510.pdf* on Canvas files
 - Fill out purchase request form... Include you phone# etc...
 - Send purchase request to yim@seas.upenn.edu
- Receiving parts may take 1 to 2 weeks (sometimes longer).
 - Purchase takes 3 business days to place order (currently)
 - Shipping takes 2-5 days to deliver.

Tentative Lab 4 Schedule

	Sun	Mon	Tues	Wed	Thurs	Fri	Sat
March	7	Today Motor Control	[4.1 motor drivers]	Spring break	Spring break	Lecture ESP32	
	14	Lab 4.1 due Design Review Parts submitted	[4.2 wifi connectivity with ESP32]	Parts returned (start)		Parts returned (latest)	
	21	[4.2a Integration and assembly]		Lab 4.2 due Wifi Demo	[RACES]	[RACES]	
	28	[4.3a Integration and assembly]		Lab 4.3 due Auto Control	[AUTO RACES]	[AUTO RACES]	

Wiring robustness...

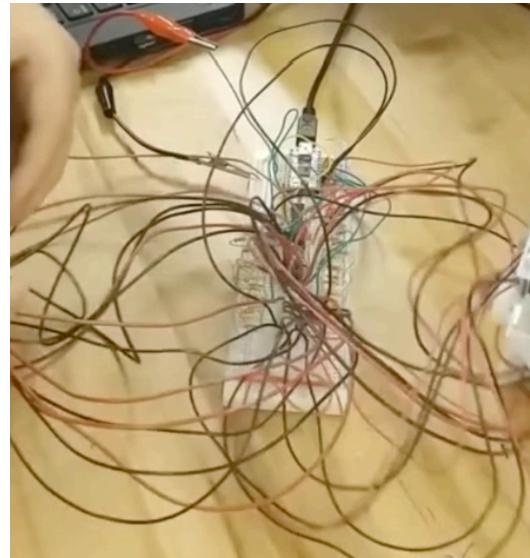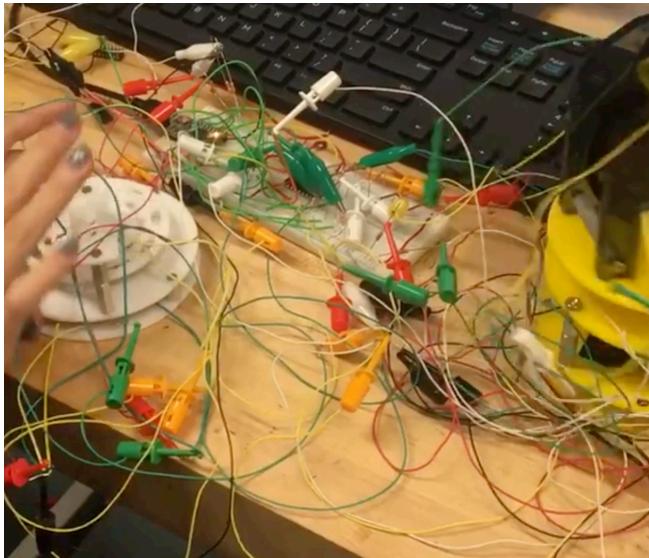- Did you experience moving a device and have it stop working?
- What can we do about this?




Connectors and cabling

- Most electromechanical failures occur at connections/connectors.
- If you need to have long wires, what can we do?



Motor leads can break...

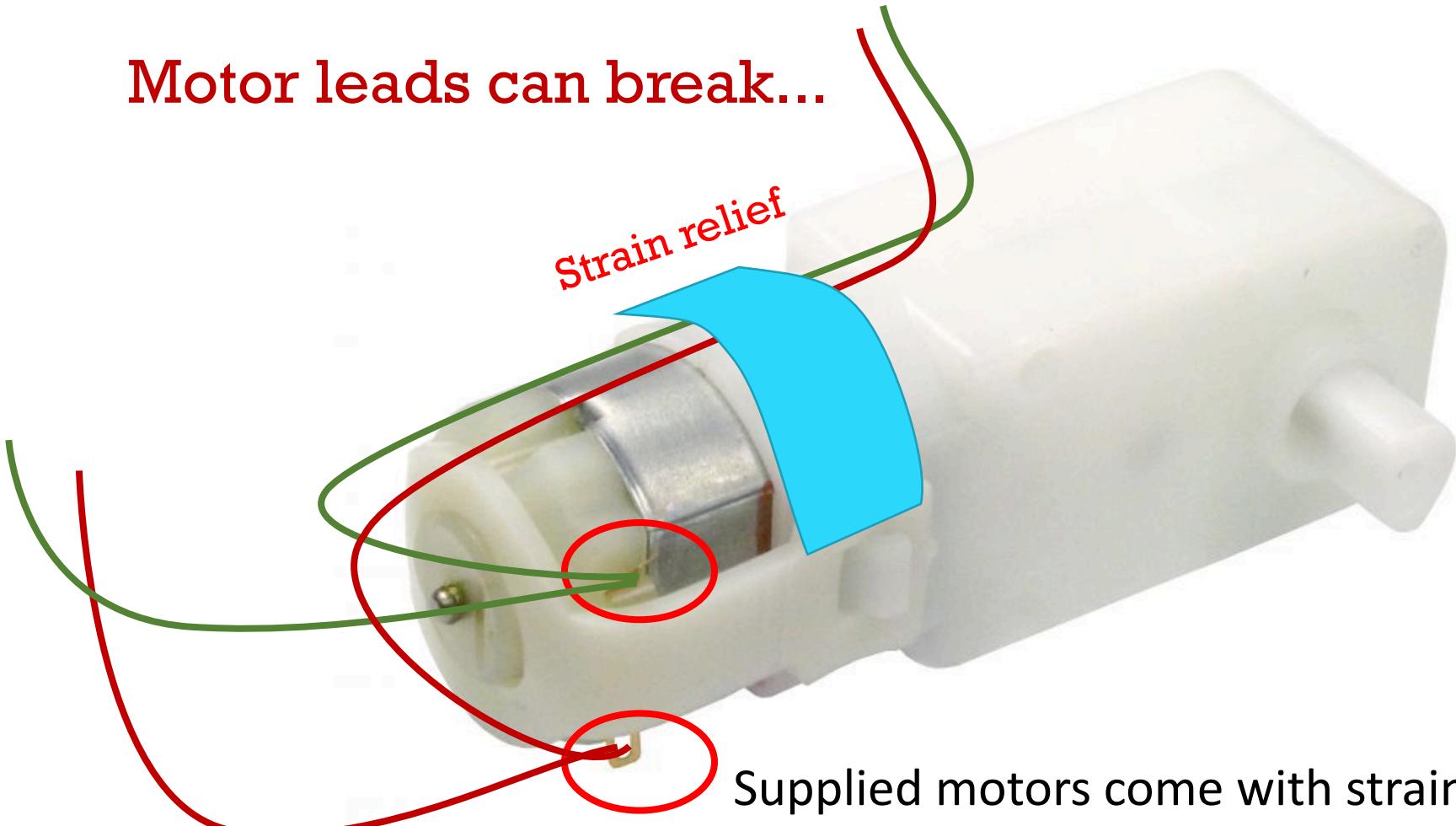

Supplied motors come with strain relief
But may not be good enough

01

MOSFET/BJT recap



Choosing MOSFET drivers (for this class)

Output Specifications

- $R_{DS(ON)}$ sets current capability (assuming you can heatsink device)
 - Look at continuous drain current

Driving Specifications

- V_{GS} Voltage required to turn on.
 - Older power MOSFETS require voltages larger than micro's normally supply $> 5V$ (not compatible)
- Q_G Total Gate Charge, - in general – not for this class.

BJT vs MOSFET

Driving

- BJT's are driven by current in base
- BJT's require $V_{be} \sim 0.7V$ to start conducting
- MOSFETS require $V_{GS(th)}$ to start (varies: 1-8V)
- MOSFETS are driven by voltage, V_{gs}

Outputs

- BJT limited by V_{ce}
- MOSFETS limited by R_{ds_on}
- MOSFETS can combine in parallel

Costs


- BJT's are cheaper for switching small currents e.g. $I_C \sim 200mA$
- MOSFETS are smaller and cheaper more efficient for switching larger currents e.g. $I_D > \sim 5A$

Summary

- BJT are current controlled
- MOSFETs are voltage controlled
- MOSFETs are the trend for large current control
- Be sure to understand V_{GS} characteristics of MOSFETs for your application


02

DC Motors + solenoid

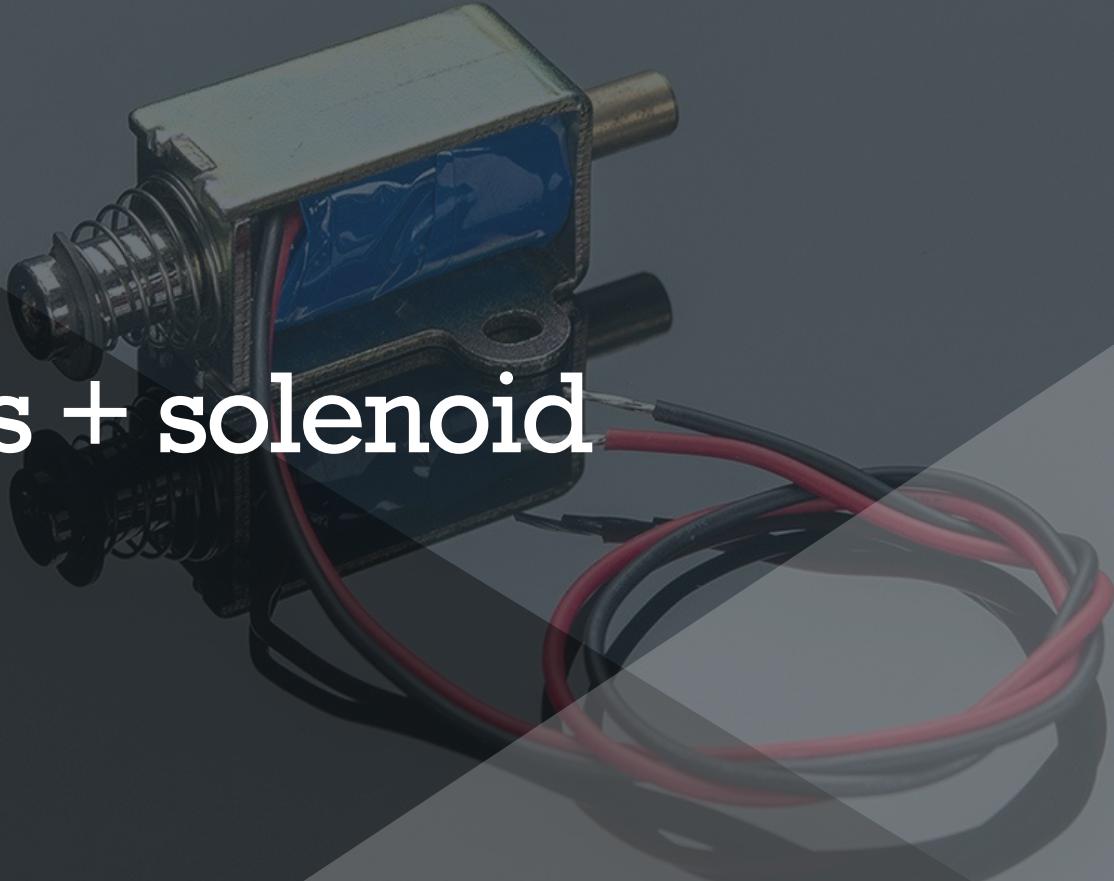


What is a solenoid?

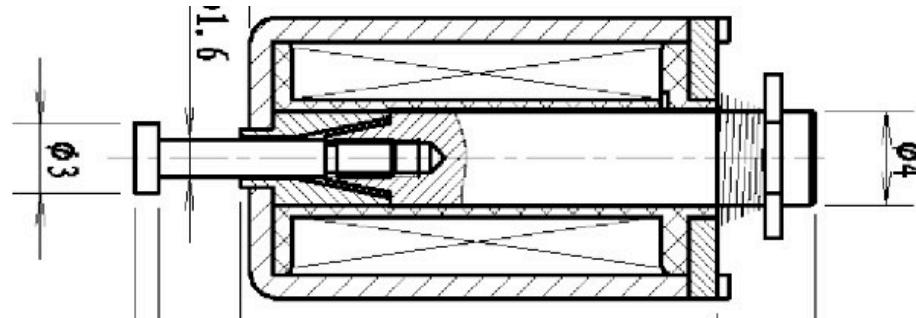- Magnetic plunger surrounded by a coil
- The plunger can move in or out to push against something.
- Moves quickly



Mini Push-Pull Solenoid (in GM lab)

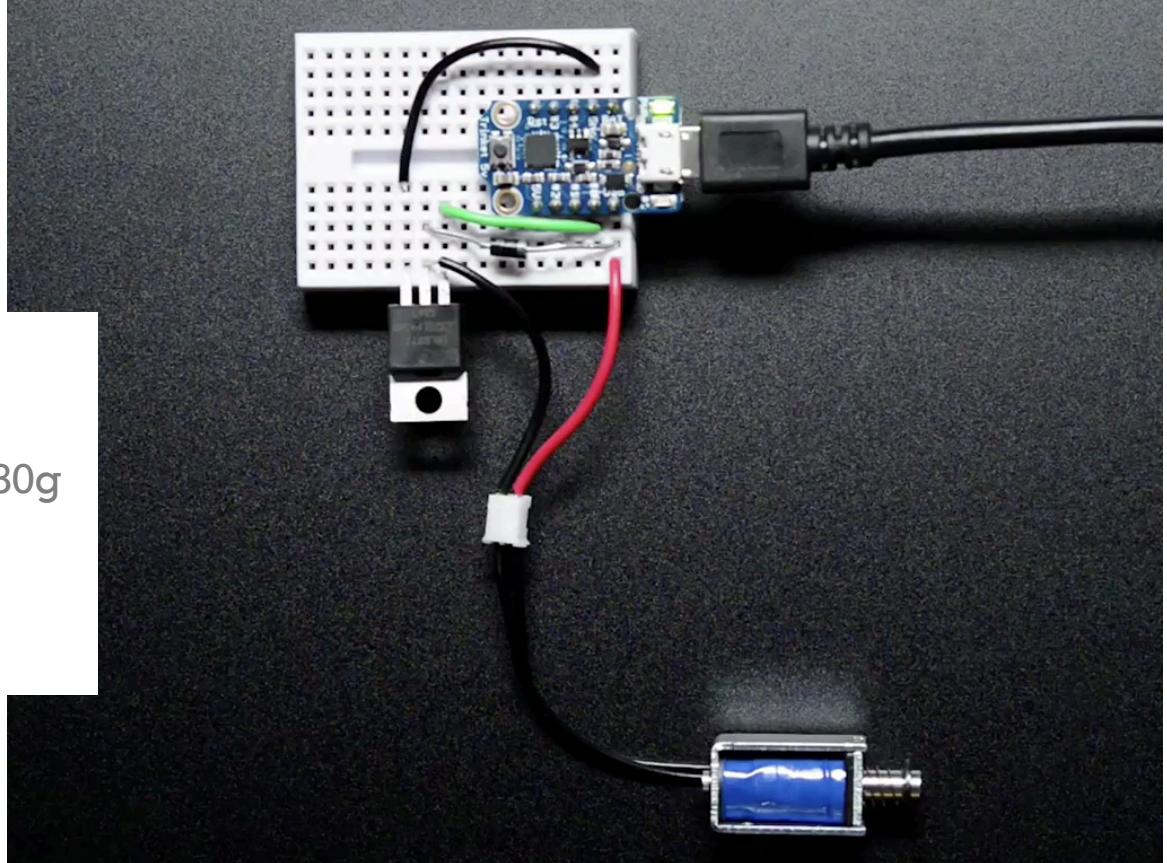- Rated Voltage: 5V
- Current (at DC 5V): 1.1A
- Throw (at DC 5V): 3mm / 80g



MEAM516 2019 – Solenoid driven music




Andrew and his team

<https://www.youtube.com/watch?v=jNhjGteu8xc&feature=youtu.be>



Shaun, Allie and their team

Ideal Electrical Model of a DC motor

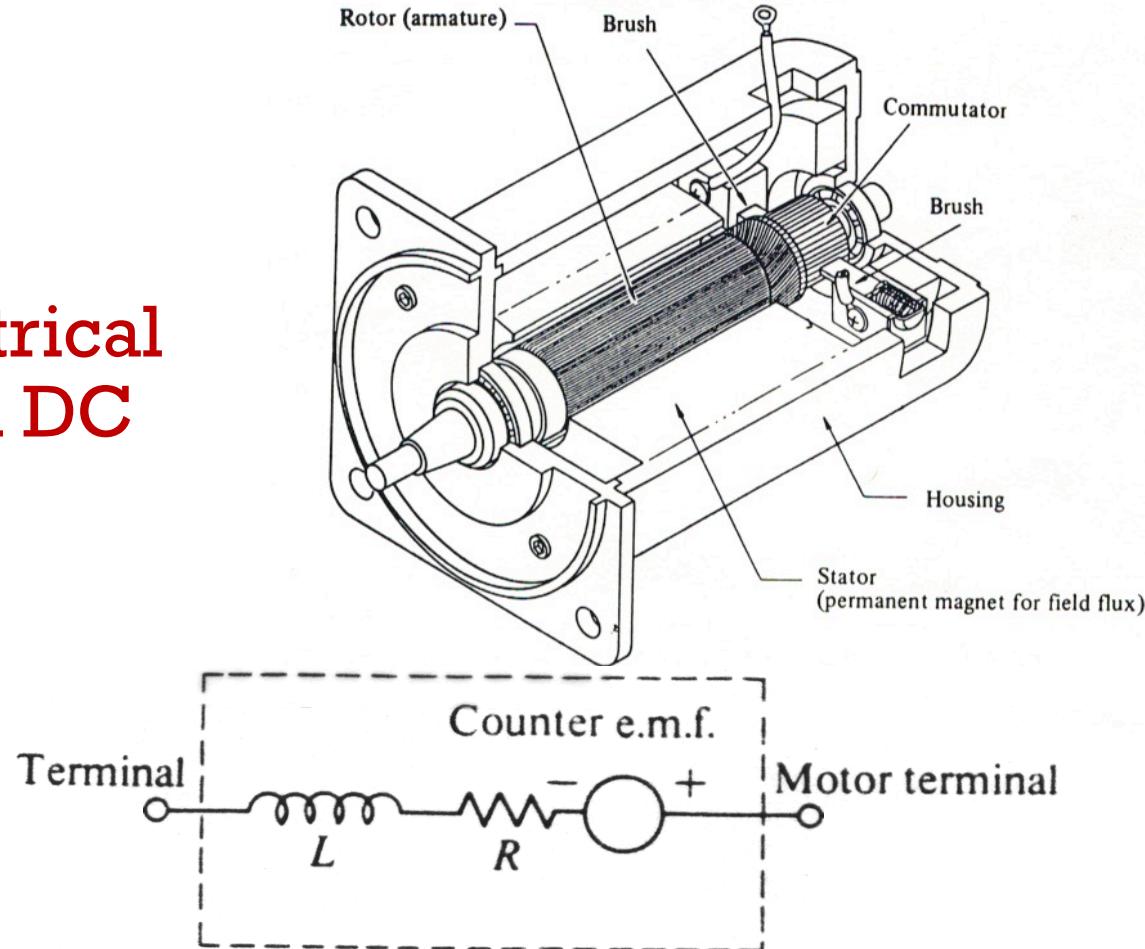


Actuators: Important properties?

Inputs:


- Voltage
- Current

Outputs:

- Speed
- Force/Torque
- Range of motion

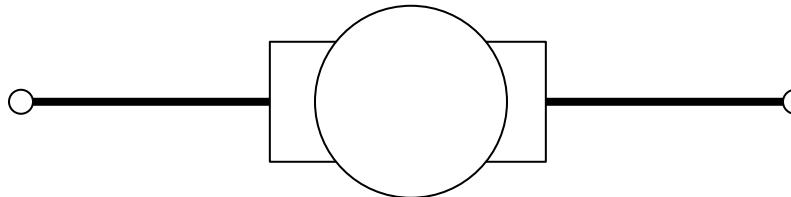

Motor

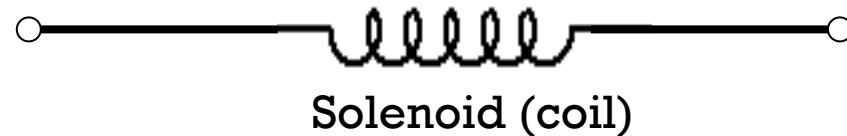


Solenoid (coil)

Basic Physics: Lorenz Force

$$\vec{F} = i\vec{l} \times \vec{B}$$

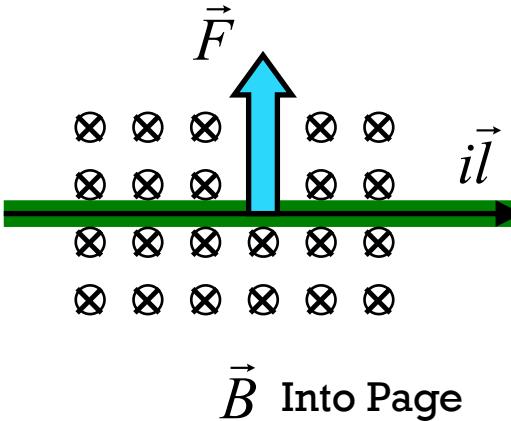Force on a Wire Carrying Current
Through a Magnetic Field




$$\tau = K_T i$$

For some motor with
torque constant K_T

Basic Physics: Faraday's Law

$$\mathcal{E} = -\frac{d}{dt} \int_A \vec{B} \cdot d\vec{A}$$

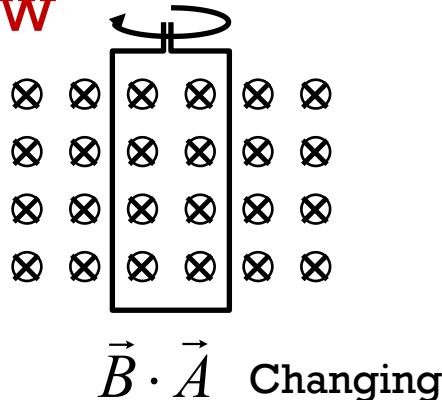Electromotive Force (Voltage)
Generated by Rate of Change of
Magnetic Flux Enclosed by a Coil





$$V = K_E \omega$$

For some motor with
speed constant K_E

Ideal Electrical Model of a DC motor (alone)

Q1: Plot Speed vs Torque

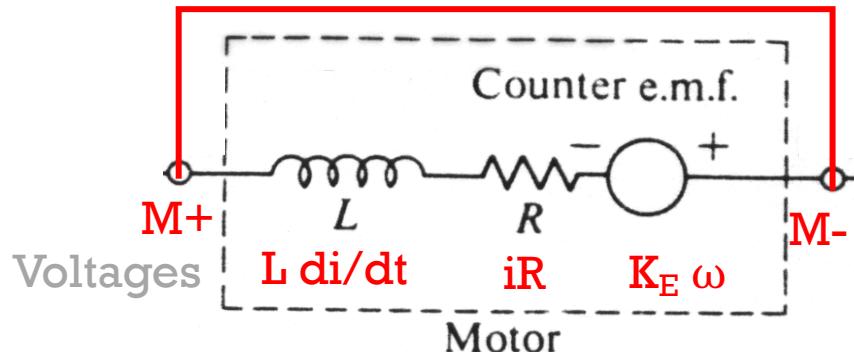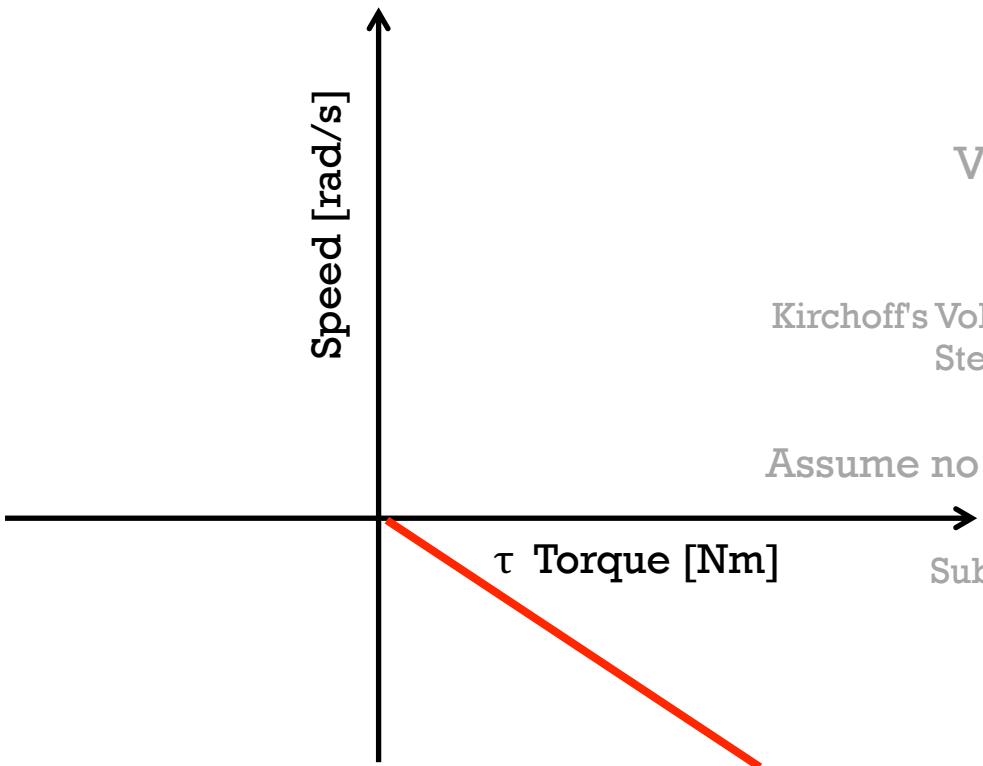

Kirchoff's Voltage Law
Steady state

Assume no friction

Substitution
Algebra

$$0 = L \frac{di}{dt} + iR + K_E \omega$$

$$0 = 0 + iR + K_E \omega$$

$$\tau = K_T i$$



$$0 = 0 + \tau R/K_T + K_E \omega$$

$$\omega = -\tau \underbrace{R/(K_T K_E)}_{\text{Motor Constants}}$$

Motor Constants

Ideal Electrical Model of a DC motor w/battery

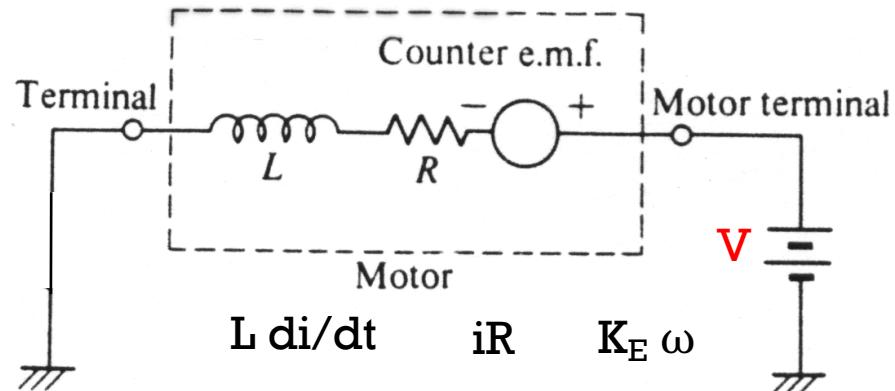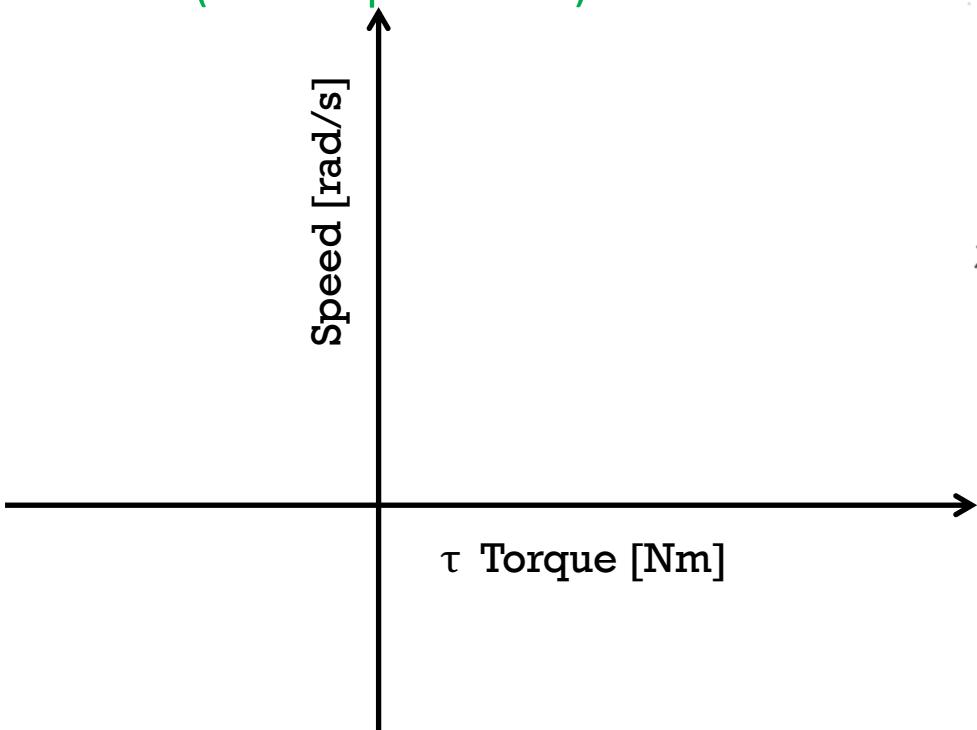Q2: Plot Speed vs Torque
(which quadrant?)



$$V = L \frac{di}{dt} + iR + K_E \omega$$

$$V = 0 + iR + K_E \omega$$


$$\tau = K_T i$$

$$V = 0 + \tau R / K_T + K_E \omega$$


$$\omega = -\tau \underbrace{R / (K_T K_E)}_{\text{Motor Constant}} + V / K_E$$

Motor Constant

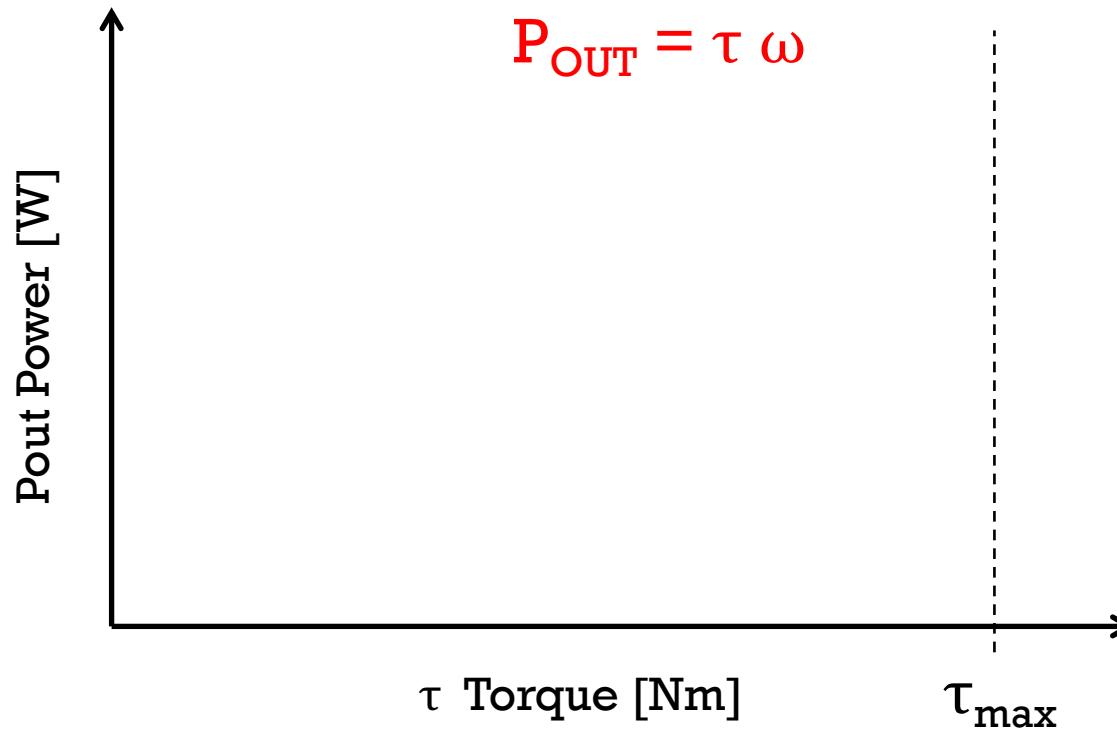
Q3: Plot (Mechanical) Output Power vs Torque (Does the curve hit the origin?)



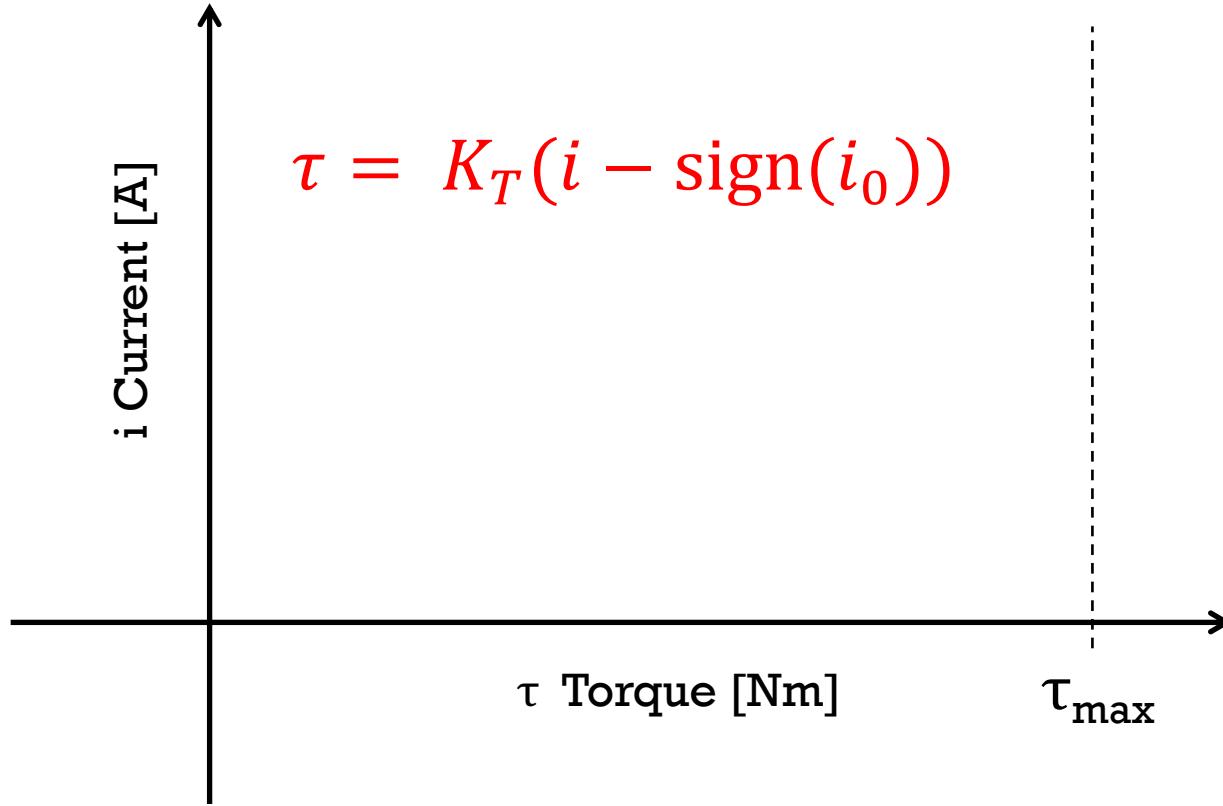
Q4: Plot Current vs Torque (Does the curve hit the origin?)



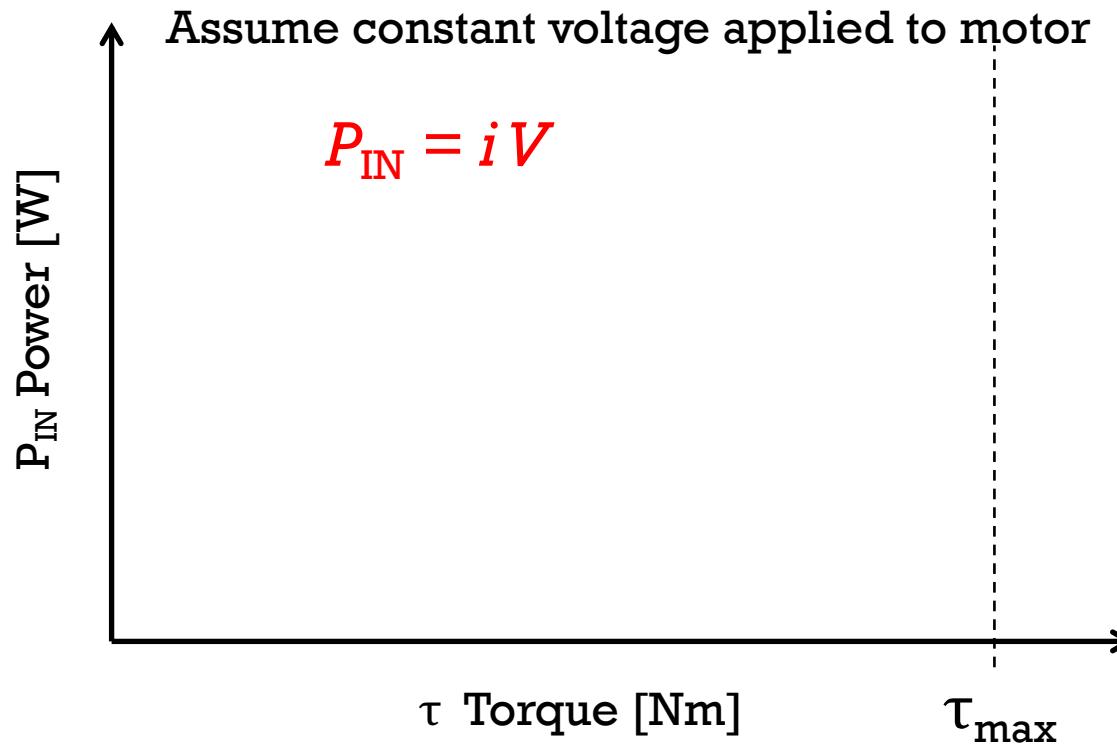
Q5: Plot (Electrical) Input Power vs Torque (Does the curve hit the origin?)



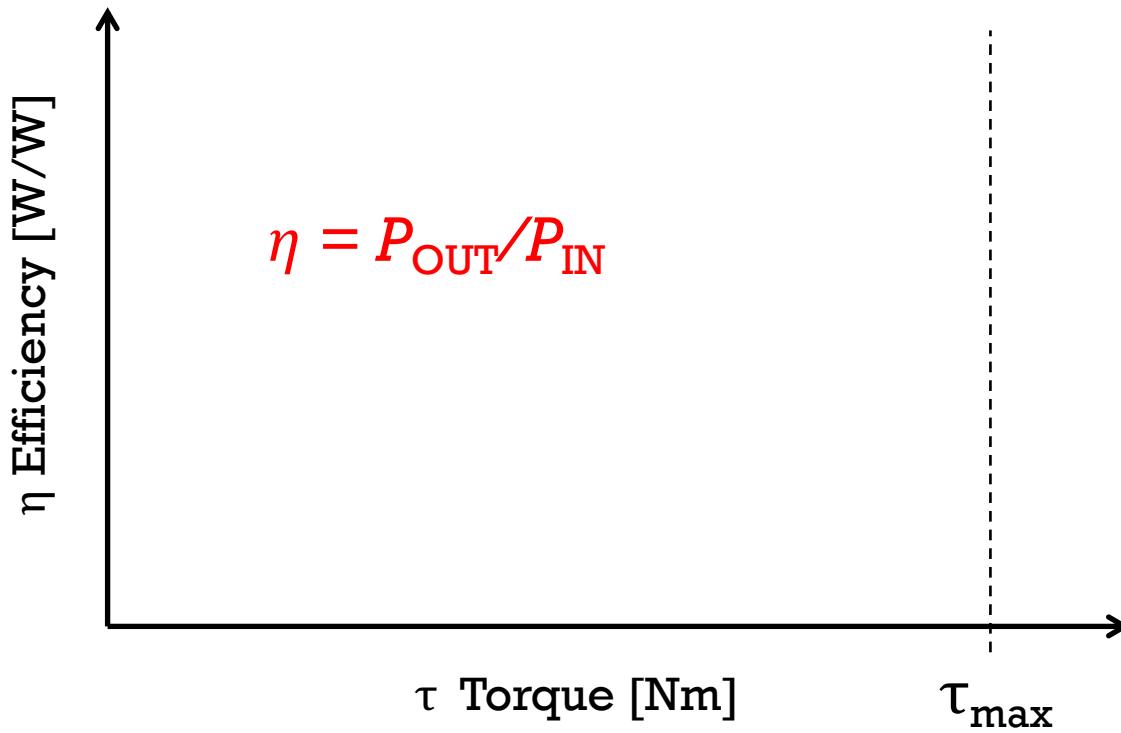Q6: Plot Power Efficiency vs Torque (where is the peak efficiency?)



Torque vs Everything (for given V)

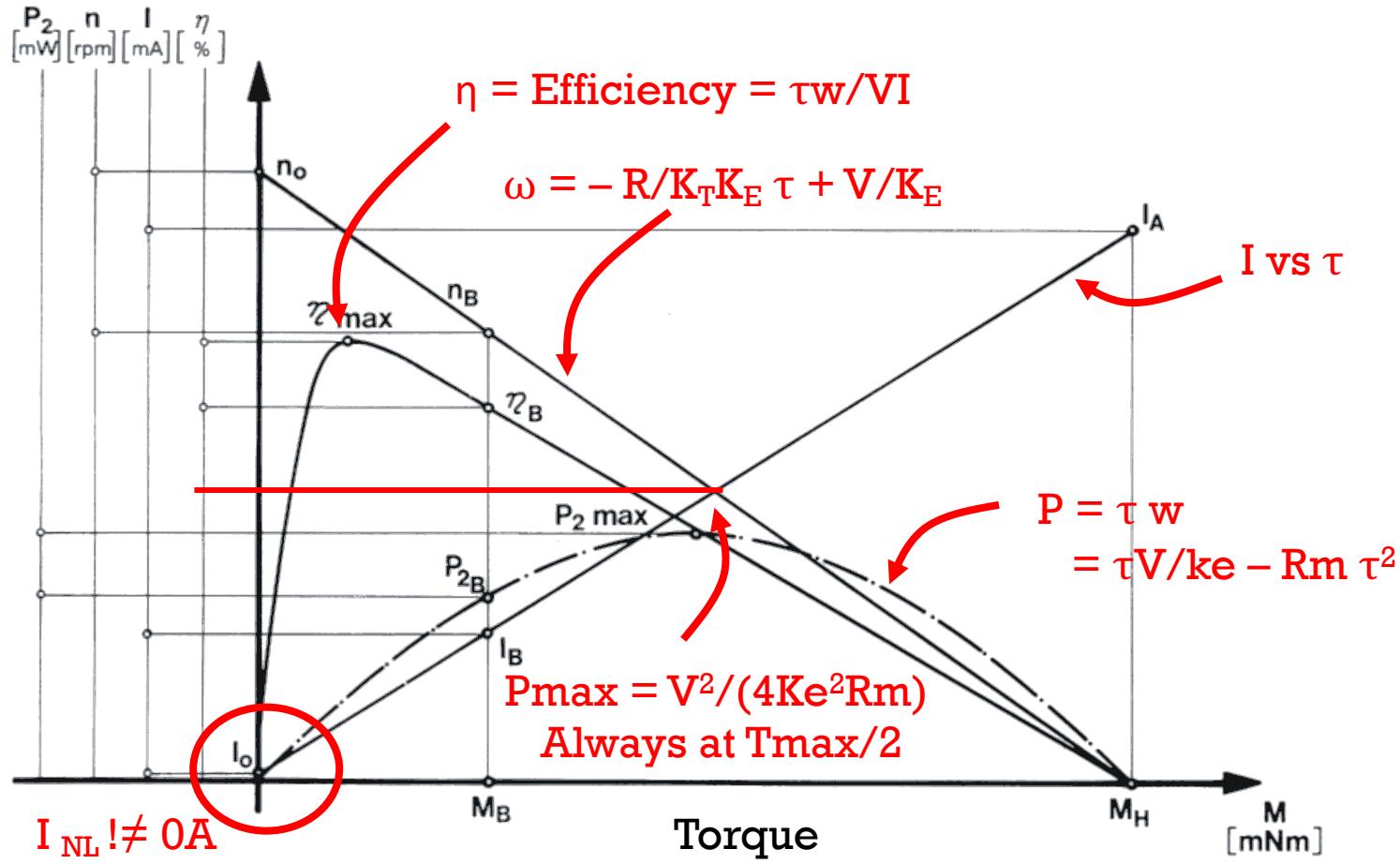

Choosing a motor

- Voltage specifications
 - indicates maximum voltage
 - doesn't say anything about motor capability
- Wattage
 - indicates maximum power
- Motor constants
 - indicate slope of torque/speed curve
- Stall torque
- Stall current
- No load speed

Pololu part #
1516
1124
2368
2367
2365
2364
992



Some terms and symbols

- K_T Torque constant [Nm/A], apply A get τ
- K_V Velocity constant [rad/s /V], apply V get ω
- $K_B = K_E$ Back EMF constant [V /Rad/s], apply ω get V

Note:

$K_T = K_E = 1/K_V$ when using SI units Nm/A :V / rad/s

$$\omega = - \frac{\tau}{K_T K_E} + \frac{V}{K_E}$$

DC Motor Specs

(Maxon Motor catalog)


Labeled by power rating

	Winding number	930	933	934	94	7	938	945
Motor Data								
1 Assigned power rating	W	6.0	6.0	6.0	6.0	6.0	6.0	6.0
2 Nominal voltage	Volt	3.0	7.2	9.0	12.0	12.0	12.0	15.0
3 No load speed	rpm	5080	9270	9460	10700	8120	7770	8460
4 Stall torque	mNm	20.9	42.5	45.7	51.7	2.7	35.1	44.4
5 Speed/torque gradient	rpm/mNm	260	225	213	211	194	227	194
6 No load current	mA	114	101	83	73	50	47	42
7 Starting current	mA	3960	5910	5160	4920	3090	2440	2680
8 Terminal resistance	Ohm	0.757	1.22	1.74	2.11	2.88	1.82	5.60
9 Max. permissible speed	rpm	11000	11000	10000	11000	10000	11000	11000
10 Max. continuous current	mA	1500	1500	1440	1220	312	300	300
11 Max. continuous torque	mNm	7.92	10.8	12.7	12.8	13.4	12.4	13.4
12 Max. power output at nominal voltage	mW	2460	9620	10800	13900	8770	6920	9590
13 Max. efficiency	%	64	73	75	76	75	74	76
14 Torque constant	mNm/A	5.28	7.19	8.85	10.5	13.8	14.4	16.6
15 Speed constant	rpm/V	1810	1330	1080	909	691	664	576
16 Mechanical time constant	ms	29	22	20	19	18	18	18
17 Rotor inertia	gcm ²	10.8	9.23	9.07	8.68	9.07	7.76	8.84
18 Terminal inductance	mH	0.07	0.12	0.18	0.26	0.45	0.48	0.64
19 Thermal resistance housing-ambient	K/W	17	17	17	17	17	17	17
20 Thermal resistance rotor-housing	K/W	2.4	2.4	2.4	2.4	2.4	2.4	2.4
21 Thermal time constant winding	s	7	6	6	6	5	6	6

Stall current?


Bearing limitation

Motor Spec Sheet

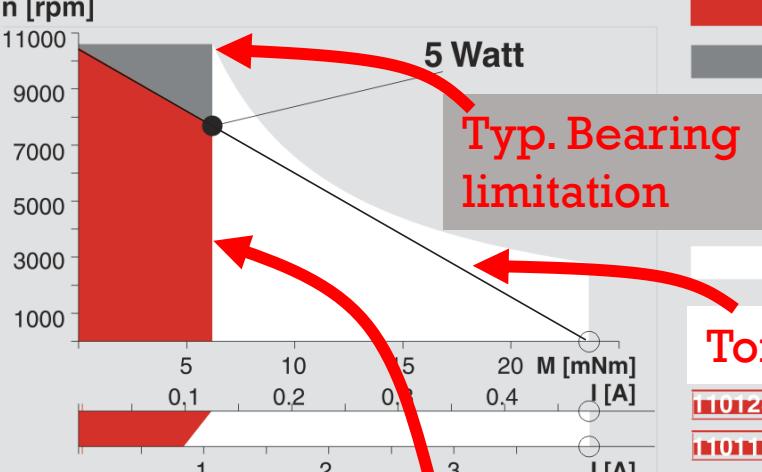Operating Ranges	Comments	Example from page 113
 <p>The graph plots speed (n) in rpm against torque (M) in mNm and current (I) in A. The red shaded area represents the recommended operating range. The grey shaded area represents continuous operation. The outer boundaries of these areas are labeled 'Typ. Bearing limitation'. The inner boundary is labeled 'Typ. Thermal limitation'. A point on the curve is marked with a black dot and labeled '5 Watt'.</p> <p>Typ. Thermal limitation</p> <p>Speed (n), torque (M), current (I): The outer edges of the values depicted represent limits for continuous and short term motor operation. Values listed in the tables (lines 3, 4, 6, 7, 12 and 13) are valid for operation at nominal voltage (line 2). These are therefore values which are only reached when operating the motor at higher voltages</p>	<p>Recommended operating range</p> <p>Continuous operation In observation of above listed thermal resistances (lines 19 and 20) the maximum permissible rotor temperature will be reached during continuous operation at 25°C ambient. = Thermal limit</p> <p>Short term operation The motor may be briefly overloaded (recurring).</p> <p>Torque Speed Curve</p> <p>110128 Motor with high resistance winding (Line 8) 110117 Motor with low resistance winding (Line 8)</p> <ul style="list-style-type: none"> ● Assigned Power Rating P_{2T} (W) (Line 1) ○ Starting current I_A at nominal voltage (Line 7) as well as related stall torque <p>M_H (mNm) (Line 4) $I_A = \frac{U}{R} \cdot 10^3$ (mA)</p> <p>110128 Winding number with the related current curve at the appropriate torque.</p>	

Motor in your kit

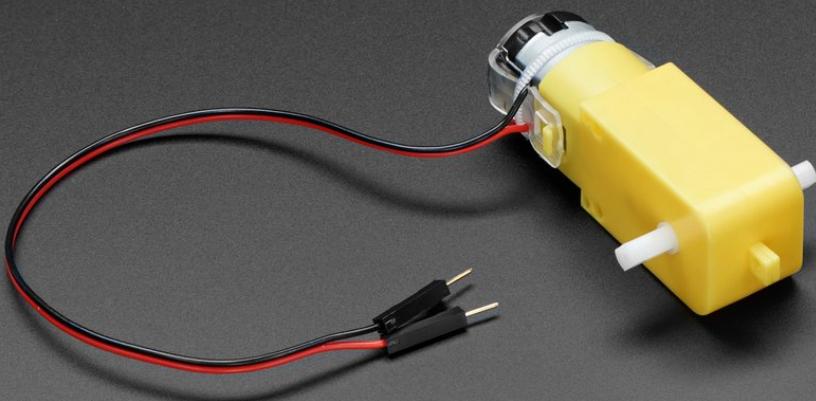
- <https://www.adafruit.com/product/3777>





- Rated Voltage: 3~6V
- Continuous No-Load Current: 150mA
- Min. Operating Speed (3V): 90 RPM
- Min. Operating Speed (6V): 200 RPM
- Stall Torque (3V): 0.4kg.cm
- Stall Torque (6V): 0.8kg.cm

Supplied DC Motor (x2)

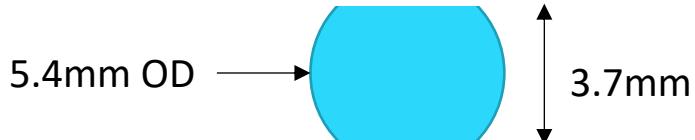- Mounting
 - 3mm x3 mounting holes
 - Using these holes is encouraged
- Shaft mount – has 2 flats
 - Can laser cut this shape hole



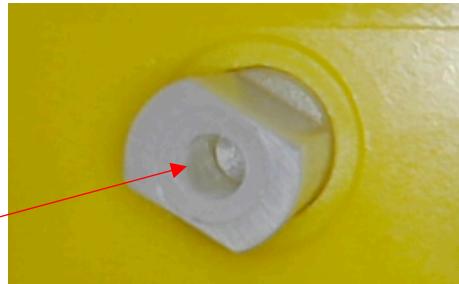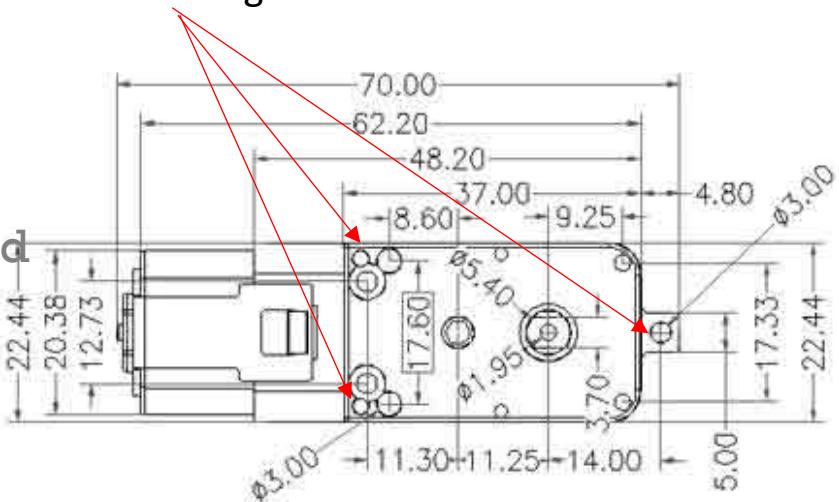
<https://www.adafruit.com/product/3777>
Mounting holes



Smooth hole
Can use #2 or #3 wood screw

03


Driving DC Motors

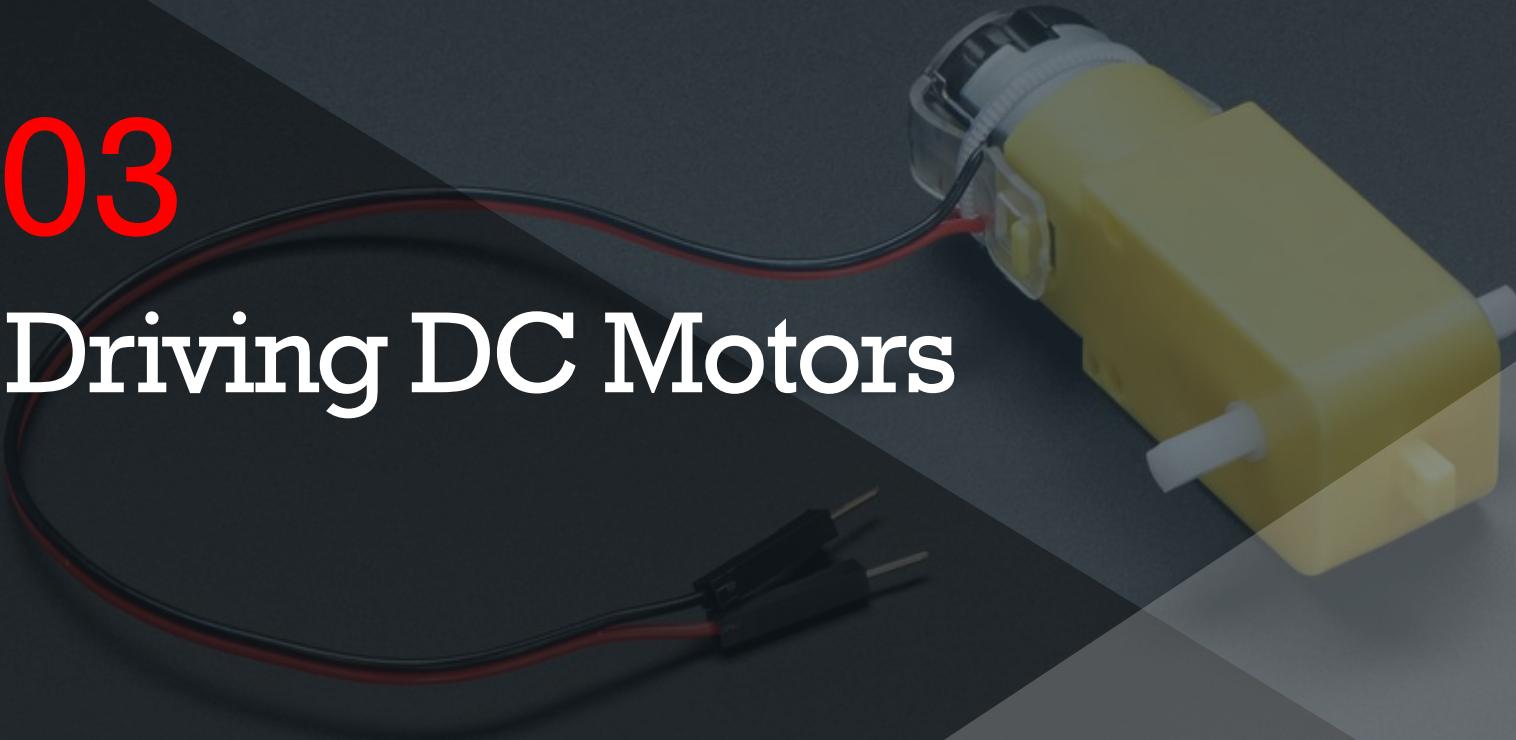

Driving a motor

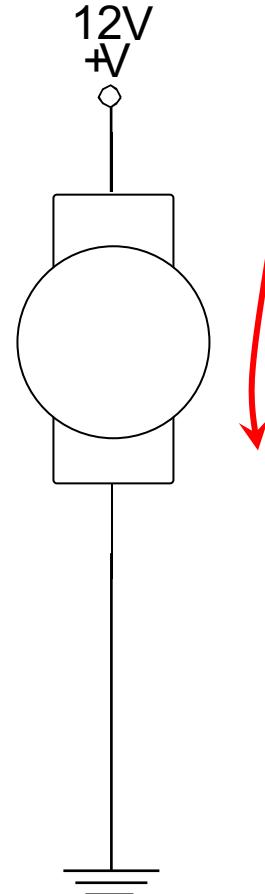Q7: To calculate how much current will flow:

- In general, what does it depend on?
- Worst case, what does it depend on?
- Can my driver (e.g. transistor) handle that much current?



Motors may require large currents

- The yellow motors in your kit ~1.5 Amps @ 5V stall
- Motors in typ. MEAM510: 1 to 6 Amps @ stall
- Motors in typ. quadrotor 5 to 30 Amps @ stall
- Motors in typ. electric car 100's of Amps


Pololu part #
1516
1124
2368
2367
2365
2364
992



GM Lab Options for Driving Large Currents

- ULN2003 Seven Darlington Array ~0.5A
- TIP31C NPN Transistor 3A
- TIP102 NPN Darlington 8A
- IRLB8721 N-channel MOSFET 25A
- IRF9520 P-Channel MOSFET ~6.8A
- FQP8P10 P-Channel MOSFET 4A
- IRF630 N-Channel MOSFET 5.9A
- SN754410 H-bridge driver 1A


Switching directions

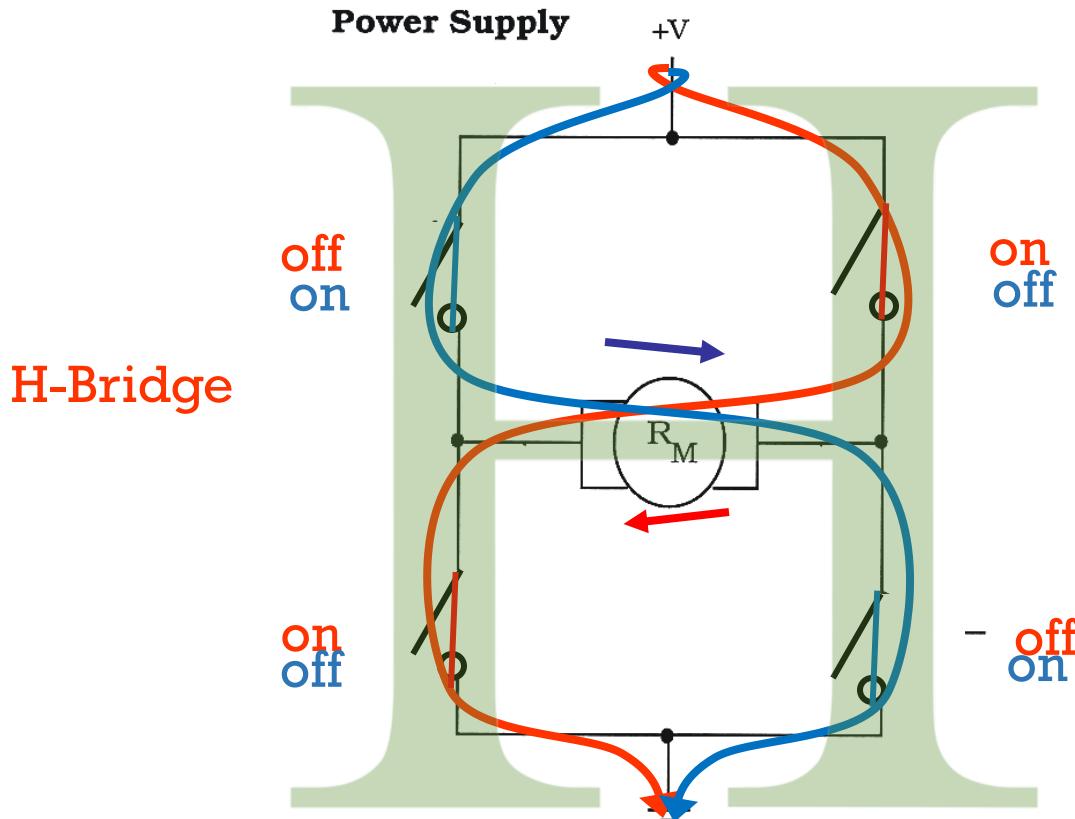


Other Switch Options

No power from supply, but
Current flows from back EMF
Acts as a brake

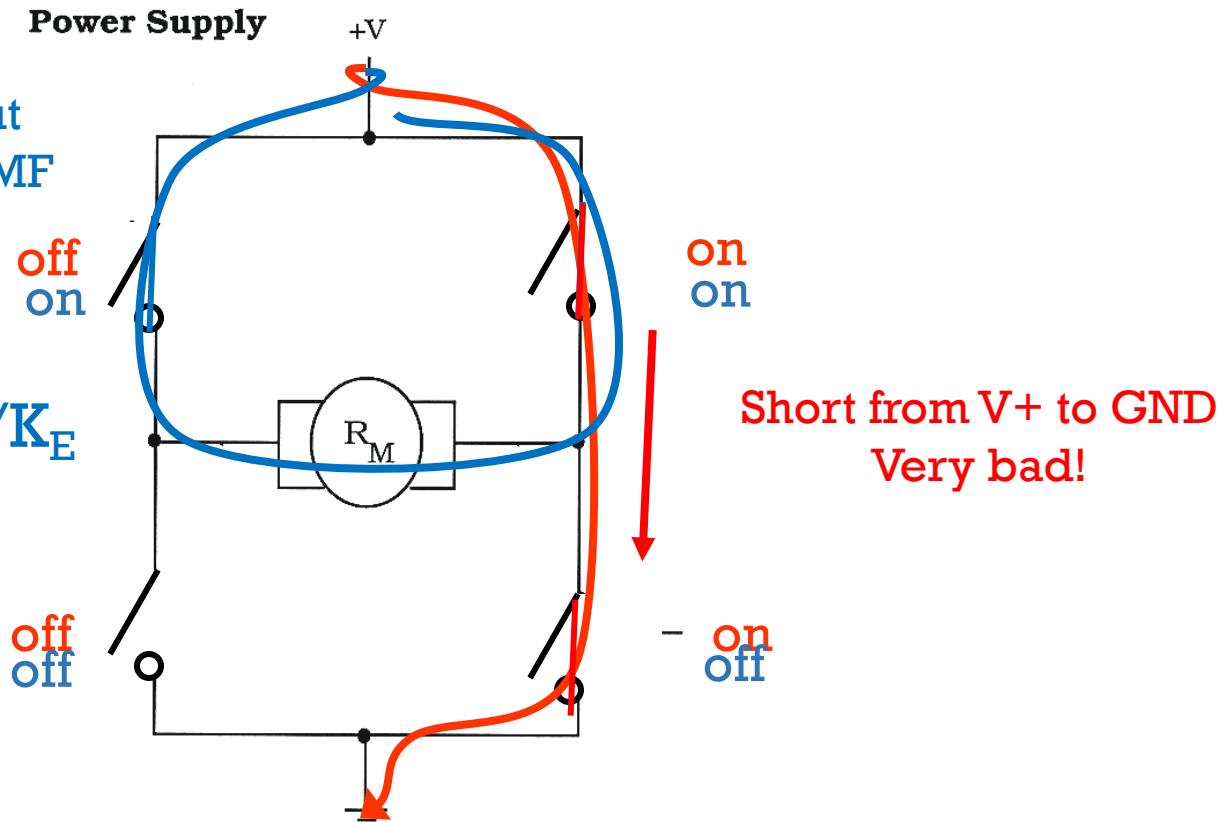
$$\omega = - \frac{R}{K_T K_E} \tau + \frac{V}{K_E}$$
$$\tau = -\omega \frac{K_T K_E}{R}$$



Half H-Bridge

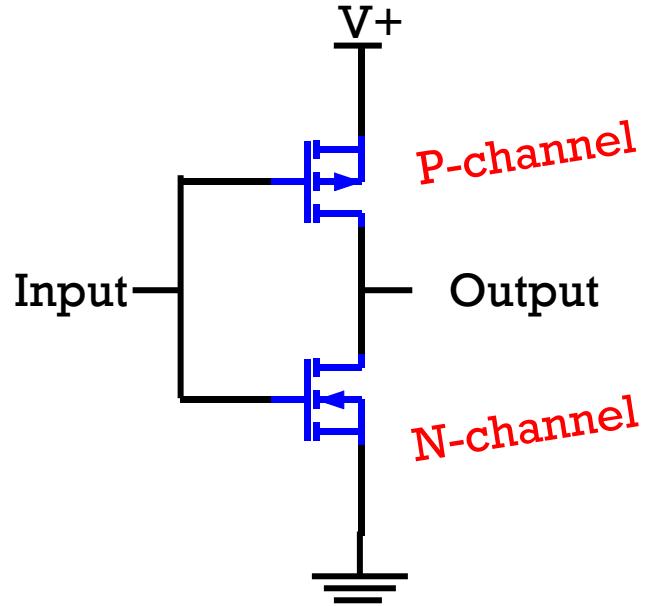

Rough schematic

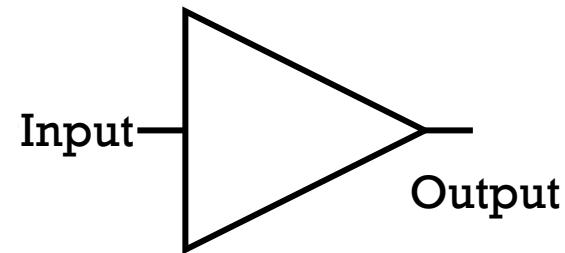



Symbol

Recall


Effect of Large Inductance

Circuit simulation package

$$v(t) = L \frac{di(t)}{dt}$$

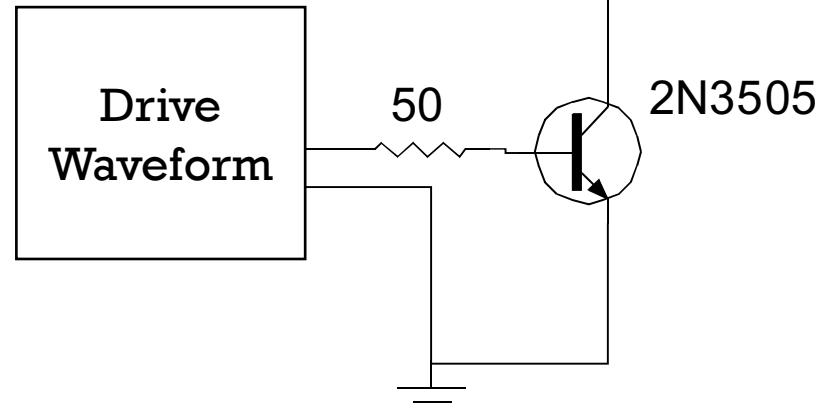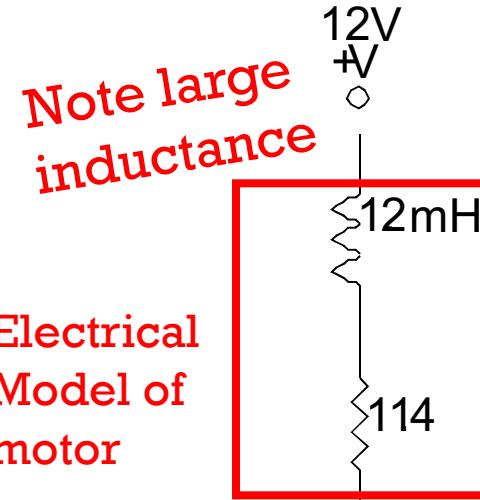


Collector Voltage

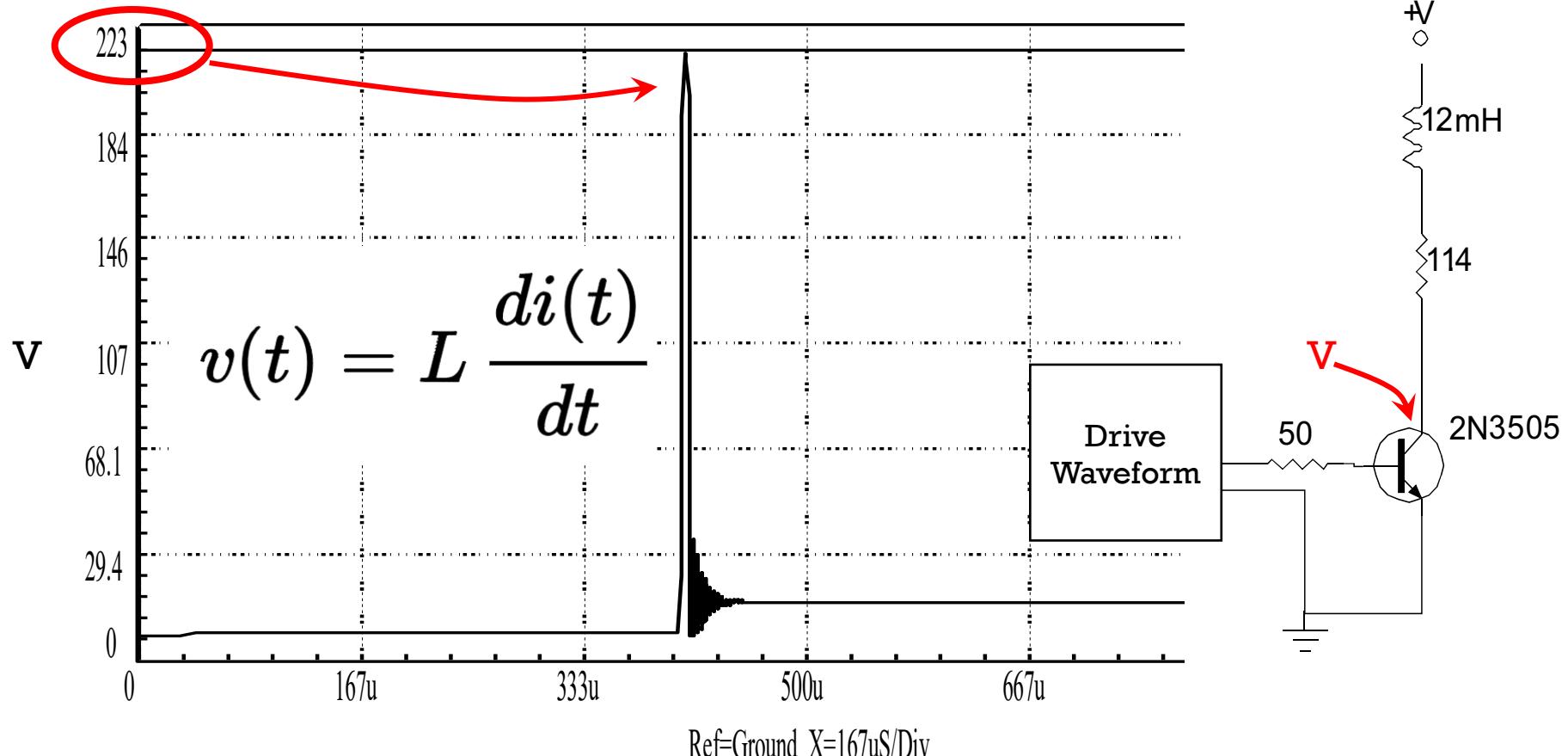

Circuit simulator (from Prof. Ed Carryer @ Stanford)

Recall Large inductance

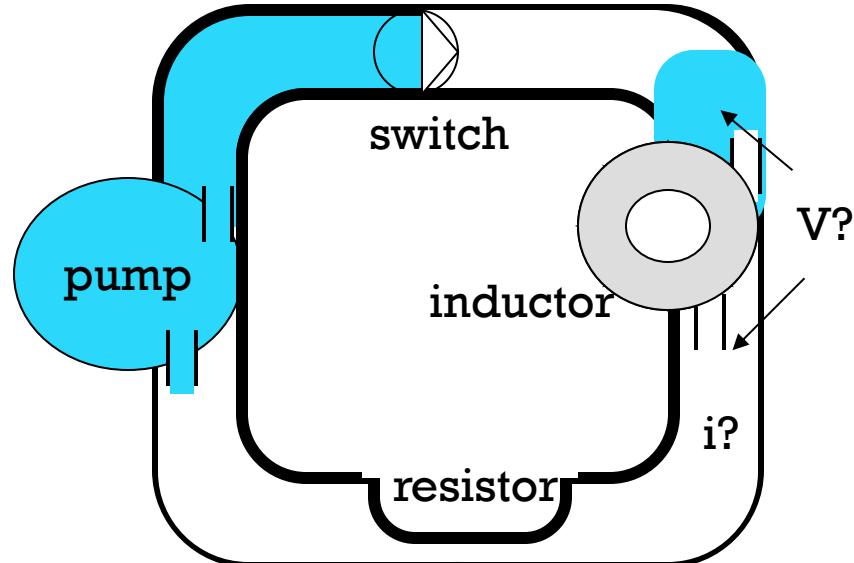

$L i$ similar to mv , momentum

Initial state, switch is off

no voltage across inductor
no current in inductor

Switch turns on

hi voltage seen on one side
no current in inductor

Steady state

voltage equal on both sides
current in inductor


Switch turns off

hi voltage on other side
no current in inductor

Steady state

voltage equal on both (0)
no current in inductor

Large inductance with clamping diode

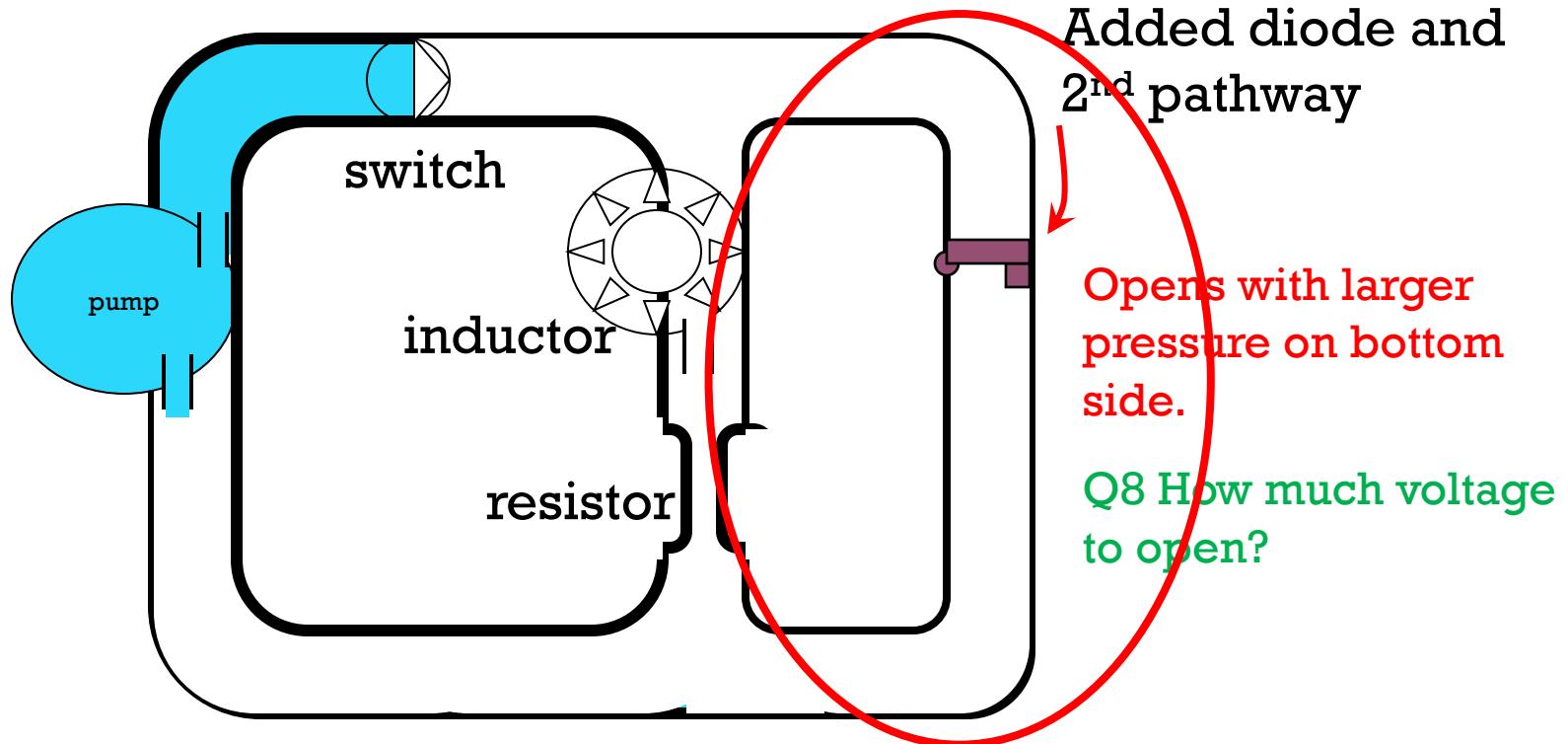



Snubber Diode

AKA Flyback Diode


AKA Clamp Diode

AKA Suppression Diode



AKA Commutation Diode

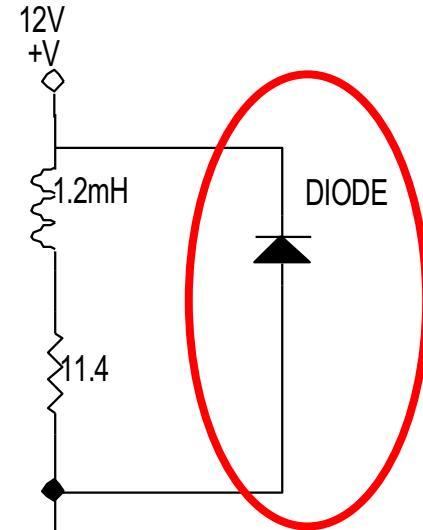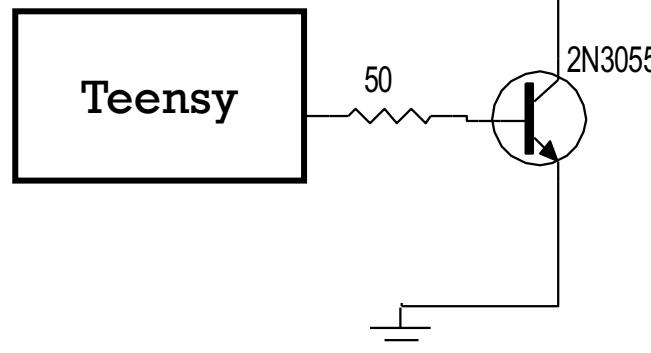

Collector Voltage with Diode Snubber

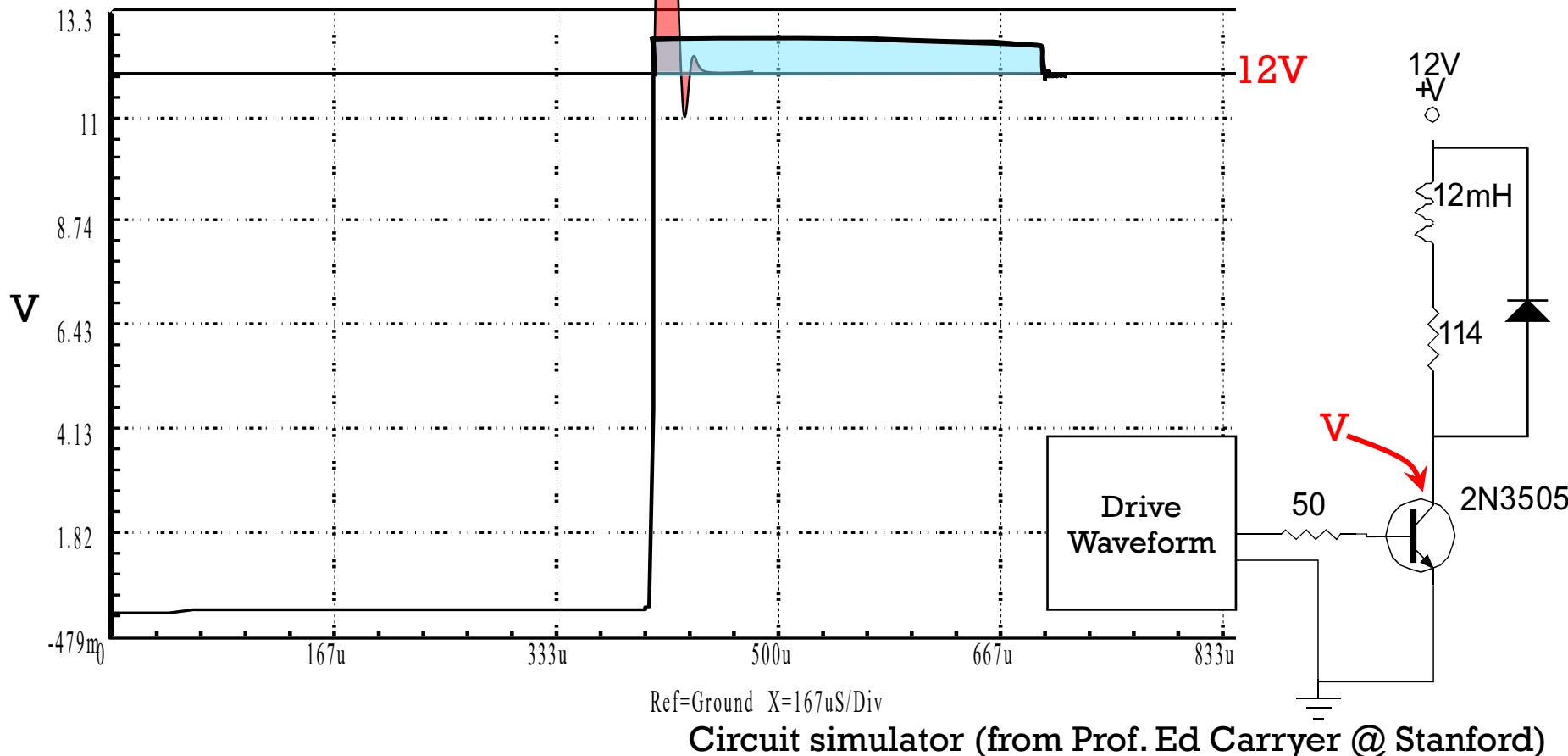


Inductor Current with Diode Snubber

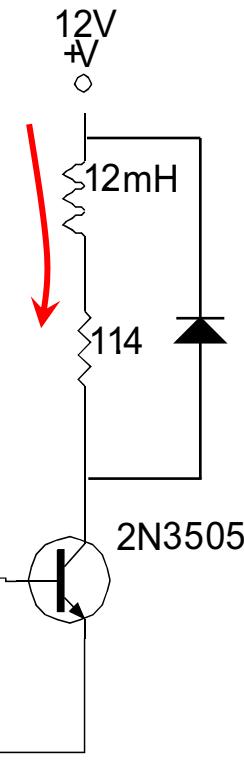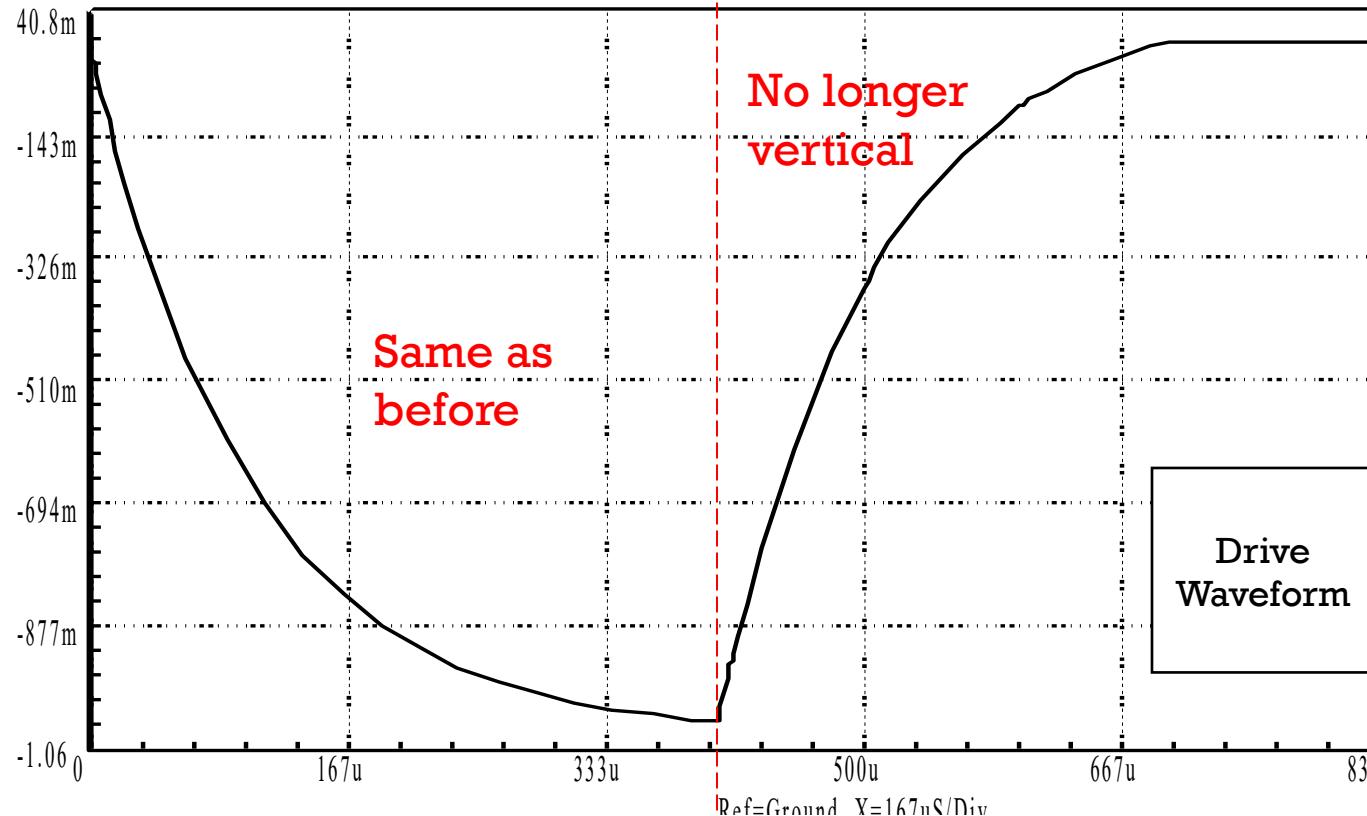


Circuit simulator (from Prof. Ed Carryer @ Stanford)

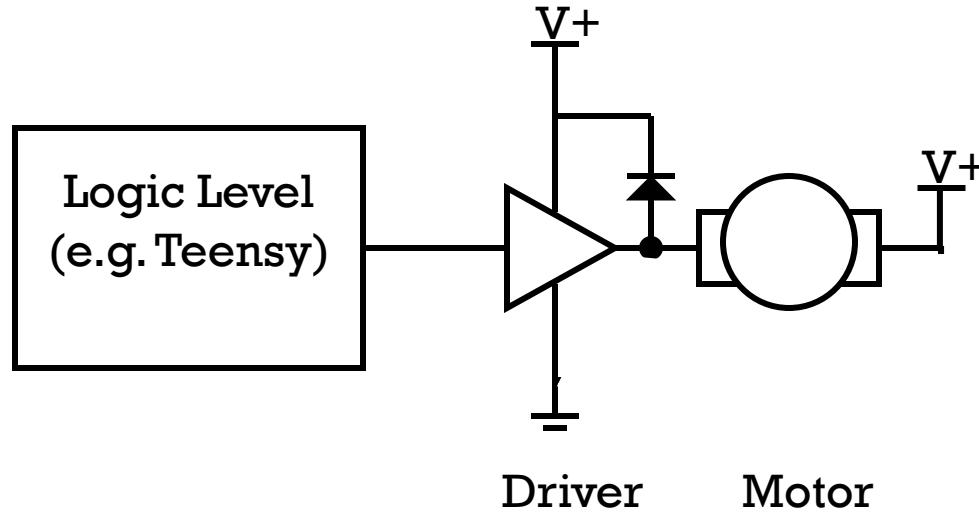So how do we drive a motor with Logic output?





Q9: Draw a snubber diode for the protecting against a negative spike

Two half-bridges w/clamping diodes

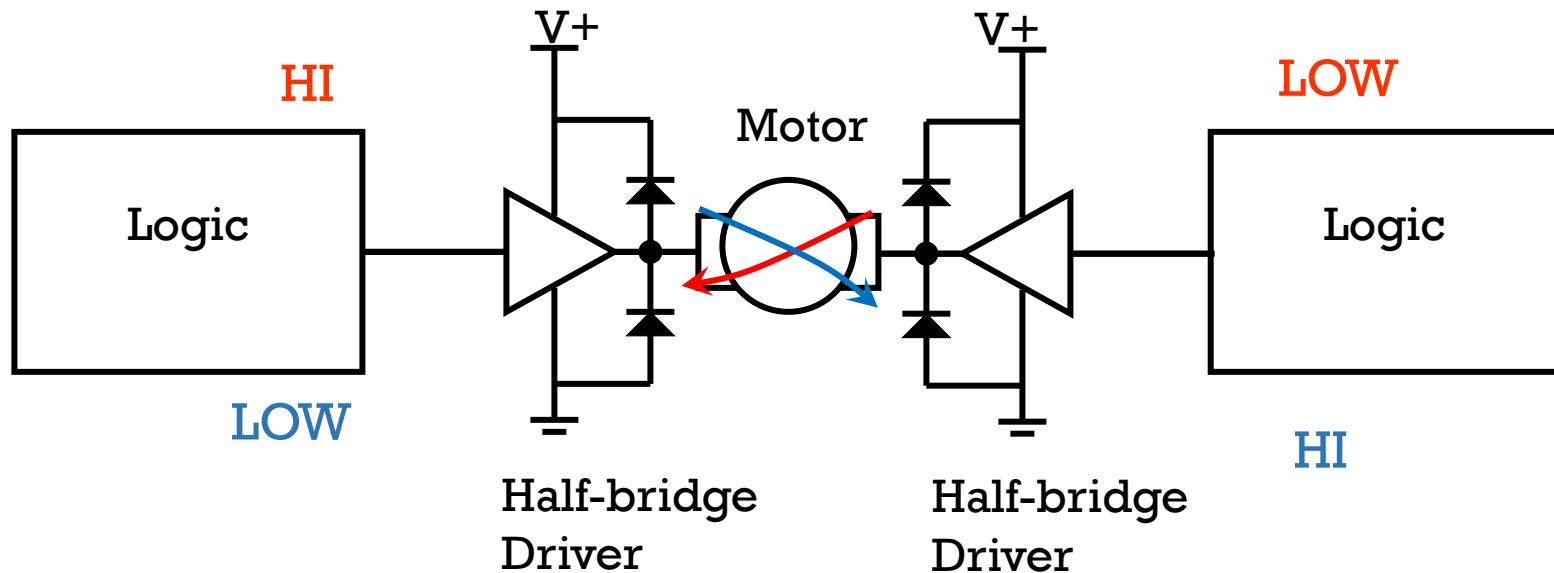



H-Bridge in your kit SN754410

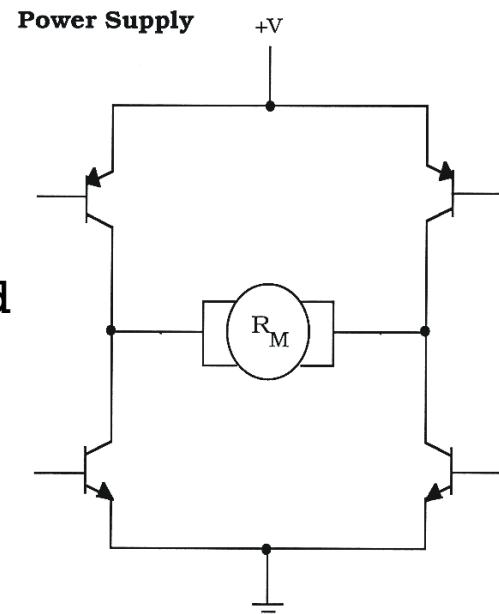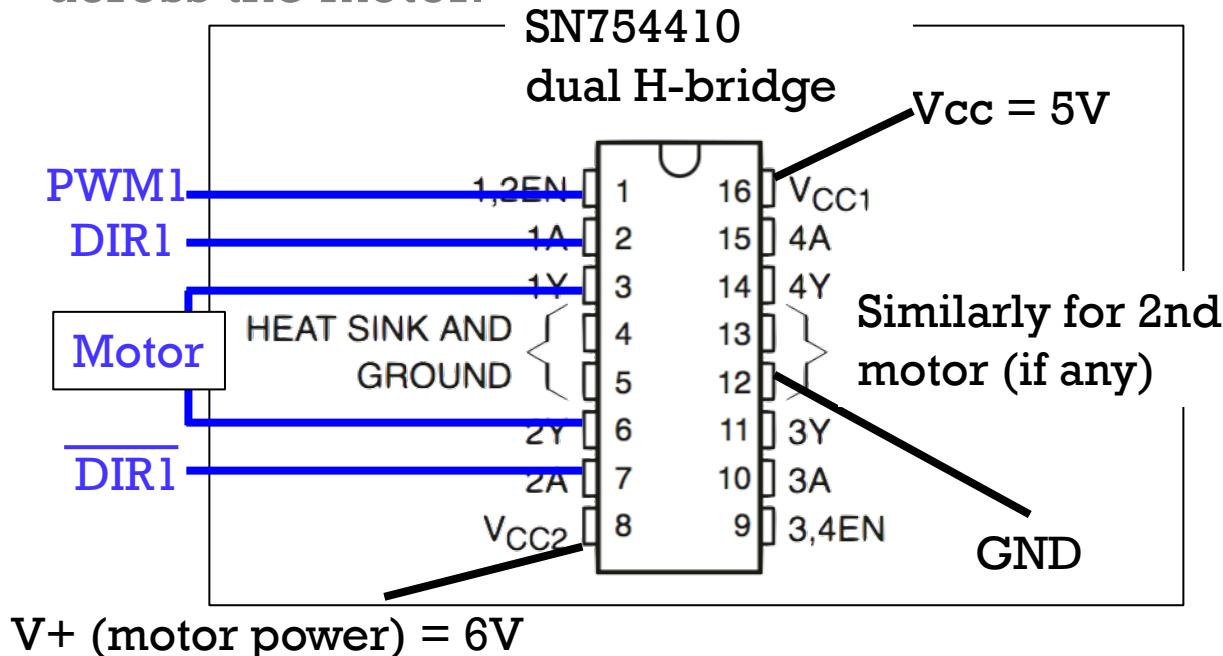- When using the h-bridge to switch directions on a motor in the circuit below, it will be equivalent to swapping 6V and ground across the motor.




SN754410 output stage w/diode clamps

From SN754410 Datasheet:

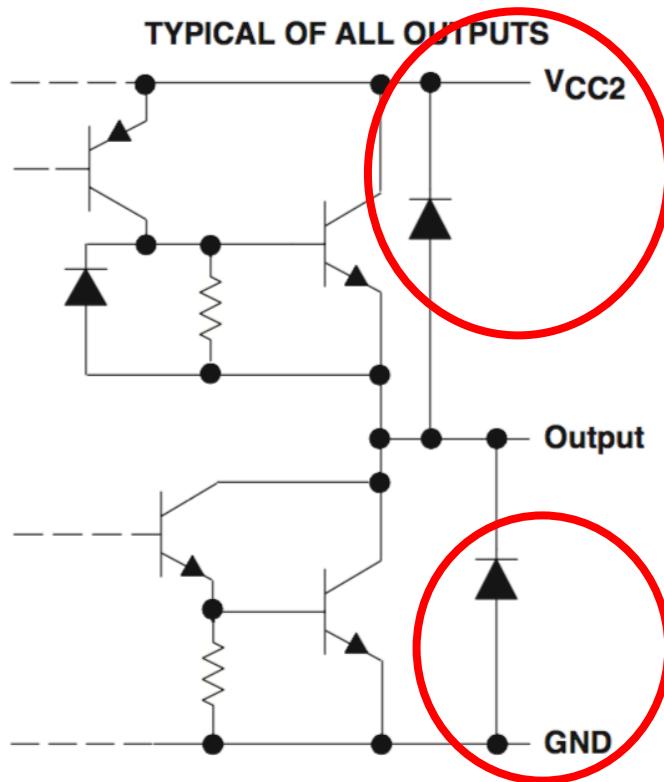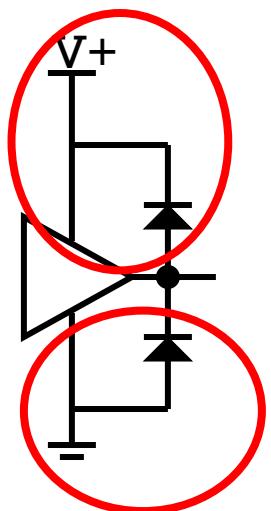


MOSFETs Body Diode

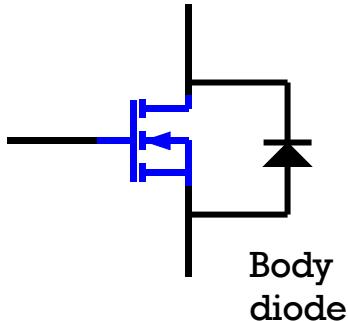
- Most FETS (MOSFETs) have an inherent diode called the *body diode*
- Turns out to be convenient for inductive protection.



From SN754410 Datasheet:

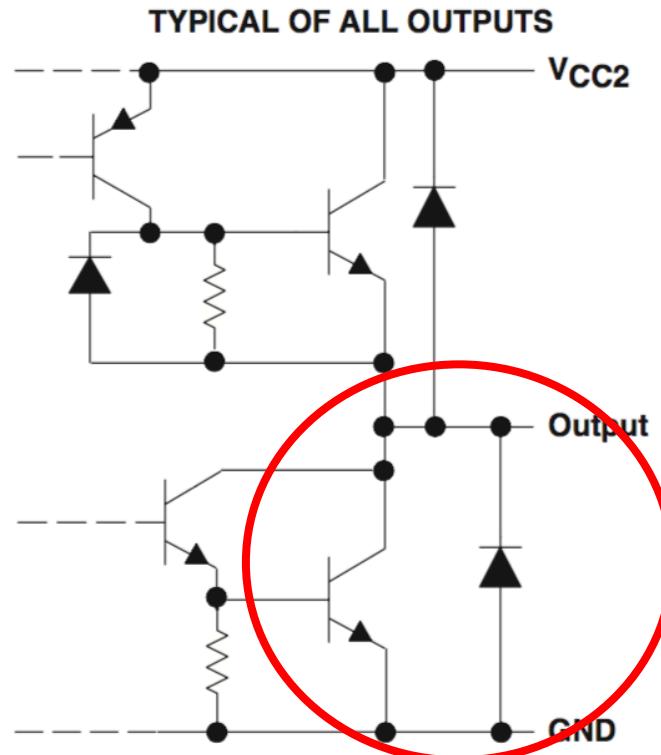

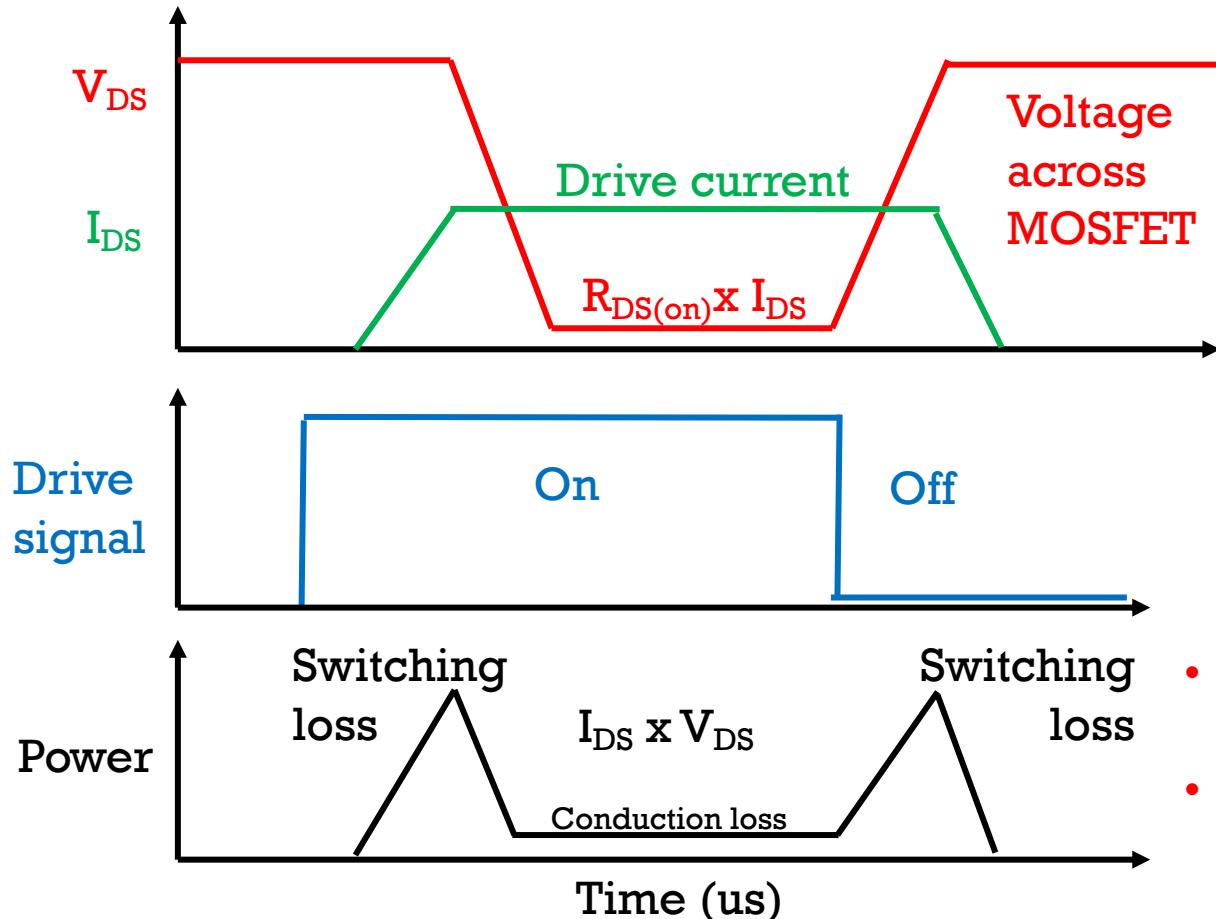MOSFET caveat when driving Large Currents



- Power is consumed in the driver during switching
 - This becomes **HEAT**.
 - 2nd most common cause of “smoking” chips in this class.

- Need to drive gate quickly (minimize resistance)
- Don't use high freq. PWM

Caveat with SN754410

SN754410 QUADRUPLE HALF-H DRIVER

SLRS007B – NOVEMBER 1986 – REVISED NOVEMBER 1995


electrical characteristics over recommended ranges of supply voltage and free-air temperature (unless otherwise noted)

PARAMETER		TEST CONDITIONS	MIN	TYP†	MAX	UNIT
V_{IK}	Input clamp voltage	$I_I = -12 \text{ mA}$		-0.9	-1.5	V
V_{OH}	High-level output voltage	$I_{OH} = -0.5 \text{ A}$	$V_{CC2}-1.5$	$V_{CC2}-1.1$		V
		$I_{OH} = -1 \text{ A}$	$V_{CC2}-2$			
		$I_{OH} = -1 \text{ A}, T_J = 25^\circ\text{C}$	$V_{CC2}-1.8$	$V_{CC2}-1.4$		
V_{OL}	Low-level output voltage	$I_{OL} = 0.5 \text{ A}$		1	1.4	V
		$I_{OL} = 1 \text{ A}$		2		
		$I_{OL} = 1 \text{ A}, T_J = 25^\circ\text{C}$		1.2	1.8	



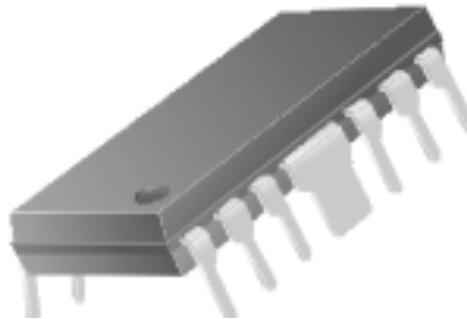
Q10: What if you were driving a motor with 5V, what is the worst case scenario for motor performance (i.e., smallest voltage across the motor?)

FAN8100


- Obsolete chip from Rochester Electronics LLC (sells large min qty obsolete stock for cheap...)
- Has better V_{OH} . Better current driving 1.5A ea channel
- Datasheet available on Canvas -> files-> Resources
- Caveat: double wide ground pins are used as heatsink fins (won't fit in protoboard)



Double pole double throw switch

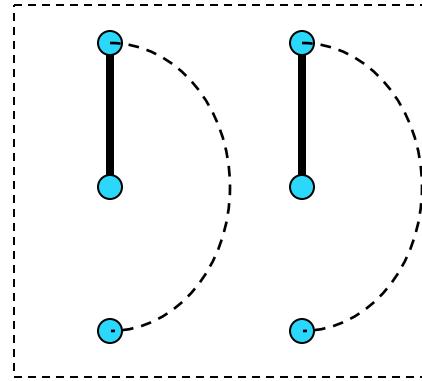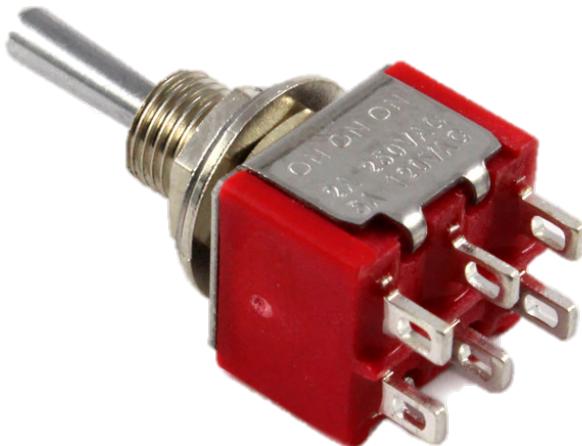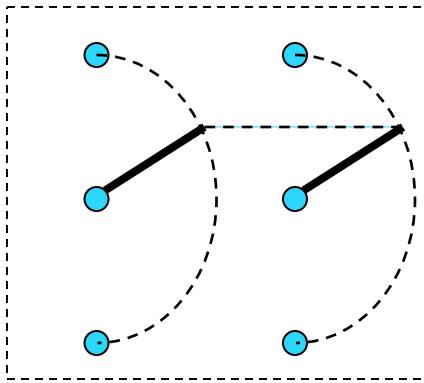


Switch
up

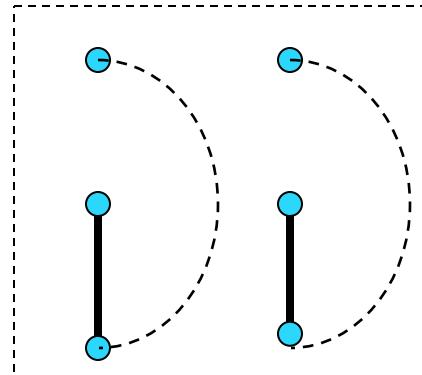

Switch
down

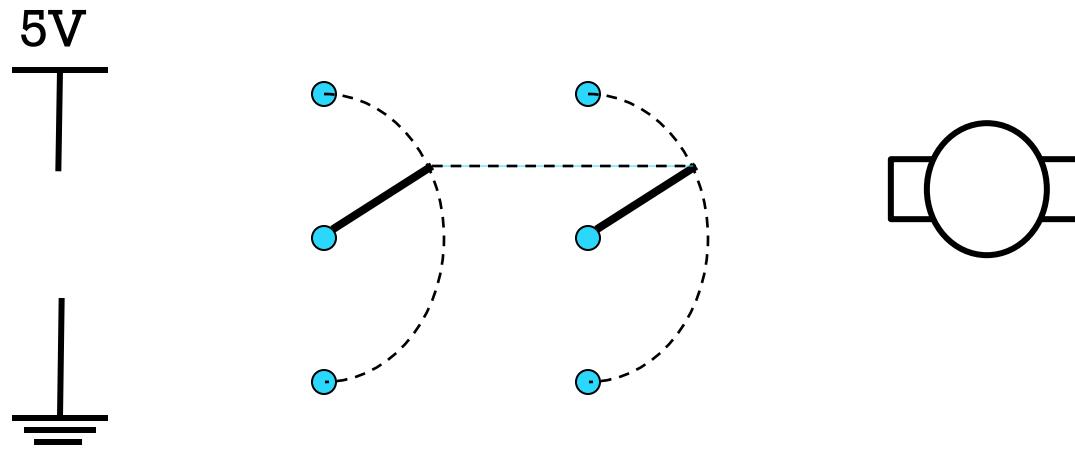Double pole double throw switch as h-bridge



Q8: Connect power ground and motor leads to the 6 leads of a DPDT connections to form an h-bridge

Summary

- Motors are more energy efficient towards higher speeds
- Motors have maximum power at half max torque.
- Large currents require special drivers.
- Driving motors and solenoids can lead to large voltage spikes.
- Snubber diodes protect from these spikes.
- H-Bridges can be used to drive current bi-directionally.
- MOSFETs are the trend for drivers. BJT's are on the way out.

Answer in Chat

Answer how you feel about each topic below with:

1. I don't understand this topic at all
 2. I don't know now, but know what to do to get by
 3. I understand some, but expect to get the rest later
 4. I understand completely already
-
- A. Transistors (BJT / MOSFET)
 - B. Choosing Motors
 - C. Driving Motors with H-bridges