

Lecture 06

Phototransistors

OpAmps

Agenda

00. Stuff – study groups, teensy

01. Phototransistors

02. Operational Amplifiers (Op Amps)

Stuff

- Do not post documents (e.g. lectures or homeworks) to sites like coursehero or chegg, violates Penn's copyright policy.
- Lectures – how is the pacing?
- Piazza queue during OH.
- Toucan Study hall not working
- TA led study groups – optional

Optional Study Groups


Luo, Rui	Chenxi Ji
Shi, Wentao	Chenxi Ji
Wan, Shenshen	Chenxi Ji
Wang, Zhenyu	Chenxi Ji
Chen, Yuqi	Chenxi Ji
Cao, Ruijie	Geli Yang
Li, Peihan	Geli Yang
Wang, Muxuan	Geli Yang
Zhao, Xinyuan	Geli Yang
Du, Yi	Geli Yang
Garza, Nicholas A	Greg Campbell
Gehrke, Rafael	Greg Campbell
Magee, Madison N	Greg Campbell
Alexandrou, Andreas	Jorge Echeverria
Grimaldi, Brian	Jorge Echeverria
Gomes, Paedyn	Jorge Echeverria
Roth, Alexander W	Kelly Babitz
Zarin, Rachel	Kelly Babitz
Aufzien, Jacob H	Kelly Babitz
Jurewicz, Ryan T	Kevin Chazotte
Merczynski-Hait, Andrew	Kevin Chazotte
Romanow, Bryan	Kevin Chazotte

Delattre, Andre J	Lilian Stoesser
Gong, Zachary P	Lilian Stoesser
Messam, Brianna	Lilian Stoesser
Banerjee, Anirban	Malavika Manoj
Nagarajan, Shravan	Malavika Manoj
Shusharin, Pavel	Malavika Manoj
Kim, Joah	Martin Yang
Kulesza, Timothy	Martin Yang
Saven, Celestina	Martin Yang
Wang, Joanna Q	Martin Yang
Adesoye, Konyin	Shivam Dehinwal
Elms, Mason P	Shivam Dehinwal
Tippana, Sahachar	Shivam Dehinwal
Woc, Michael	Shivam Dehinwal
Fedrick, Shaun	Tony Qiu
Li, Jason	Tony Qiu
Ren, Joshua C	Tony Qiu
Fox, Christopher T	Walker Gosrich
Sarda, Sheil	Walker Gosrich
Tamakloe, Ralph S	Walker Gosrich

Random Teensy Things

- Using Pins F4-F7 are special (need to disable JTAG for ADC or GPIO)
`teensy_disableJTAG();`
 - Better to avoid float if possible on the Atmega. It is about 100x's slower than int operations and takes up a lot of memory.

```
teensy disableJTAG();
```

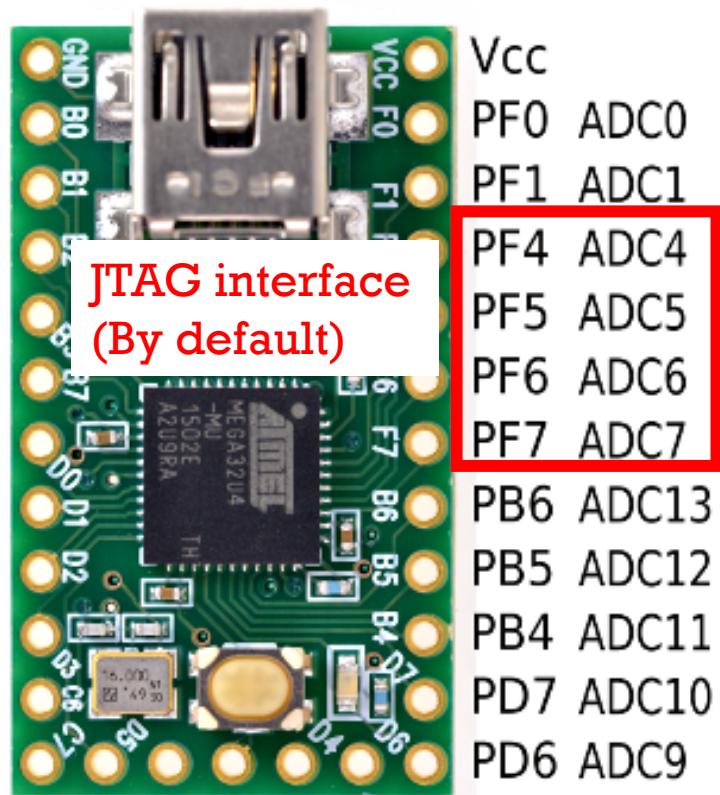



01

Phototransistor




BJT Transistors

Bipolar Junction Transistors

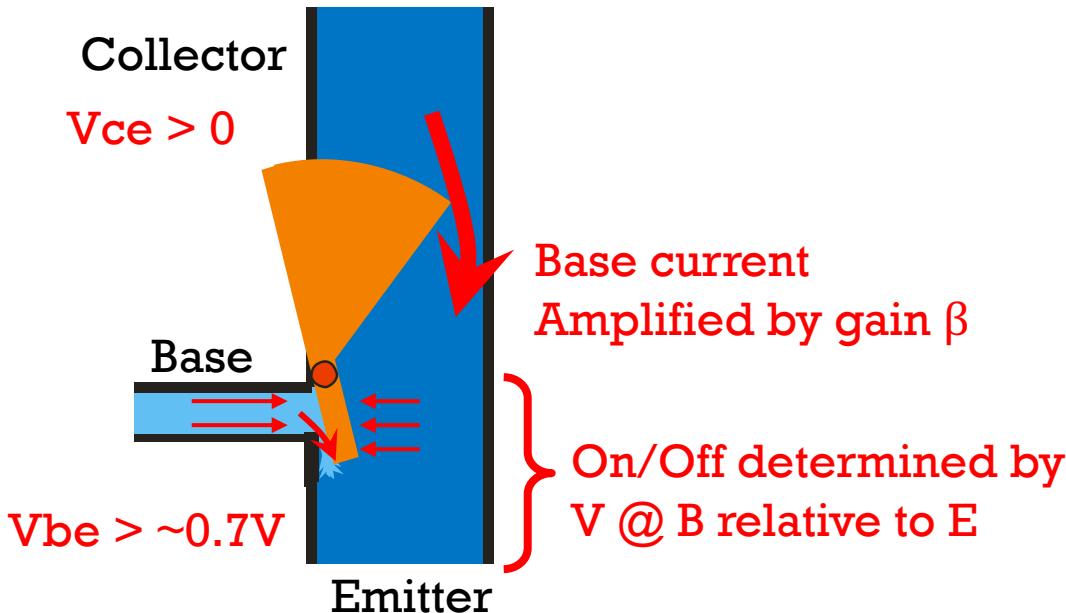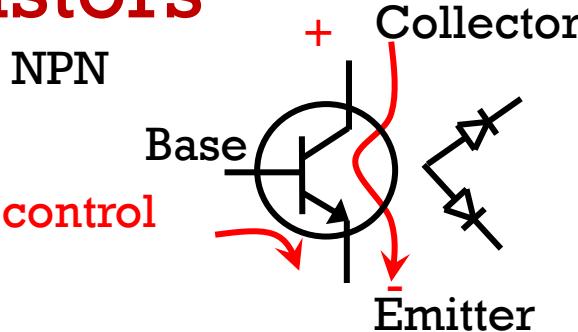


Phototransistors

NPN


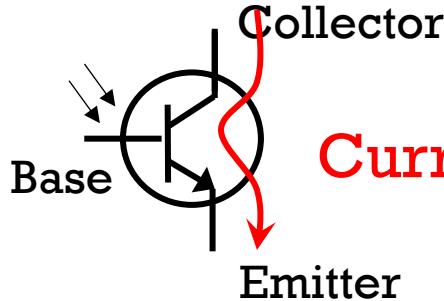


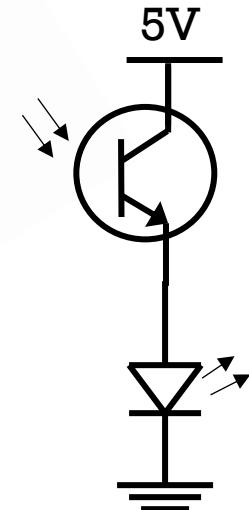- Just two leads (no base)
 - Looks just like a diode...
- Light into base causes current to flow.
- If V_C is larger than V_E , (typically $> 0.4V$) then more light means more current I_{CE}




What happens if
circuit is exposed
to a bright room?

Phototransistors: How to use?

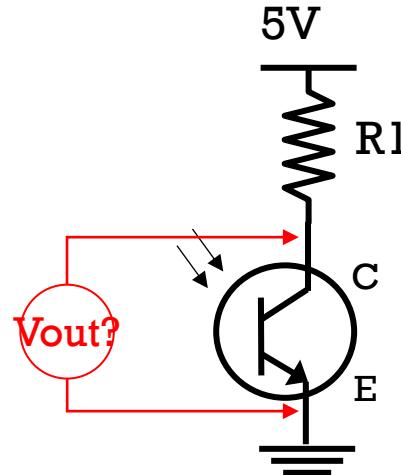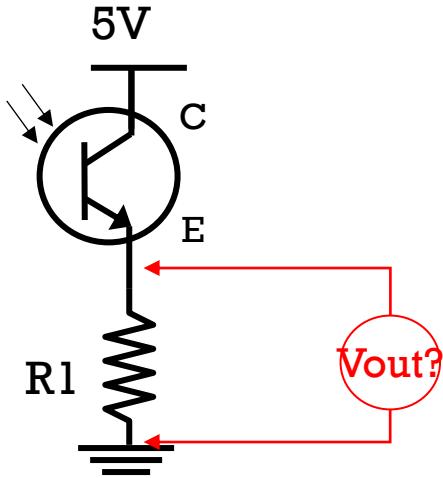


Q1: In Chat: Does Vout go up or down with more light?

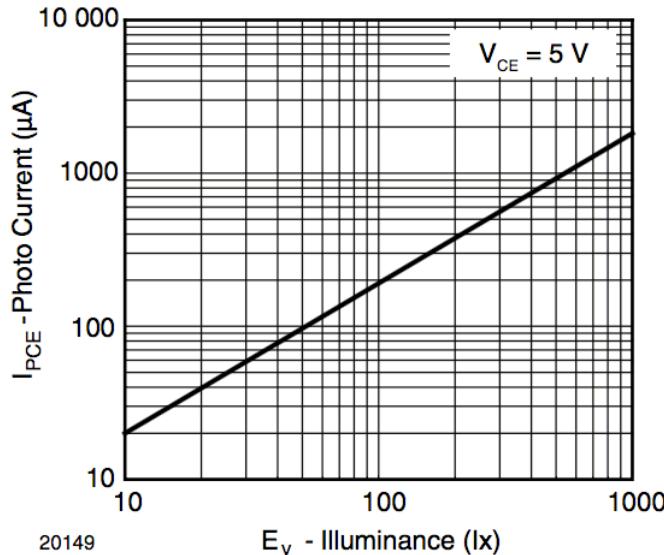Q1a: In Chat: What happens if we make R_1 larger?



Sensitivity

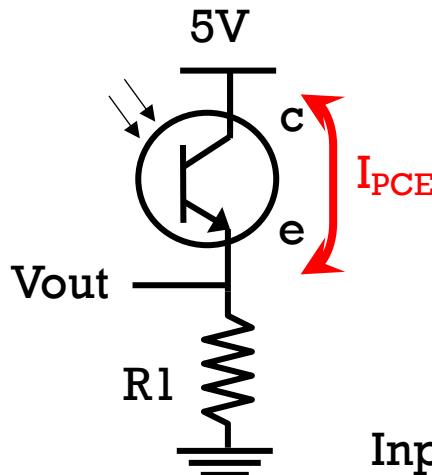

Case	R_1	100Ω	1000Ω	10Ω
Light 1	I_{PCE}	2mA	2mA	2mA
	V_{out}	0.2V	2V	0.02V
Light 2	I_{PCE}	3mA	3mA	3mA
	V_{out}	0.3V	3V	0.03V




Input range ΔI_{PCE} 1mA 1mA 1mA
 Output range ΔV_{OUT} 0.1V 1V 0.01V Not sensitive!

How much more gain is there from ^ this case to ^ this case

Phototransistors: How to use?




If we pretend the photo response is independent of V_{ce} , for a given light condition how does doubling R_1 change the **current** through R_1 ?

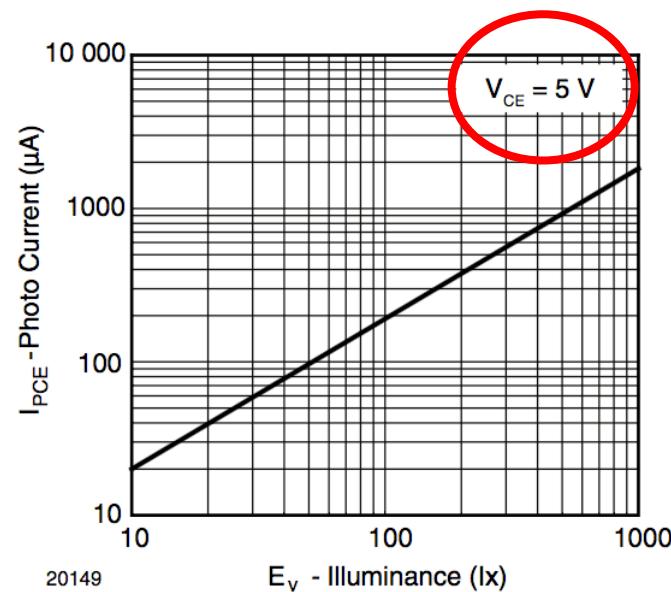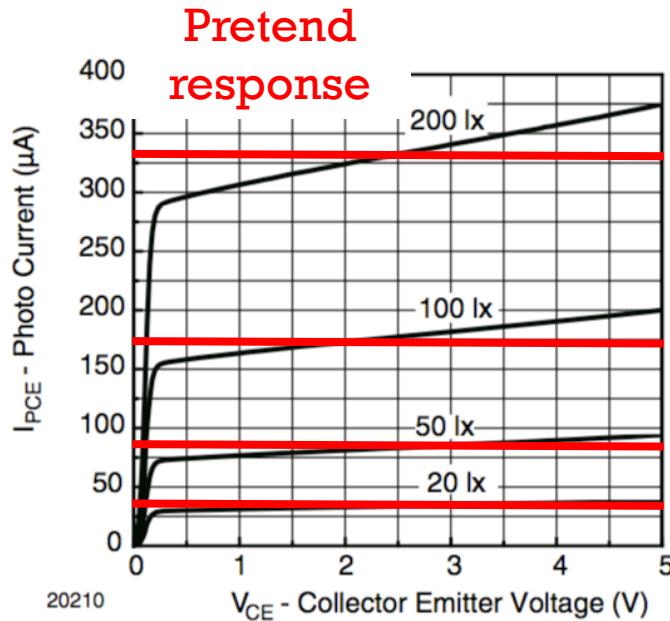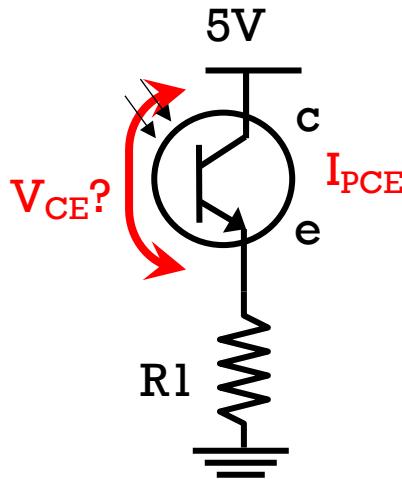Q2: In Chat: If we pretend the photo response is independent of V_{ce} , for a given light condition how does doubling R_1 change the **voltage** across R_1 ?




Phototransistors: How to use?

What happens if R_1 is really large?

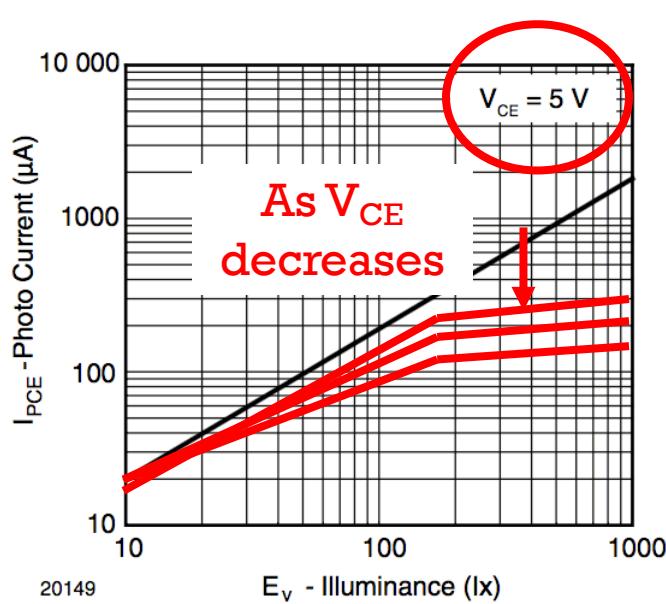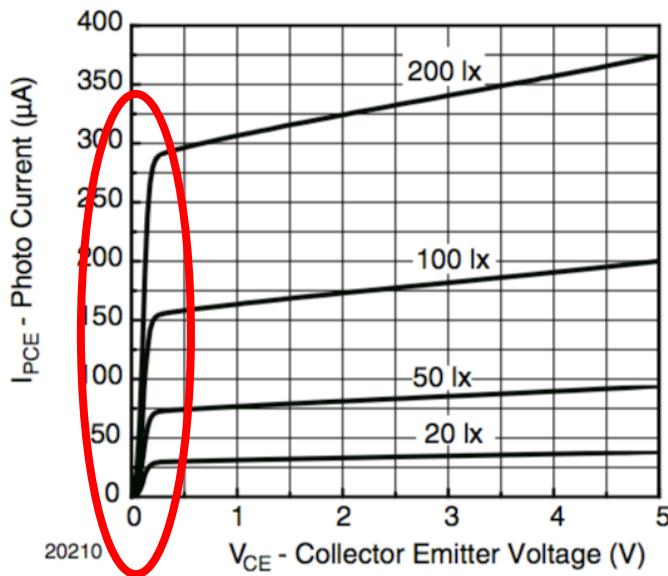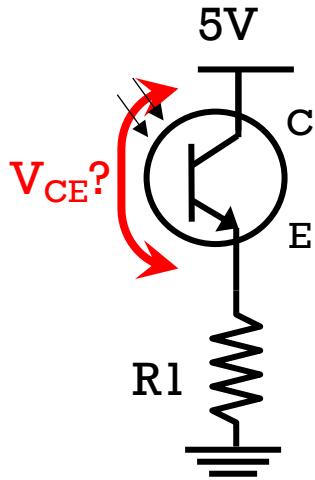

Typically sensors need to be amplified

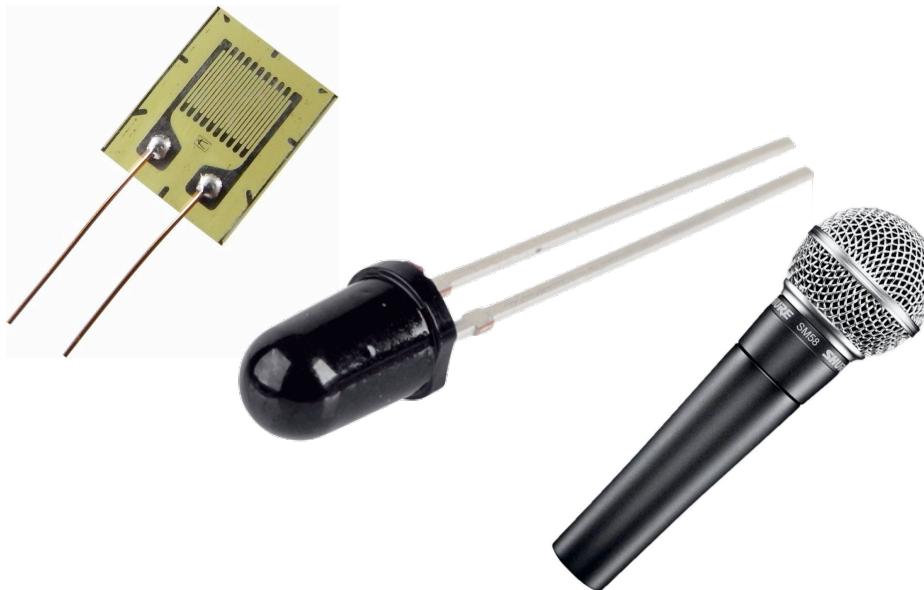
- Strain gauges
- Photodiodes
- Audio signals
- The amount of amplification is called **GAIN**
 - Gain = Output/Input
 - (Usually) gain = V_{out}/V_{in}



02




Op Amps

Operational Amplifier

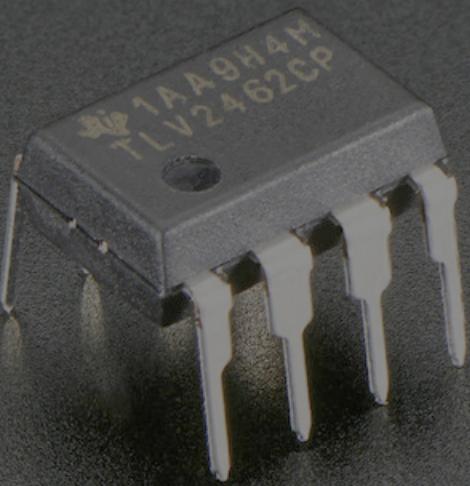

Op Amp

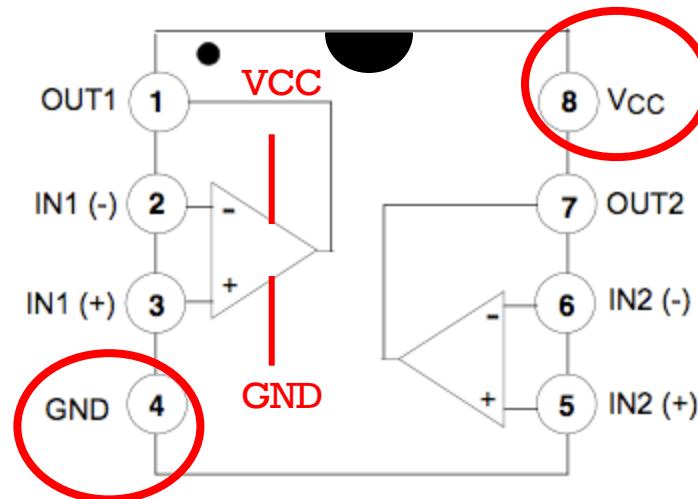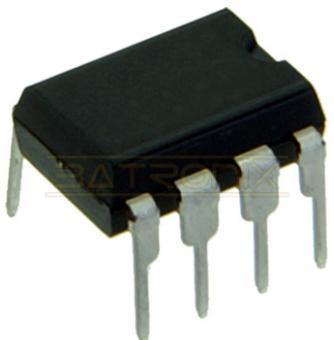
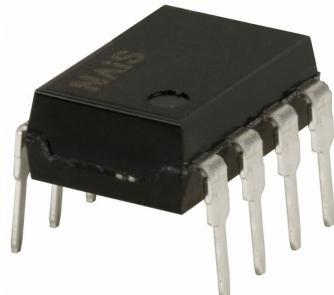
- LM358 in GMLab, generic, low cost, single supply dual opamp.



view from the top (pins going into the page)


Better opamp MCP6044 (in your kit)

- Quad opamp (4 of them) A, B, C and D

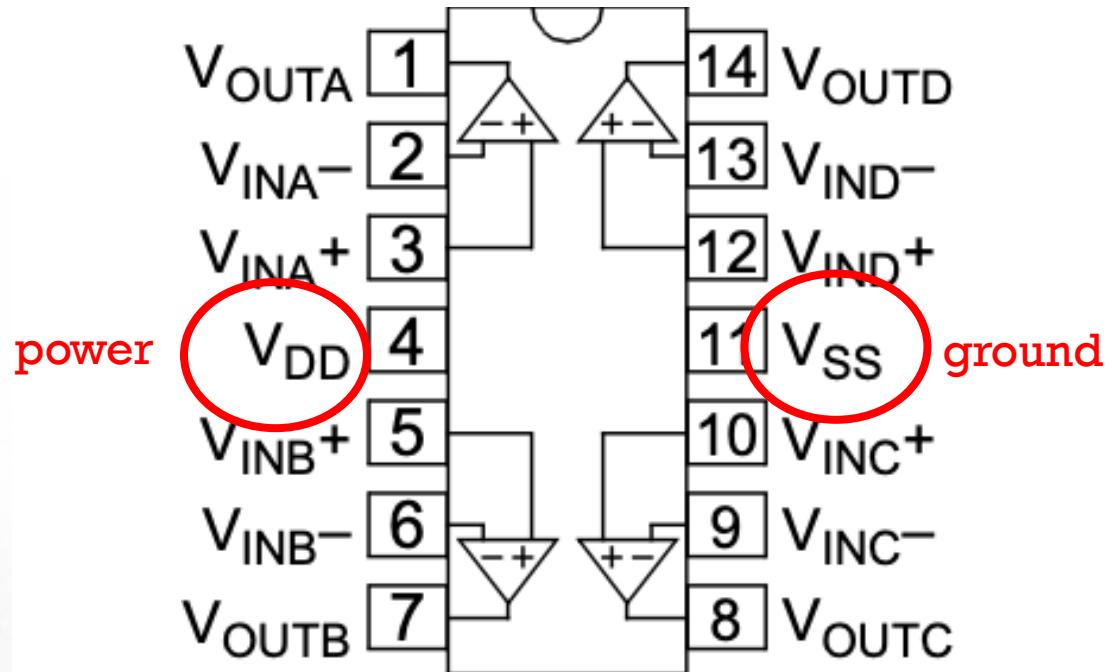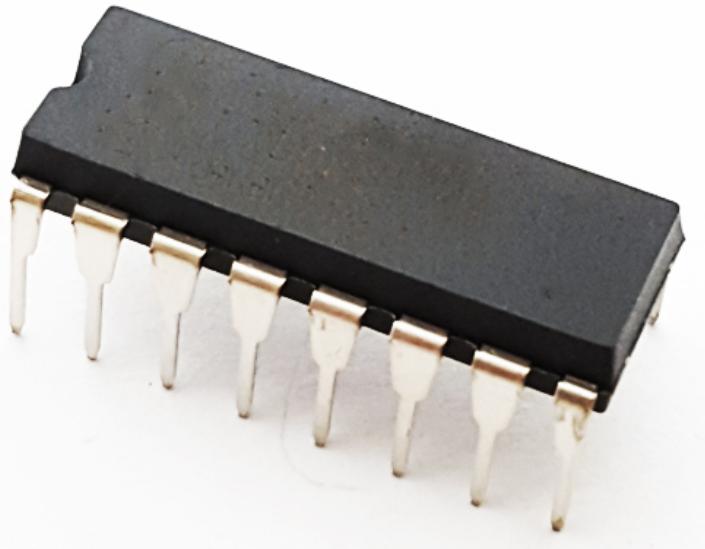

view from the top (pins going into the page)

The Ideal Operational Amplifier

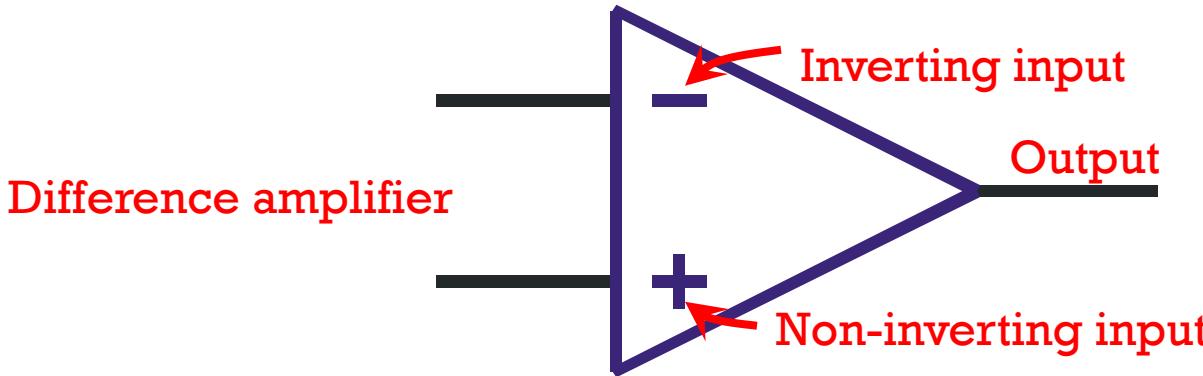


Inverting (V)		Noninverting (V)	Output (V)
Higher	>	Lower	Goes down
Lower	<	Higher	Goes up


Gain is the ratio between difference and output
Gain is very high, consider it infinite.

1st Golden rule: Inputs draw no current

Opamp water analogy

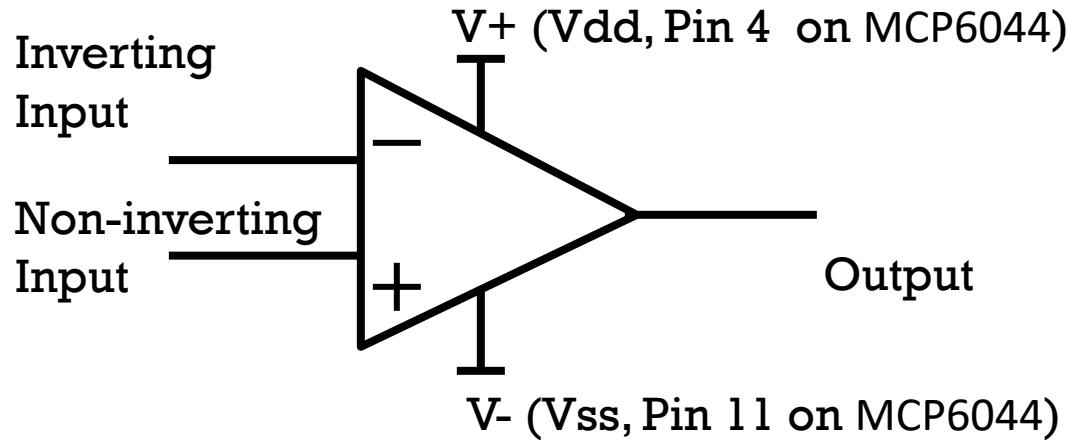


Opamp water analogy

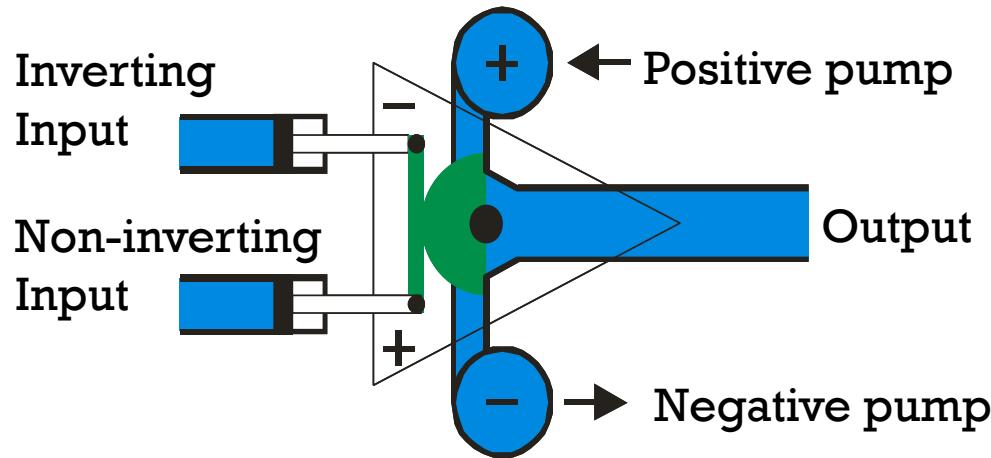


Opamp water analogy

Inverting input
has higher
potential

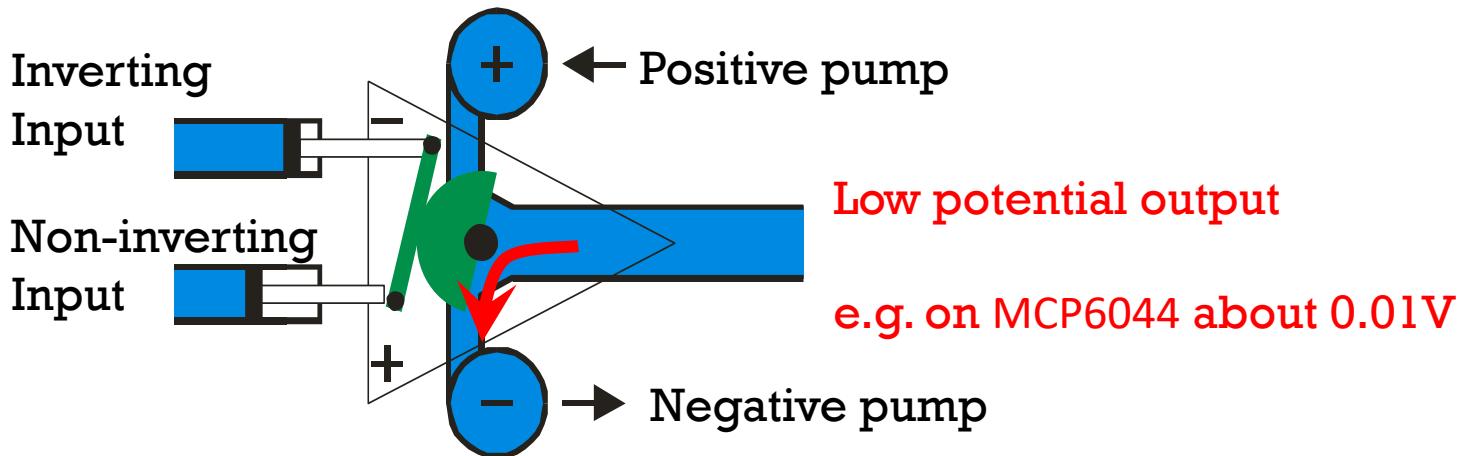


Opamp water analogy

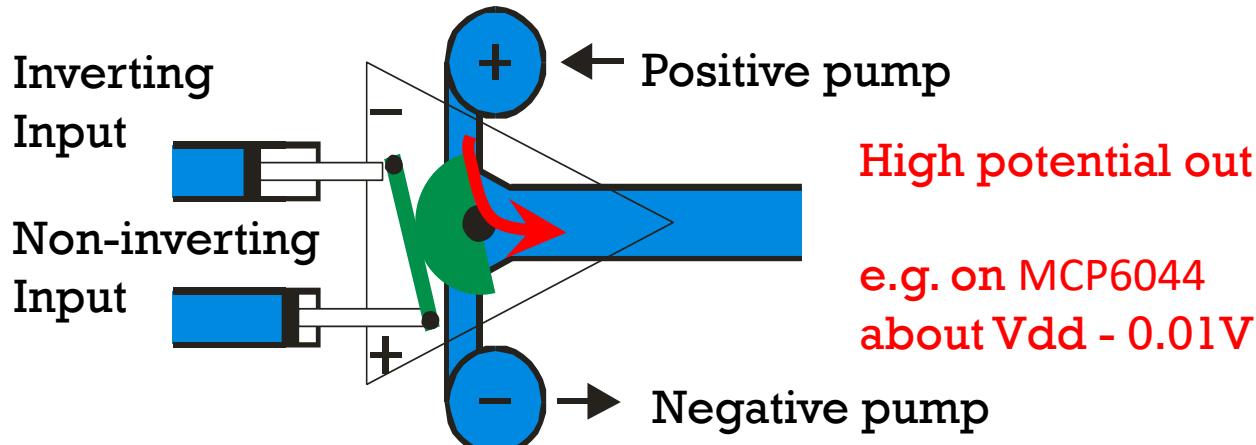

Non-inverting input has higher potential

Negative Feedback

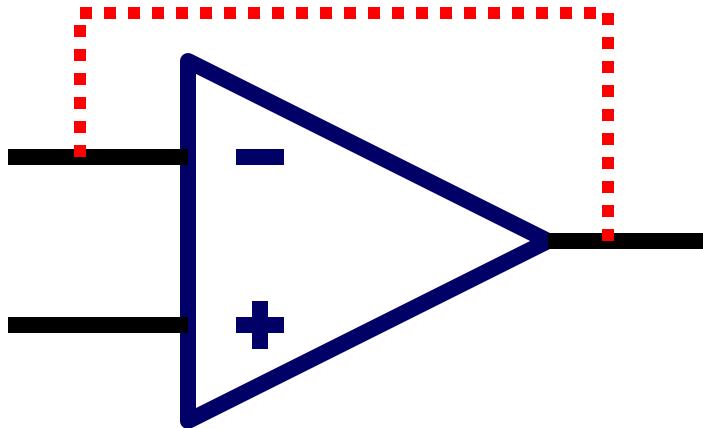


(-)V		(+)V	output?	
higher	>	lower	Output drives (-) lower	Until (-) and (+) match
lower	<	higher	Output drives (-) higher	

2nd golden rule: Inputs are at same potential (V)

If in negative feedback

Opamp water analogy (Negative Feedback)

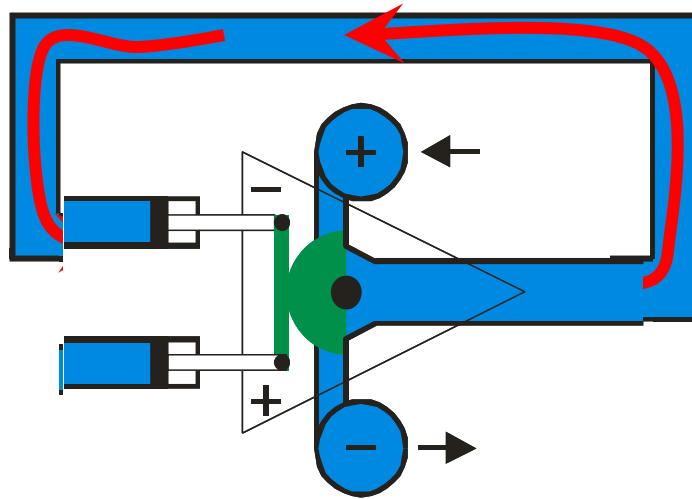

If non-inverting input has higher potential with negative feedback, output drives the non-inverting input lower until it's equal.

Golden Rules of Ideal Opamps

1. Inputs draw no current
2. Inputs are at the same potential
(when in feedback)

The Inverting Amplifier

$$i_1 - i_2 - i_3 = 0$$


[Kirchoff's current law]

$$i_3 = 0$$

[1st rule]

$$i_1 = i_2$$
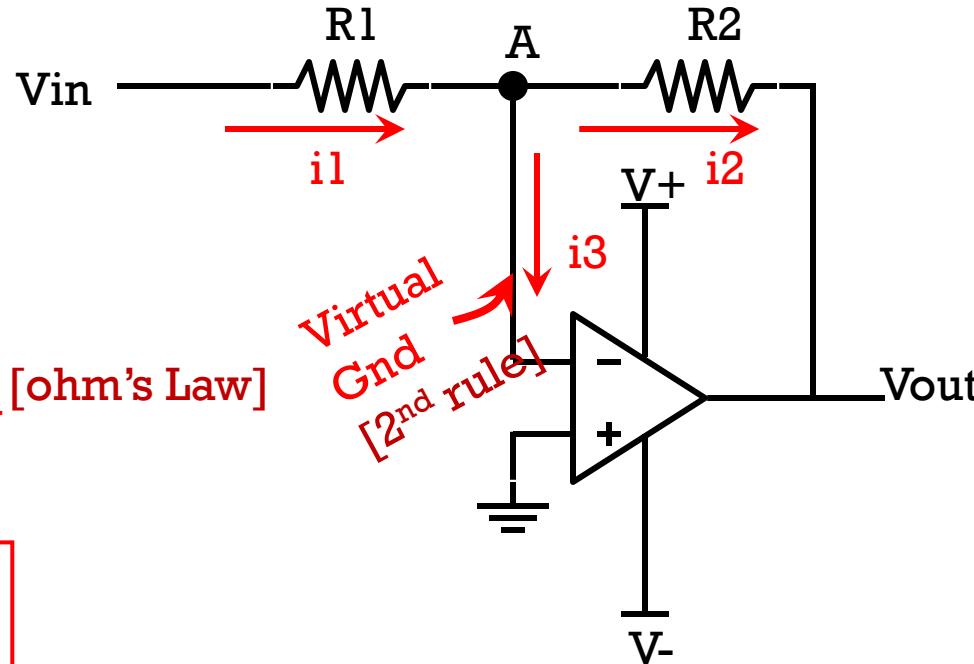
$$\frac{V_{in} - V_A}{R_1} = \frac{V_A - V_{out}}{R_2} \text{ [ohm's Law]}$$



$$\frac{V_{out}}{V_{in}} = \frac{-R_2}{R_1}$$


Gain

You can choose resistors to get desired gain

1st Golden rule: Inputs draw no current

2nd golden rule: Inputs are at same potential (V)

The Inverting Amplifier Exercise

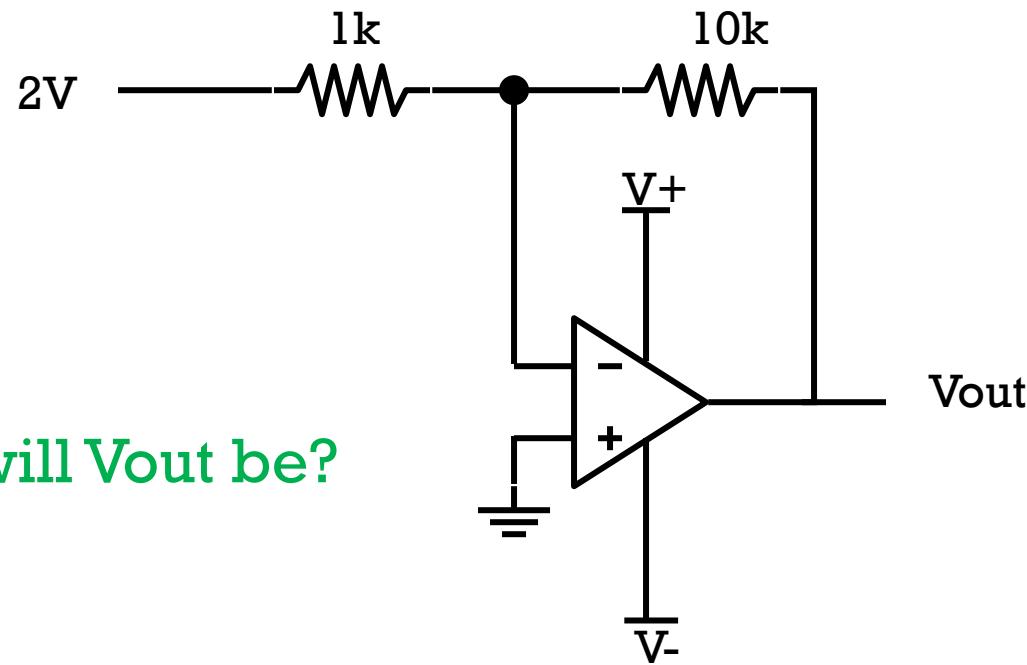




Q3: What will V_{out} be?

The Inverting Amplifier Exercise

$$i_3 = 0$$

$$i_1 = i_2$$
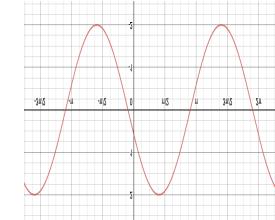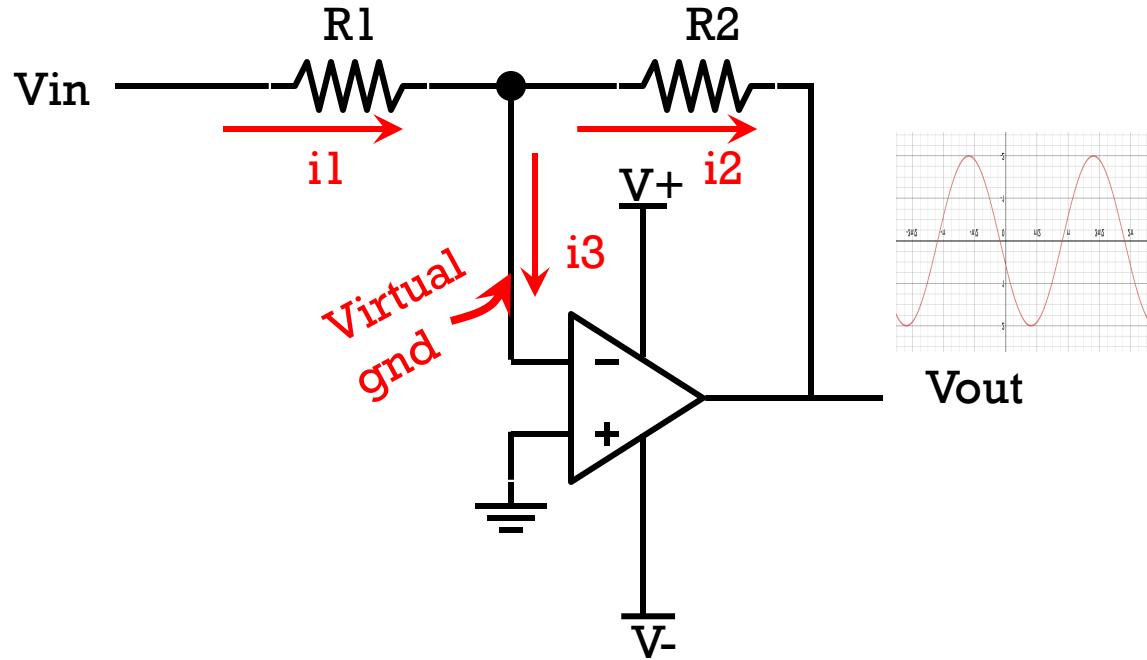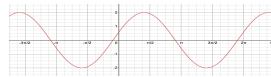
$$\frac{V_{in} - 0}{R_1} = \frac{0 - V_{out}}{R_2}$$




Vout

We have a sine wave peaks at +1V and -1V at Vin

Q4 In Chat: What values of R1 and R2 will give us an output flipped sine wave peaks at +5V and -5V?

The Non-Inverting Amplifier

[1st rule] $i_1 = i_2$

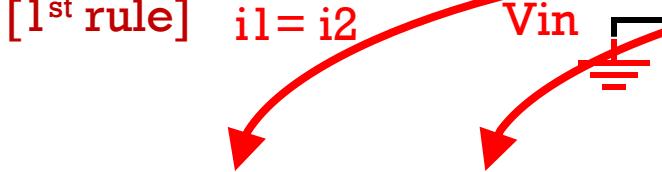

[2nd rule]

V_{in}

A

R2

i_1

i_2

V_+


V_{out}

$$[ohm's\ Law] \frac{V_{in} - 0}{R_1} = \frac{V_{out} - V_{in}}{R_2}$$


$$\frac{V_{in}}{V_{out} - V_{in}} = -\frac{R_1}{R_2}$$

$$\boxed{\frac{V_{out}}{V_{in}} = 1 + \frac{R_2}{R_1}}$$

Gain

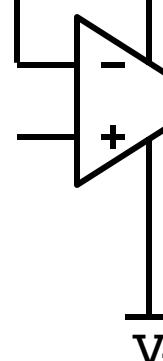

The Non-Inverting Buffer

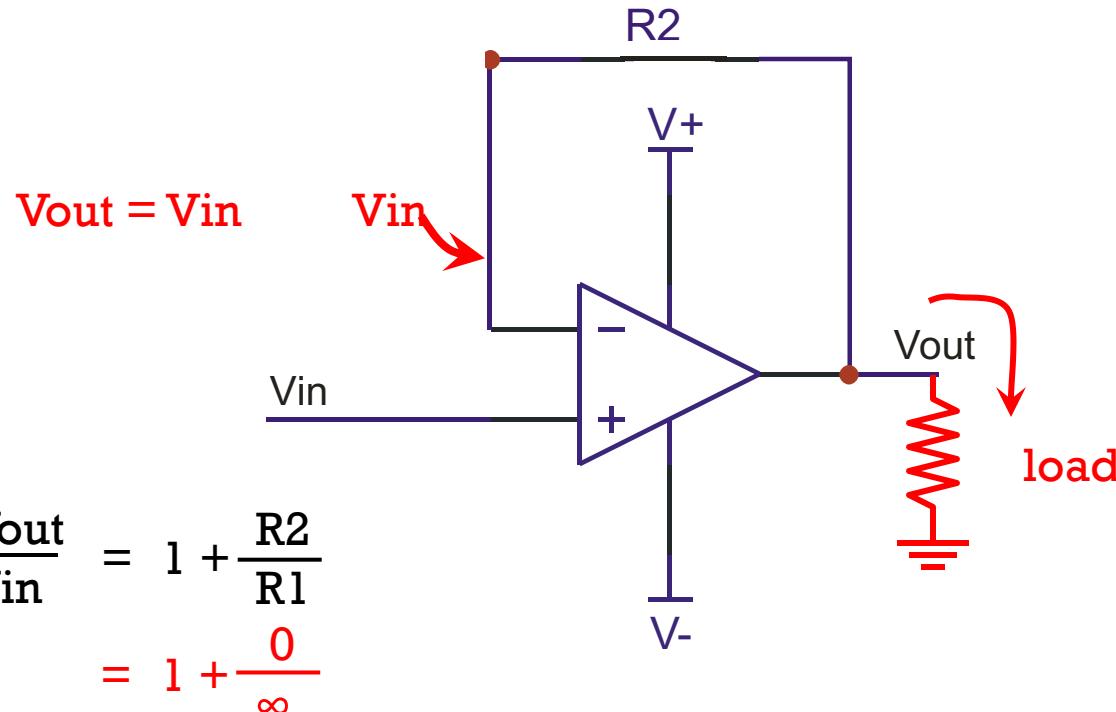


Isolate input, from current stand point
(no (very little) current will flow from accessing V_{in})

Amplifying photosensor signals.

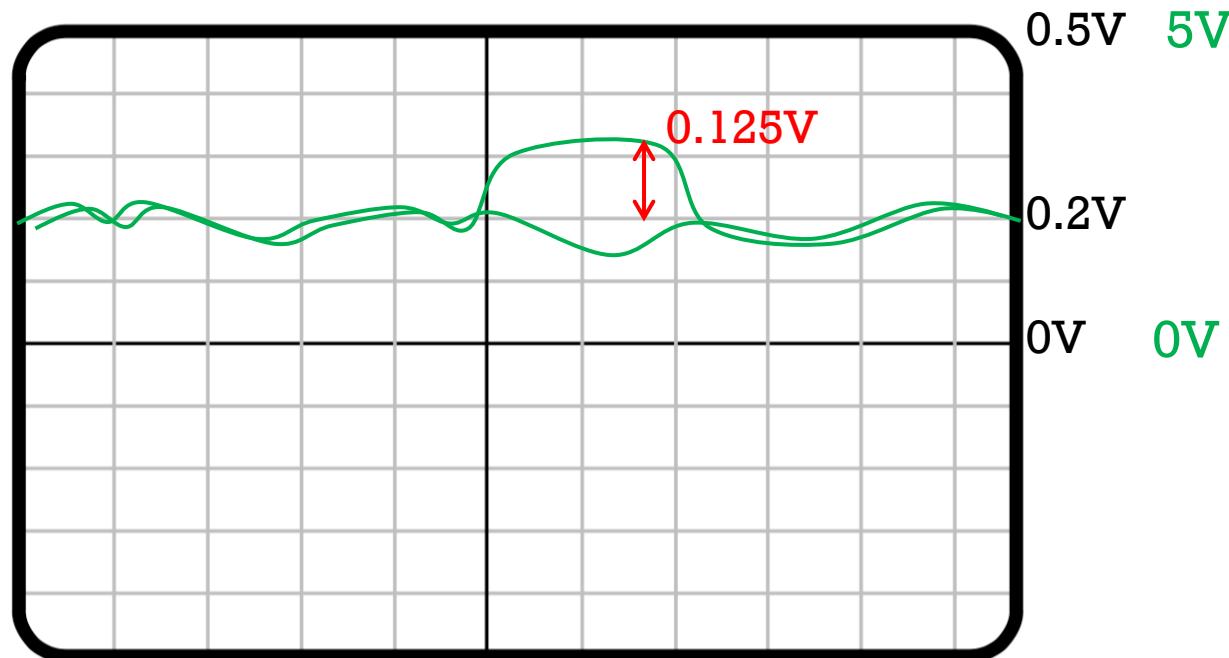
Q5: Draw and hold the scope trace when signal is amplified 40x and the scale of the scope changes to 5V.



Scope output of a photo sensor circuit (unamplified)



Signal Conditioning: Amplification

Must consider **Gain** and DC **Offset**

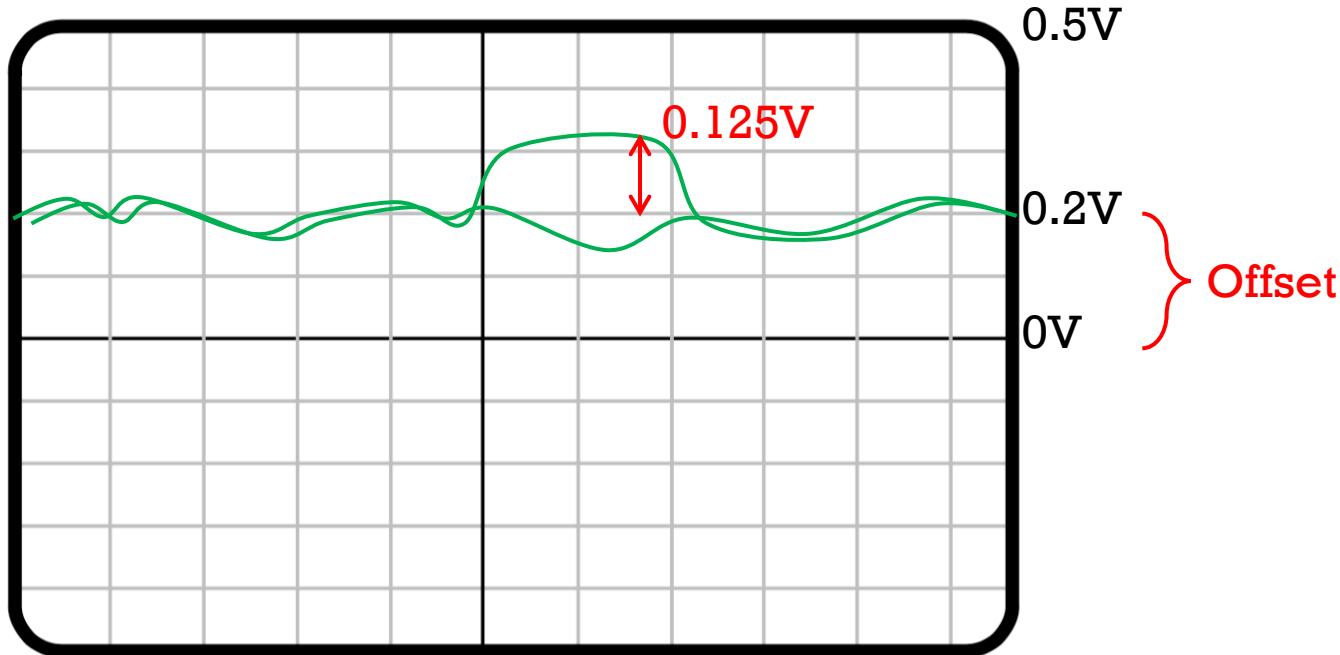

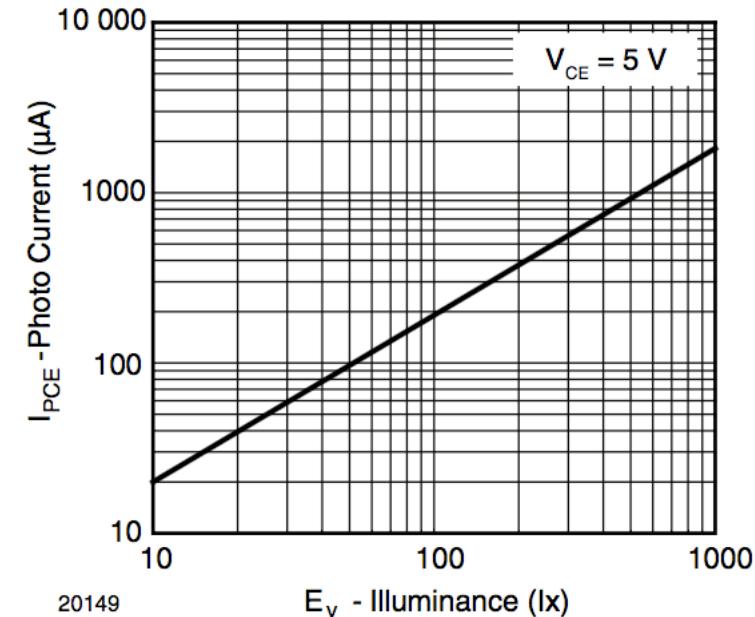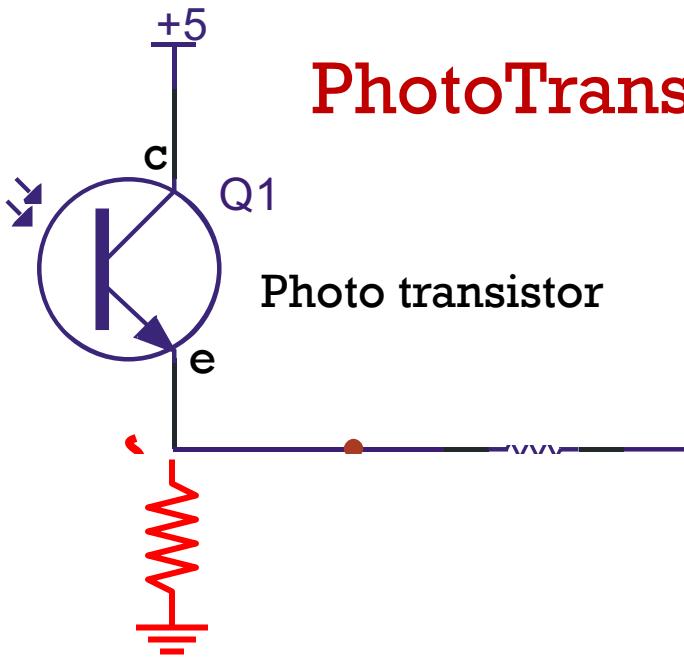


20149

$$V_{out} = - i_{PCE} R_2 \quad [\text{ohm's Law}]$$

Transresistive configuration

PhotoTransistor

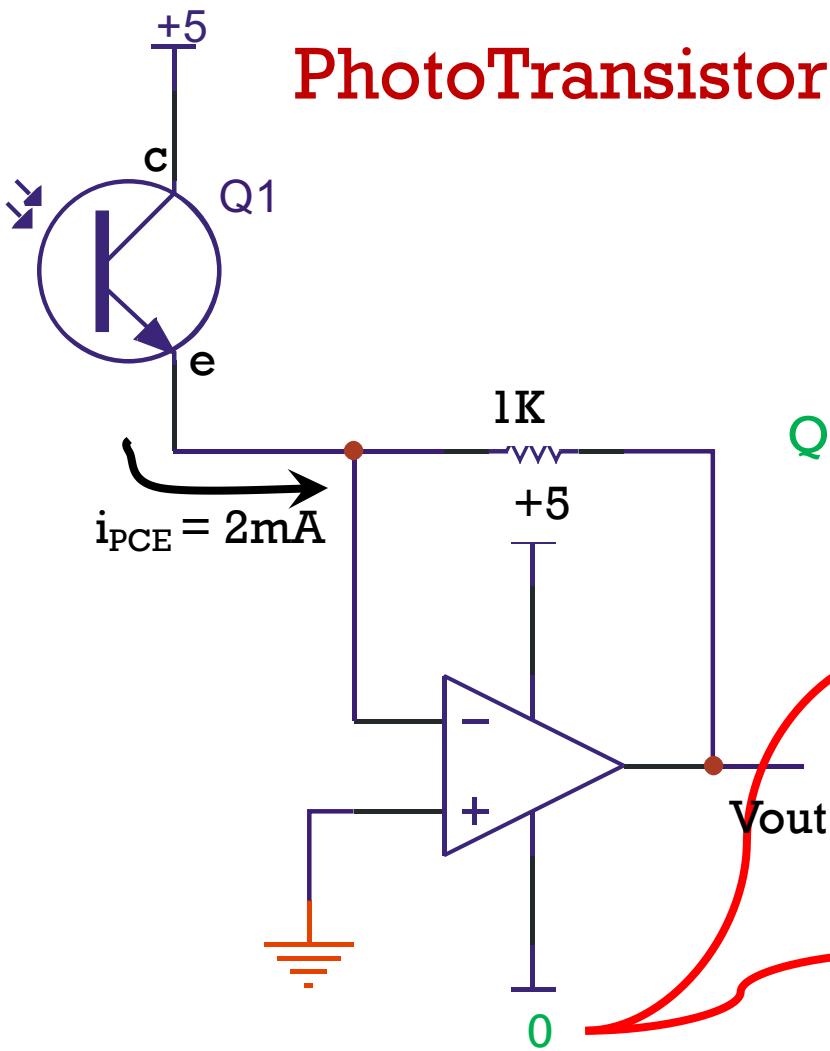


$$V_{out} = - i_{PCE} R_2$$

Q6: What is V_{out} in this case?

With dual supply:
 $V_{out} = -2\text{V}$

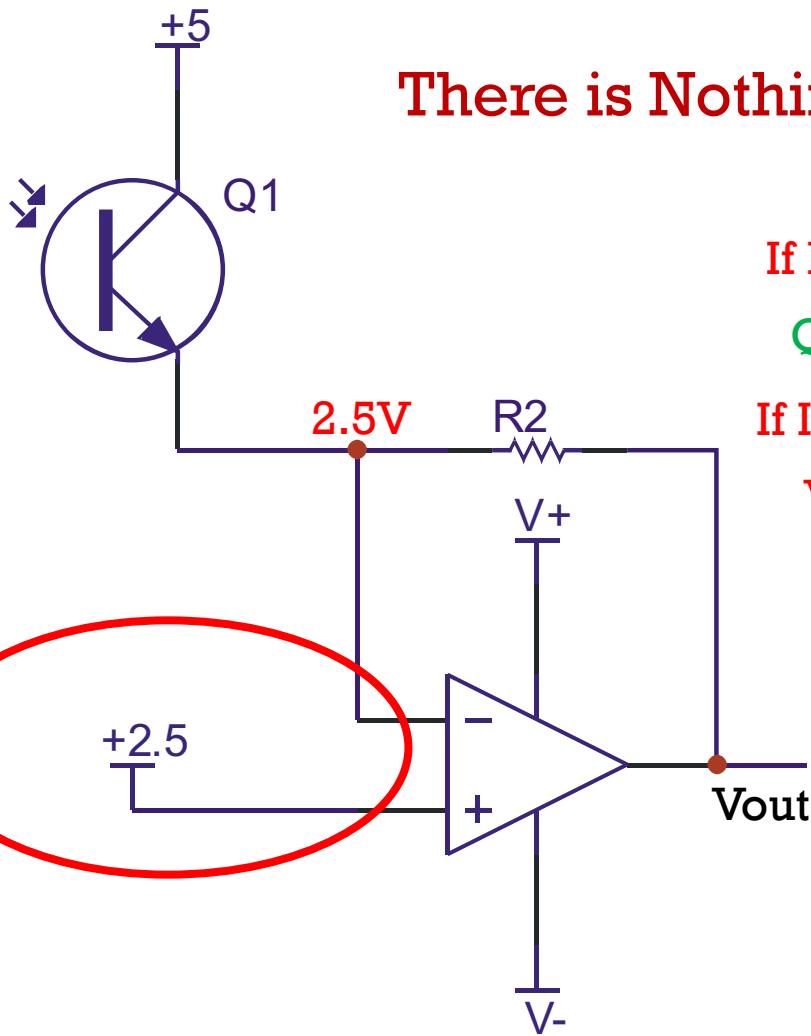Q7: How about now?

With single supply
Should be $V_{out} = -2$, but
 $V_{out} = 0$





There is Nothing Magic about Ground

If $I_{PCE} = 0 \text{ mA}$


$Q_8: V_{out} = ?$

If $I_{PCE} > 0$

$V_{out} < 2.5V$

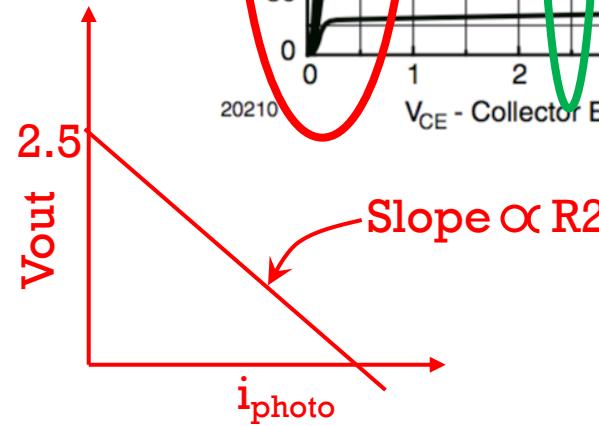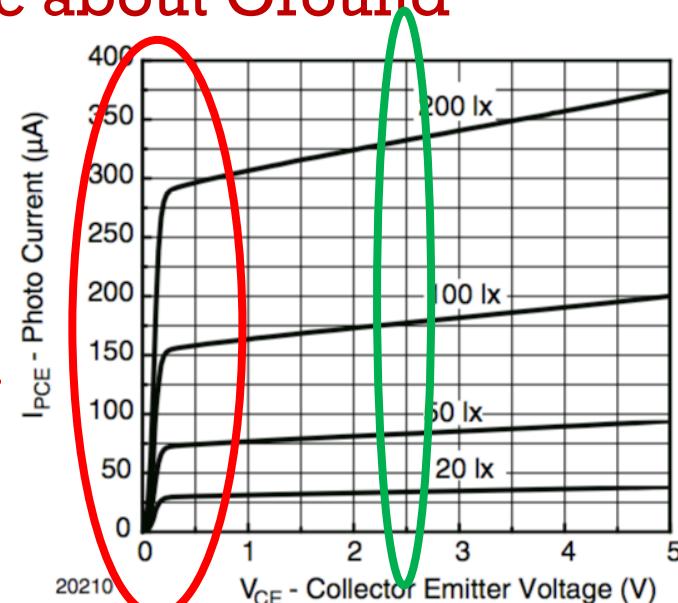


Another Application

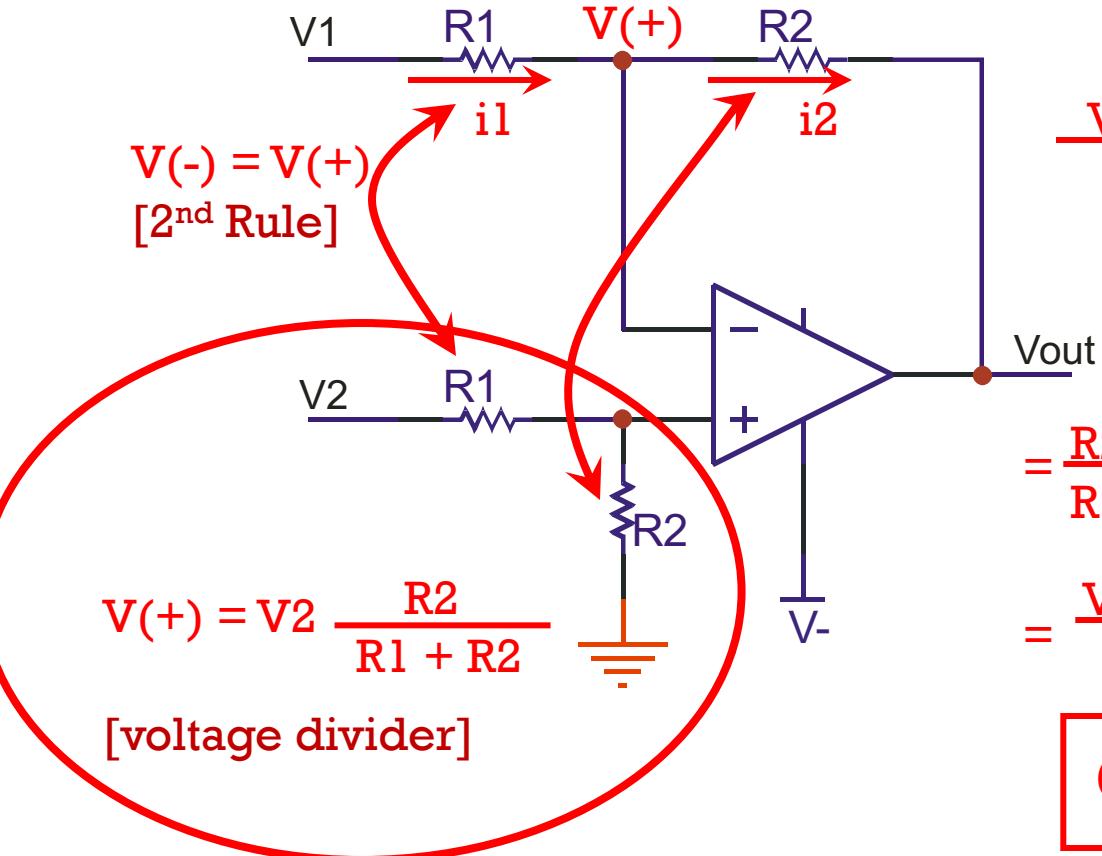

(Subtraction) with multiplier

Still Another Application

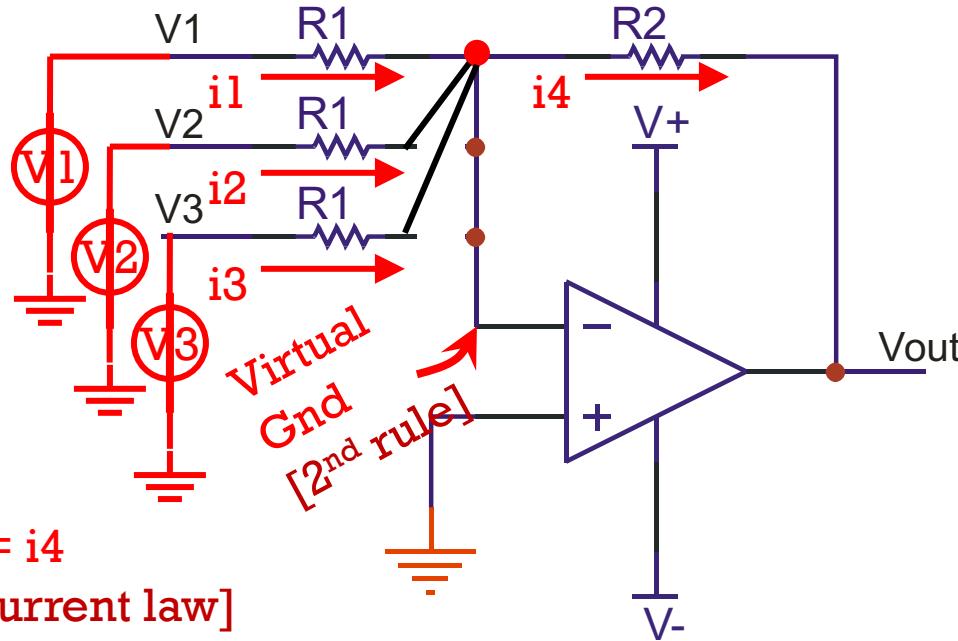

$$i_1 + i_2 + i_3 = i_4$$

[Kirchoff's current law]



$$\frac{V_1}{R_1} + \frac{V_2}{R_1} + \frac{V_3}{R_1} = -\frac{V_{out}}{R_2}$$

[Ohm's law]

$$(V_1 + V_2 + V_3) \frac{R_2}{R_1} = -V_{out}$$

(Addition) with multiplier

Example problem:

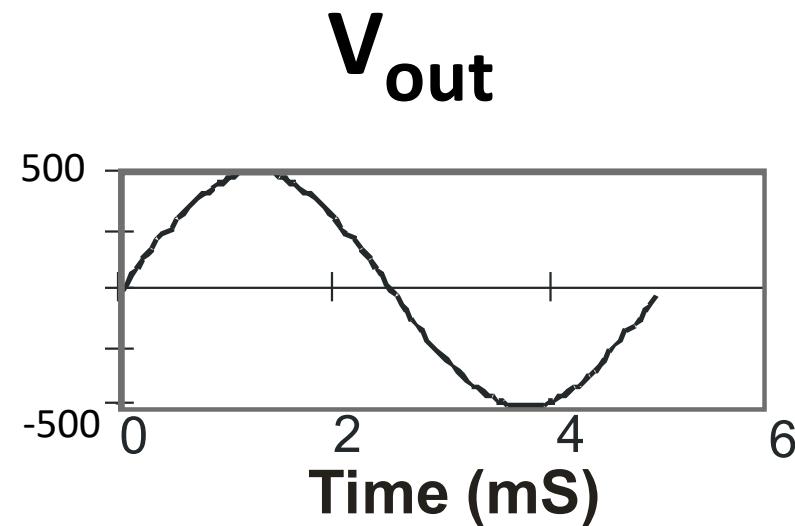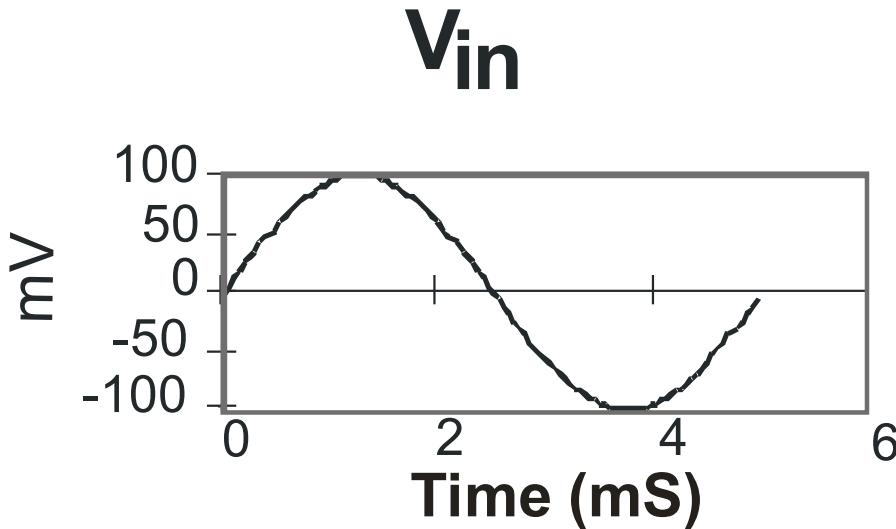


V_{in} is a sine wave with amplitude 200mV (peak-to-peak)

Q9: Design circuit such that:

V_{out} has a 1V (pk-pk) sine wave centered at 0V with same phase

Example Solution


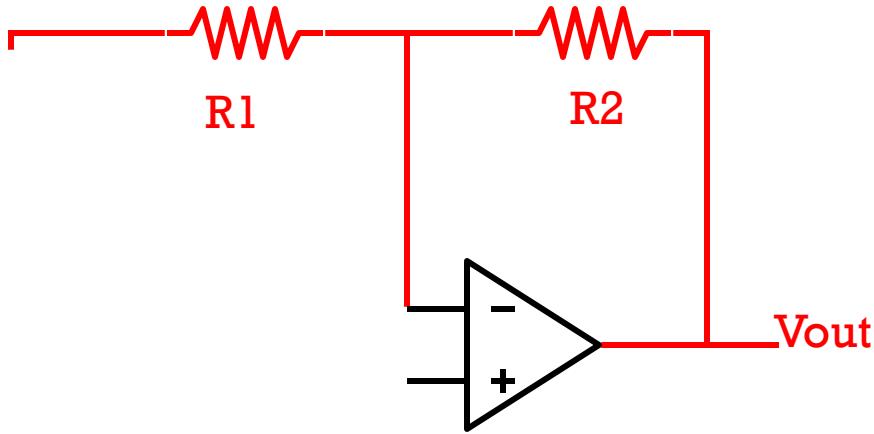


Example Solution

Op Amp Design Methodology

1. Decide inverting or not
2. Decide gain (V_{out}/V_{in})
3. Find offset
 1. Create current equation for node at $V(-)$
 2. Use ohm's law to introduce R_1 , R_2 , V_{out} , V_{in} and V_{offset}
 3. Pick a known value for V_{in} and V_{out} .
 4. Solve for unknown V_{offset} .

Example with offset

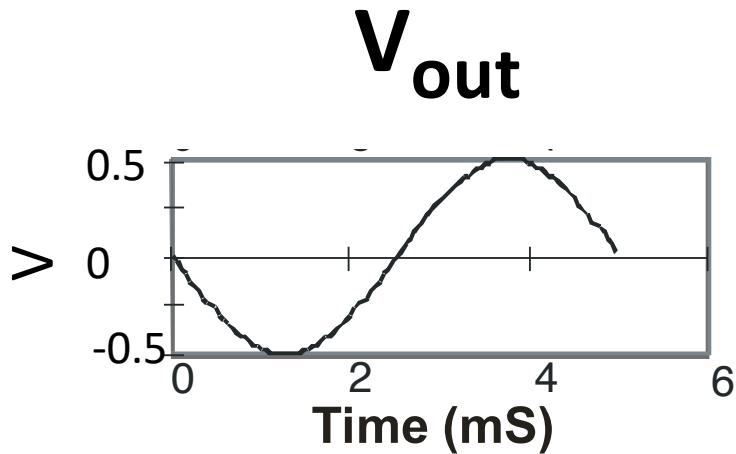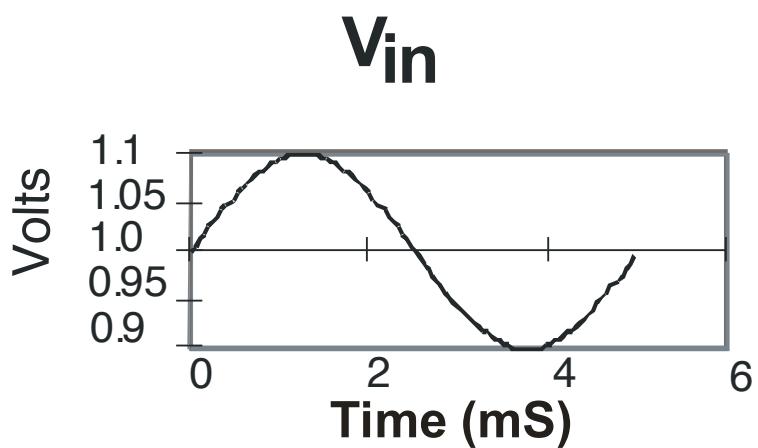

V_{in} sine wave with amplitude 200mV (pk-pk) centered on 1V

V_{out} should be a 1V (pk-pk) sine centered at 0V, 180° out of phase

Example with offset Solution

1) Inverting

2) Gain = $-R_2/R_1$

We want gain of 5

Consider a point, when

$V_{in} = 1.0V$, then $V_{out} = 0V$


$$i_1 = i_2$$

$$i_2 = \frac{V_{offset} - 0}{5R}$$

$$i_1 = \frac{1.0 - V_{offset}}{R}$$


$$V_{offset}(6R) = 5R - 0(R)$$

$$V_{offset} = 5/6V$$

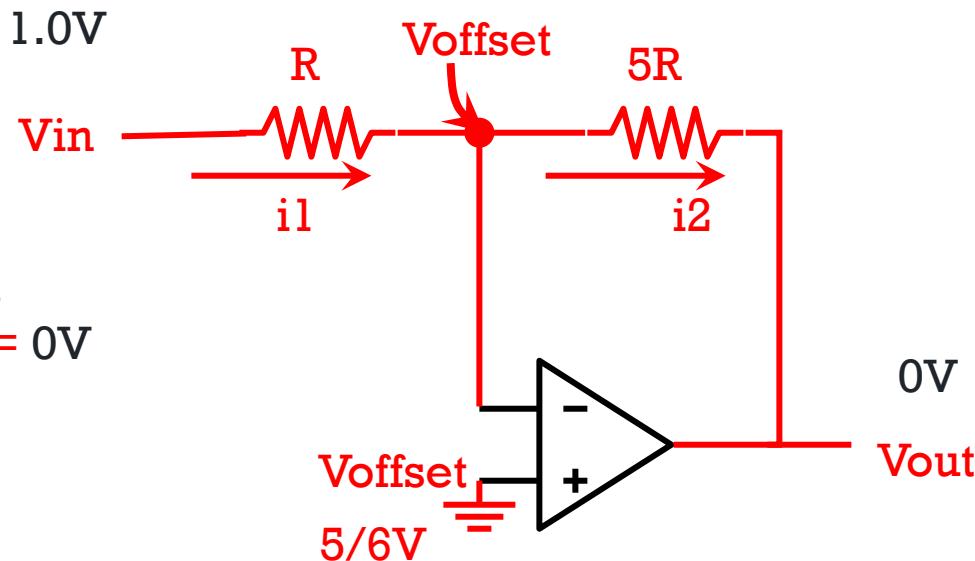

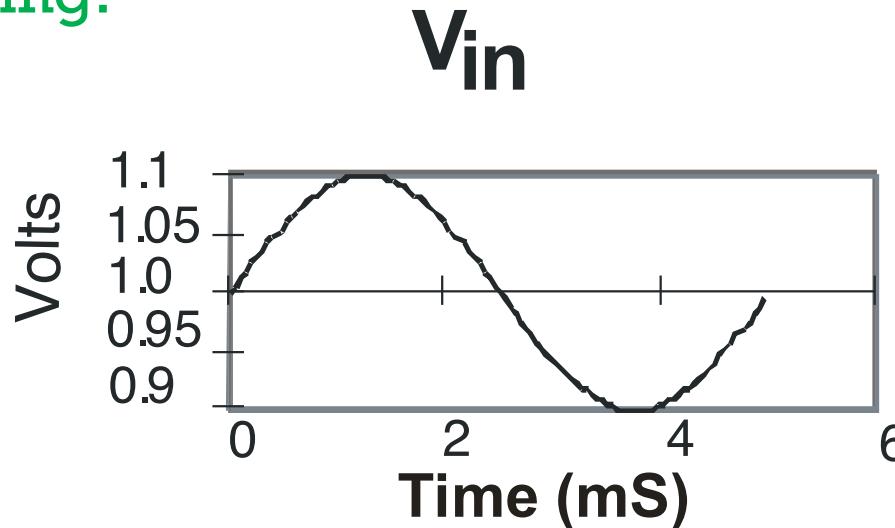Q10: Is there a way to center V_{out} about 0V leaving V_{offset} at 0 if the input is high frequency?

Practice problem: Design an opamp circuit for the following:



V_{in} sine wave with amplitude 200mV (pk-pk) centered on 1V

V_{out} should be a 5V (pk-pk) sine centered on 2.5V and in phase.

Summary

- Phototransistors can be used with just a resistor
- OpAmp Golden Rules:
 1. Inputs draw no current
 2. Inputs are at the same potential (in feedback)
- Signal conditioning includes **gain** and **offset**.
- Alternating signals of specific frequencies among ambient signals easier if you AC couple (add a capacitor in line).

Office Hour Discussion

Is there anything you found particularly useful or broken during office hours?

Use Raise Hand function in Zoom

Answer in CHAT

Answer how you feel about each topic below with:

1. I don't understand this topic at all
2. I understand a little, but will need help
3. I understand half, but expect to get the rest later
4. I understand completely already

A. Op Amps

B. Timer Input Capture


C. Phototransistors

Debugging Code

- If you feel you need help with C or programming in general.
<https://www.onlinedbg.com/>
- Has an online debugger that lets you track the flow of code.
- Note: ATmega specific things won't work (PORTD, Timers etc.)
- Looking into setting it up so we can actually debug ATmega code (e.g. put includes and fake stubs so things can compile).

Debugging Electronics

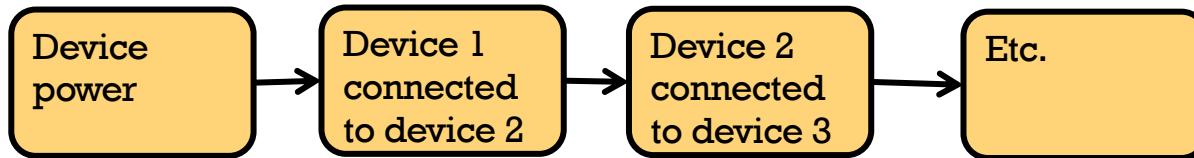- Hardware and Software piece - need to check both
- Break your system apart into pieces
 - viewed as linked via inputs and outputs
 - Ideally a chain of parts with 1 output from one part going to 1 input in the next part.



- Check known voltage at each part starting with power and ground.