

Lecture 05

Debouncing Switches,
Photosensors and Input
Capture

Agenda

00. Misc Lab 1 Issues: schematics

01. Capacitor Transient Behavior

02. Switches

03. Timer Input Capture

04. Photosensors

05. Phototransistors

Lab 1 issues:

- Toucan study hall not quite working.
 - Study groups: (private chat) Are you working with others, would you like to work with others.
- Ideal submission format:
 - One pdf file, with links to youtube or vimeo videos.
 - Later we'll ask for separate code that we can run.
- Programming using floats and ints

```
int i;  
float f;
```

```
i = 10;  
f = i/40;
```

```
int i;  
float f;
```

```
i = 10;  
f = i/40.0;
```

```
int i;  
float f;
```


```
i = 10;  
f = (float)i/40.0;
```

Promotion happens at evaluation

Drawing Circuit Schematics

- Connecting wires have big dot. (not jogs).
- Don't put 4 connecting wires at one point
- Label pin numbers on outside of symbol
- Use functional symbols - not wiring diagram
- Use standard symbol orientation
 - Gnd on bottom, Vcc on Top,
 - NPN w/emitter typically on bottom
- Signals input to output from left to right (typically)

Example

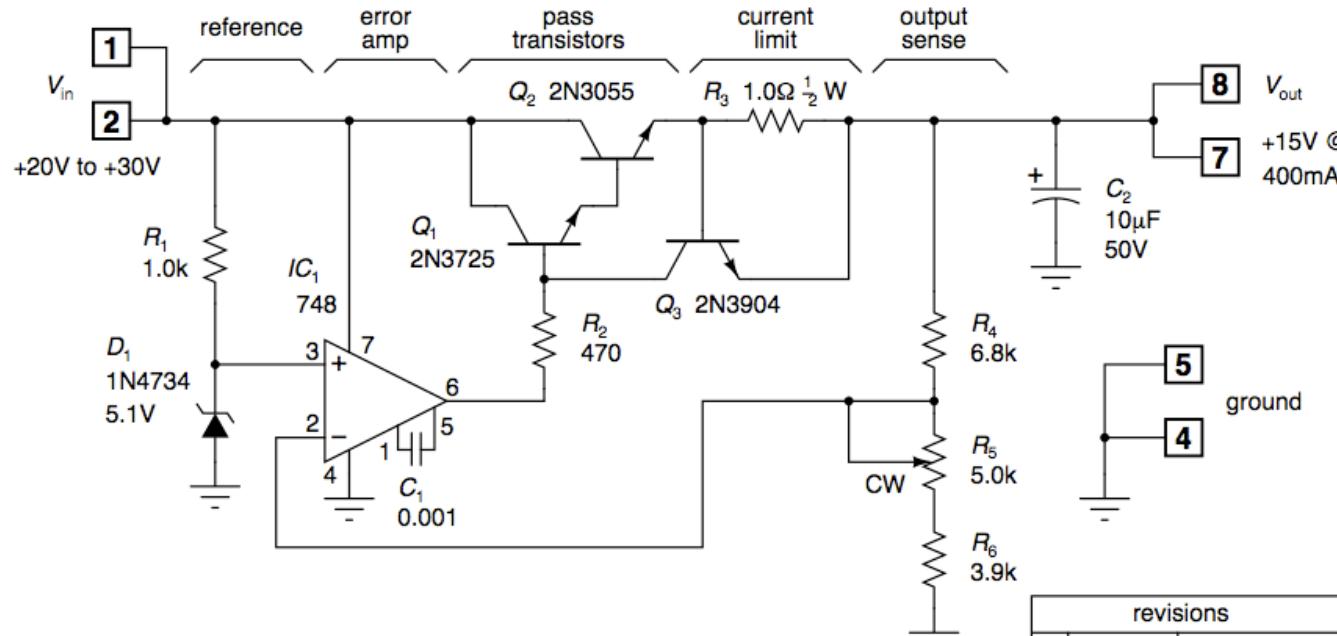

NOTES:

1. Q_2 on Wakefield 421AX heat sink
(18W at 600mA short circuit)
2. adjust R_5 for $V_{\text{out}} = +15.0 \pm 0.1V$
3. mates with cinch 50-10A-20

revisions

1	10-3-78	C_1 was 100pF
2		
3		

+15 volt regulator



drawn by	PH	9-16-78	ASSY NO.
checked by	WH	9-23-78	PS-15.4

01


Capacitor Transient Behavior



Capacitor Transient Behavior

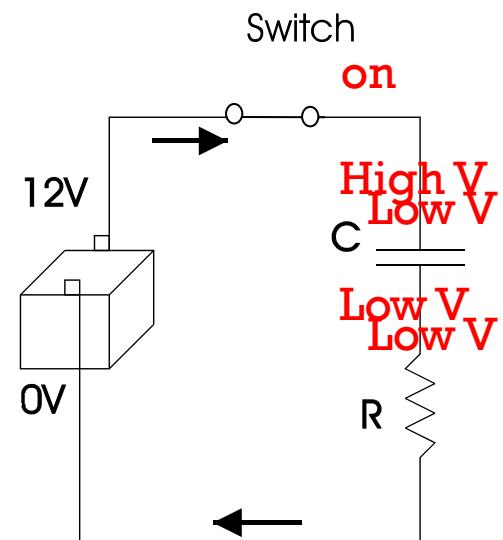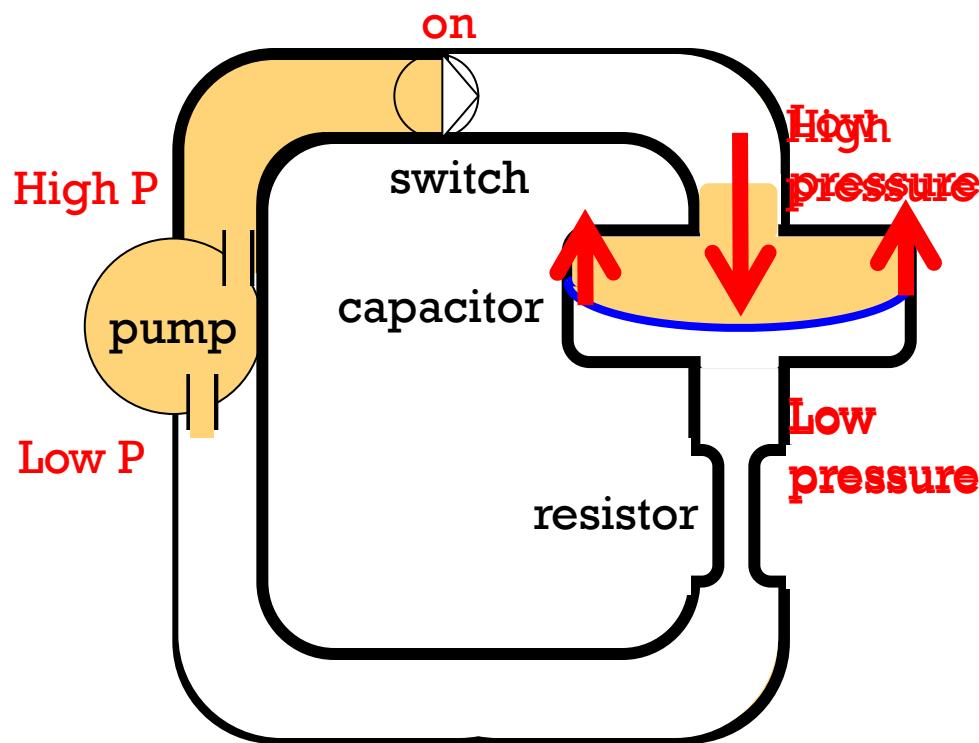

At Steady State, Full Capacitor

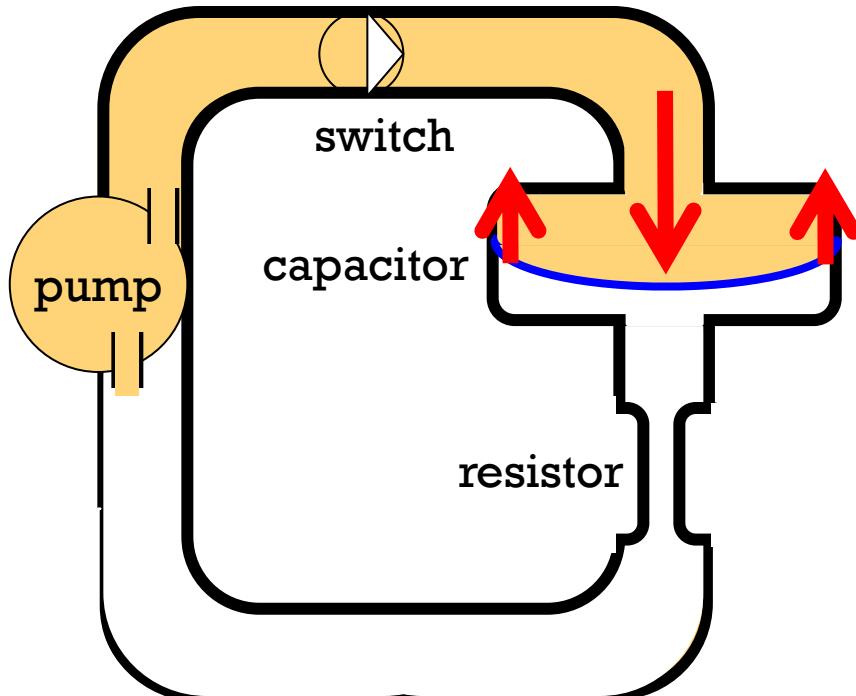

Membrane is fully stretched



Force on membrane up
equals force from pump
pressure down
Stops flow

No water crosses membrane
No electrons cross gap of
capacitor


Capacitor Transient Behavior

Q1: Draw & hold what happens to graph with larger C?

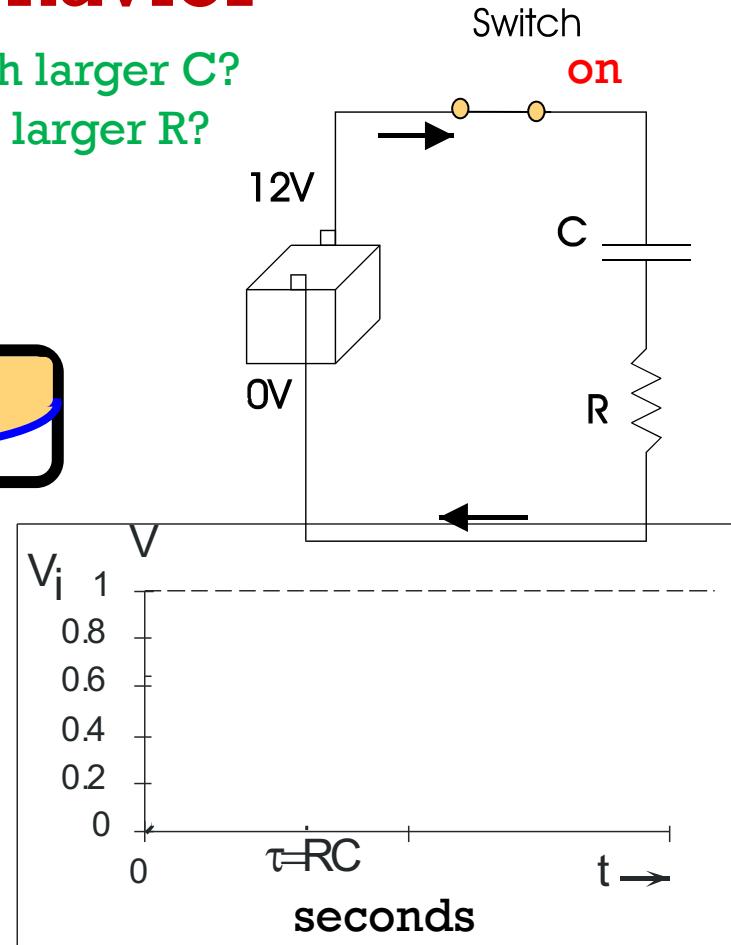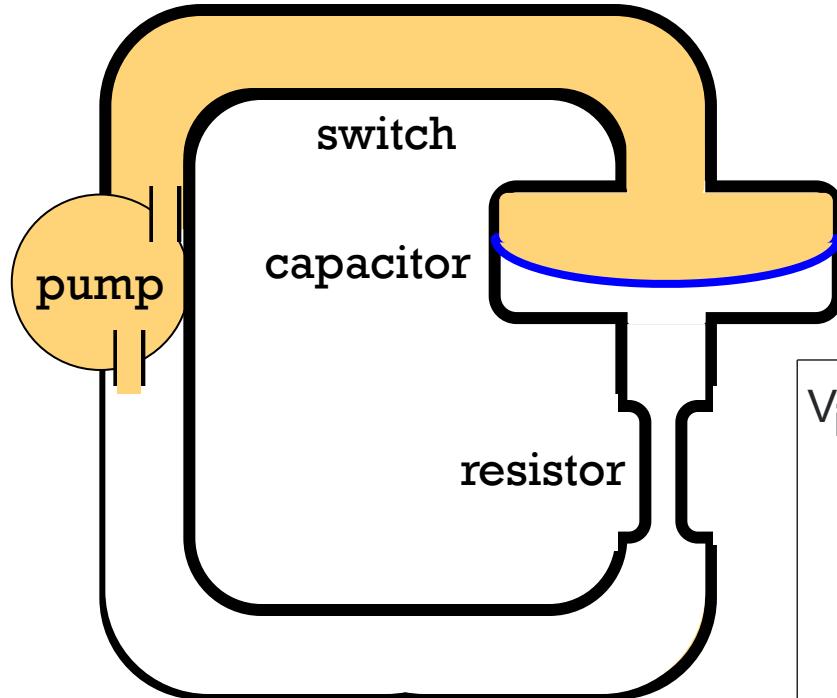Q2: Draw&hold what happens to graph with larger R?




Flow "through" capacitor

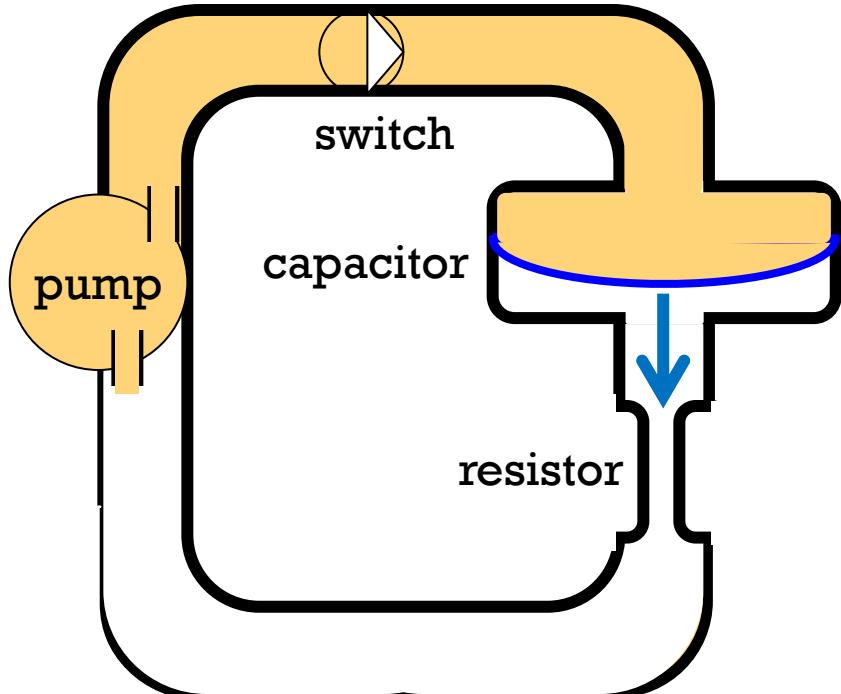

The initial motion of membrane pushes flow out of capacitor. How much depends on size of capacitor.


But it stops flow in steady state.

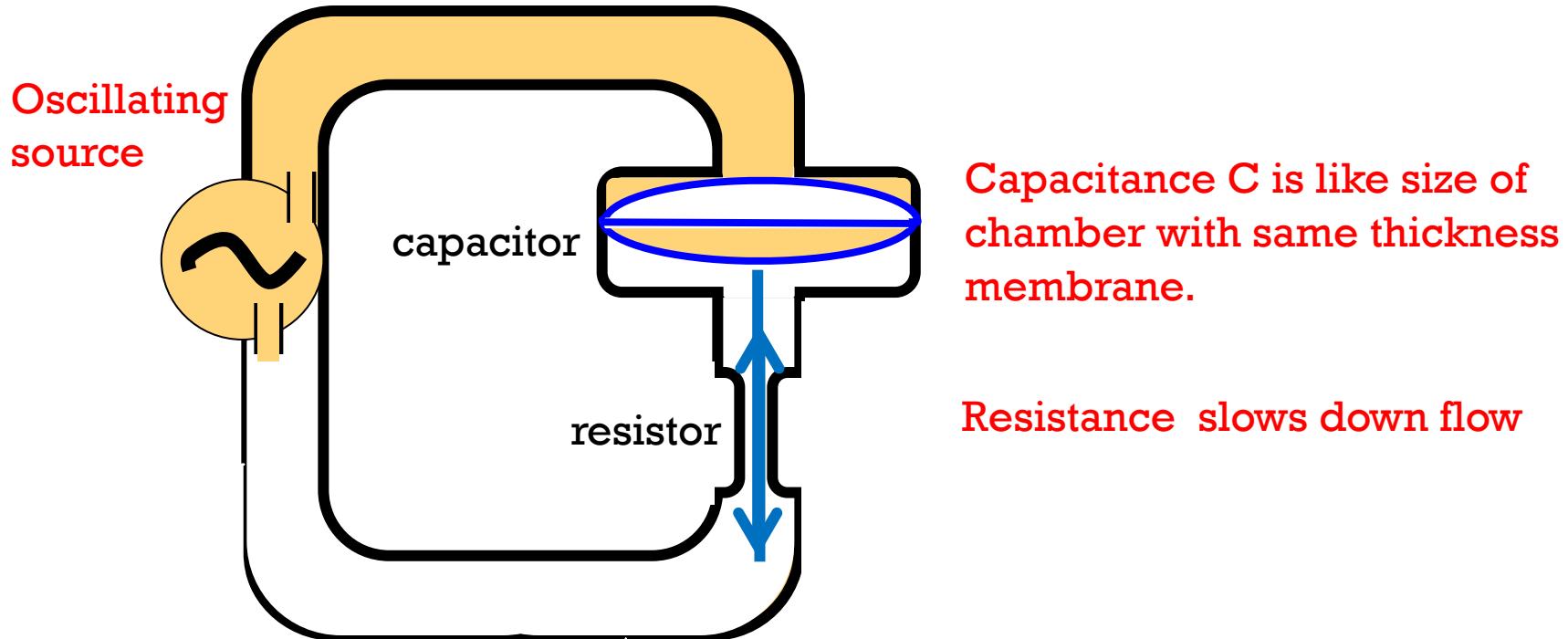Capacitor with oscillating voltage source




Combining oscillating signals


$$y = \sin(x)$$

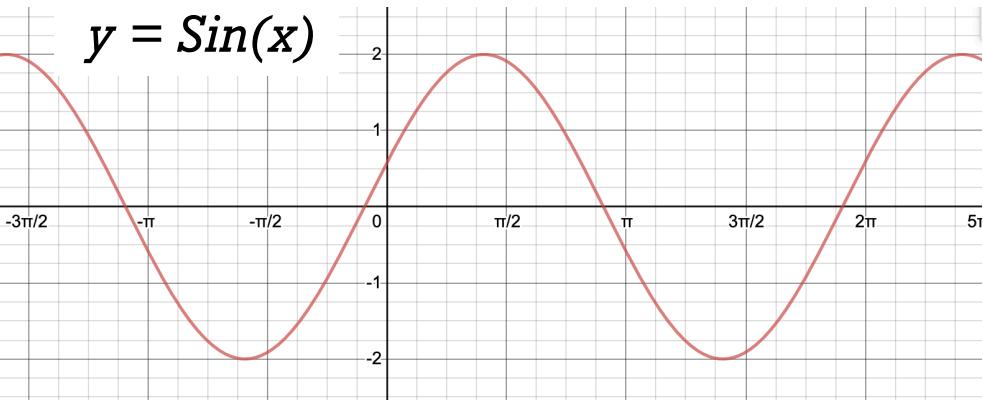


$$y = \sin(10x)$$

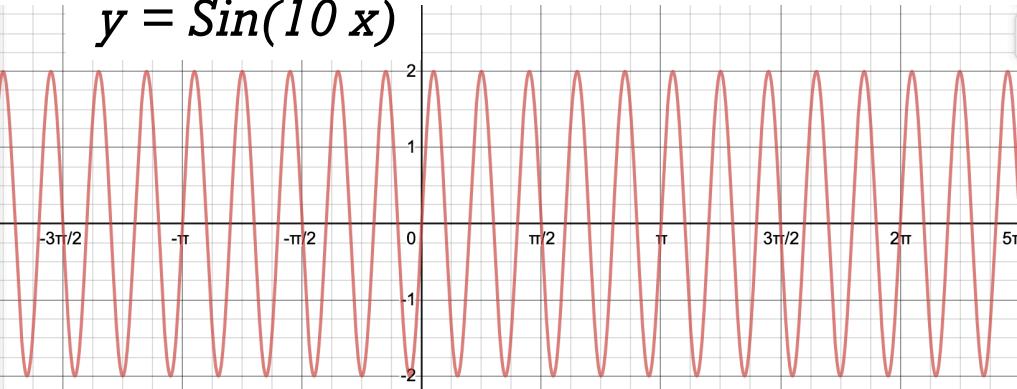

$$y = \sin(x) + \sin(10x)$$

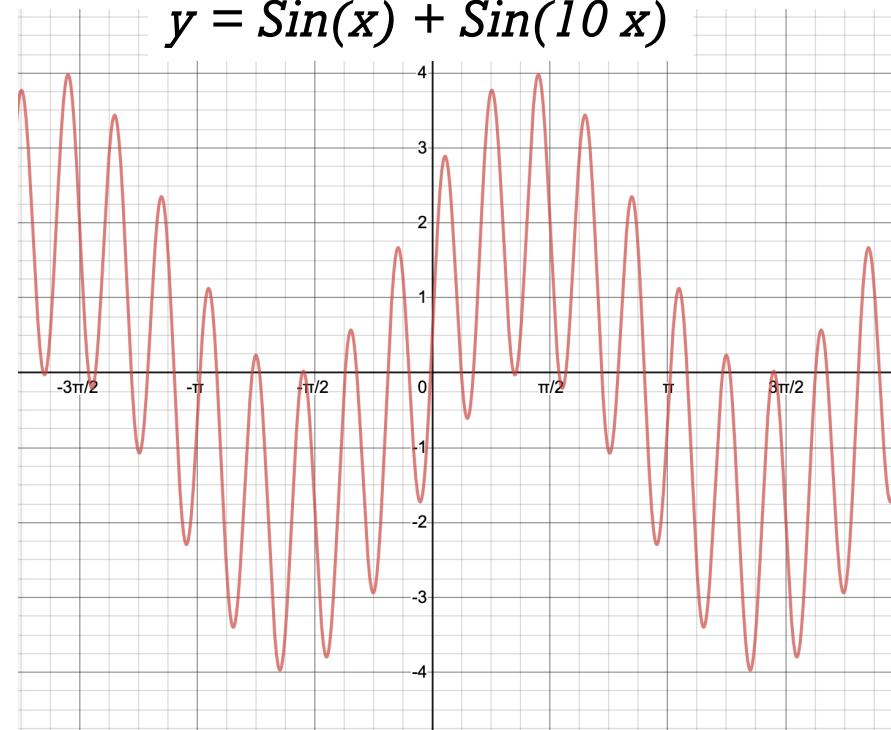

Capacitor in a filter

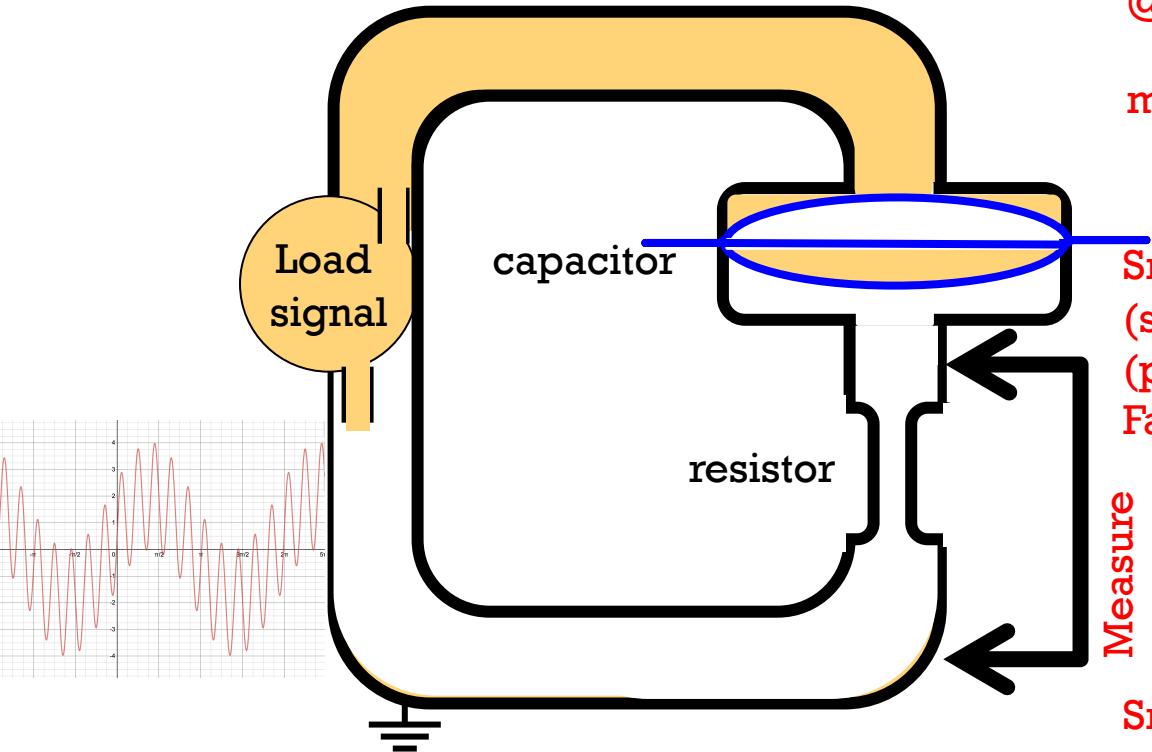


@ steady state: stops flow
(cap consumes voltage)

@ high freq: low resistance
(cap consumes DC, leaves all moving voltage for resistor)


High pass filter!

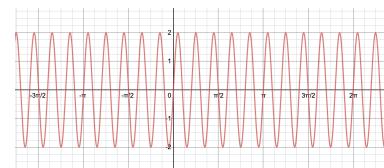Smaller C,
(stiffer membrane)
(pushes back w/less motion)
Faster time constant




Smaller R,
(More flow)
(allows more motion in C)
Faster time constant


Another filter configuration

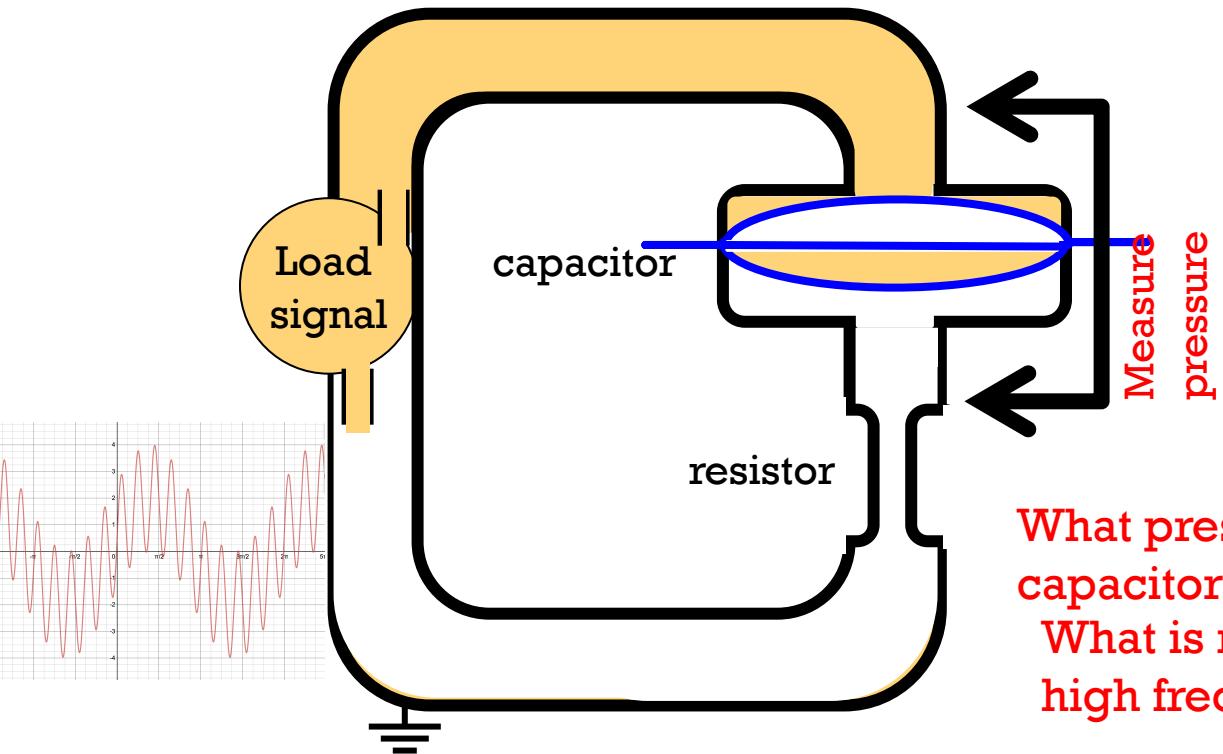

What pressure is measured across capacitor when signal is low freq?
What is measured when signal is high freq?

Low Pass filter!

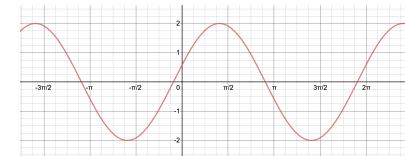


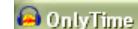

File Edit View Project Generate Effect Analyze Help




Audio filters work the same

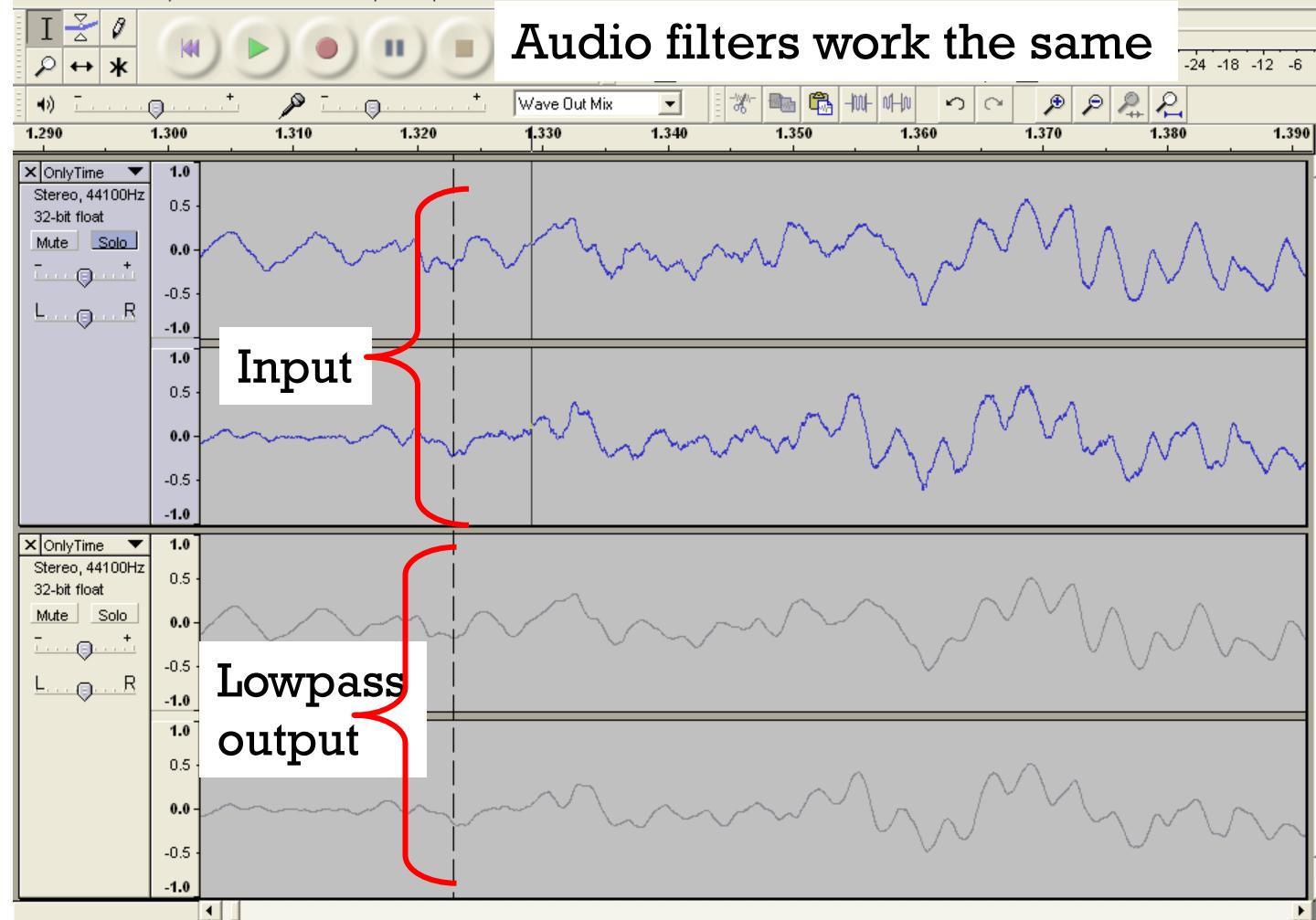


Capacitors in filters

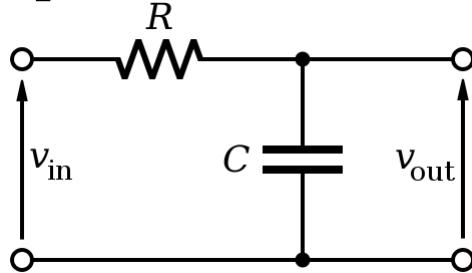- Two main configurations
 - Capacitors in parallel with source



Low Pass filter


- Capacitors in series with source

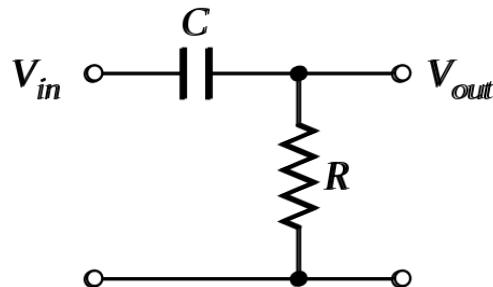

High Pass filter


Capacitors in filters

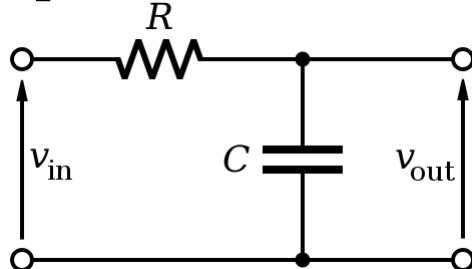- Two main configurations
 - Capacitors in parallel with source



Low Pass filter

- Capacitors in series with source

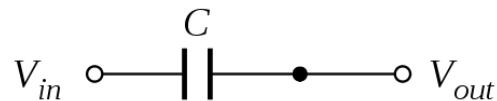


AC coupling




AC coupling

- Removes DC component.

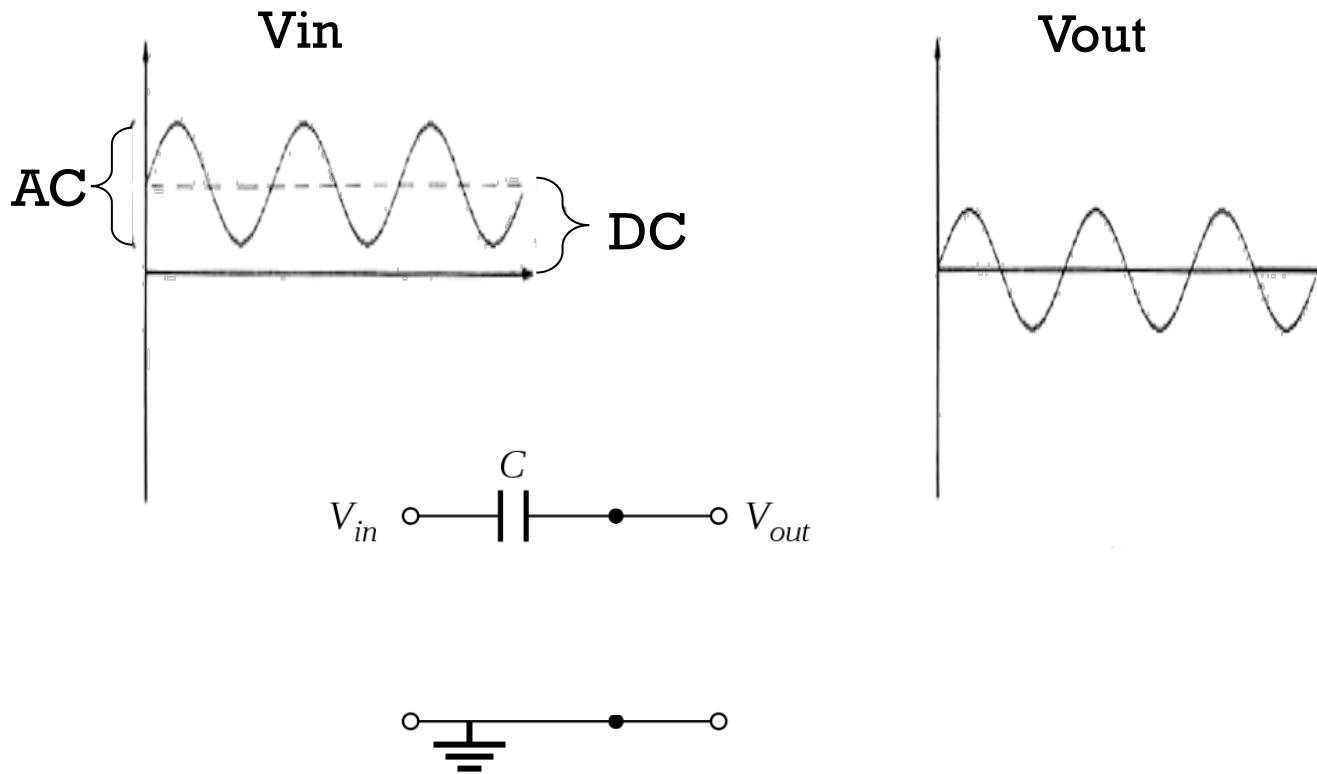


Filter effect on square wave

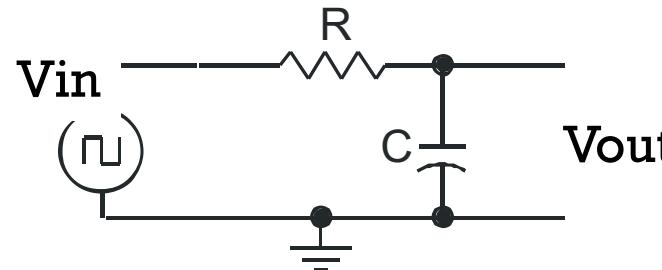

Low pass filter


$$V_{out} = V_{in} / \sqrt{1 + \omega^2 R^2 C^2}$$

(for sinusoid)

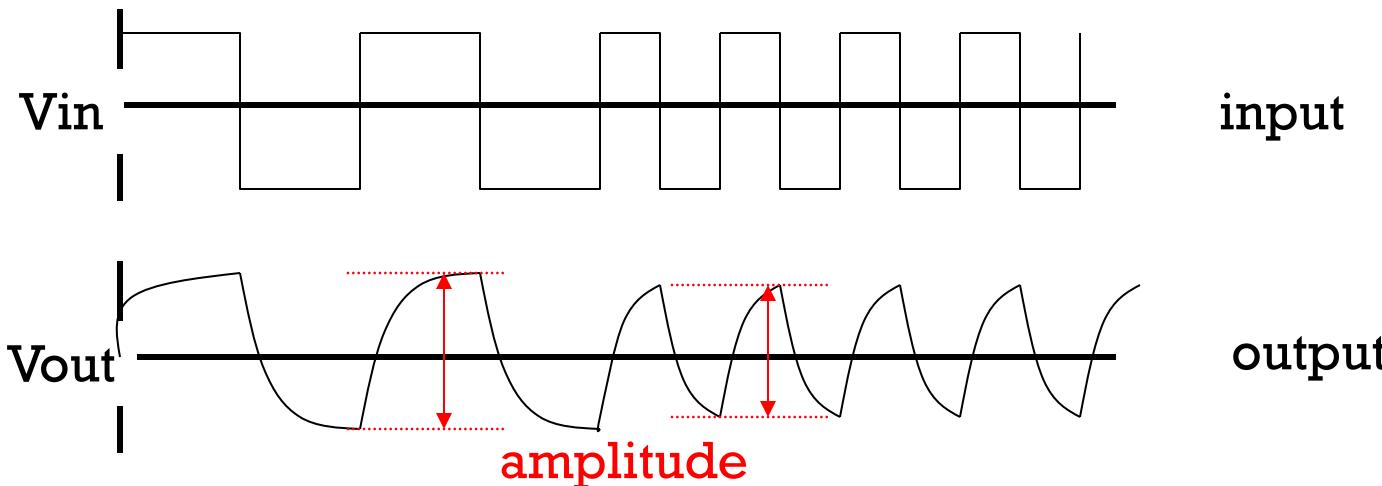


High frequencies are attenuated

The Frequency Domain

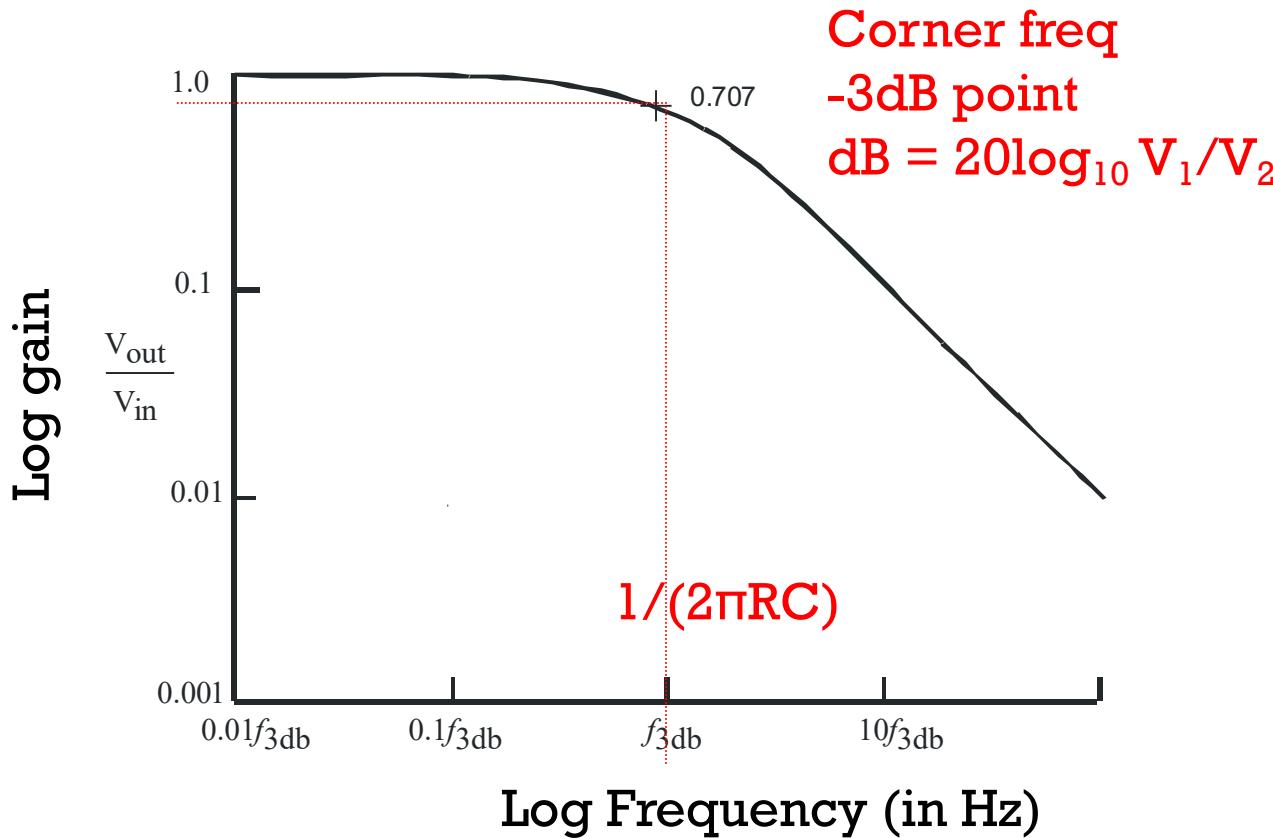

AC couple vs High Pass

$\sin(10x)$

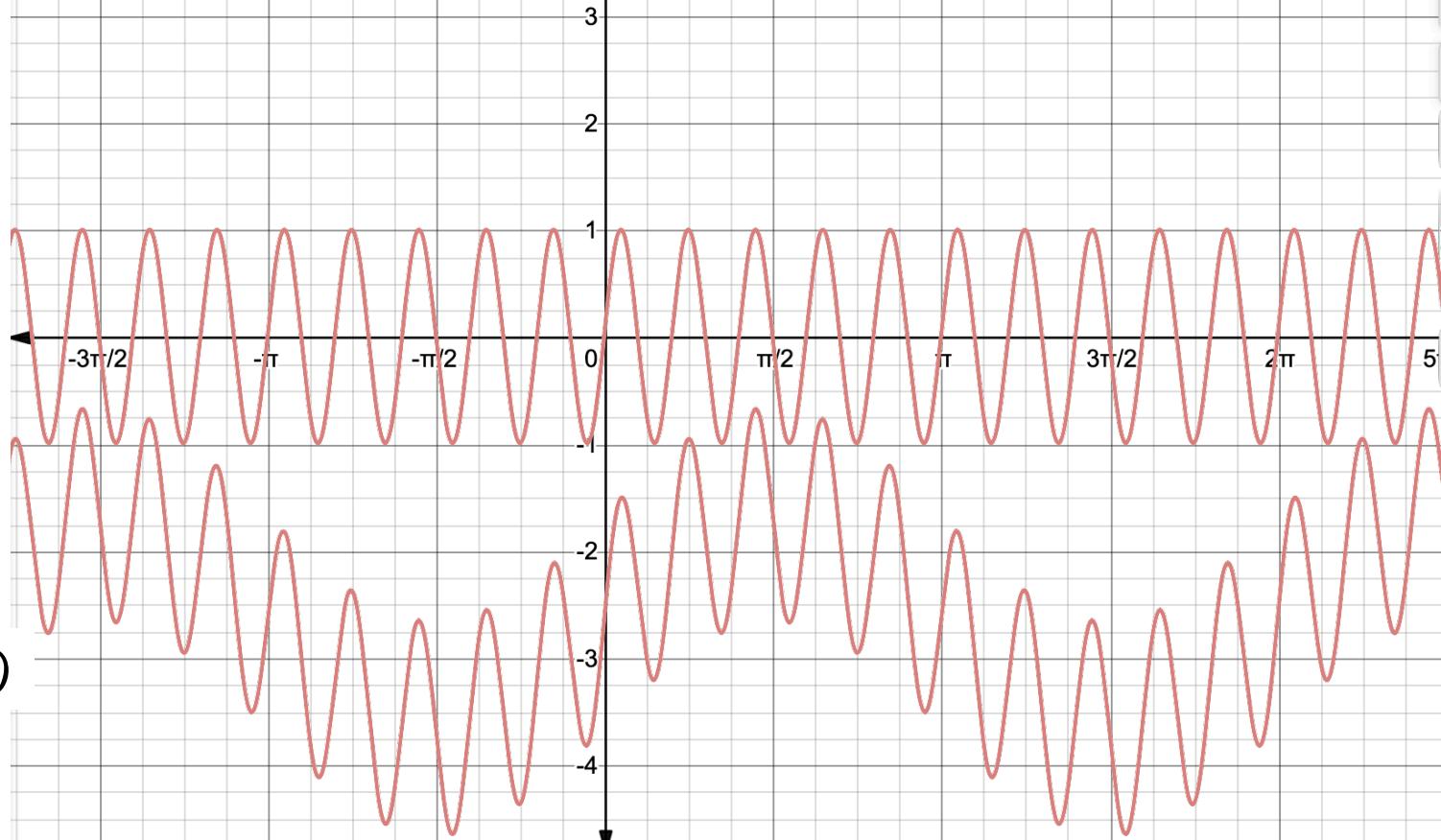

02





Switches




Switch Terms

Poles	# of circuits	Single pole (SP) Double pole (DP) Multipole (MP)
Throws	# of possible circuits	Single throw (ST) Double throw (DT) Multithrow (MT)
NC	Normally closed	
NO	Normally open	
Momentary	Switch holds state while held	
Toggle	Two stable positions	
Slide / Rocker / Push button	Type of action	

Switch Types

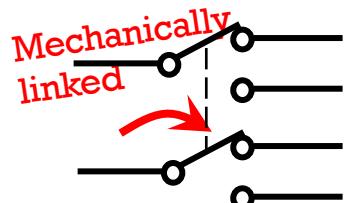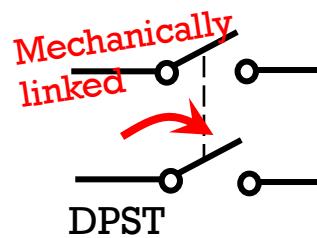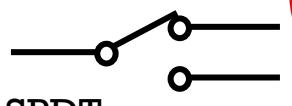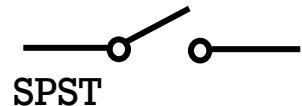

Rocker

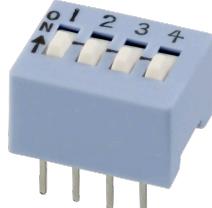


Slide




Toggle



Momentary

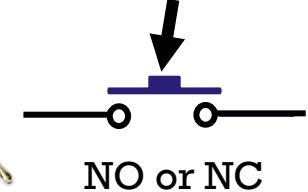

Limit switch

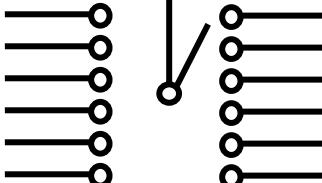



MPMT



Rotary


Switch bouncing

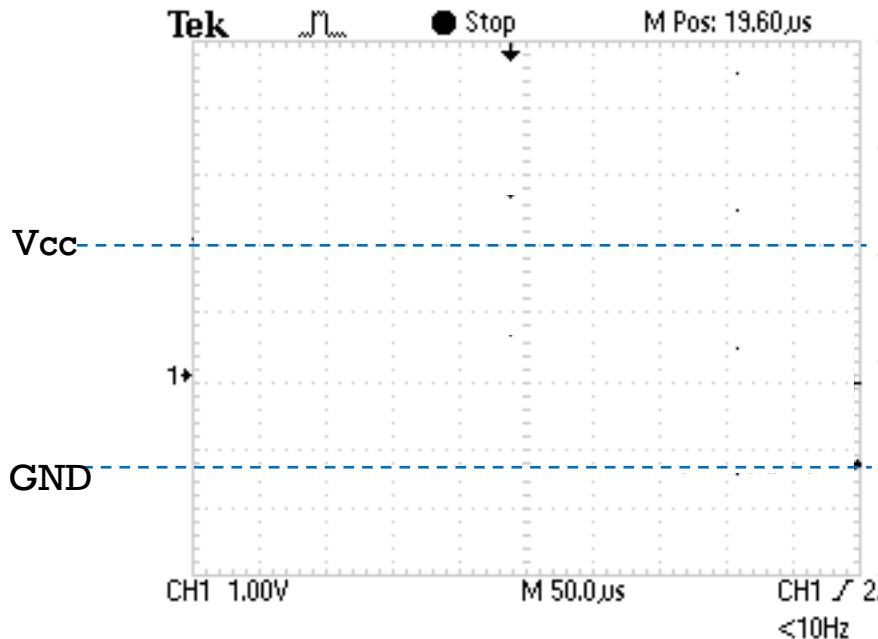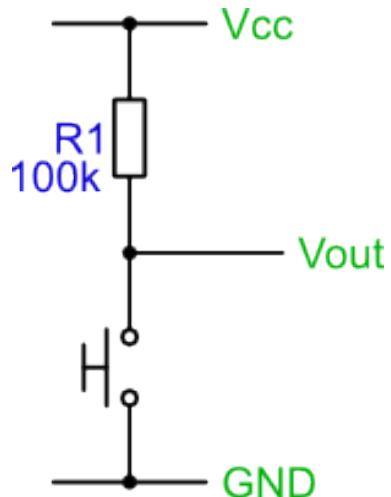Q3 Draw and hold what the scope will show as the button is pushed down?




Switch debouncing in hardware (RC)

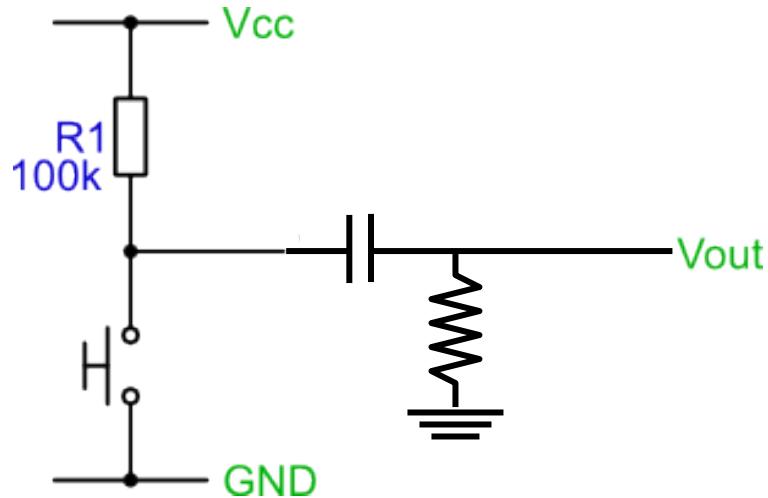Q4: Circle and hold the circuit that will debounce the switch



Circuit A

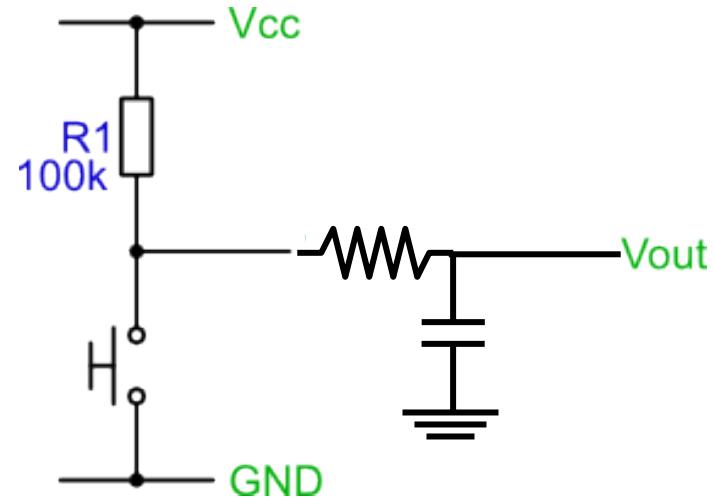

Circuit B

Detecting Button Presses



```
#include "teensy_general.h"
#include "t_usb.h"

#define PRINTNUM(x) m_usb_tx_uint(x); m_usb_tx_char(10); m_usb_tx_char(13)

void checkPC7() {
    int pinstate = bit_is_set(PINC,7);
    PRINTNUM(pinstate);
}

int main(){
    m_usb_init();      // init USB for print statements
    set(PORTC,7);     // turn on pull up on PC7

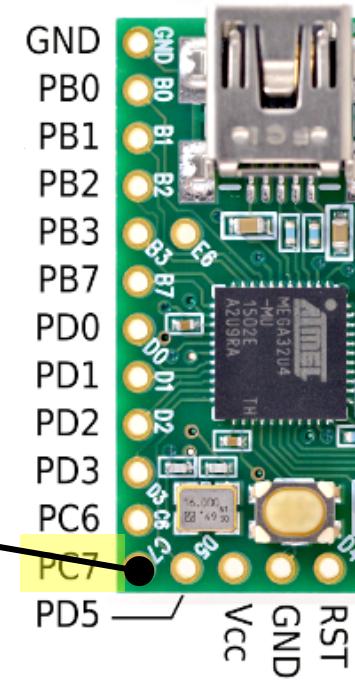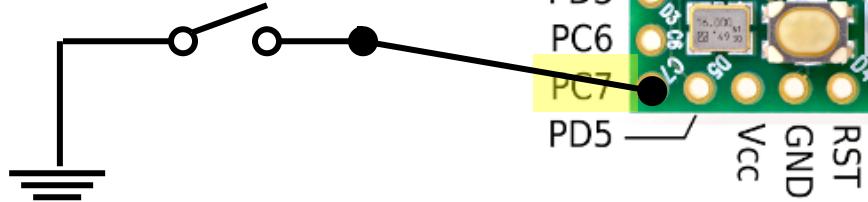    while(1) {
        checkPC7();
    }
}
```



Detecting Button (on/off) State Change

```
#include "teensy_general.h"
#include "t_usb.h"

#define PRINTNUM(x) m_usb_tx_uint(x); m_usb_tx_char(10); m_usb_tx_char(13)
```


```
void checkPC7() {
    int pinstate = bit_is_set(PINC,7);
    PRINTNUM(pinstate);
}
```

```
int main()
{
    m_usb_init();
    set(POR);

    while(1)
        checkPC7();
}
```

```
    void checkPC7() {
        static int oldstate;
        int pinstate = bit_is_set(PINC,7);

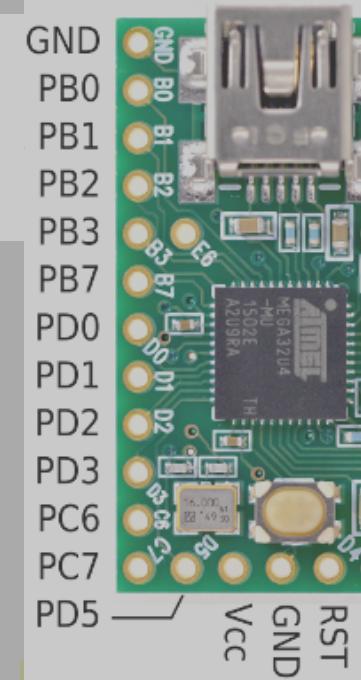        if (pinstate != oldstate) {
            PRINTNUM(pinstate);
        }
        oldstate = pinstate;
    }
}
```



03

Timer Input Capture



Timer Input Capture



- Recording a time stamp for events.
- Uses input functions on a pin combined with timer.
- Automatically and precisely captures timer with a hardware event.
- Can be more precise than polling.


Using Timer 3 to measure time of event (no input capture)

```
// same includes and #define as previous program...
void waitforpress() {
    while( bit_is_set(PINC,7)) ; // wait while PC7 is high
    while(!bit_is_set(PINC,7)) ; // wait until PC7 stops being low
    PRINTNUM(TCNT3);
}

int main(){
    m_usb_init(); // init USB for print statements
    set(TIMERBITS); set(MORETIMERBITS); // Start timer3 with /1024 prescaler
    set(PORTC,7); // turn on pull up on PC7


    while(1) {
        m_usb_tx_string("first hit ");
        waitforpress();
        m_usb_tx_string("second hit ");
        waitforpress();
    }
}
```

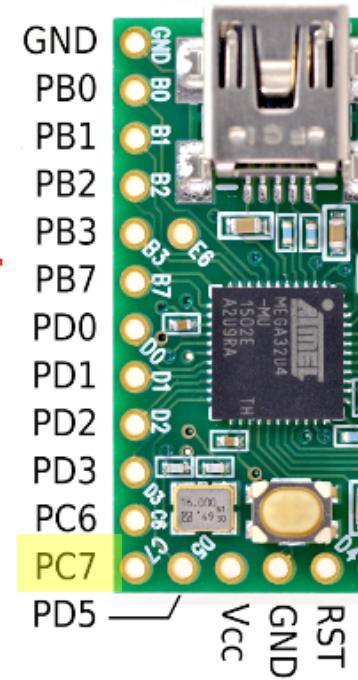DON'T COPY AND PASTE THIS CODE FOR LAB 2.
THERE ARE ERRORS IN THIS CODE



Timer/Counter Input Capture

“Free running” counter

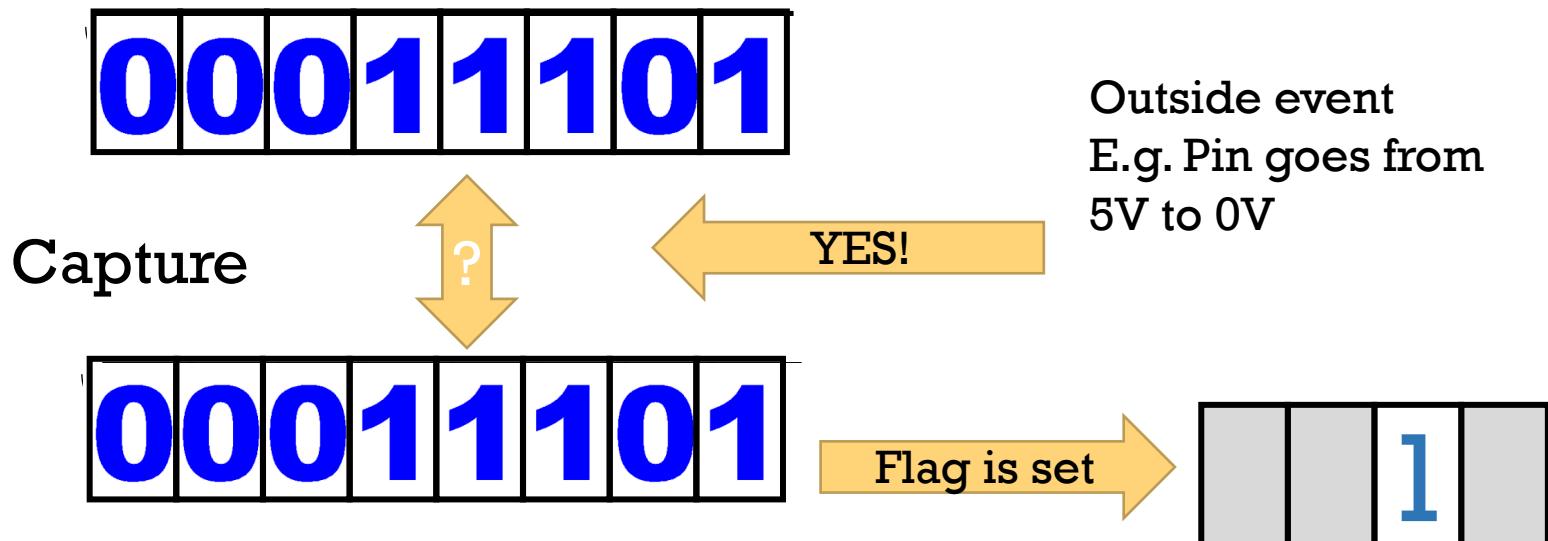


Input Capture Register

(Teensy has two 16bit registers ICR1, ICR3)

Input Capture Registers


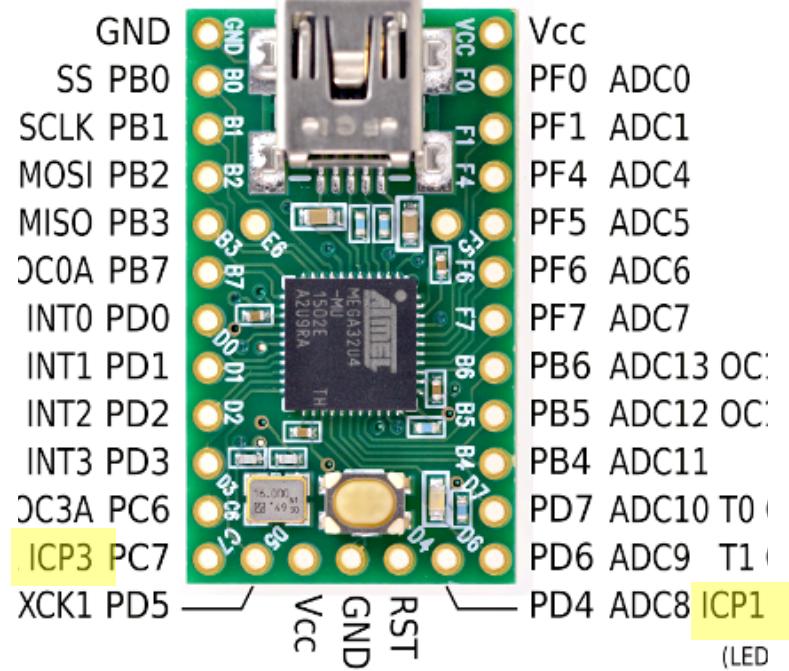
- Only need to start timer counting
- Two channels
 - Timer 1 ICP1 (Pin D4); ICR1 Register
 - ICF1 flag bit set in TIFR1
 - Timer 3 ICP3 (Pin C7); ICR3 Register
 - ICF3 flag bit set in TIFR3
- Options:
 - Rising or Falling Edge



Timer 1	Timer 3	Function
TCCR1B: ICES1	TCCR3B: ICES3	
0	0	store timer value on falling edge (default)
1	1	store timer value on rising edge

Input Capture on Timer 3 Example:

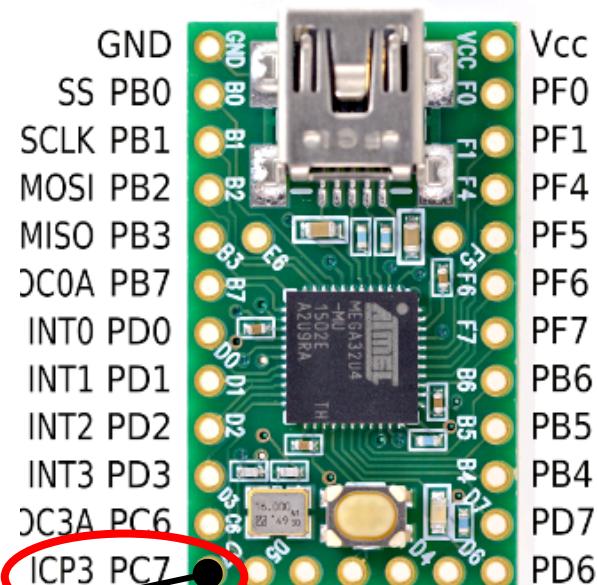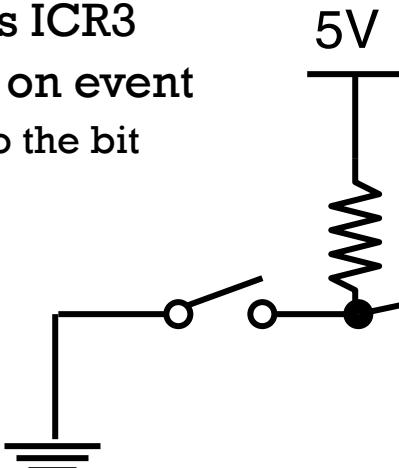- Use Timer 3 to printout time between two button presses
 - Switch to PC7 (also input capture pin ICP3)
 - Timer Input Capture Register is ICR3
 - IC Flag is set in TIFR3, bit ICF3 on event
 - Flag is cleared by **writing** a 1 to the bit



Using Input Capture to measure event

```
// same includes and #define as previous program...
void waitforpress() {
    while( bit_is_set(PINC,7)) ; // wait while PC7 is high
    while(!bit_is_set(PINC,7)) ; // wait until PC7 stops being low
    PR1NTNUM(TCNT3)
}
```

```
int main() {
    m_us_t m_us;
    set(m_us);
    set(m_us);

    while(1) {
        void dosomething() { // dummy routine to pretend that we have other things to do
            _delay_ms(500); // same as teensy_wait(500);
        }

        void waitforpress() {
            while(!bit_is_set(TIFR3,ICF3)) ; // check input capture flag
            set(TIFR3, ICF3); // clear flag by writing 1 to flag (!)
            PR1NTNUM(ICR3);
        }
    }
}
```

Timer Overflow

- What is the maximum time Timer 3 can contain?
 - Depends on clockspeed
 - We can slow down the system clock
 - We can prescale the clock into the timer
 - 16bit register (counts to 65535)
- Max timer prescaler is /1024
 - Without clockdivide -> 4.2

Onboard crystal @ 16MHz **0**

Clockdivide
E.g. /4

System clock @ 4MHz **0**

Timer prescaler
E.g. /2

Timer @ 2MHz

00000

- Q5: What do we lose by slowing down clock?

Using Input Capture to measure event

```
// same includes and #define as previous program...
void waitforpress() {
    while( bit_is_set(PINC,7)) ; // wait while PC7 is high
    while(!bit_is_set(PINC,7)) ; // wait until PC7 stops being low
    PRINTNUM(TCNT3)
}
```

```
int main() {
    m_us
    set()
    set()

    while()
        m_
        wa
        m_
        wa
    }

    void waitforpress() {
        while(!bit_is_set(TIFR3,ICF3)) dosomething();
        set (TIFR3, ICF3); // clear flag by writing 1 to flag (!)
        tperiod = ICR3-oldtime;
        oldtime = ICR3;
        PRINTNUM(tperiod); // time between hits
    }
}
```

Timer Register Wrapping Math Issue?

```
void waitforpress() {  
    while(!bit_is_set(TIFR3, ICF3))    dosomething();  
    set (TIFR3, ICF3); // clear flag by writing 1 to flag (!)  
    tperiod = ICR3-oldtime;  
    oldtime = ICR3;  
    PRINTNUM(tperiod);  
}
```

- Normally $ICR3 > oldtime$ as $ICR3$ is read after $oldtime$ has been stored and the timer is free running.

$tperiod = ICR3-oldtime;$

Q6: In Chat: What happens if $ICR3$ wraps (>65535) in the calculation? TCNT3 Overflow: Changes from $0xFFFF$ to $0x0000$

Timer Register Wrap Issue?

- 2's complement math takes care of this issue.
- TCNT and the variables are unsigned integers. They can't go negative.

When you subtract a larger int from a smaller int:

```
tperiod = ICR3 - oldtime;
```

It becomes the same as if the smaller number had 65536 added to it.


```
tperiod = 65536 + ICR3 - oldtime;
```

- Issue is if **more than one full** overflow has occurred.

04

Photosensors

Illuminance vs Flux

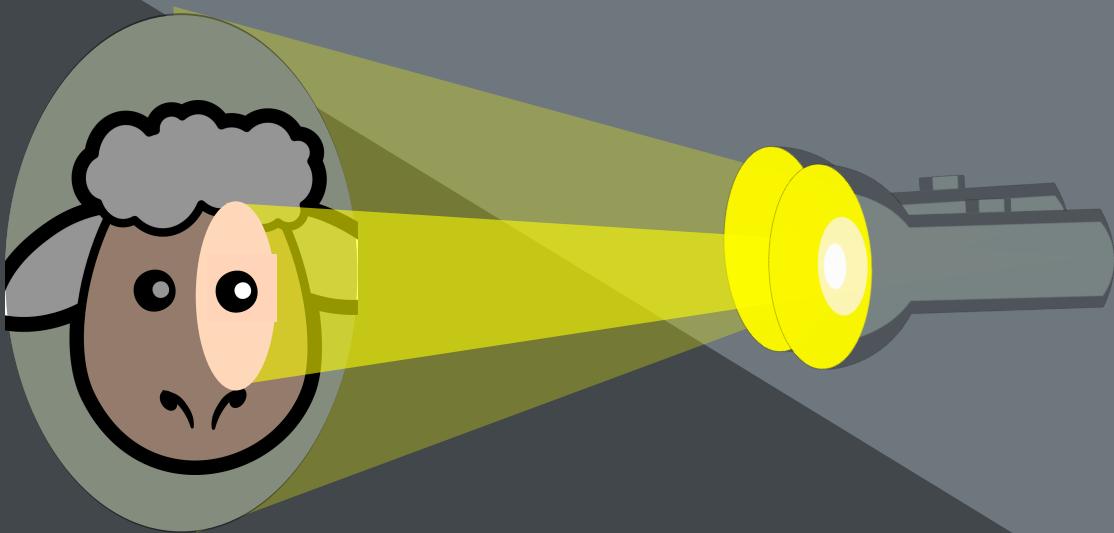


- Luminous Flux: **Lumens**
 - Visible light frequencies
- Radiant Flux: **Watts**
 - All frequencies
- Illuminance: **Lux**

Flashlight with “zoom lens”

- Same luminous flux (total light energy) (**Lumens**)
- Different brightness (**Lux**)

Order of Magnitude Examples

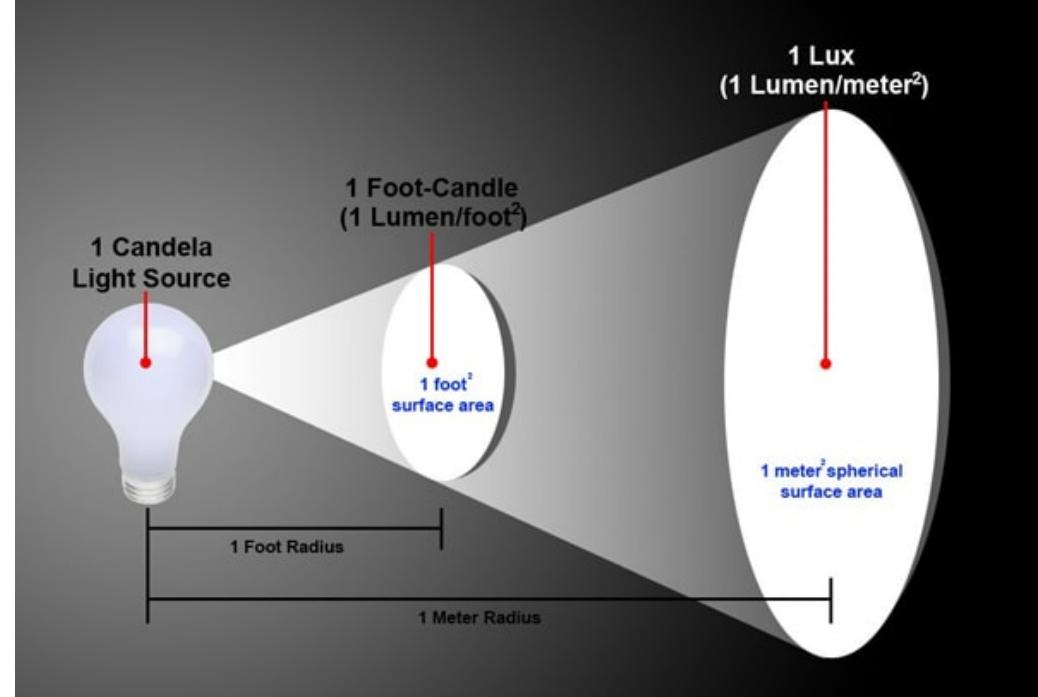


Low light
50 lux



Office
500 lux



Rain
10,000 lux

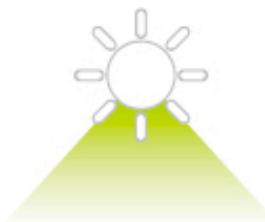


Direct Sun
100,000 lux

Light Frequencies

- Many semiconductor are sensitive or emit at infrared frequencies.

IR LED

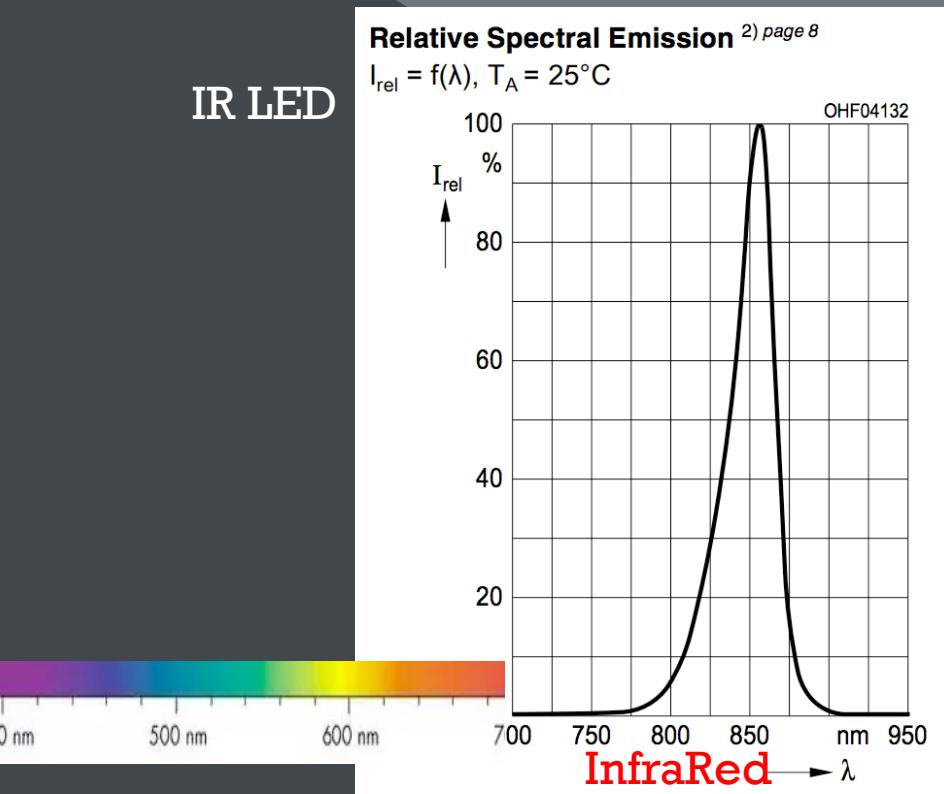

TEPT4400 PhotoTransistor

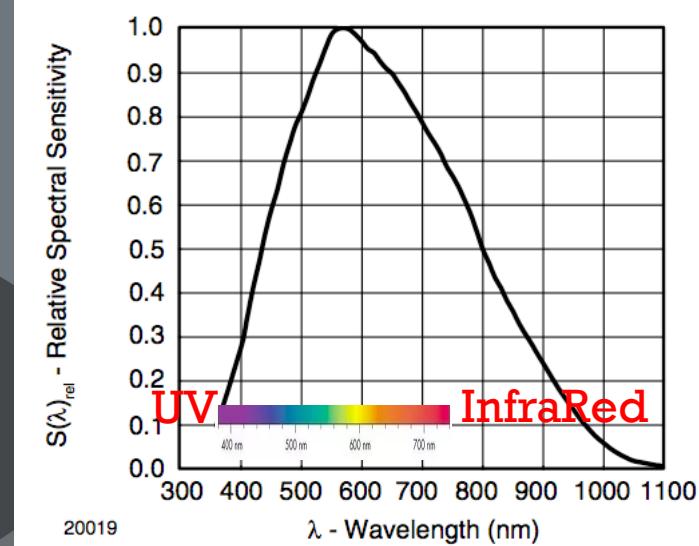


Fig. 7 - Relative Spectral Sensitivity vs. Wavelength

Phone camera IR debugging tool.



Photo Sensor Examples



- Phototransistor
 - Easy to use, relatively high sensitivity
 - Cheap and robust
- Photodiode
 - Very Fast (nS)
 - High dynamic range
- CdS photo cell
 - Color response like human eye
 - Very slow (~1-100mS)
- Photovoltaic cell
 - Linear response to incident light
 - Fragile
 - Slow (depending on size)


05

Phototransistors




BJT Transistors

Bipolar Junction Transistors

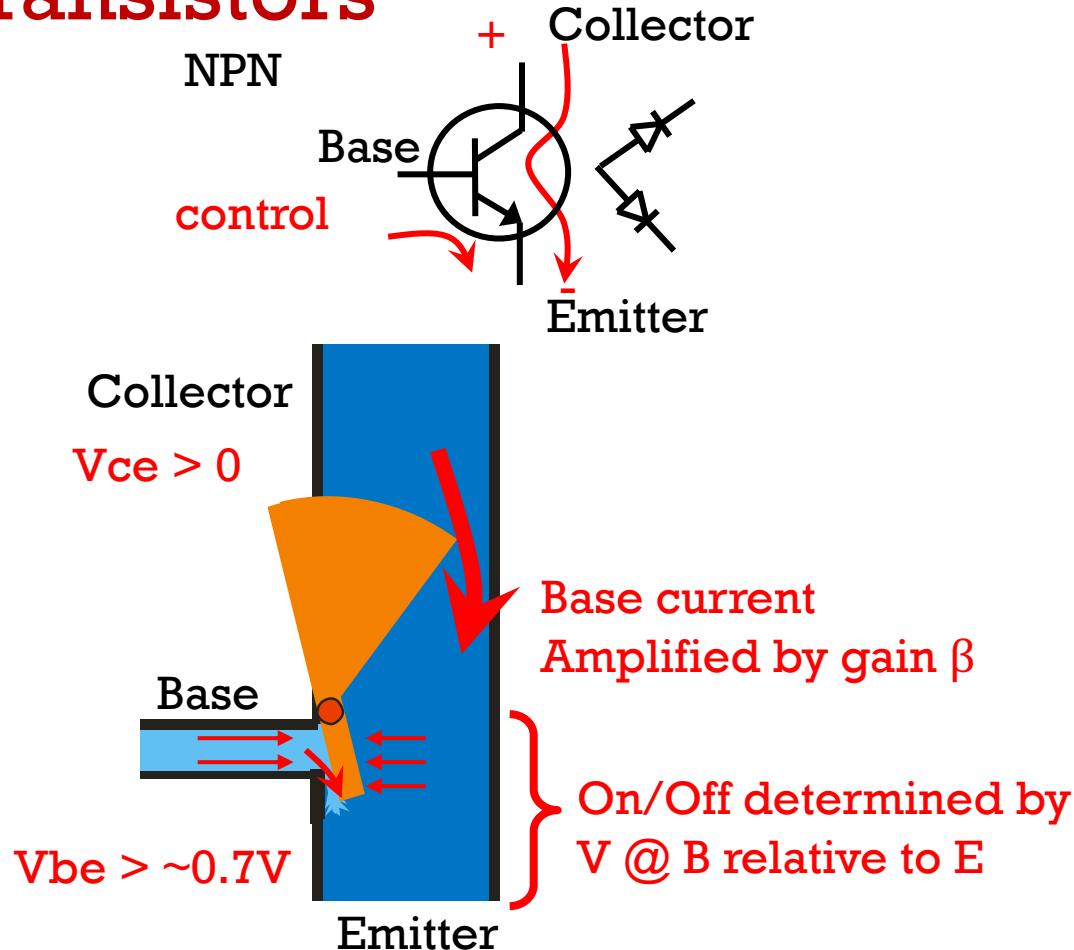


Phototransistors


NPN

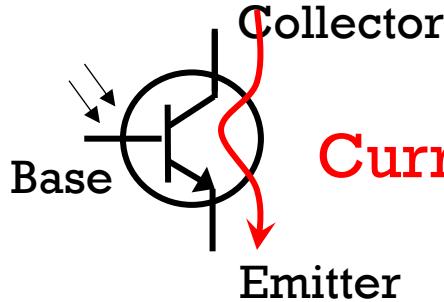

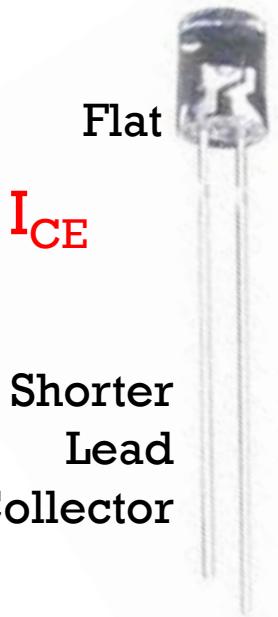
- Just two leads (no base)
 - Looks just like a diode...
- Light into base causes current to flow.
- If V_C is larger than V_E , (typically $> 0.4V$) then more light means more current I_{CE}




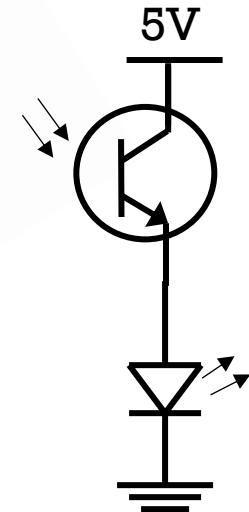
Q7: What happens if circuit is exposed to a bright room?



Phototransistors: How to use?



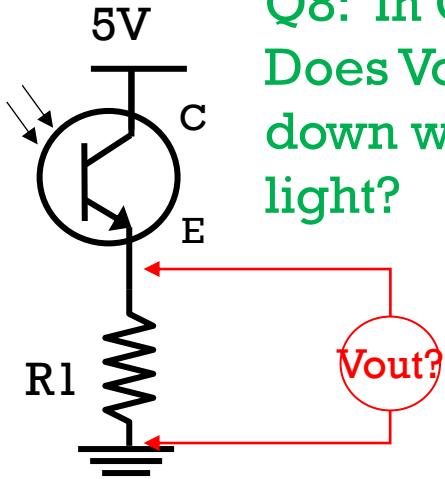


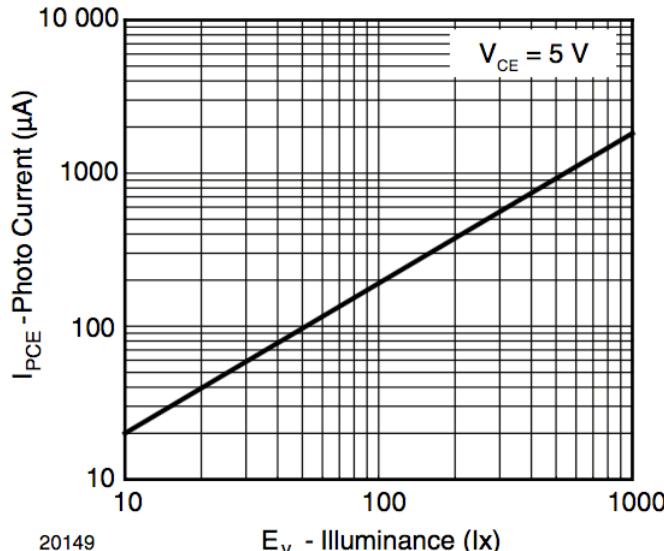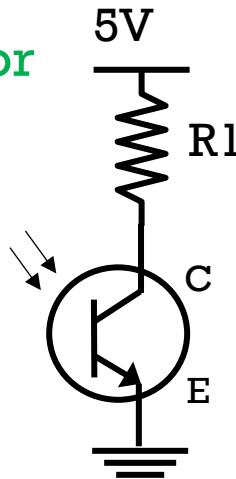Q8: In Chat
Does V_{out} go up or
down with more
light?



- Q9: In Chat: How does value of R_1 effect sensitivity?
- Q10: Can R_1 be too big?

Phototransistors: How to use?

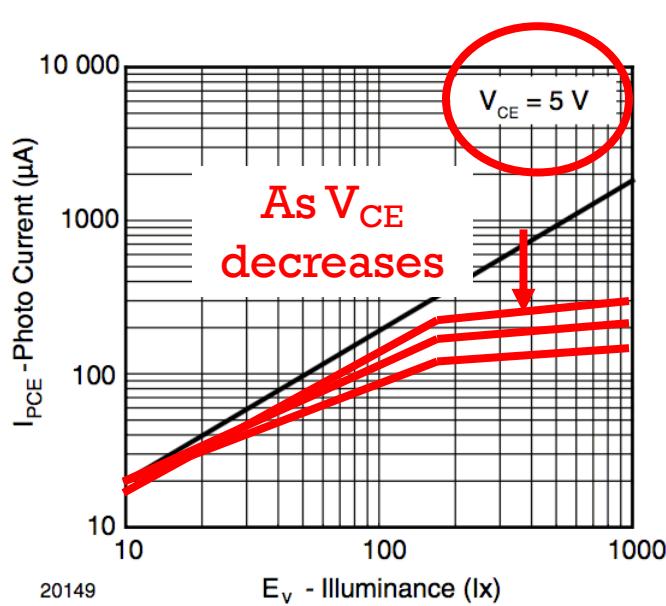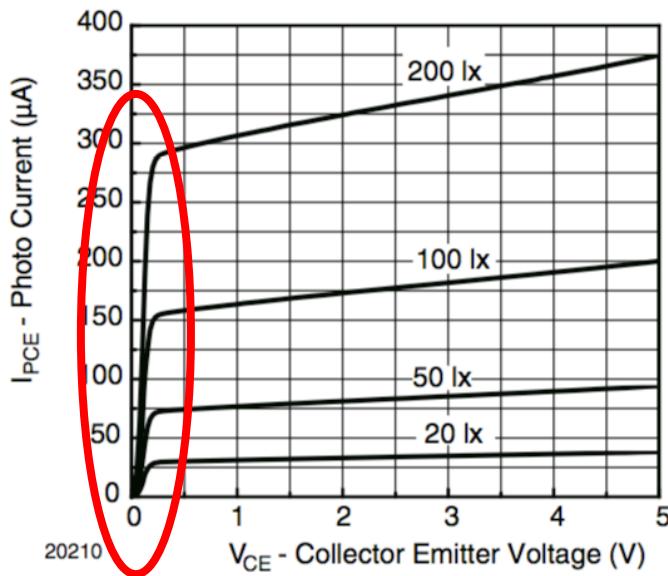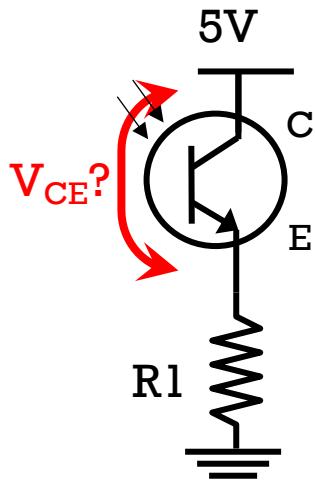

Summary

- Input capture can get high resolution timing independent of what processor is doing – as long as you handle multiple overflow and don't miss events.
- Phototransistors vary current (in voltage divider-like setup)
- Bigger resistances convert small currents to large voltages (ohm's law). Can increase gain on current output sensors. Opposite for resistance based sensors.

Answer in CHAT

Answer how you feel about each topic below with:

1. I don't understand this topic at all
2. I don't know now, but know what to do to get by
3. I understand some, but expect to get the rest later
4. I understand completely already


- A. Capacitors Highpass/Lowpass
- B. Timer Input Capture
- C. Phototransistors

Debugging Code

- If you feel you need help with C or programming in general.
<https://www.onlinegdb.com/>
- Has an online debugger that lets you track the flow of code.
- Note: ATmega specific things won't work (PORTD, Timers etc.)
- Looking into setting it up so we can actually debug ATmega code (e.g. put includes and fake stubs so things can compile).

Debugging Electronics

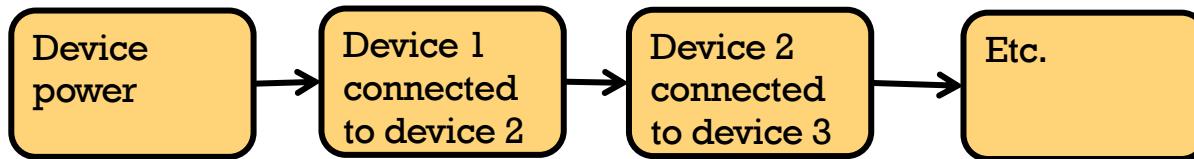- Hardware and Software piece - need to check both
- Break your system apart into pieces
 - viewed as linked via inputs and outputs
 - Ideally a chain of parts with 1 output from one part going to 1 input in the next part.



- Check known voltage at each part starting with power and ground.