

Lecture 04

Logic Input/Output

Pullup Resistors

Agenda

00 . Misc Teensy stuff

01. Logic Gates

02. Digital Input / Logic Levels

03. Pullups

04. Schmidtt Triggers

Stuff

- 9/5-9/11: **67** students tested positive for COVID19
- **Interactive Questions** – incentive for fast and correct
 - End of course prizes: most often 1st 10 correct answers
- **Acronyms on Piazza** – don't worry about registers acronyms.
 - <http://medesign.seas.upenn.edu/index.php/Guides/Teensy>

Sample C code

```
/* Name: main.c
 * Author: <insert name here>
 * Copyright: <insert your copyright message here>
 * License: <insert your license reference here>
 *
 */
/* Project: put project name here or lab number...
 * Author: Thomas Edison
 * Copyright (C) 1883 Thomas Edison - All Rights Reserved
 *
 * You may use, distribute and modify this code under the
 * terms of the GNU GPLv3.0 license.
 */
```

Teensy Clock speed

Clock Speed:

- The default speed of the Teensy might not be 16Mhz. It might be 8Mhz (based on hardware fuses burned in by the PJRC). Add this line to be sure it is 16Mhz. (see pg 39 on atmega docs on canvas)

```
teensy_clockdivide(0);
```

teensy_wait();

- Uses a built_in macro. It cannot take variables, so wrap `teensy_wait(1);` in a for loop if you want variable delay times. (assume 16Mhz clock)

Printing via USB

- Download `t_usb.h` and `t_usb.c` from
<http://medesign.seas.upenn.edu/index.php/Guides/MaEvArM-usb>
- Put `t_usb.c` in `src/` directory and `t_usb.h` in `inc/`
- Add `#include "t_usb.h"`
- Use *realterm* on GMlab PC's. Download *putty* for PC or mac or use *screen* on mac. (Need to find `/dev/tty.usbmodem####`)
- Must initialize the USB before it will work
 - `m_usb_init();` // put this near top of code
- Example print statements for debugging.
 - `m_usb_tx_string("inside for loop\n");`
 - `m_usb_tx_hex(PORTD);` // prints the status of the port
 - `m_usb_tx_int(x);` // x is an integer variable


Printing via USB on Teensy example

```
#include "teensy_general.h"
#include "t_usb.h"
int main(void)
{
    int count=0;
    teensy_clockdivide(0); //set the clock speed
    teensy_led(ON);        // turn on the on board LED
    m_usb_init();

    for(;;){
        /* insert your main loop code here */
        teensy_led(TOGGLE); // switch the led state
        teensy_wait(1000);   // wait
        m_usb_tx_string("\ncount ");
        m_usb_tx_int(count++);
    }
    return 0; /* never reached */
}
```

Using OscilloSorta with 5V signals

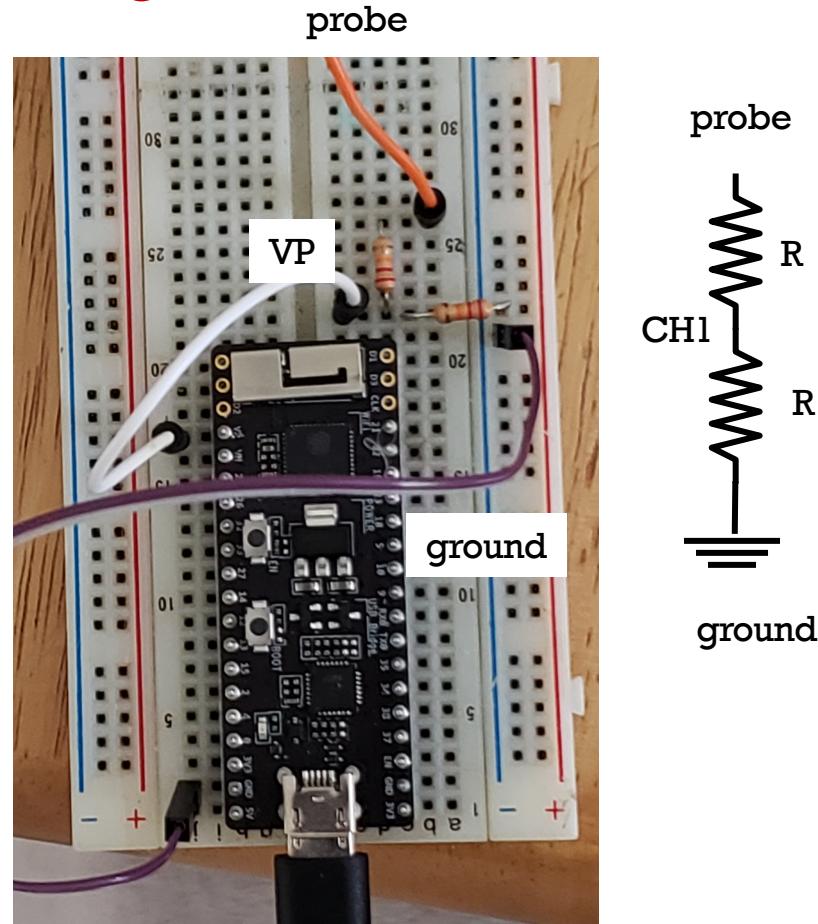- OscilloSorta only measures upto 3.3V, use a voltage divider to scale output. Just remember to multiply readings by the ratio.
- E.g. 2:1 voltage divider can measure upto 6.6V -> multiply scope readings by 2
- Tutorial and instructions:
Files->resources->Lab 0 Extras->
OscilloSorta V1.1 Tutorial.pdf





01

Digital Input Logic Levels

Digital Input

- We can set a pin on a port to be INPUT we can read whether something is controlling that pin to be HIGH or LOW.


PORTD

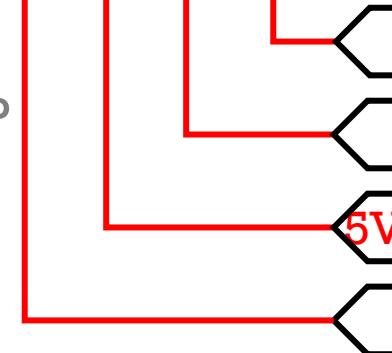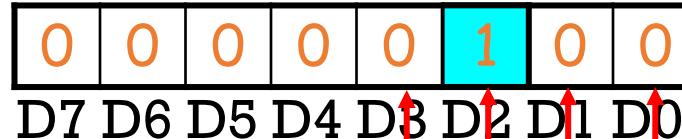

- What register would seem natural to read to check the PD2?



```
clear(DDRD,2);
if (PORTD == 0x04)
    dosomething();
```

- This doesn't work for the ATmega32U4.

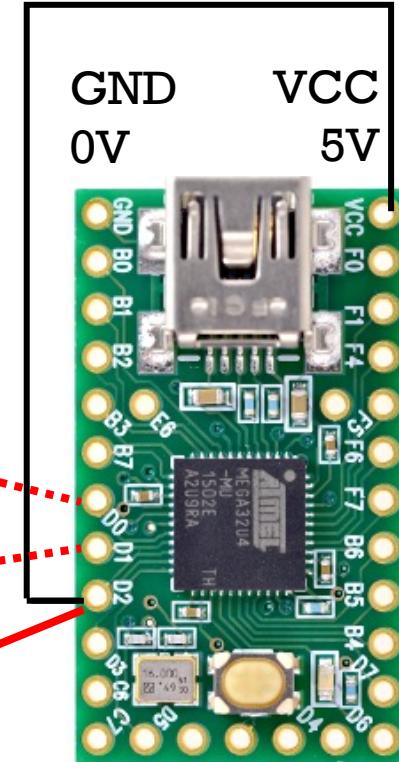

Digital Input on ATMEGA32

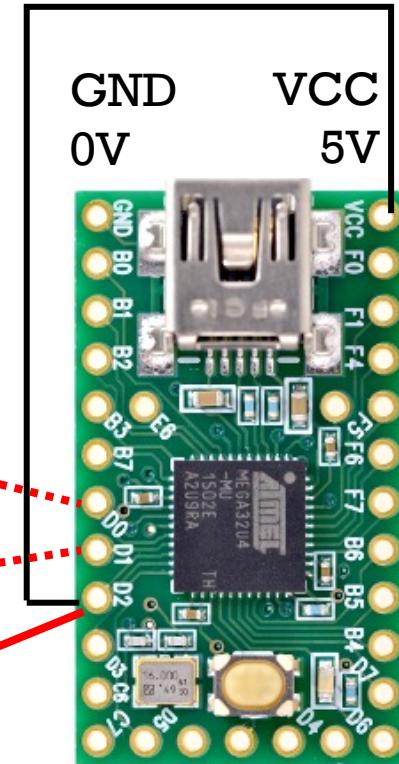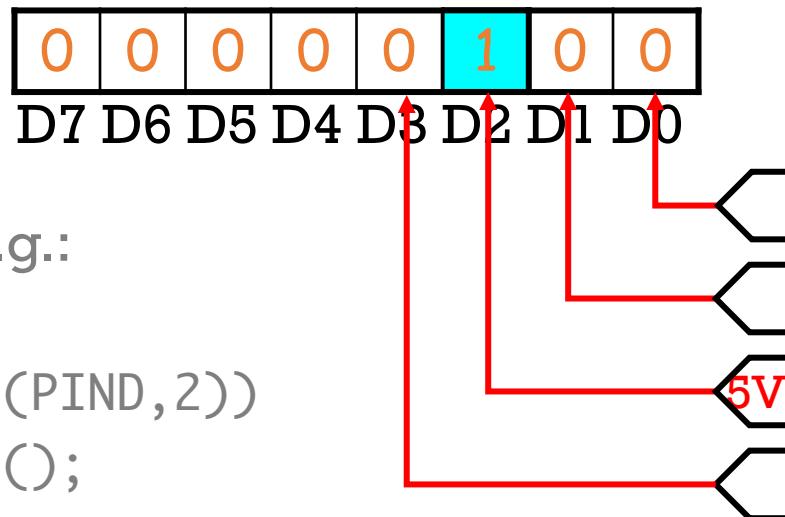- While standard on many MCU: read same register you write to, Atmega uses a different register for reading



- Instead use PINx. e.g.:

```
clear(DDRD,2);
```

```
if (bit_is_set(PIND,2))  
    dosomething();
```


`bit_is_set()` and `bit_is_clear()` is similar to `set()` and `clear()`

02

Combinatorial Logic Gates

Digital Inputs and Outputs

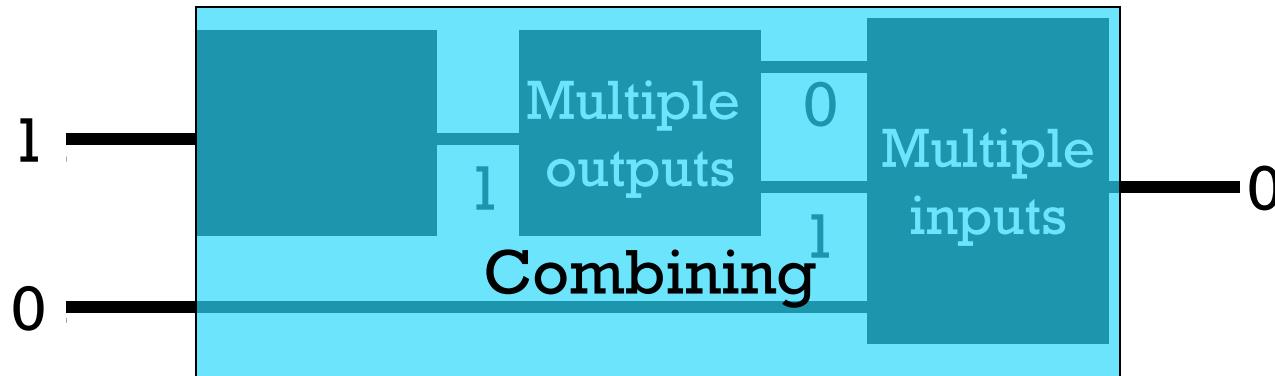- Black boxes, one end is the input, one end is the output






- Digital I/O has logical ones and zeros at inputs and outputs

1 = TRUE

0 = FALSE

Combinatorial Logic Gates


Inverter

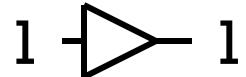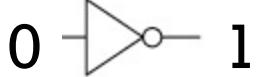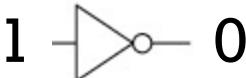

Digital buffer



Xor

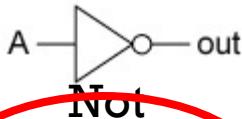


Not



Nand



Nor

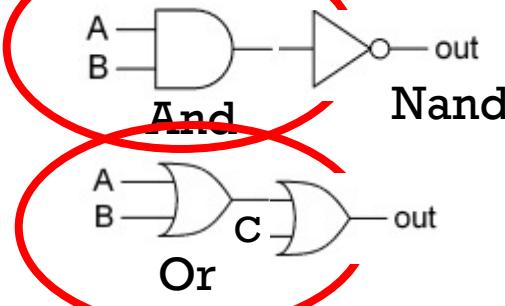

Or

Truth table

INPUT	OUTPUT
A	Not A
1	0
0	1

INPUT	OUTPUT
A	A OR B
0	0
1	1
0	1
1	1

GM Lab ministore




Has variety of logic gates.

Feel free to browse, or to go to <http://digikey.com> and get your own
But be sure to get DIP packages that can go into your protoboard.

Simple Logic


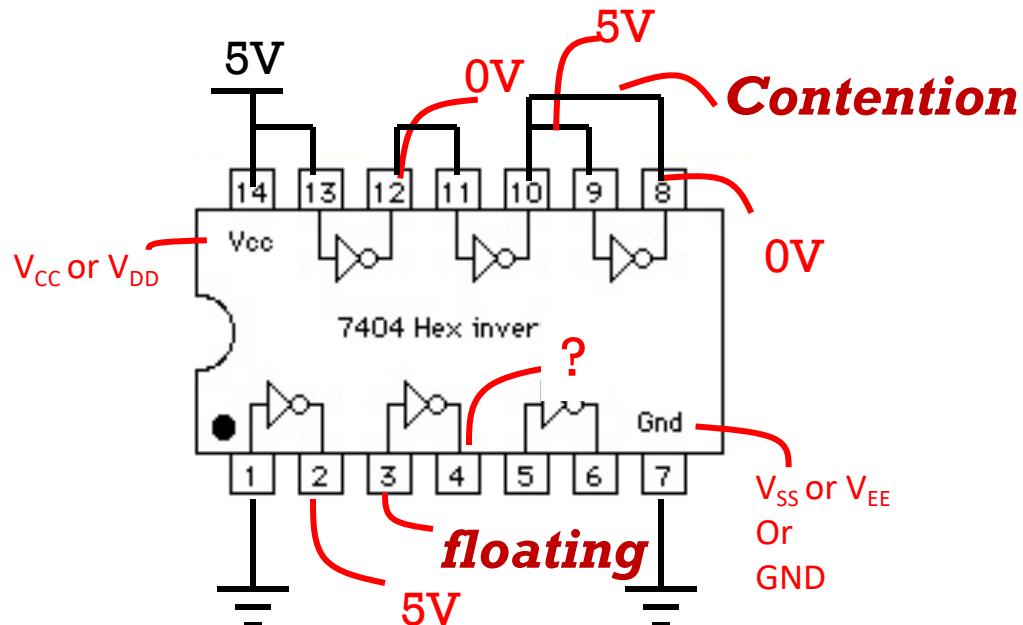
- Logical ONE = high = 5V
- Logical ZERO = low = 0V



Digital Logic
requires
POWER and GND



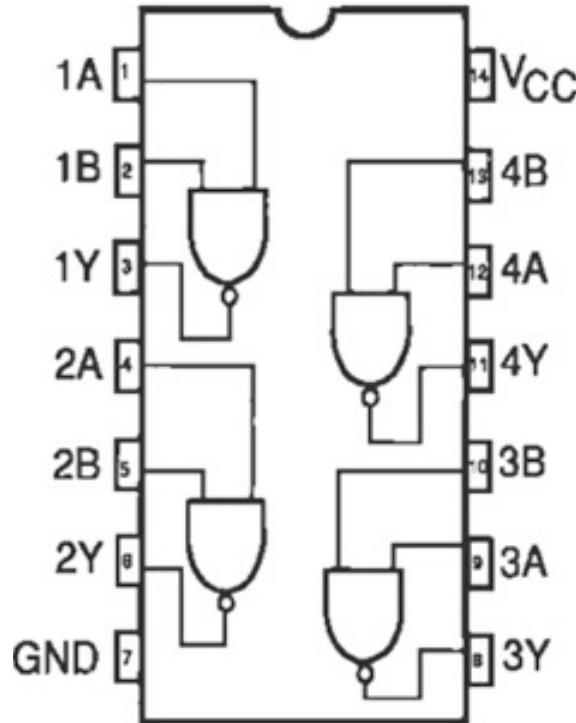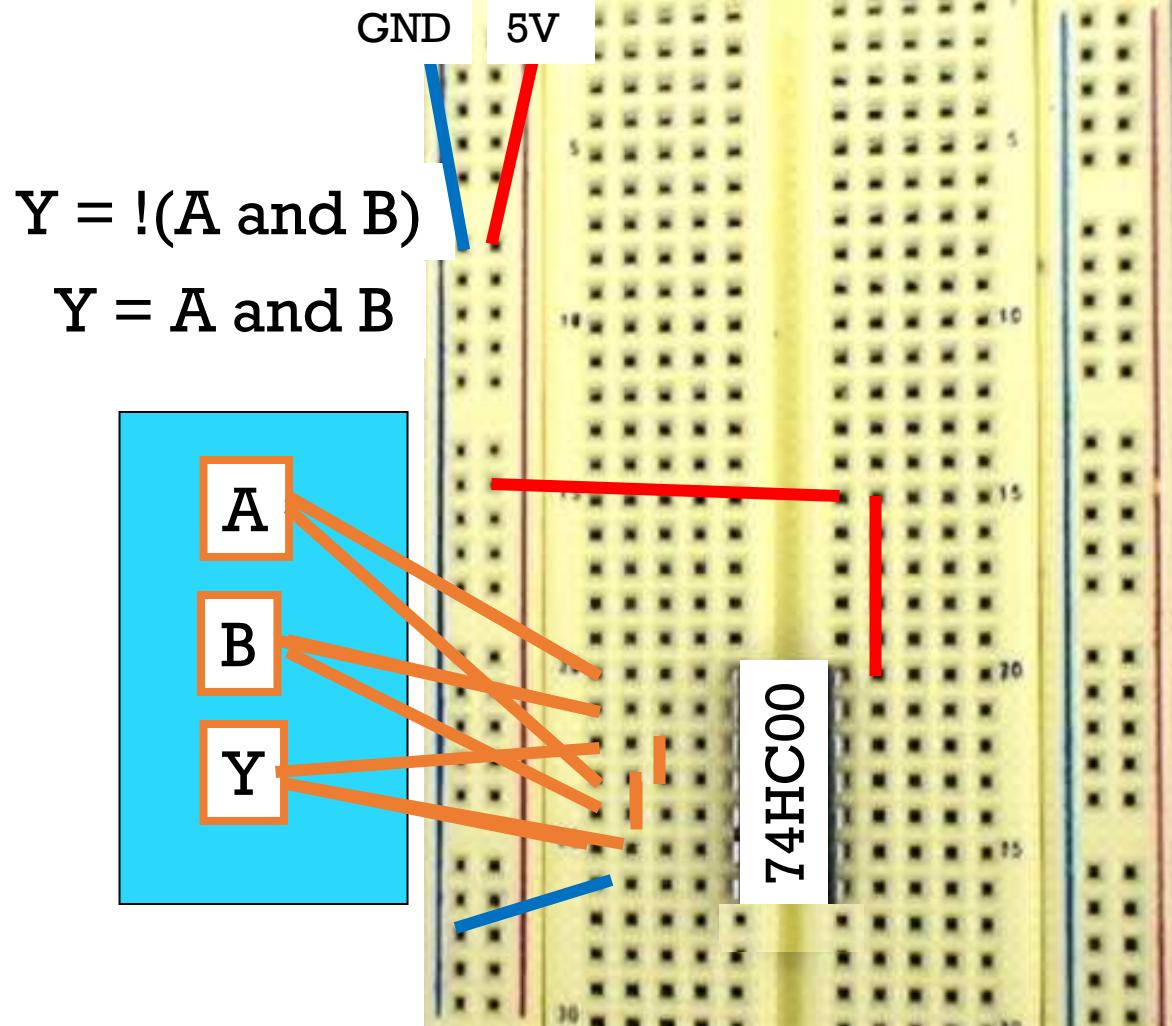Hex Inverters
7404 74LS04,
74HCT04, 74C04
74ALS04... etc.



Digital Input/Output States



Three possible states:

1. HIGH
2. LOW
3. Tri-state (high-impedance)

Internal Mode	Internal state	External state	Result
OUTPUT	High	High	High
OUTPUT	High	Low	CONTENTION
OUTPUT	High	Float	High
OUTPUT	Low	High	CONTENTION
OUTPUT	Low	Low	Low
OUTPUT	Low	Float	Low
INPUT	Float	High	High
INPUT	Float	Low	Low
INPUT	Float	Float	unknown



Human Logic

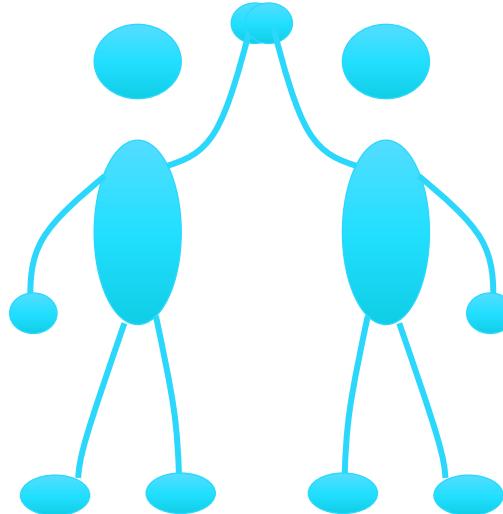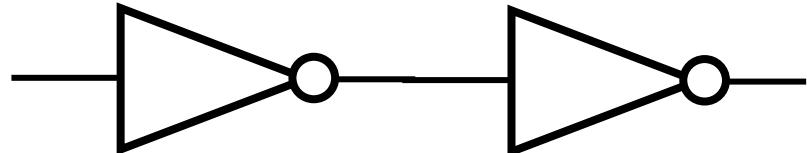- Hold hands,
 - Left is input, Right is output
-
- Upraised hand is logic high (true)
 - Lowered hand is logic low (false)



Human Logic Levels

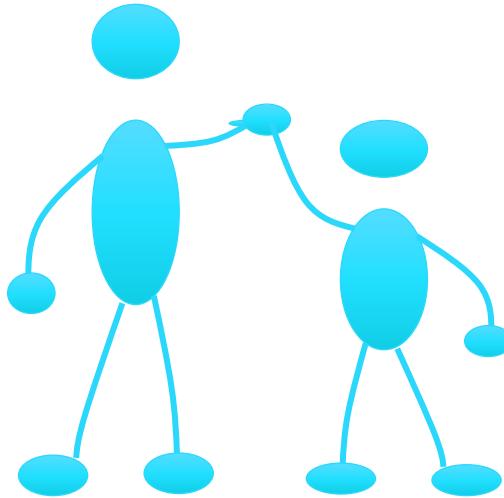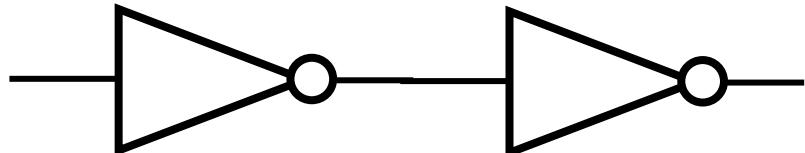- Hold hands,
- Left is input, Right is output
- Praised hand is logic high (true)
- Lowered hand is logic low (false)
- How high is high? What if you have short arms?



DC Electrical Characteristics

(Note 4)

74HC04

**For V_{CC}=5
~3.5V**

**For V_{CC}=5
~1.5V**

**For V_{CC}=5
~4.5V**

**For V_{CC}=5
~0.5V**

Symbol	Parameter	Conditions	V _{CC}	T _A = 25°C		T _A = -40 to 85°C	T _A = -55 to 125°C	Units
				Typ	Guaranteed Limits			
V_{IH}	Minimum HIGH Level Input Voltage		2.0V		1.5	1.5	1.5	V
			4.5V		3.15	3.15	3.15	V
			6.0V		4.2	4.2	4.2	V
V_{IL}	Maximum LOW Level Input Voltage		2.0V		0.5	0.5	0.5	V
			4.5V		1.35	1.35	1.35	V
			6.0V		1.8	1.8	1.8	V
V_{OH}	Minimum HIGH Level Output Voltage	$V_{IN} = V_{IL}$ $ I_{OUT} \leq 20 \mu A$	2.0V	2.0	1.9	1.9	1.9	V
			4.5V	4.5	4.4	4.4	4.4	V
			6.0V	6.0	5.9	5.9	5.9	V
		$V_{IN} = V_{IL}$ $ I_{OUT} \leq 4.0 \text{ mA}$ $ I_{OUT} \leq 5.2 \text{ mA}$	4.5V	4.2	3.98	3.84	3.7	V
			6.0V	5.7	5.48	5.34	5.2	V
V_{OL}	Maximum LOW Level Output Voltage	$V_{IN} = V_{IH}$ $ I_{OUT} \leq 20 \mu A$	2.0V	0	0.1	0.1	0.1	V
			4.5V	0	0.1	0.1	0.1	V
			6.0V	0	0.1	0.1	0.1	V
		$V_{IN} = V_{IH}$ $ I_{OUT} \leq 4.0 \text{ mA}$ $ I_{OUT} \leq 5.2 \text{ mA}$	4.5V	0.2	0.26	0.33	0.4	V
			6.0V	0.2	0.26	0.33	0.4	V

Q1a: What is the minimum voltage output that will be recognized as a valid logic high on a 74LS00?

Voltage Specified?

recommended operating conditions

		SN54LS00			SN74LS00			UNIT
		MIN	NOM	MAX	MIN	NOM	MAX	
V _{CC}	Supply voltage	4.5	5	5.5	4.75	5	5.25	V
V _{IH}	High-level input voltage	2			2			V
V _{IL}	Low-level input voltage			0.7			0.8	V
I _{OH}	High-level output current			-0.4			-0.4	mA
I _{OL}	Low-level output current			4			8	mA
T _A	Operating free-air temperature	-55		125	0		70	°C

electrical characteristics over recommended operating free-air temperature range (unless otherwise noted)

PARAMETER	TEST CONDITIONS †	SN54LS00			SN74LS00			UNIT
		MIN	TYP‡	MAX	MIN	TYP‡	MAX	
V _{IK}	V _{CC} = MIN, I _I = -18 mA			-1.5			-1.5	V
V _{OH}	V _{CC} = MIN, V _{IL} = MAX, I _{OH} = -0.4 mA	2.5	3.4		2.7	3.4		V
V _{OL}	V _{CC} = MIN, V _{IH} = 2 V, I _{OL} = 4 mA			0.25	0.4		0.25	0.4
	V _{CC} = MIN, V _{IH} = 2 V, I _{OL} = 8 mA						0.35	0.5
I _I	V _{CC} = MAX, V _I = 7 V			0.1			0.1	mA
I _{IH}	V _{CC} = MAX, V _I = 2.7 V			20			20	μA
I _{IL}	V _{CC} = MAX, V _I = 0.4 V			-0.4			-0.4	mA
I _{OS§}	V _{CC} = MAX	-20		-100	-20		-100	mA
I _{CCH}	V _{CC} = MAX, V _I = 0 V	0.8	1.6		0.8	1.6		mA
I _{CCL}	V _{CC} = MAX, V _I = 4.5 V	2.4	4.4		2.4	4.4		mA

$$V_{OH} > V_{IH}$$

$$V_{OL} < V_{IL}$$

Q1b

How do we
tell how
"strong" the
output is if
in
contention?

recommended operating conditions

		SN54LS00			SN74LS00			UNIT
		MIN	NOM	MAX	MIN	NOM	MAX	
V _{CC}	Supply voltage	4.5	5	5.5	4.75	5	5.25	V
V _{IH}	High-level input voltage	2			2			V
V _{IL}	Low-level input voltage		0.7			0.8		V
I _{OH}	High-level output current			-0.4			-0.4	mA
I _{OL}	Low-level output current		4			8		mA
T _A	Operating free-air temperature	-55		125	0		70	°C


electrical characteristics over recommended operating free-air temperature range (unless otherwise noted)

PARAMETER	TEST CONDITIONS †	SN54LS00			SN74LS00			UNIT
		MIN	TYP‡	MAX	MIN	TYP‡	MAX	
V _{IK}	V _{CC} = MIN, I _I = -18 mA			-1.5			-1.5	V
V _{OH}	V _{CC} = MIN, V _{IL} = MAX, I _{OH} = -0.4 mA	2.5	3.4		2.7	3.4		V
V _{OL}	V _{CC} = MIN, V _{IH} = 2 V, I _{OL} = 4 mA		0.25	0.4		0.25	0.4	V
	V _{CC} = MIN, V _{IH} = 2 V, I _{OL} = 8 mA					0.35	0.5	
I _I	V _{CC} = MAX, V _I = 7 V		0.1			0.1		mA
I _{IH}	V _{CC} = MAX, V _I = 2.7 V			20			20	µA
I _{IL}	V _{CC} = MAX, V _I = 0.4 V			-0.4			-0.4	mA
I _{OS§}	V _{CC} = MAX	-20		-100	-20		-100	mA
I _{CCH}	V _{CC} = MAX, V _I = 0 V	0.8	1.6		0.8	1.6		mA
I _{CCL}	V _{CC} = MAX, V _I = 4.5 V	2.4	4.4		2.4	4.4		mA

Logic Levels

Valid Output
Levels


Valid
Recognized
Input Levels

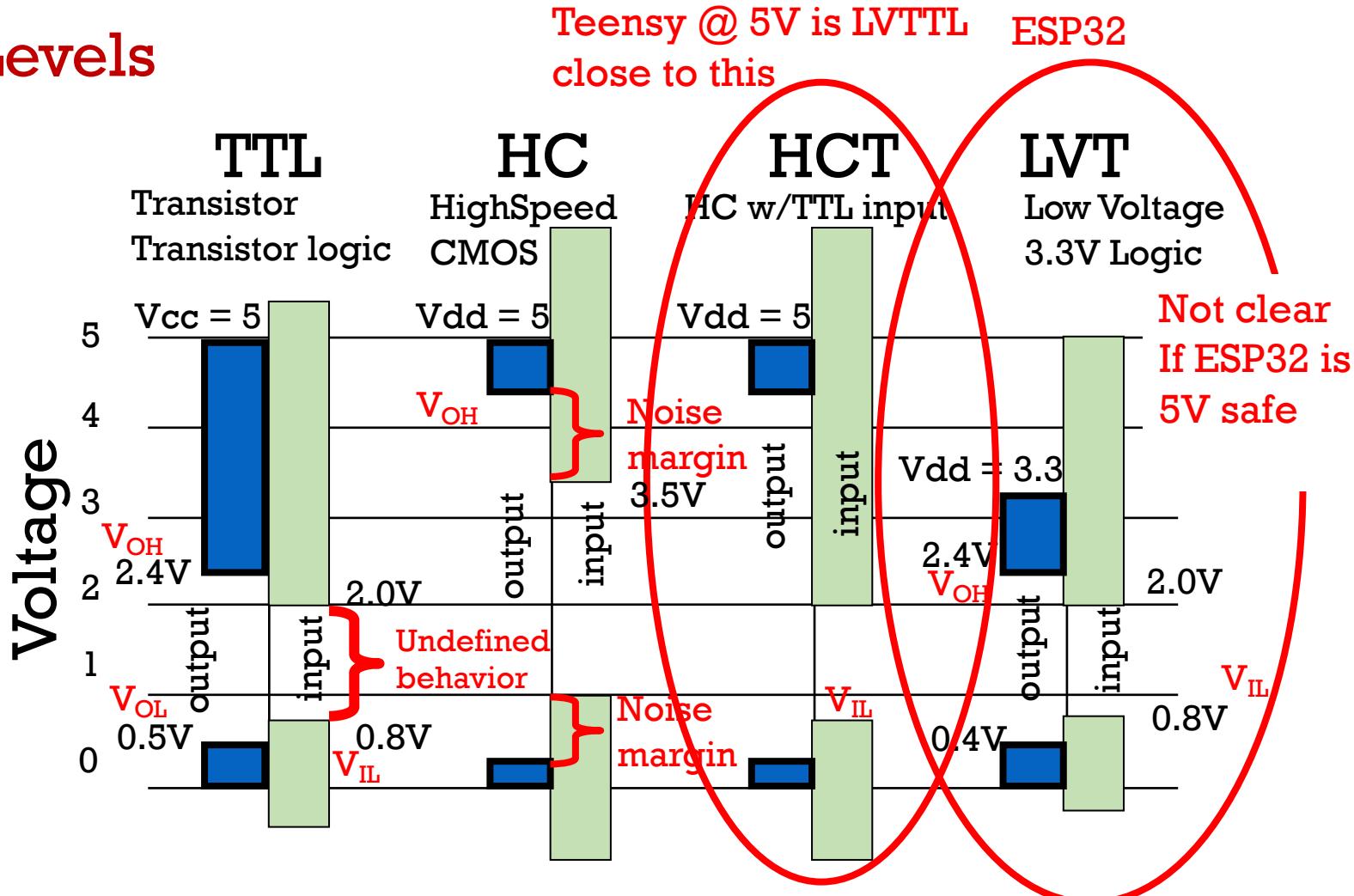

03

Pullup resistors

Switches in actuation

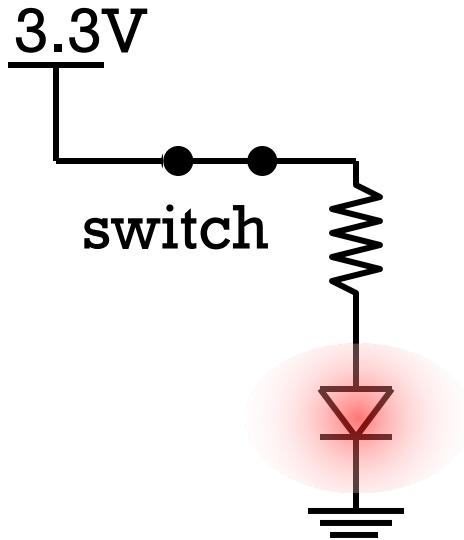

Hook up LED to power through an SPST switch



Switches in sensing

Q2: How can a switch be used to generate two different voltages to indicate the two states 0V and 5V of the switch?

5V




—● Vout


(e.g. to an input port)



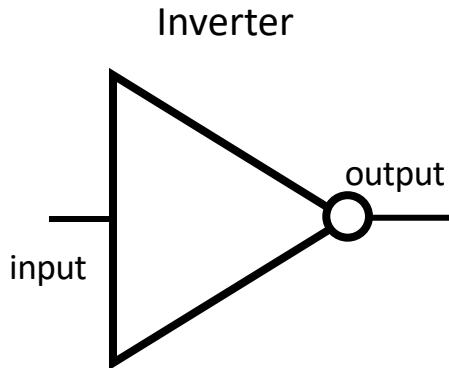
TTL Output (totem pole) vs Open Collector (OC)



Inverting output stage
Totem Pole Driven

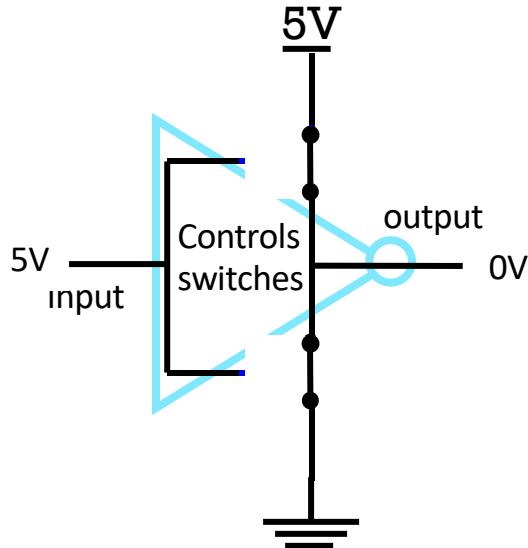

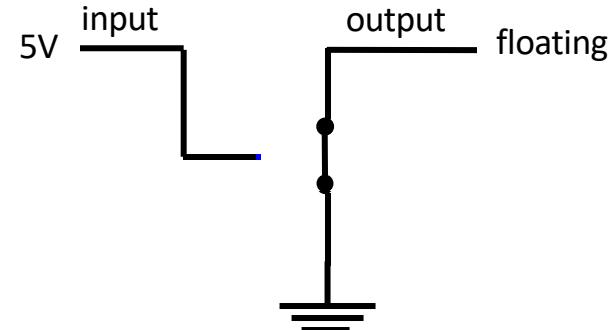Inverting output stage
Open Collector / Open Drain




Pull-up Resistors

What size Resistor should we use?

- If **too small** current capability of output not strong enough for valid logic low
- If **too large** the input impedance may not be high enough for valid logic high
- Also if **too large** output may be too slow. (e.g. problem for serial communications)
- **A rule of thumb is to use a resistor that is at least 10 times smaller than the value of the input pin impedance.** (e.g. $1\text{k}\Omega$ to $10\text{k}\Omega$)

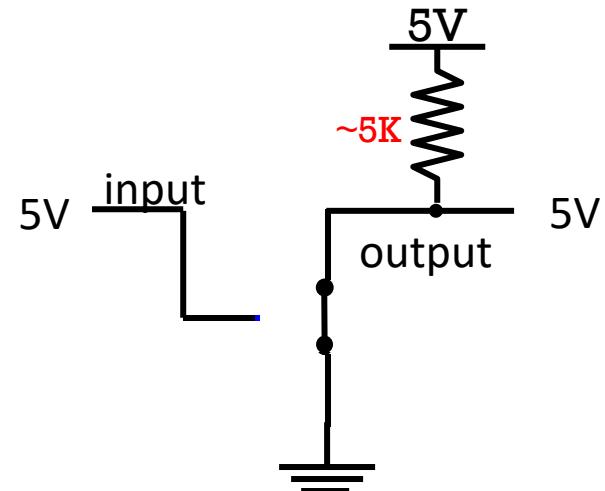Inverting output stage
Open Collector / Open Drain



Read more http://www.resistorguide.com/pull-up-resistor_pull-down-resistor/


Digital Input/Output States

Three possible states:

1. HIGH
2. LOW
3. Tri-state (high-impedance)

Internal Mode	Internal state	External state	Result
OUTPUT	High	High	High
OUTPUT	High	Low	CONTENTION
OUTPUT	High	Float	High
OUTPUT	Low	High	CONTENTION
OUTPUT	Low	Low	Low
OUTPUT	Low	Float	Low
OC w/pullup	High	High	High
OC w/pullup	High	Low	Low
OC w/pullup	High	Float	High
OC w/pullup	Low	High	CONTENTION
OC w/pullup	Low	Low	Low
OC w/pullup	Low	Float	Low


Wired NOR, Wired OR

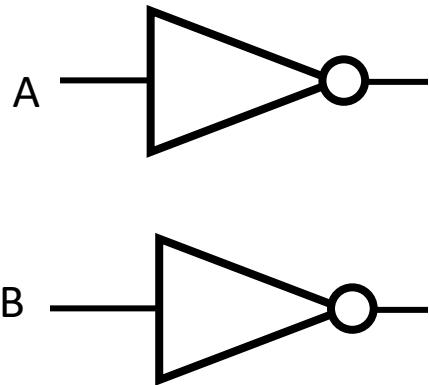


Q3: Truth table example

INPUT		OUTPUT
A	B	
0	0	1
1	0	
0	1	
1	1	

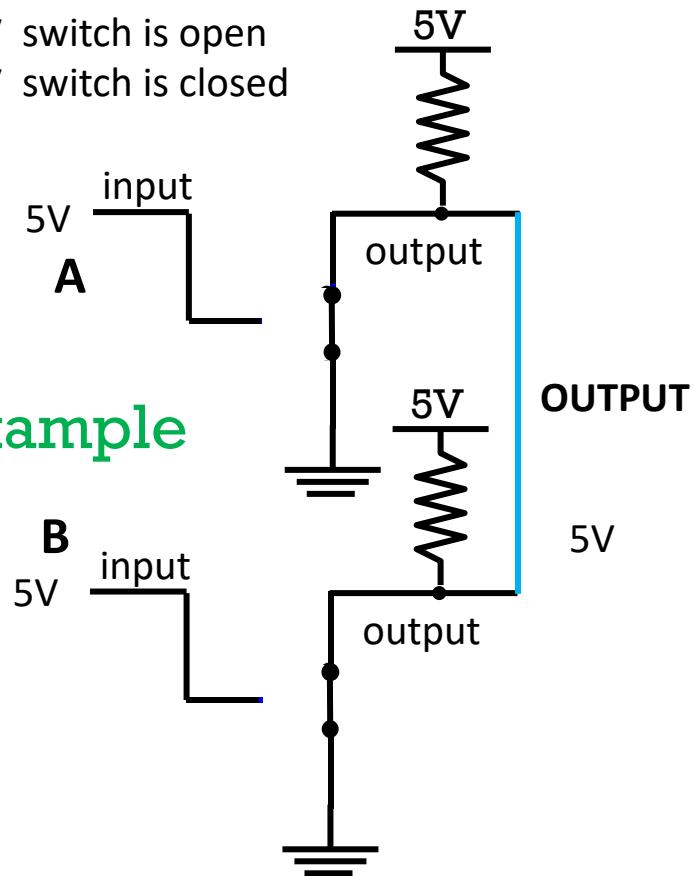0=0V switch is open
1=5V switch is closed



Human Wired-OR (wired NOR)

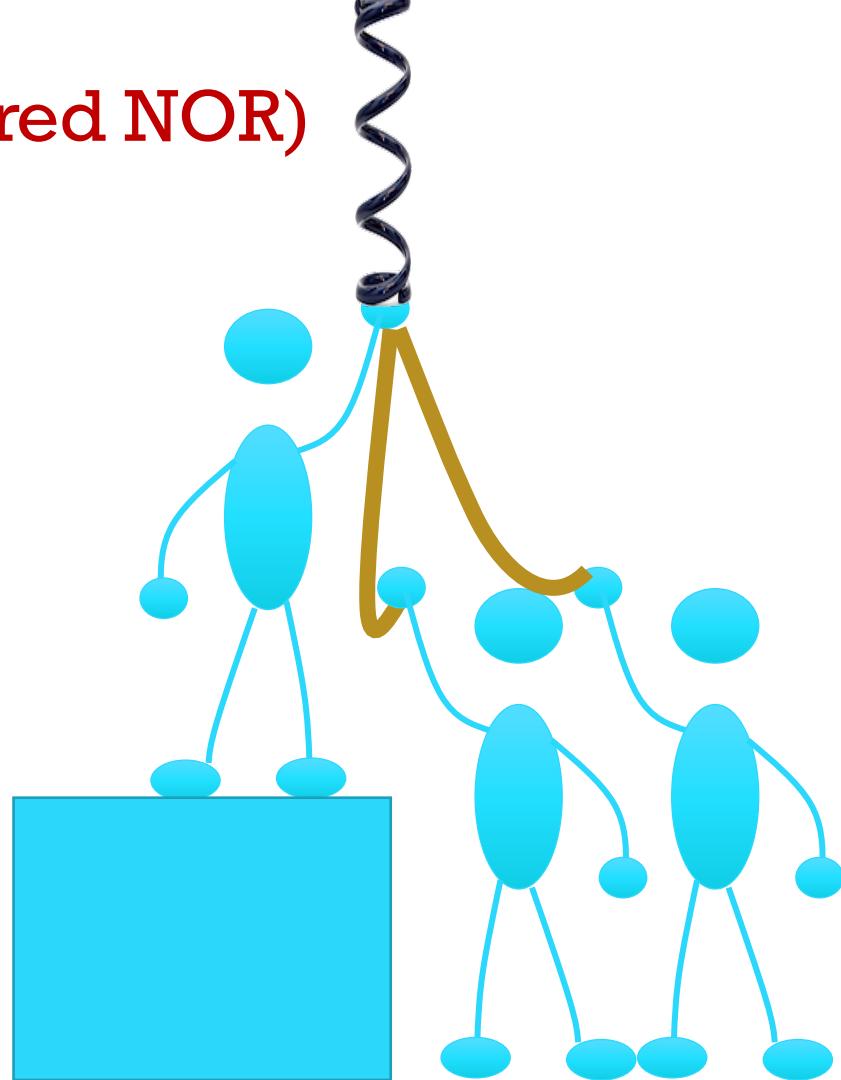

ATMEGA32 Internal Pullups


- Every port has a switchable weak internal pullup (20-50k) when in input mode. (Doesn't make sense in output mode)
- By writing 1 to PORTx to turn on (*when in input mode*), or 0 to PORTx to turn off
- Example:

```
clear(DDRD,4);      // PORTD bit 4 is an input  
set(PORTD,4);      // write a 1 to port, turn ON pullup  
clear(PORTD,4);    // write a 0 to port, turn OFF pullup
```

04

Schmitt Triggers

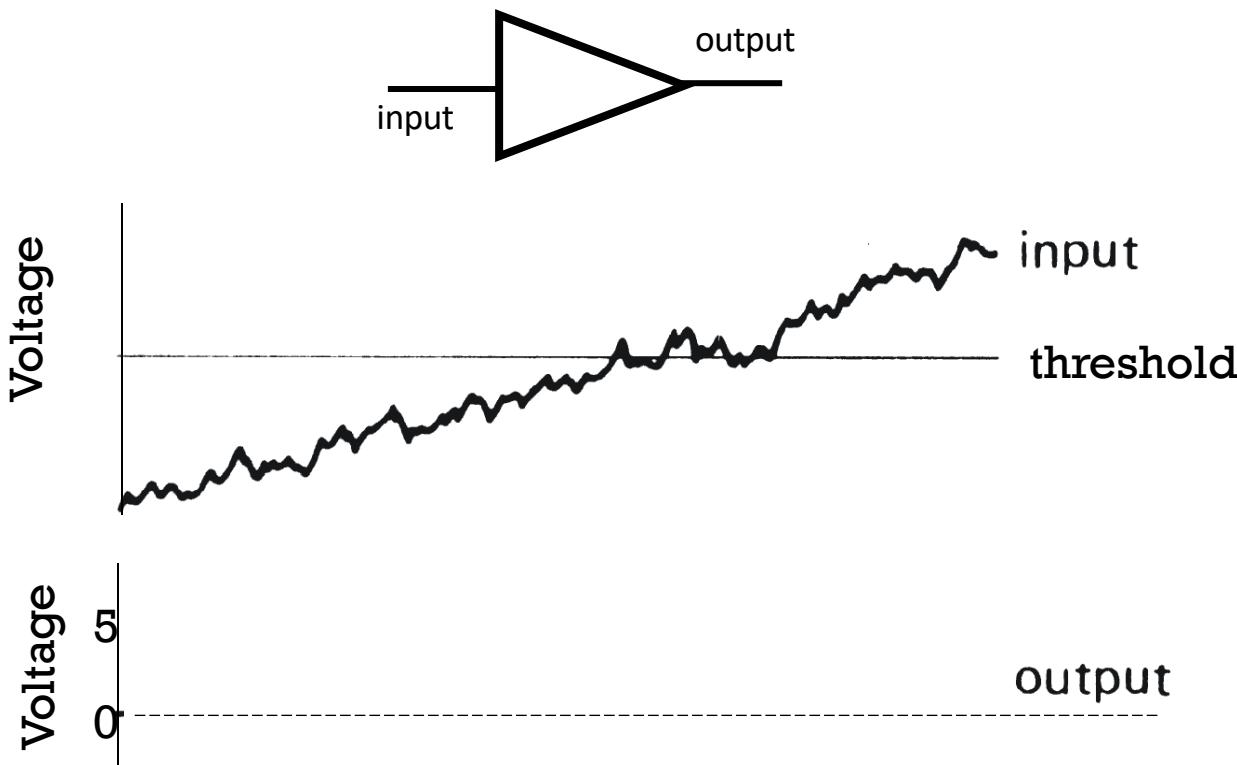Noisy input, what would logic output look like?



MM54HC14/MM74HC14

Hex Inverting Schmitt Trigger

General Description



The MM54HC14/MM74HC14 utilizes advanced silicon-gate CMOS technology to achieve the low power dissipation and high noise immunity of standard CMOS, as well as the capability to drive 10 LS-TTL loads.

The 54HC/74HC logic family is functionally and pinout compatible with the standard 54LS/74LS logic family. All inputs are protected from damage due to static discharge by internal diode clamps to V_{CC} and ground.

Features


- Typical propagation delay: 13 ns
- Wide power supply range: 2–6V
- Low quiescent current: 20 μ A maximum (74HC Series)
- Low input current: 1 μ A maximum
- Fanout of 10 LS-TTL loads
- Typical hysteresis voltage: 0.9V at $V_{CC} = 4.5V$

Connection and Schematic Diagrams

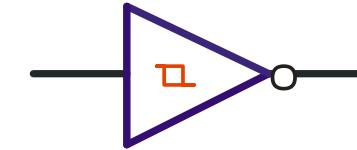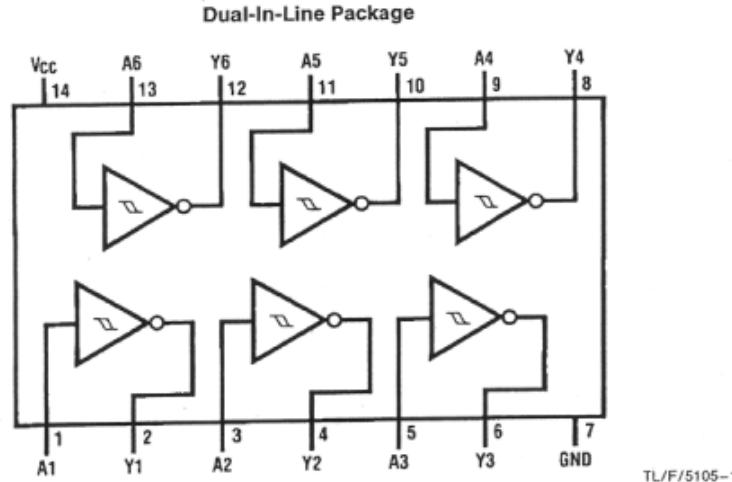

Uses
Hysteresis
on input

Q4 Now what would the output look like?

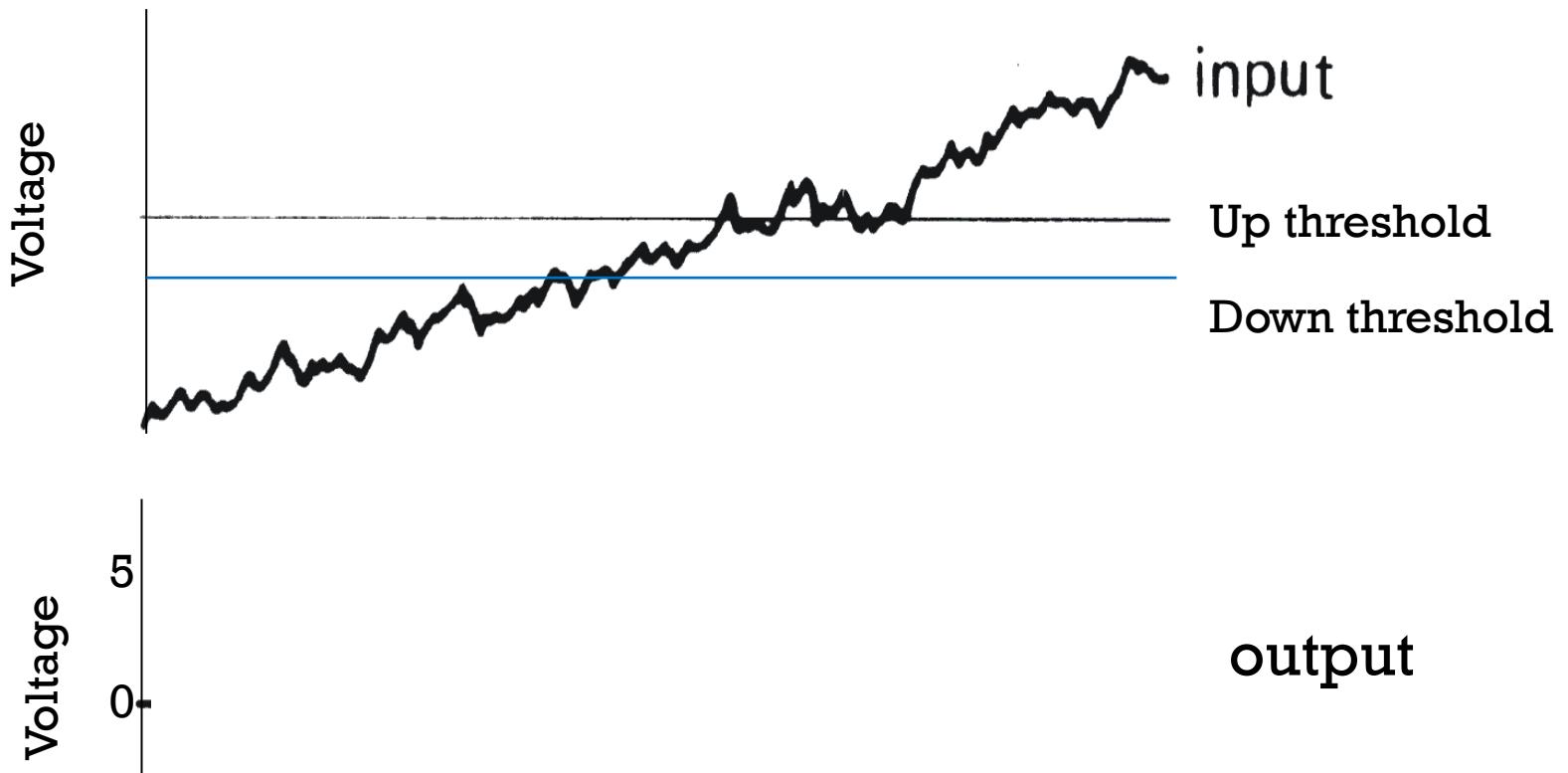

74HC14

Our $V_{CC} = 5$, but look at 4.5 for an example

PARAMETER	V_{CC}	$T_A = 25^\circ C$			SN54HC14		SN74HC14		UNIT
		MIN	TYP	MAX	MIN	MAX	MIN	MAX	
V_{T+}	2 V	0.7	1.2	1.5	0.7	1.5	0.7	1.5	V
	4.5 V	1.55	2.5	3.15	1.55	3.15	1.55	3.15	
	6 V	2.1	3.3	4.2	2.1	4.2	2.1	4.2	
V_{T-}	2 V	0.3	0.6	1	0.3	1	0.3	1	V
	4.5 V	0.9	1.6	2.45	0.9	2.45	0.9	2.45	
	6 V	1.2	2	3.2	1.2	3.2	1.2	3.2	
$V_{T+} - V_{T-}$	0.2	0.6	1.2	0.2	1.2	0.2	1.2	0.2	V
	4.5 V	0.4	0.9	2.1	0.4	2.1	0.4	2.1	
	6 V	0.5	1.3	2.5	0.5	2.5	0.5	2.5	

What voltage swing do we need to guarantee transitions?

Summary

- USB Print statements take time to execute
- Pullups help to use a switch for setting logic states
- Don't connect outputs together.
- Valid logic levels depend on convention with some “noise margin”
- Schmidt trigger inputs add hysteresis for cleaning non-valid logic outputs (e.g. analog signals)

Answer in CHAT

Answer how you feel about each topic below with:

1. I don't understand this topic at all
2. I don't know now, but know what to do to get by
3. I understand some, but expect to get the rest later
4. I understand completely already

- A. Teensy printing
- B. Logic Levels
- C. Pullup Resistors