

02

Basic Electronics Review

Basic Electronics

- What we will review:
 - Basics of voltage and current
 - Using instruments to measure them
 - Resistance
 - Capacitance
 - Combining them

Basic Circuits Review

- We make things happen with voltage and current
- We sense things by measuring voltage or current
- We compute things by varying voltage or current


Basic Circuits Review

- Water Analogy
 - Voltage \rightarrow Pressure
 - Current \rightarrow Flow
 - Resistance \rightarrow \sim Fluid shear
 - Capacitance \rightarrow \sim Elastic membrane



Hydraulic Analogy Reference

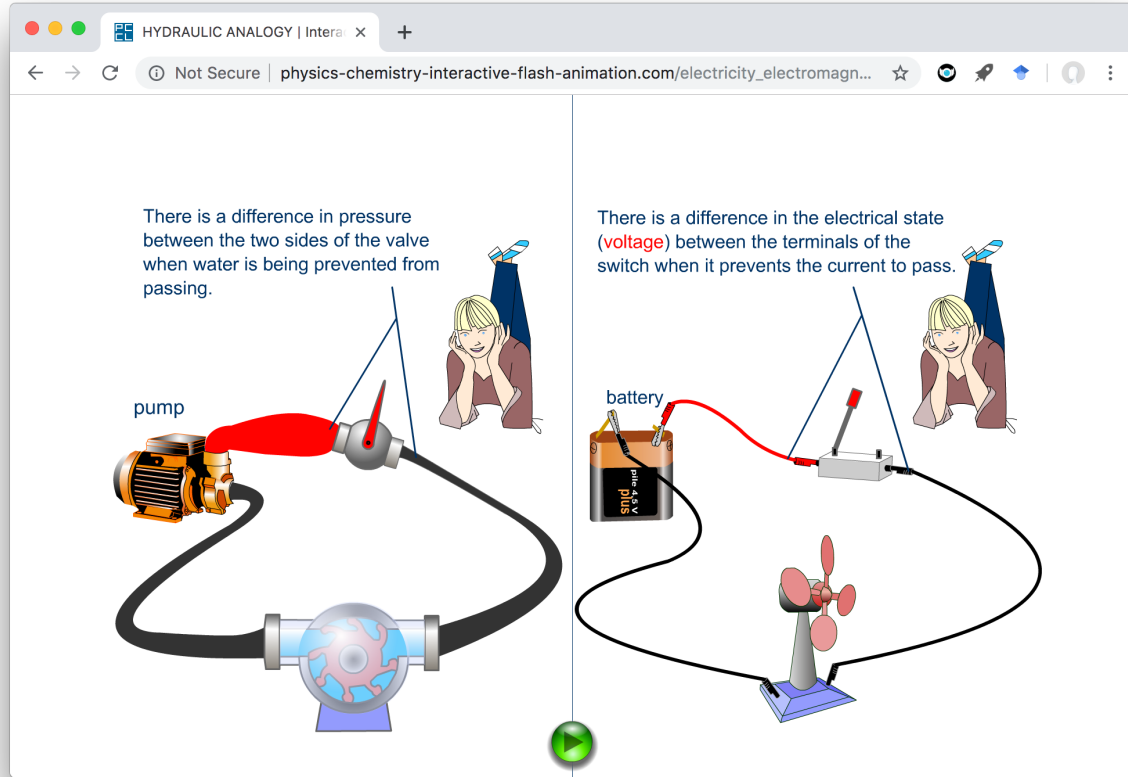
- Electrons (or alternatively positive ions) are analogous to water molecules.
- Conservation of mass (ions/electrons) applies even if they are flowing.



http://www.physics-chemistry-interactive-flash-animation.com/electricity_electromagnetism_interactive/hydraulic_analogy_difference_voltage_current.htm

Circuits and Circuitlab.com

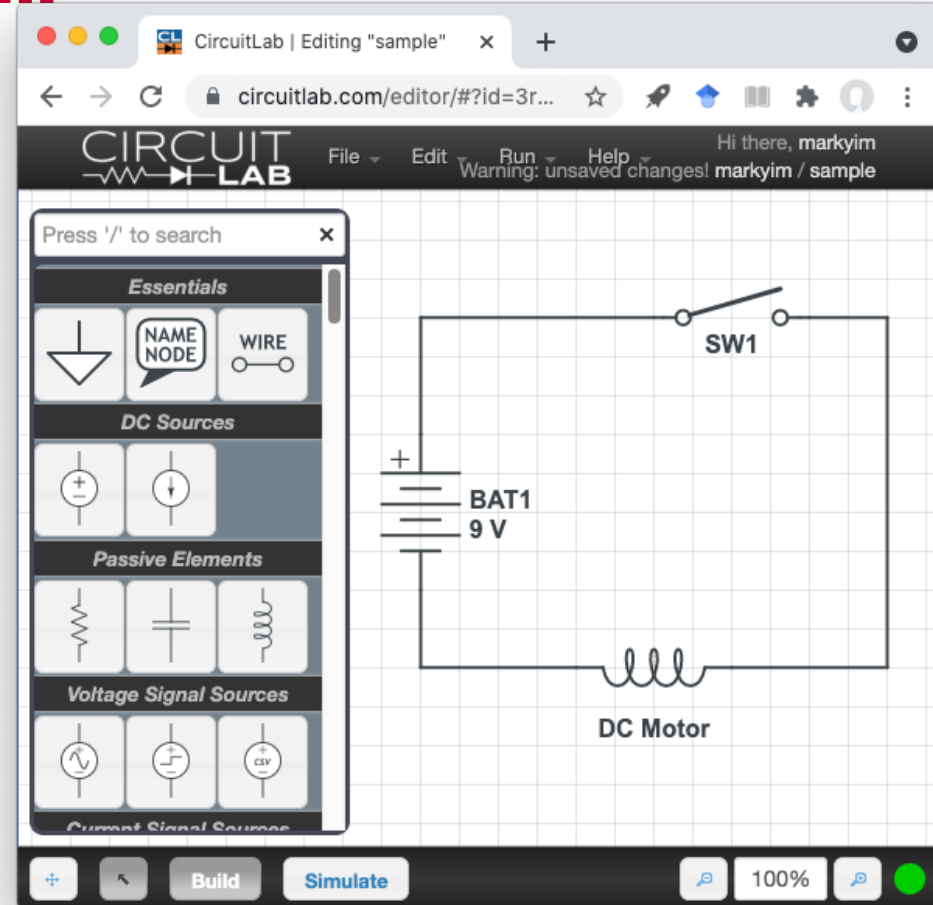- Symbols represent components connected with perfect conductors.
- Create an account (All upenn.edu email have student accounts)
- Use this to create diagrams for homeworks and project reports.



Voltage Sources

Symbols

UniPolar


Cell



Battery



BiPolar (AC)

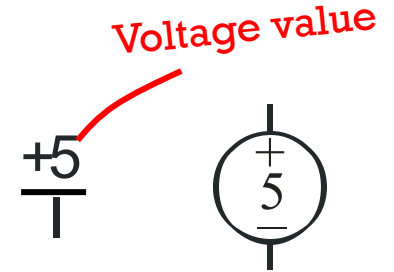

Power supplies

Properties

Constant Voltage, independent of the amount of current

Up to some power limit


Examples

Batteries


Power Supplies,

Signal Generators, (function generators)

Measuring Voltage

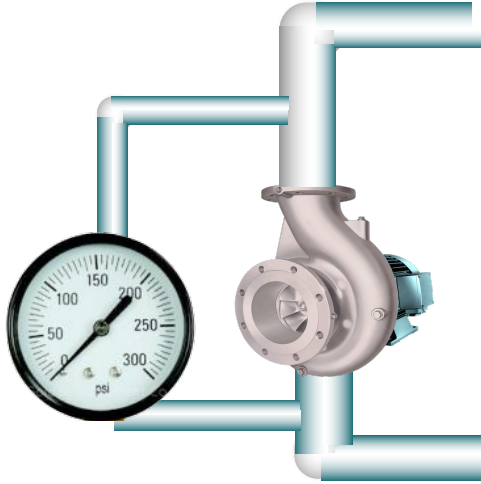

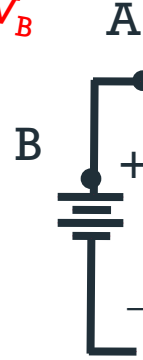Lines in a circuit diagram assume no resistance
 $V_A = V_B$



Voltage @ A

Assume relative to negative
(usually called ground)

Voltage is like differential pressure

Measured between two points


“The voltage at point A with respect to point B”

“The voltage across...”


“The voltage at point A...”

Assumes measurement device draws no current

Measuring Voltage in Real Life

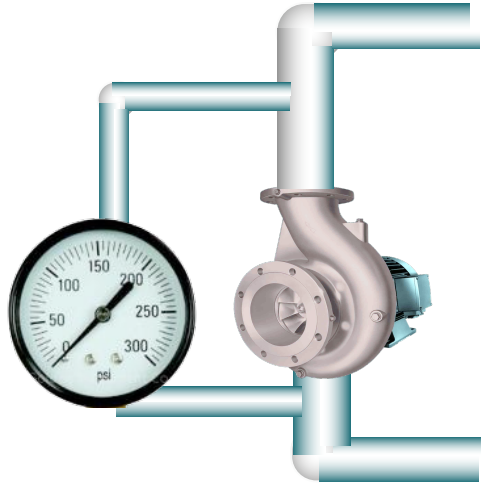

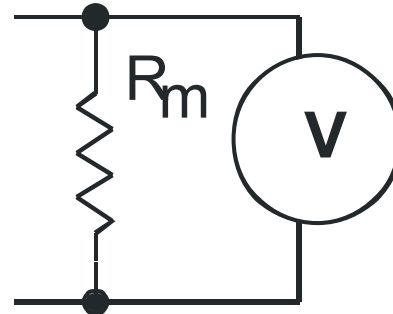Measurement is Imperfect
Draws tiny current/flow



Digital Volt
Meter


DVM DMM




Digital Multi-Meter



Current

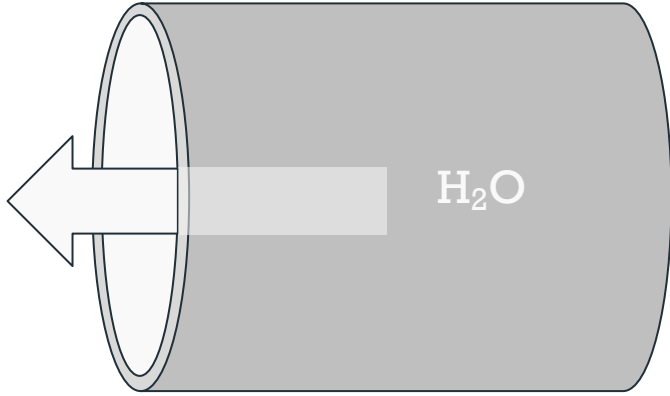

Flow of Water

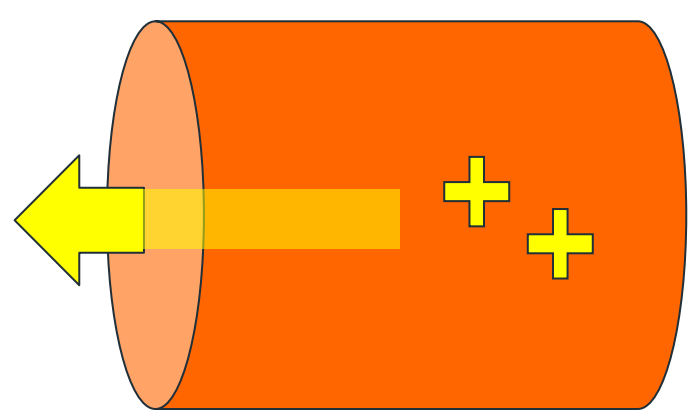

Flow of Charge

We use Benjamin Franklin's Current

Positive charge flow → In a circuit, current flows FROM positive TO negative

Unit = Amperes (A)

Sometimes referred to as i

Current Sources

Symbols



Properties

Delivers a constant current flow independent of voltage

Examples


There are no natural current sources

We can build circuits to approximate a current source

Power supplies typically have C.C. (constant current) mode

Voltage Paradox

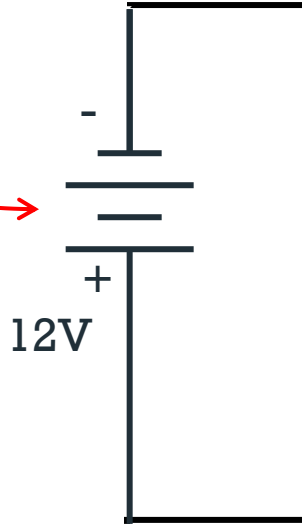Ideal battery supplies
as much current as
necessary to keep
voltage difference
constant (e.g. 12V)




Ideal connections have
0 resistance, allowing as
much current to flow to
keep the voltage across
the wire 0


Measuring Current

Current is measured through a point

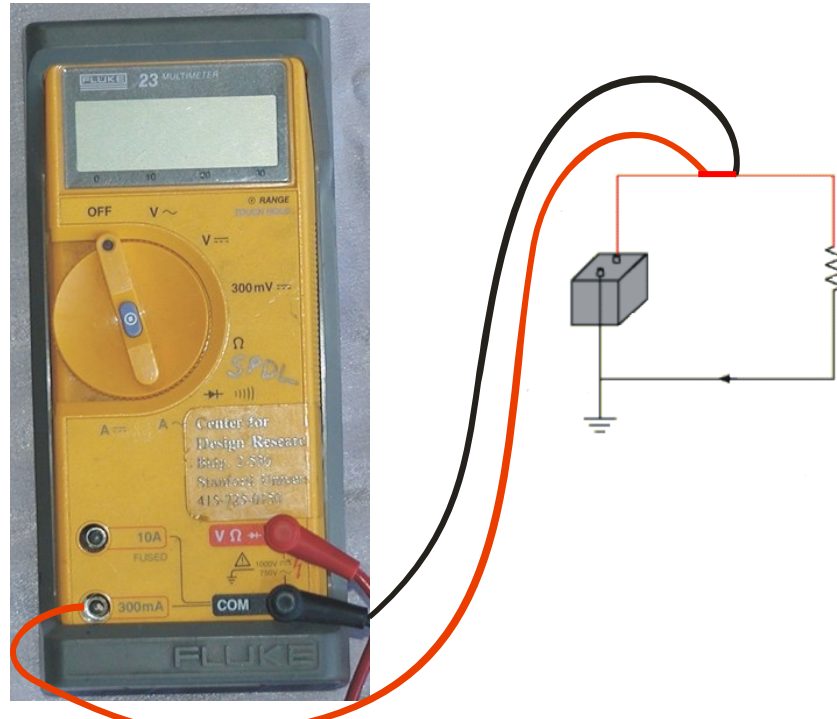To Measure: break the circuit at that point and insert the measuring instrument. We will use a DMM.



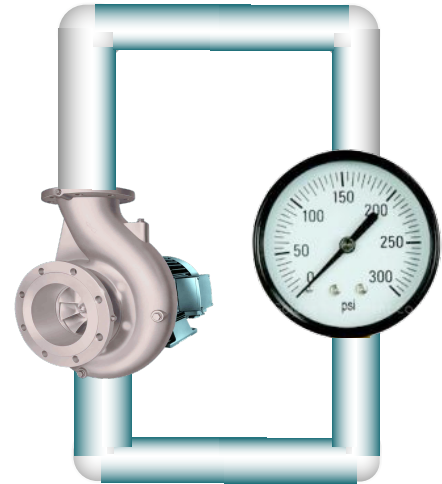Ammeter is fused,
Fuse is easy to blow. often
blown in MEAM equipment.



Electricity in Actuation


- Apply a voltage, amount of current through device determines magnitude.
- LED: apply a voltage, the amount of current determines how bright.
- Motor: apply voltage, the amount of current determines how much torque.

$$\text{Power} = \text{Volts} * \text{Current}$$

Resistance

Constriction
creates
Resistance to water flow

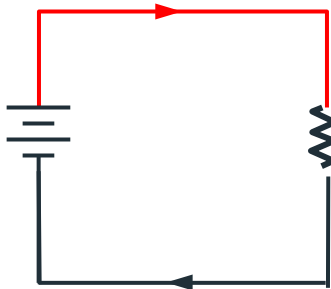Conceptually pipes with 0
resistance are infinitely
wide



The Resistance to Flow



Resistor creates
resistance to current flow

Units = Ohms


V vs I Behavior described by
Ohm's Law

$$V = I R$$

Volts = Amperes * Ohms

Resistors

Symbols

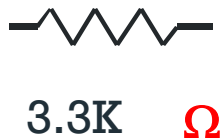

Properties

Constant resistance independent of variables

Dissipates power $VI = I^2R = \frac{V^2}{R}$ For this class typ 1/8W, 1/4 W

3 digits: 10% to 2% accuracy Markings: color coded bands represent value

1st sig. Digit,

2nd sig. Digit,

number of zeros,

silver/gold


4 digits: 1% and better accuracy

1st sig. Digit,

2nd sig. Digit,

3rd sig. Digit,

number of zeros

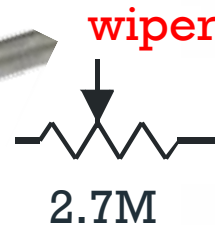

potentiometer




Though many are temperature sensitive


Measuring Resistance

Force a small current
($\sim 0.02\text{mA}$) to flow and then
measure the voltage drop

We will use the DMM for this

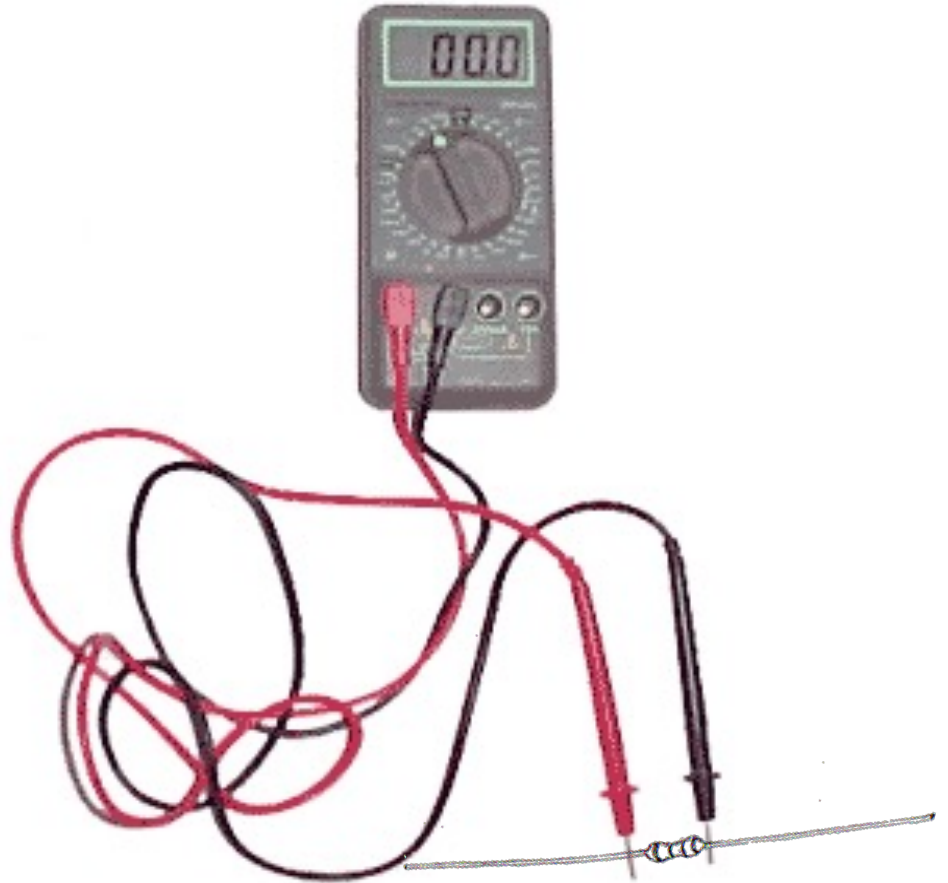

Measuring Resistance in situ

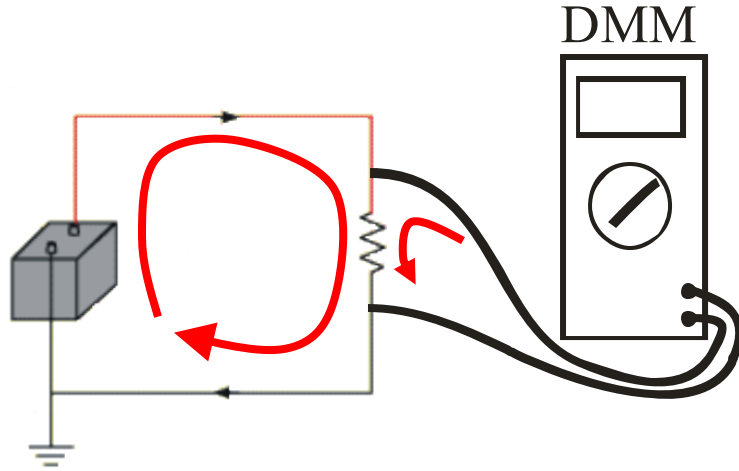

Will the DMM give the value of resistor?

NO!

Ground

Symbols



Earth Gnd




Analog Gnd

n/a for this course


For this class, it is useful to think of it as a symbol that provides a reference point, often but not always the most negative point.

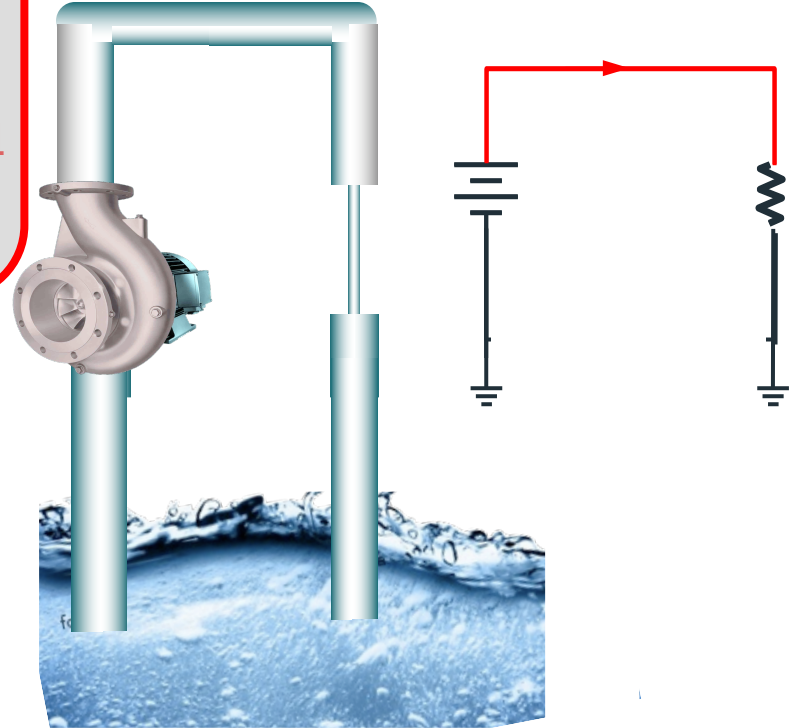More generally – outside of this course, it is an integral path in the current flow that can mean other things.




Like reservoir

Combining Resistance in Series

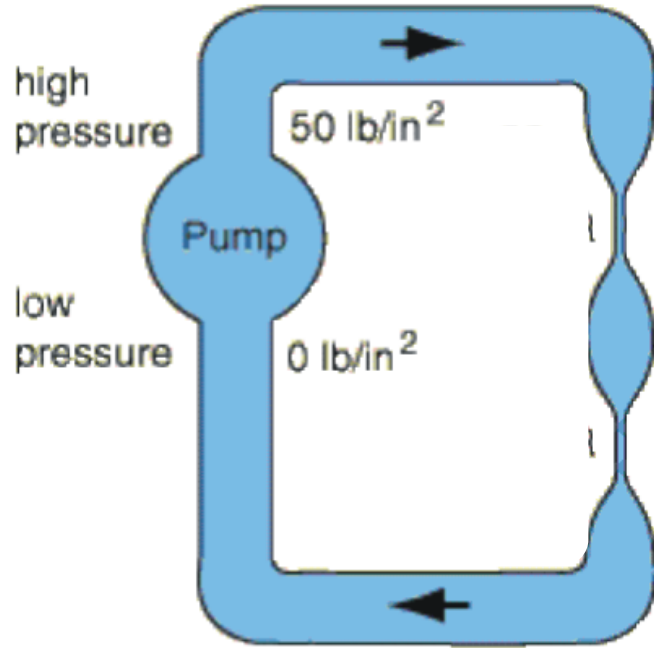

$$R_{Total} = R_1 + R_2$$

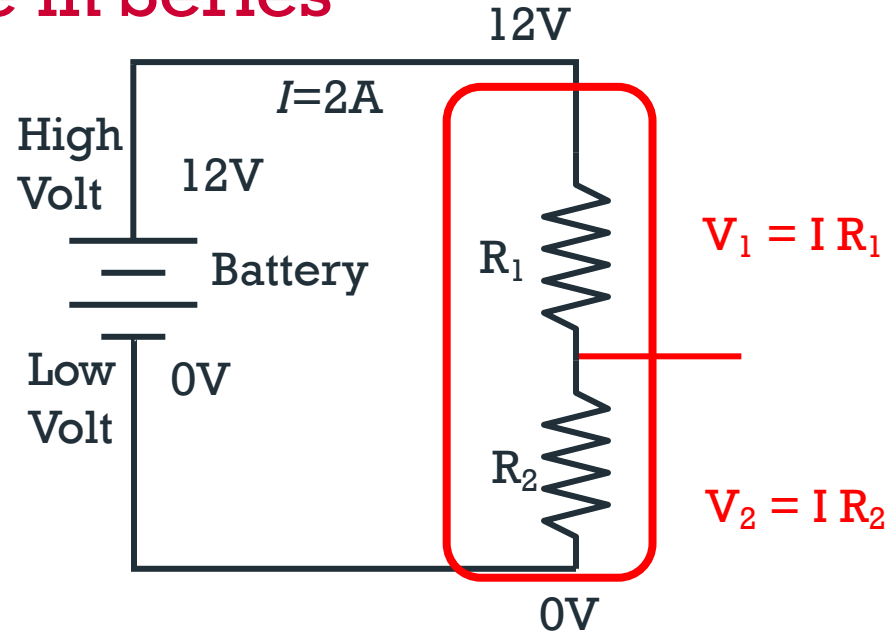

Ohms law



$$V_{total} = I R_{total}$$

Kirchoffs
Voltage law:

$$V_1 + V_2 = V_{total}$$

$$I R_1 + I R_2 = I R_{total}$$

Combining Resistance in Parallel

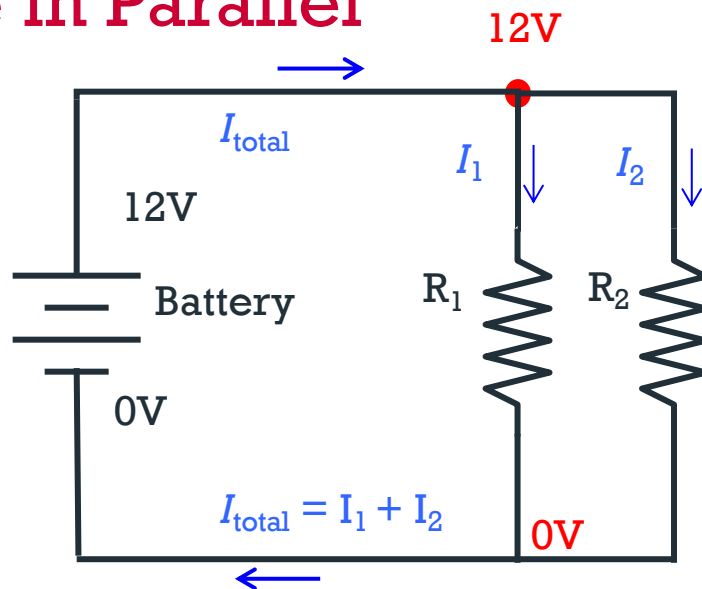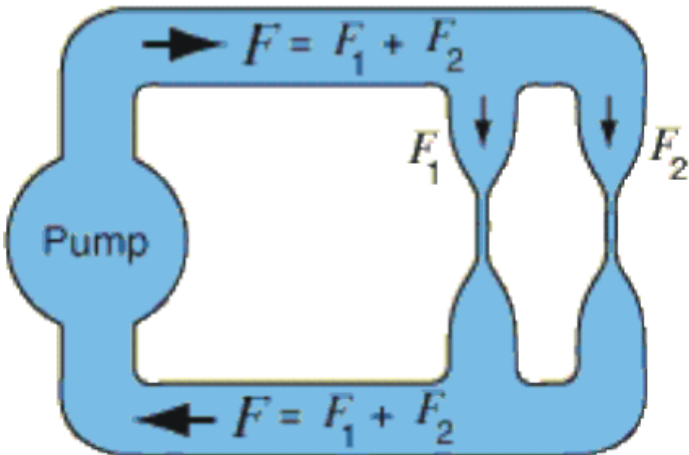

$$\frac{1}{R_{Total}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R_{Total} = \frac{R_1 R_2}{R_1 + R_2}$$

Ohm's law:




$$V_{total} = I_{total} R_{total} = I_1 R_1$$

$$V_{total} = I_{total} R_{total} = I_2 R_2$$


Kirchoff's
Current law:

$$-I_1 - I_2 + I_{total} = 0$$


Voltage Divider & Potentiometers

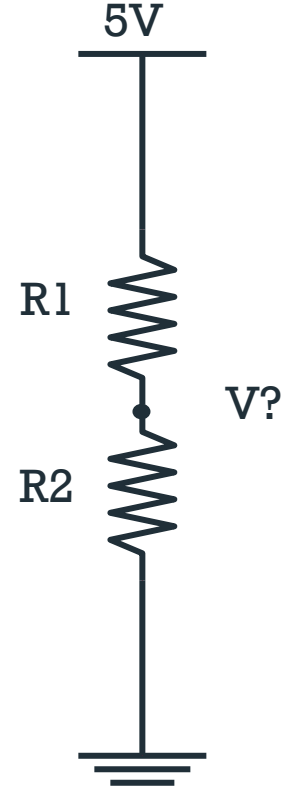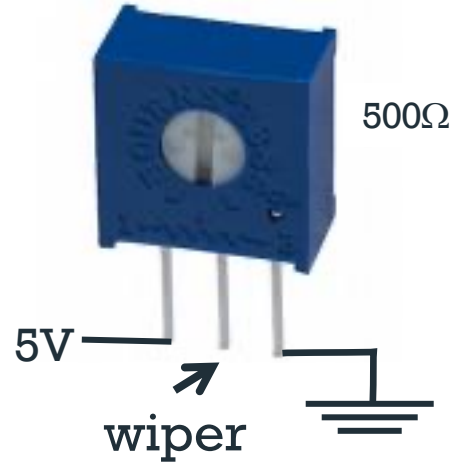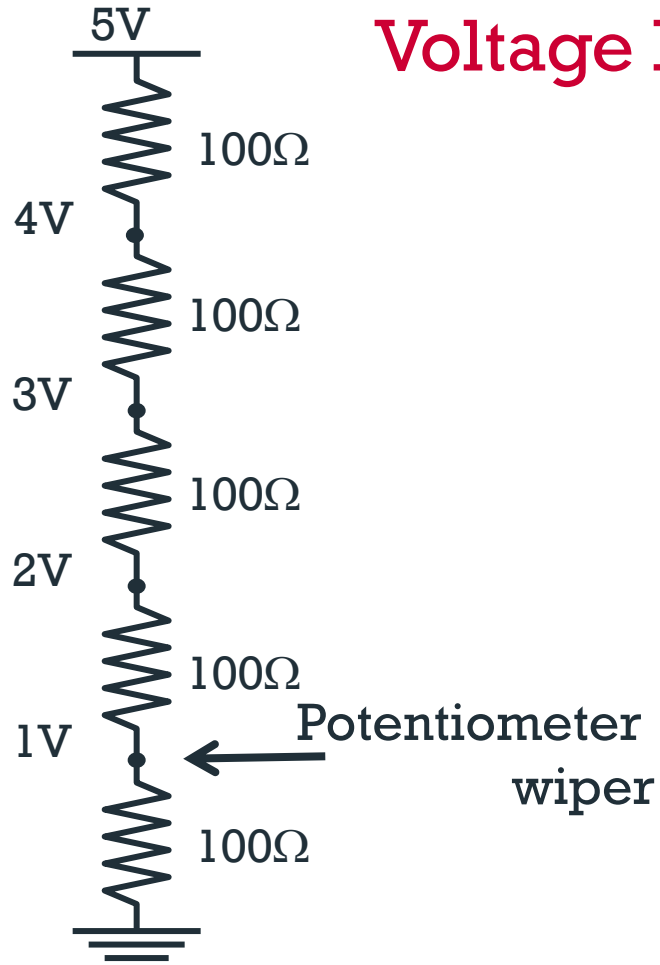

Voltage Divider Analogy

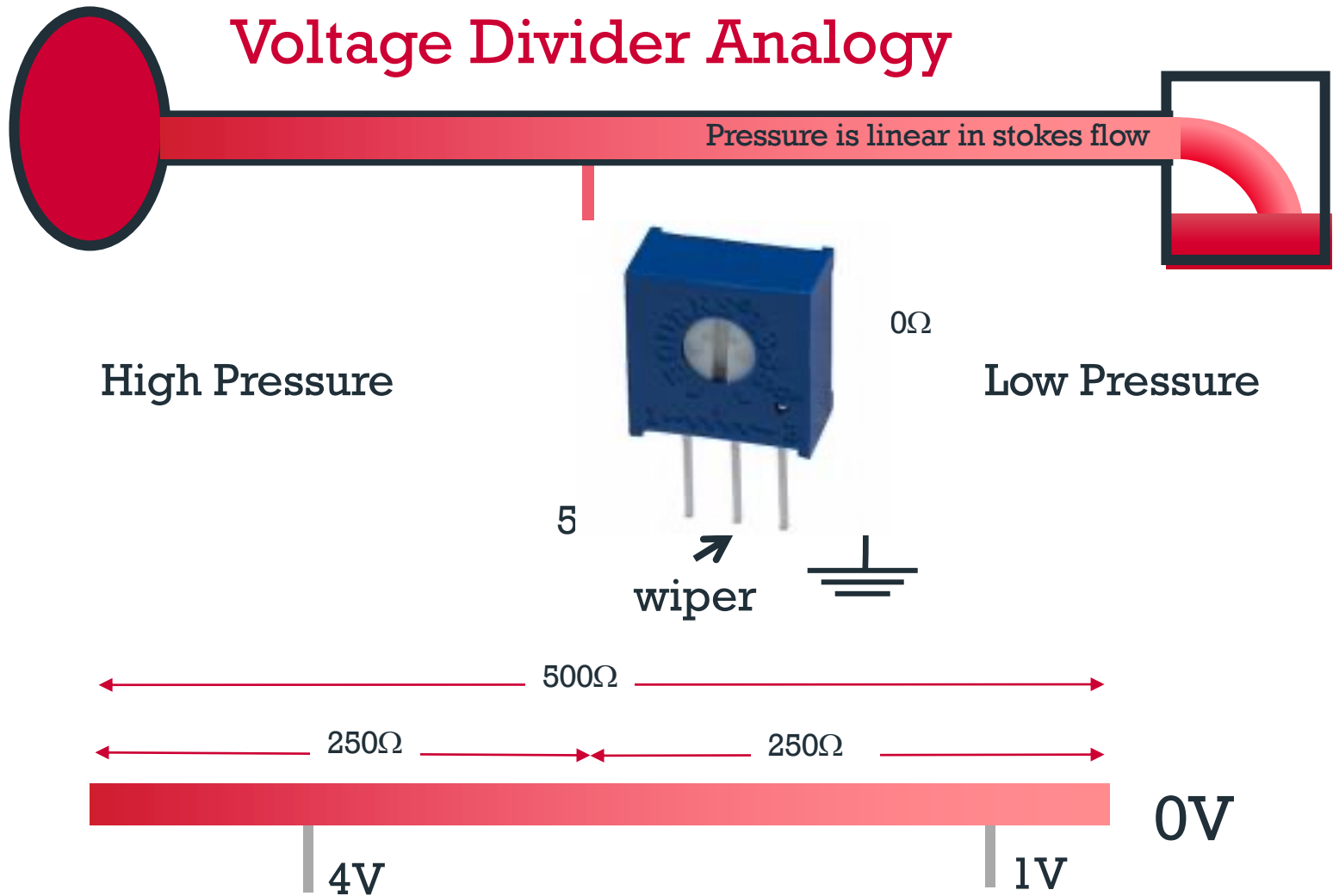

Voltmeter non-ideality

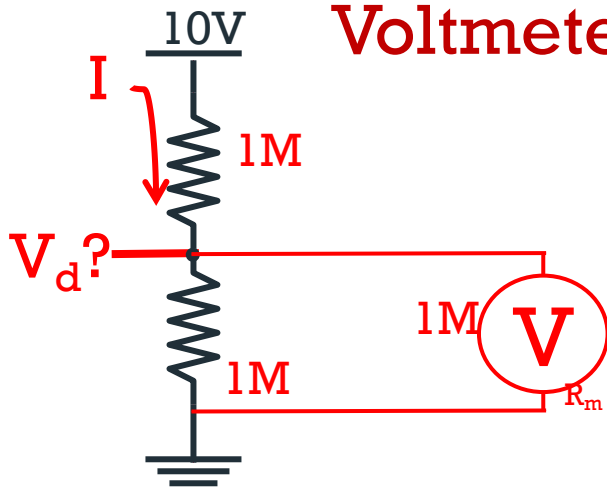

$$I = \frac{10V}{R_1 + R_2}$$

$$V_d = I R_2$$

$$V_d = 10V \frac{10K}{10K + 10K}$$

cheap meters, $R_m = \sim 1M \Omega$

good meters, $R_m = \sim 10M \Omega$

Example 1: $R_1 = R_2 = 10K \Omega$

$$10K + 9.9K$$

$$\frac{10,000M}{1.010M}$$

V_d should be 5.00 but measured is 4.975V

Example 2: $R_1 = R_2 = 1M \Omega$

Use 1/4W resistors
 $10\Omega \ll R \ll 10M\Omega$

Question 1: V_d should be 5.00 but measured is ??? V

Capacitors

Symbols



nonPolar



Polar



Euro



Integrating
Charge (storage)

Properties

Characteristic Equations:

$$I = C \frac{dV}{dT}$$

$$V = \frac{1}{C} \int IdT$$

Markings

Polar vs Non-Polar

Polar may EXPLODE

Electrolytics mark (-)

Tantalums mark (+)

Values

Capacitance

uF (10^{-6}) if polar

Longer lead

Voltage rating

pF (10^{-12}) if nonPolar

103 (pF) = $10 \times 1000\text{pF}$

See <http://kilohm.info/3-digit-capacitor/103>

Examples



Mylar



Monolythic
Cermamic



Ceramic




Tantalum




Electrolytic

Capacitors

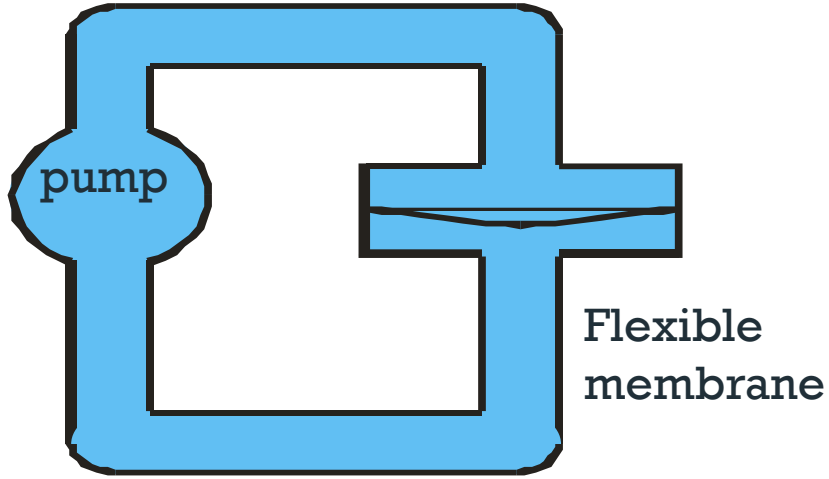

Charge storage

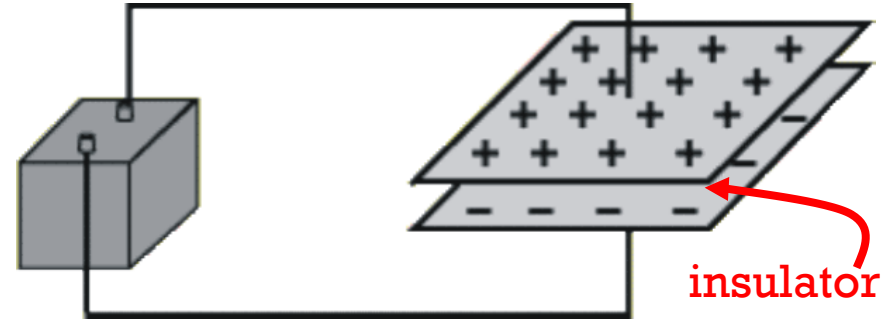

Unit = Farad

$$I = C \frac{dV}{dT}$$

pico pF = 10^{-12}F

micro uF = 10^{-6}F

Capacitors in parallel & Series

$$I = C \frac{dV}{dT}$$

$$I = I_1 + I_2 = C_1 \frac{dV}{dt} + C_2 \frac{dV}{dt}$$



$$I = (C_1 + C_2) \frac{dV}{dt} = C_{eq} \frac{dV}{dt}$$

$$I_1 = I_2 = C_1 \frac{d(V - V_1)}{dt} = C_2 \frac{dV_1}{dt}$$

$$C_1 \frac{dV}{dt} - C_1 \frac{dV_1}{dt} = C_2 \frac{dV_1}{dt}$$

$$\frac{dV_1}{dt} = \frac{C_1}{C_1 + C_2} \frac{dV}{dt}$$
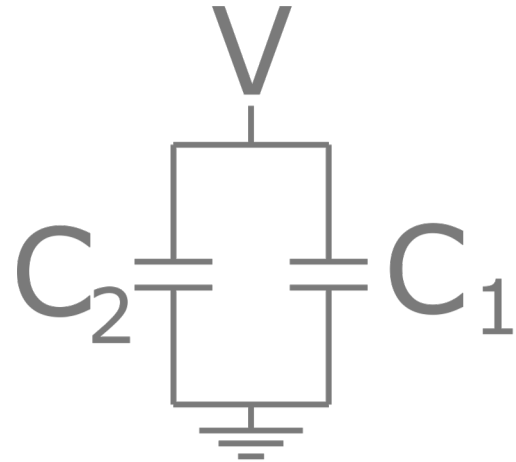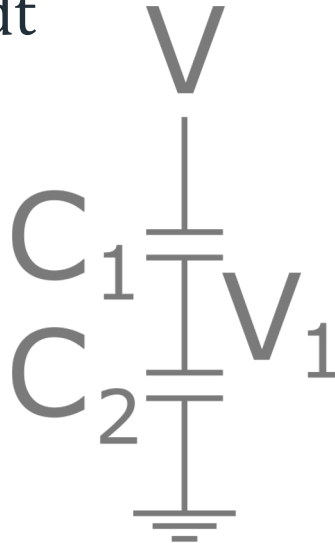
$$I = C_2 \frac{dV_1}{dt} = \frac{C_1 C_2}{C_1 + C_2} \frac{dV}{dt}$$




Protoboard "Solderless Breadboard"

Vertical bus typically
used for power
(red for positive
blue/black for negative)

Use solidcore wires to
make connections from
one row to another

Google solderless breadboard
<https://www.youtube.com/watch?v=6WReFkfrUIk>

Connected vertically

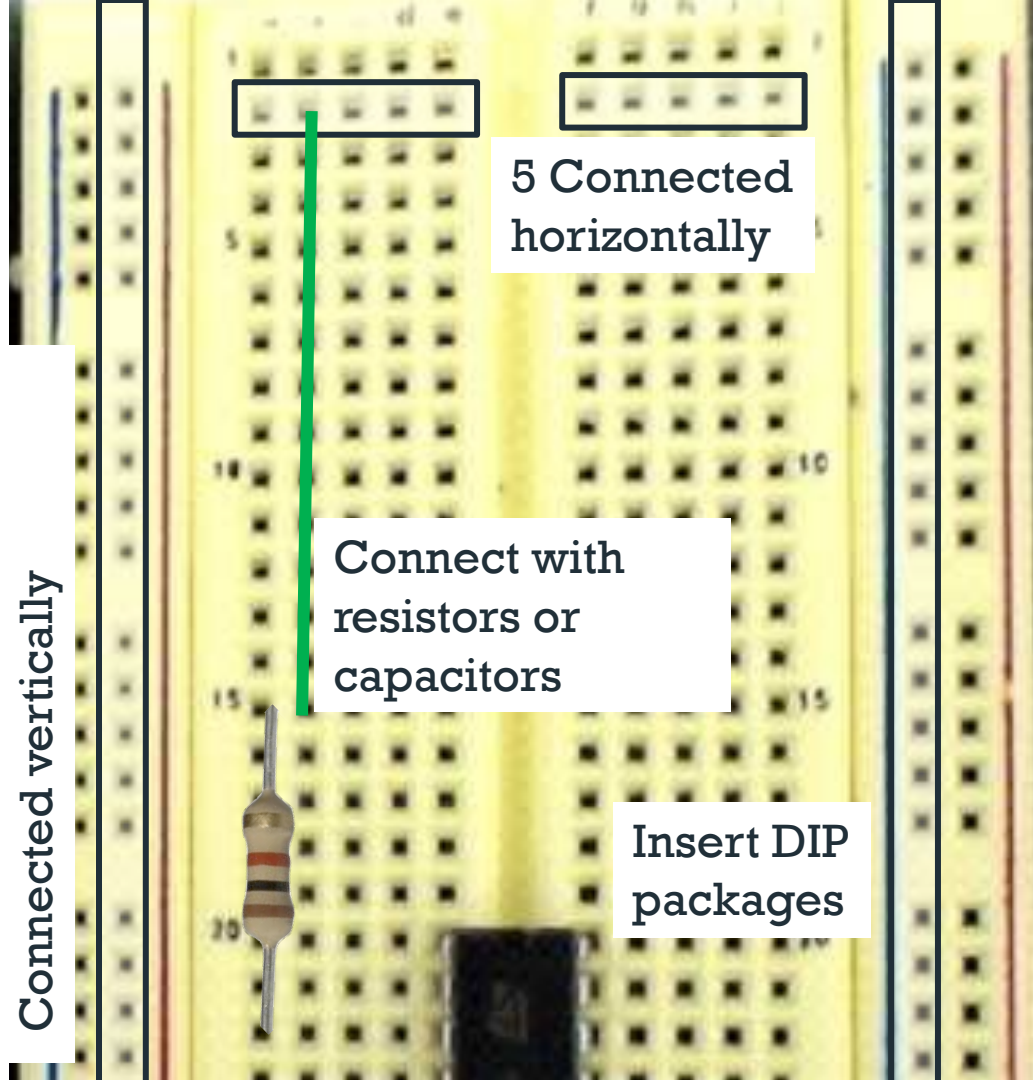

5 Connected
horizontally

Connect with
resistors or
capacitors

Insert DIP
packages

Things to do before next Wednesday:

- Pickup classkit from TA during Office Hours (OH).
- If you are unregistered and want to take this course:
 - Juniors: Email Katie (meamugra@seas), cc:me
 - All others can add the course as normal.
- If you want to place out of this course:
 - Send request email to yim@seas.upenn.edu to get tested.
- Lab 0: Equipment usage - is due next Wednesday
 - Recitation Friday will cover some of the material that is due