

Lecture 14

DC Motors and driving them

Stuff

COVID19 RED PASS


- Non-compliance red pass. Starting next week you will not be allowed in academic spaces (e.g. GMlab)
- To remove non-compliance Go to Dubois or Houston hall for screening test. No reservation required.
- Schedule bi-weekly tests to prevent redpass non-compliance.

Other news: laser cutting/3D printing at Tangen Hall

https://venturelab.smapply.io/prog/venture_lab_membership/

- Open and free to all university students
- Takes up to 15 days to process

 Waldo Music – Feel it still – by Portugal the man



More Waldo stuff

- Grouped choreography: After 3.1, similar architecture projects will be grouped and have an optional "dance" routine to composite together into more interesting music video.
- Long Stem Potentiometers are back in stock. If you choose to use a different sensing modality you will receive extra credit.
- Waldo project feedback on Piazza thread:
 - Is my idea too difficult (hard to gauge difficulty)?
 - Is my idea too easy (will be graded poorly for lack of ambition)?

Agenda

- 01. DC Motors + Solenoids
- 02. Driving DC motors with H-bridges


Motor Types

- Many kinds of electric motors:
 - DC motors,
 - AC motors,
 - Brushless motors,
 - Stepper motors,
 - Variable reluctance
 - Permanent magnet
- We will only focus on **DC motors**
 - Most common small motor
 - Simplest to control
 - Cheapest



Where to use motors in this class?

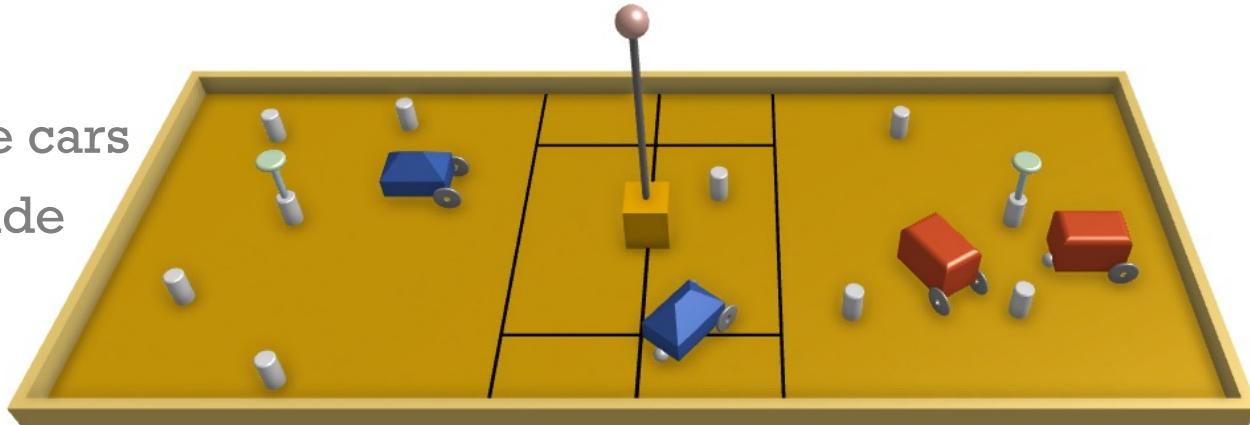
- Lab 4 will include little cars
- Final project will include a mobile base



- You may choose motors that will enable fast/strong mobile bases.
- There maybe contact (pushing contests) between vehicles. The winner will often be determined by the chosen motor.


02

DC Motors + solenoid

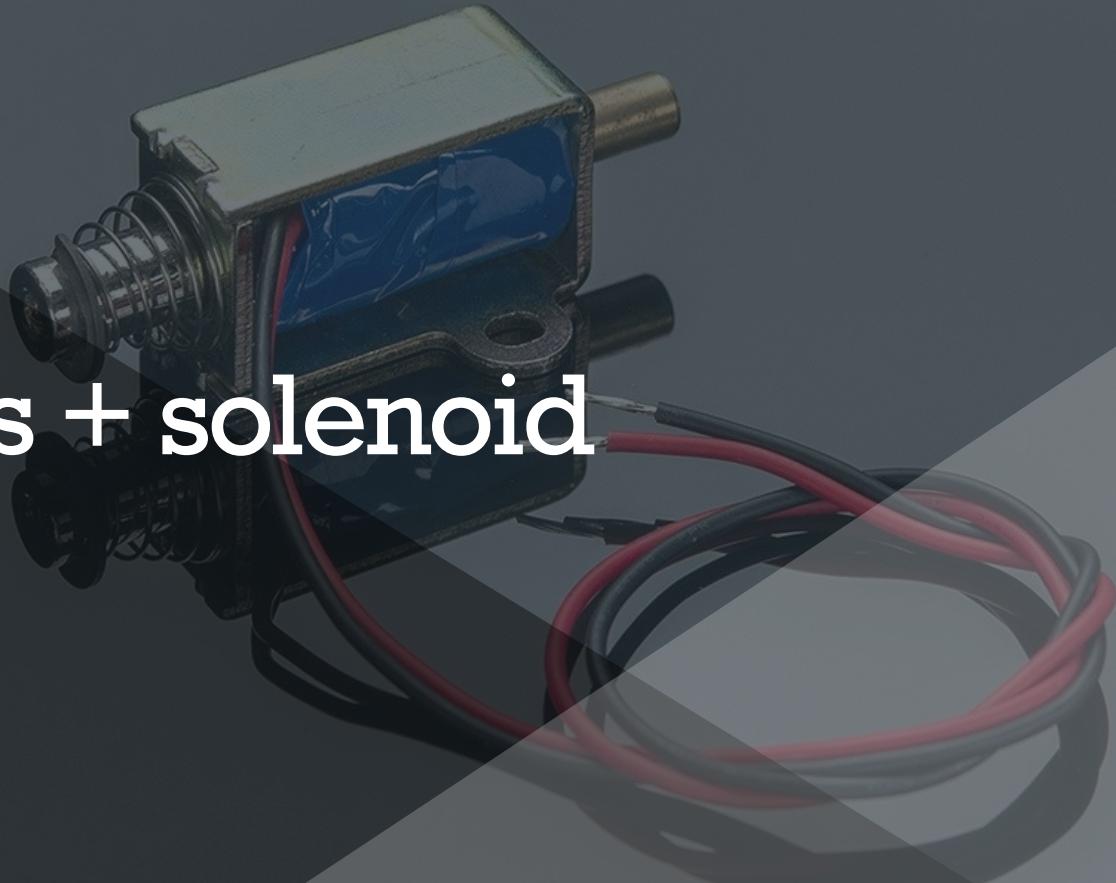


What is a solenoid?

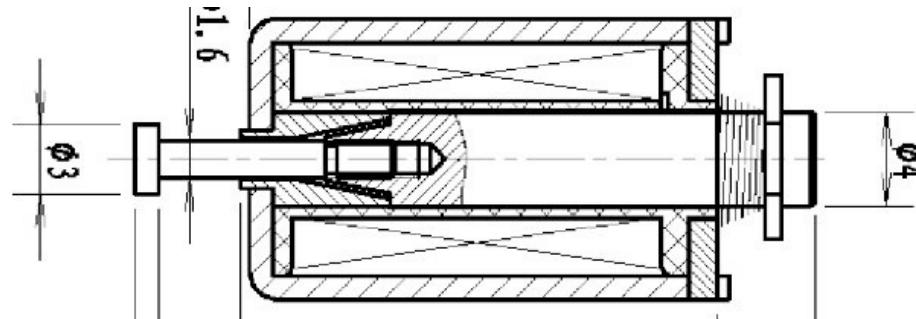- Magnetic plunger surrounded by a coil
- The plunger can move in or out to push against something.
- Moves quickly



Mini Push-Pull Solenoid (in GM lab)

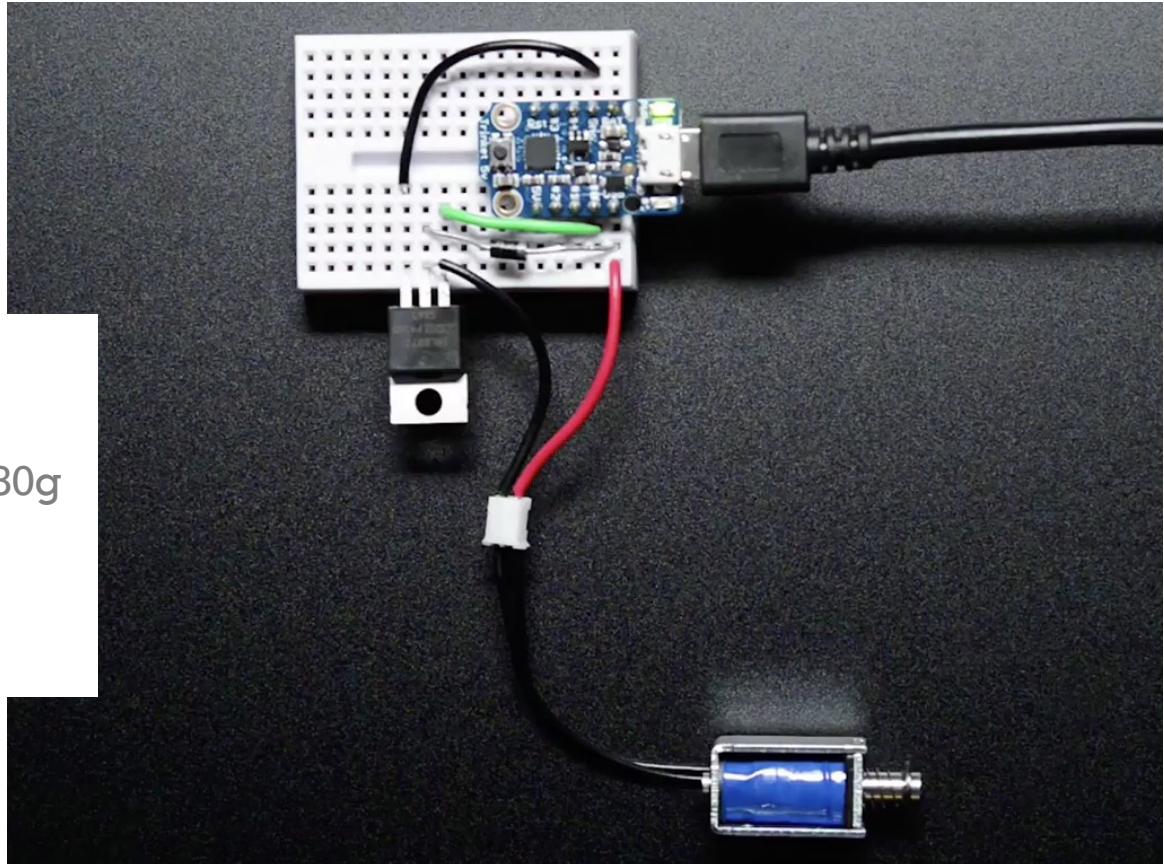- Rated Voltage: 5V
- Current (at DC 5V): 1.1A
- Throw (at DC 5V): 3mm / 80g



MEAM516 2019 – Solenoid driven music




Andrew and his team

<https://www.youtube.com/watch?v=jNhjGteu8xc&feature=youtu.be>



Shaun, Allie and their team

Ideal Electrical Model of a DC motor

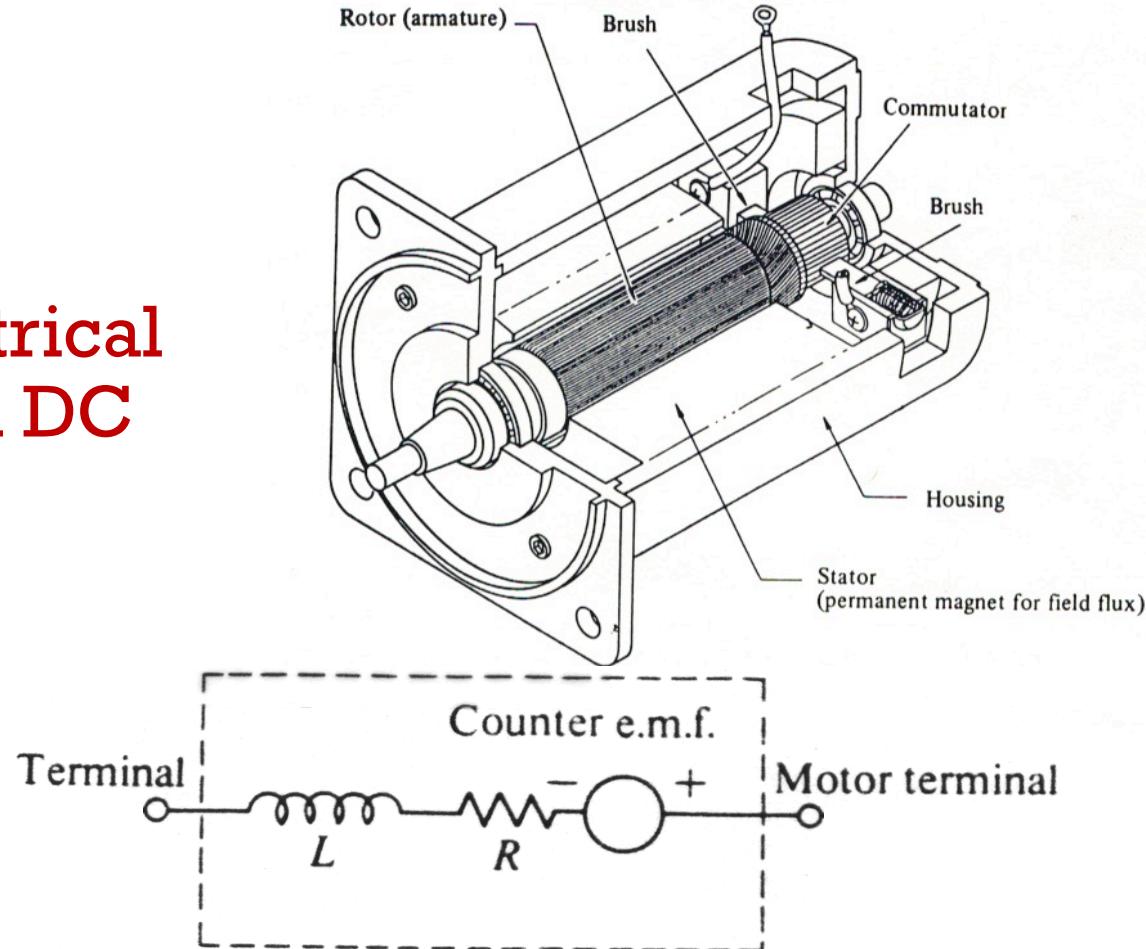


Actuators: Important properties?

Inputs:


- Voltage
- Current

Outputs:

- Speed
- Force/Torque
- Range of motion

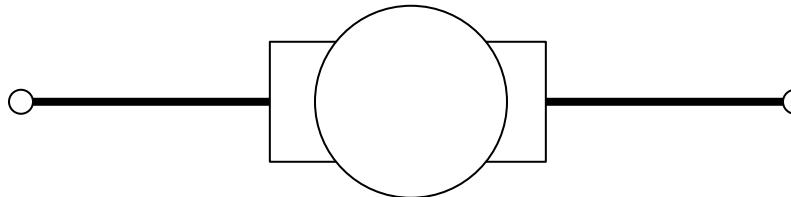

Motor

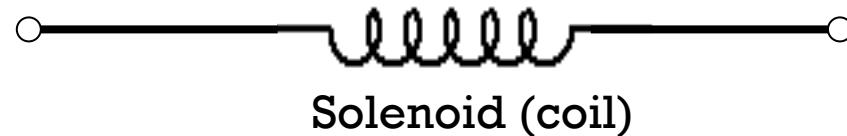


Solenoid (coil)

Basic Physics: Lorenz Force

$$\vec{F} = i\vec{l} \times \vec{B}$$

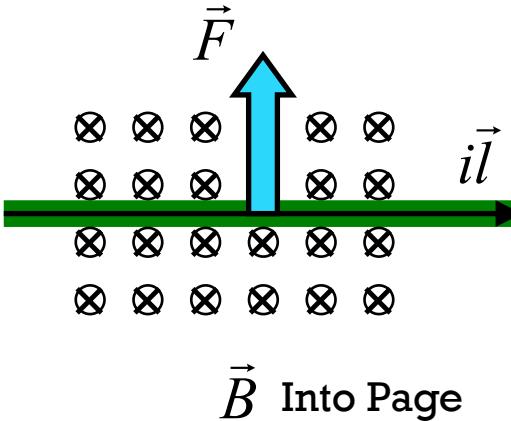Force on a Wire Carrying Current
Through a Magnetic Field




$$\tau = K_T i$$

For some motor with
torque constant K_T

Basic Physics: Faraday's Law

$$\mathcal{E} = -\frac{d}{dt} \int_A \vec{B} \cdot d\vec{A}$$

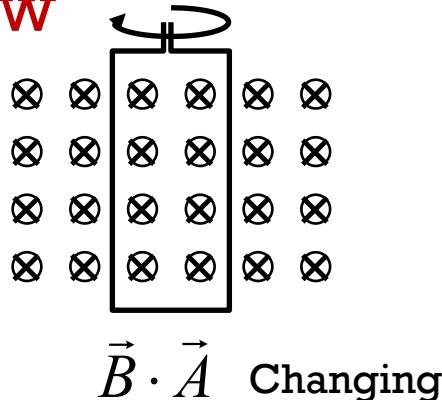Electromotive Force (Voltage)
Generated by Rate of Change of
Magnetic Flux Enclosed by a Coil





$$V = K_E \omega$$

For some motor with
speed constant K_E

Ideal Electrical Model of a DC motor (alone)

Q1: Plot Speed vs Torque

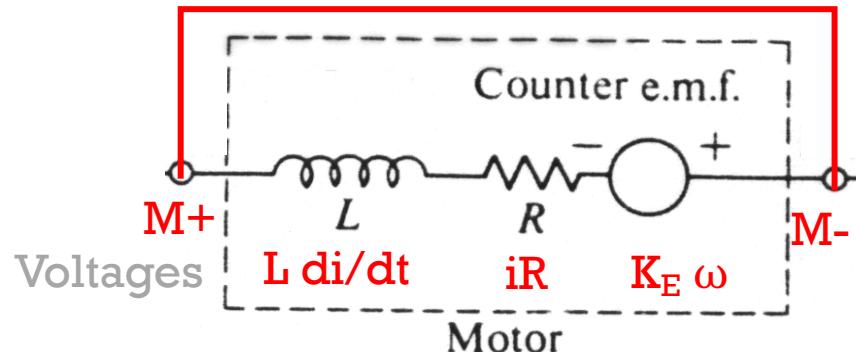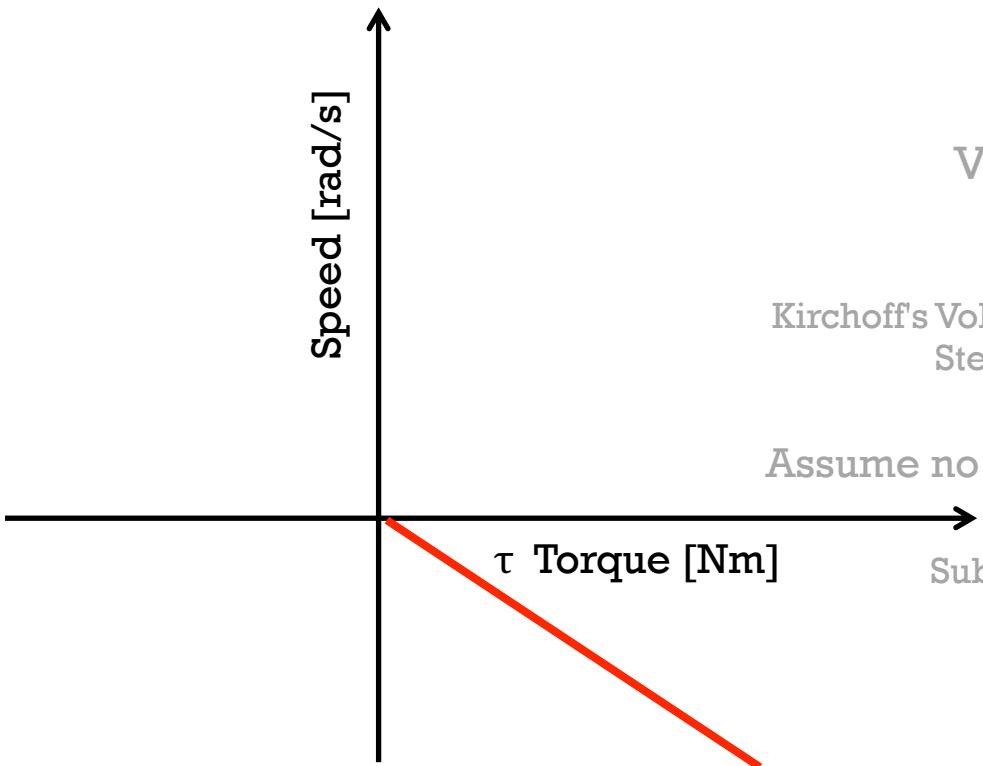

Kirchoff's Voltage Law
Steady state

Assume no friction

Substitution
Algebra

$$0 = L \frac{di}{dt} + iR + K_E \omega$$

$$0 = 0 + iR + K_E \omega$$

$$\tau = K_T i$$



$$0 = 0 + \tau R/K_T + K_E \omega$$

$$\omega = -\tau \underbrace{R/(K_T K_E)}_{\text{Motor Constants}}$$

Motor Constants

Ideal Electrical Model of a DC motor w/battery

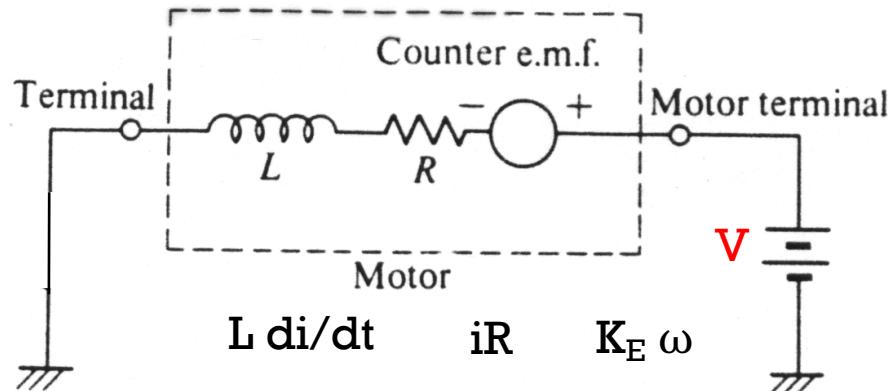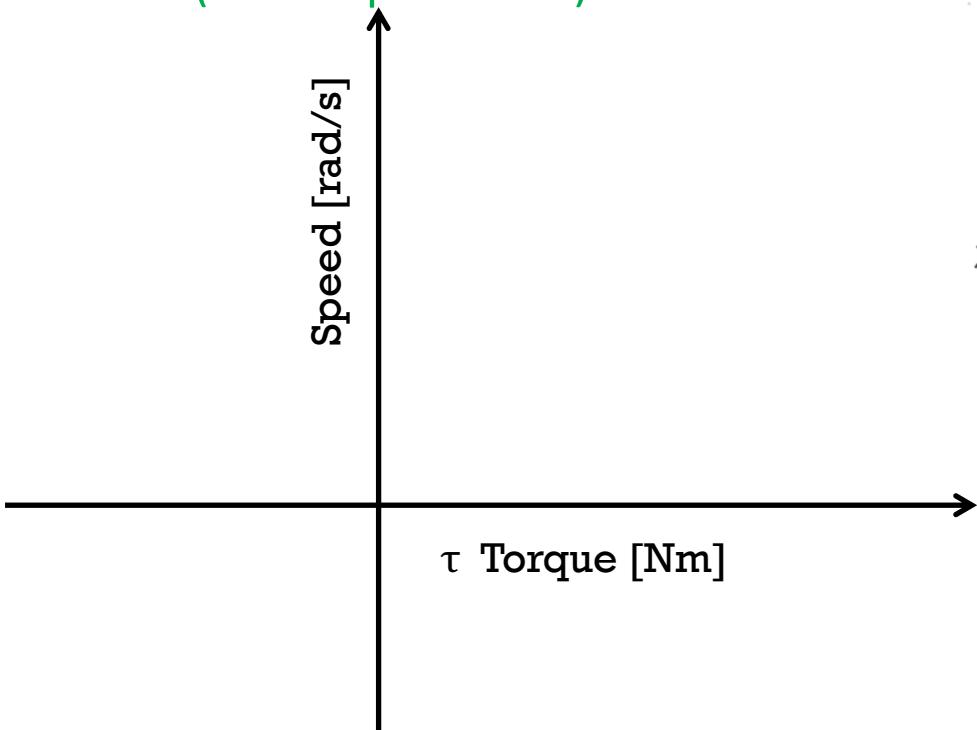Q2: Plot Speed vs Torque
(which quadrant?)



$$V = L \frac{di}{dt} + iR + K_E \omega$$

$$V = 0 + iR + K_E \omega$$


$$\tau = K_T i$$

$$V = 0 + \tau R / K_T + K_E \omega$$


$$\omega = -\tau \underbrace{R / (K_T K_E)}_{\text{Motor Constant}} + V / K_E$$

Motor Constant

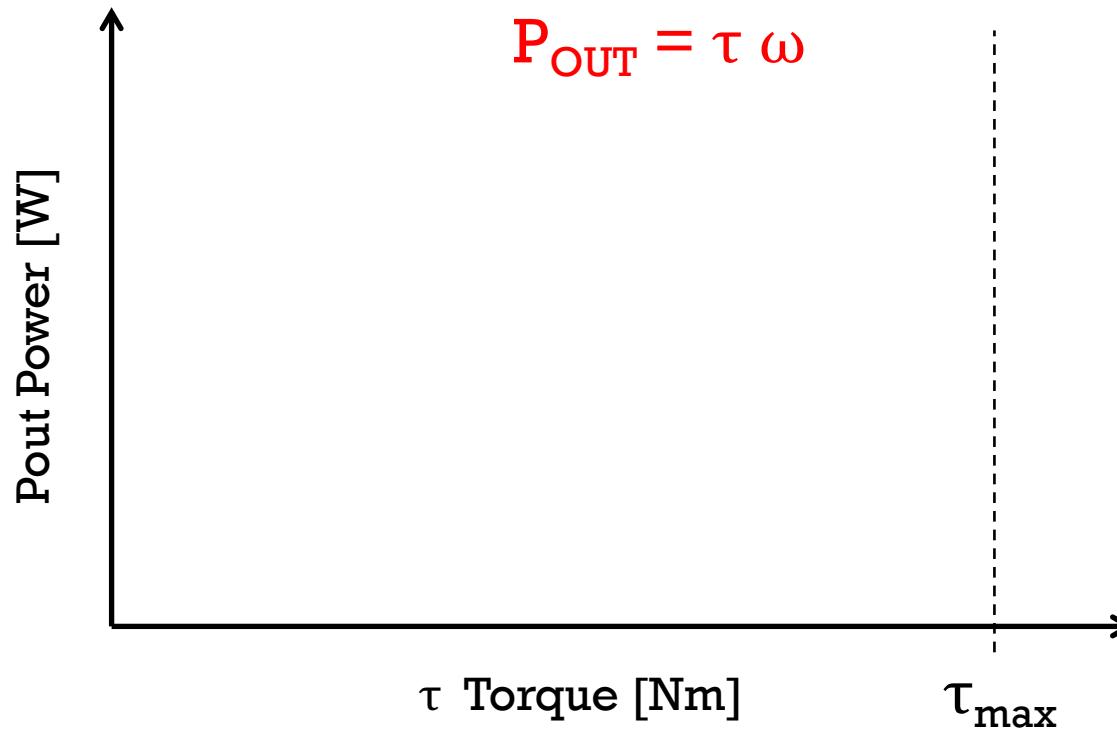
Q3: Plot (Mechanical) Output Power vs Torque (Does the curve hit the origin?)



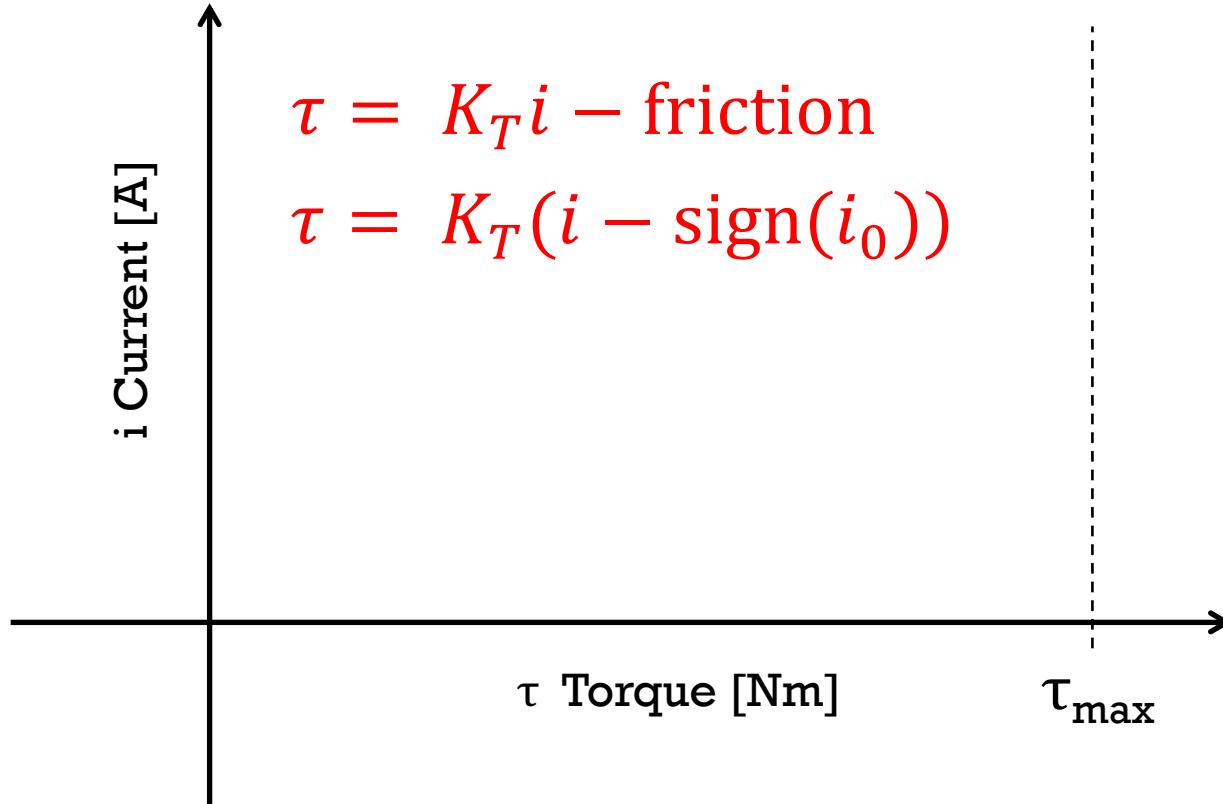
Q4: Plot Current vs Torque (Does the curve hit the origin?)



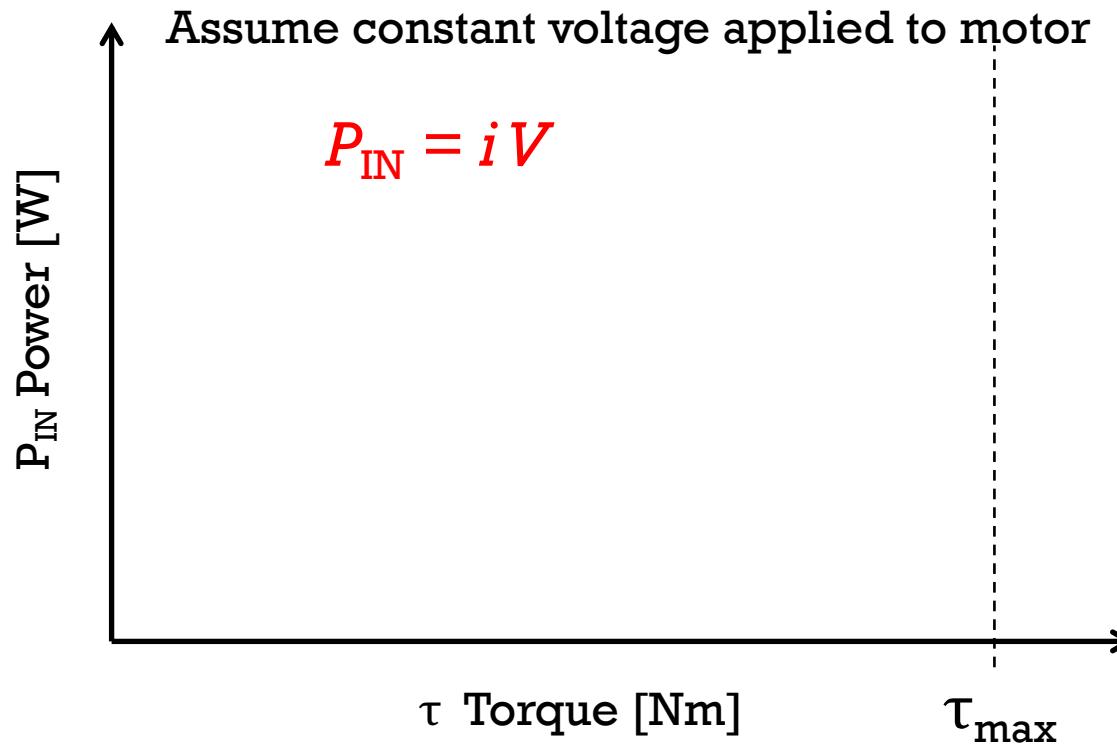
Q5: Plot (Electrical) Input Power vs Torque (Does the curve hit the origin?)



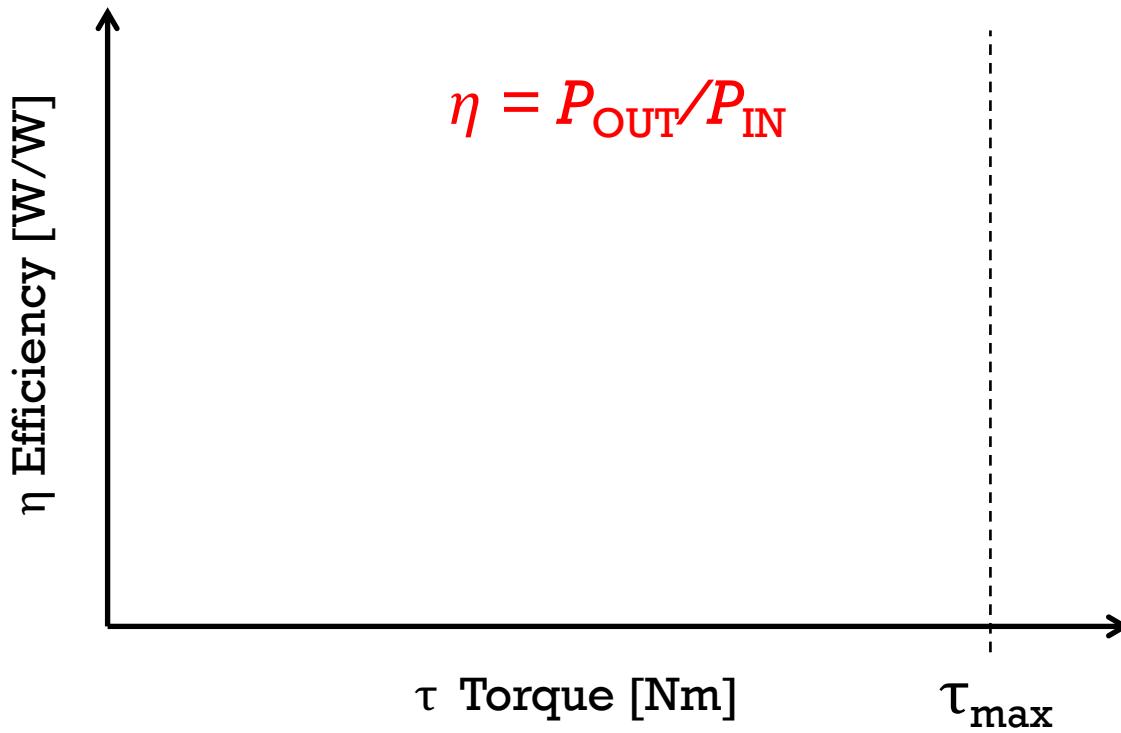Q6: Plot Power Efficiency vs Torque (where is the peak efficiency?)



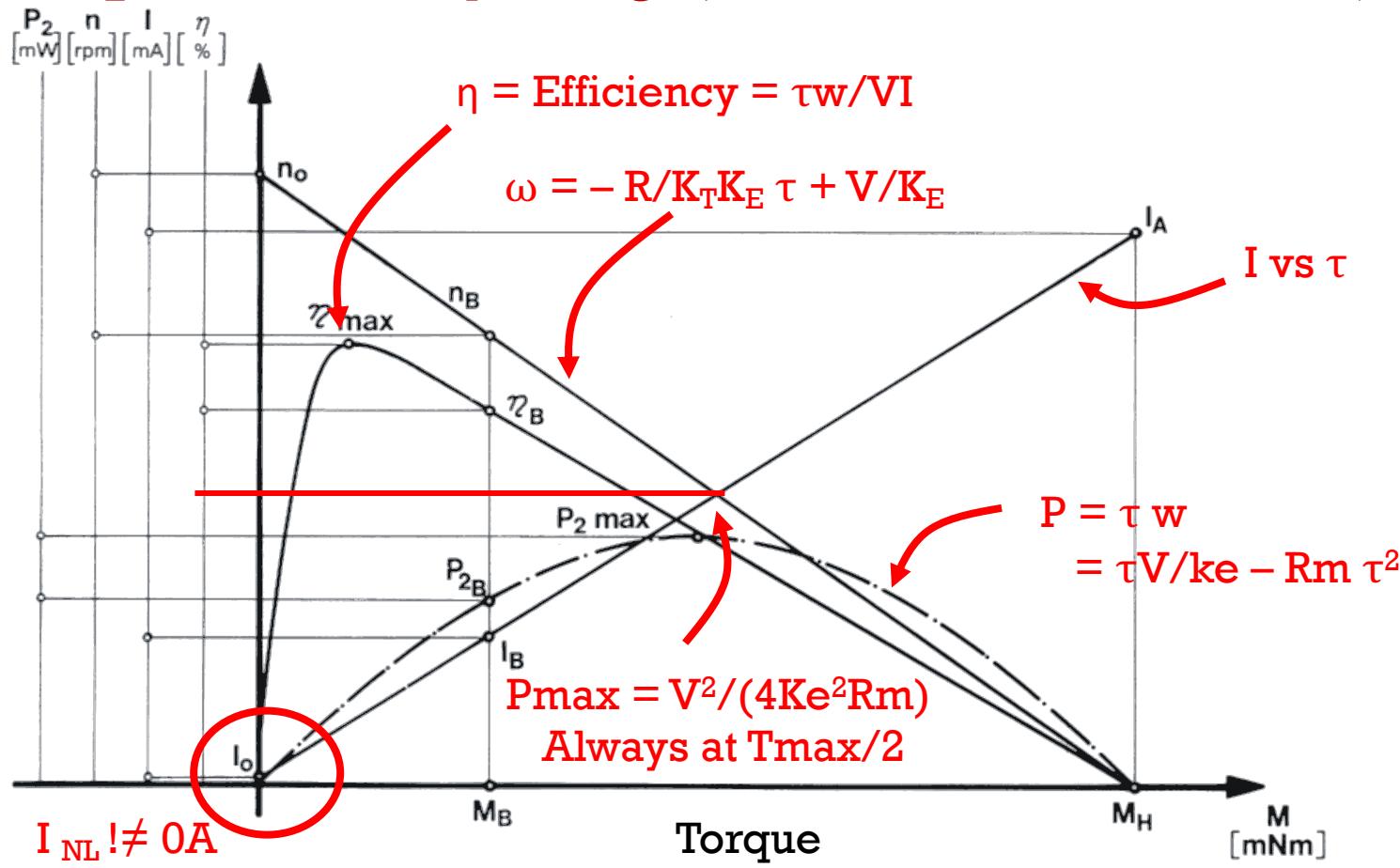Torque vs Everything (for constant motor V)



Choosing a motor

- Voltage specifications
 - indicates maximum voltage
 - doesn't say anything about motor capability
- Wattage
 - indicates maximum power
- Motor constants
 - indicate slope of torque/speed curve
- Stall torque
- Stall current
- No load speed

Pololu part #
1516
1124
2368
2367
2365
2364
992



Some terms and symbols

- K_T Torque constant [Nm/A], apply A get τ
- K_V Velocity constant [rad/s /V], apply V get ω
- $K_B = K_E$ Back EMF constant [V /Rad/s], apply ω get V

Note:

$$K_T = 1.3524 K_E \text{ [oz-in/A ; V/kgpm]}$$

$$K_T = K_E = 1/K_V \text{ when using SI units Nm/A : V / rad/s}$$

$$\omega = -\tau R/K_T K_E + V/K_E$$

Motor exercise

You are handed a motor. The only documentation that you can find shows that the motor chosen has $K_t = 9.33 \text{ in.-oz./A}$ and produces 2.8 in.-oz. at stall when driven at 12V. The design requires that the motor deliver 0.4 in.-oz. at 1500 rpm. The motor was supposed to be driven from a 12V supply. Your boss has asked you:

- a) How can I find out how much current the motor will draw at stall ?
- b) What is K_e ?
- c) How can I find the coil resistance ?
- d) Will the design meet the requirements for torque at the given speed? If not, what changes could you suggest? .
- e) Estimate the current required when running at the design point.

You may assume that there are no internal losses within the motor.

for reference: $K_T = 1.3524K_E [\text{oz-in/A} ; \text{V/krpm}]$

DC Motor Specs

(Maxon Motor catalog)


Labeled by power rating

	Winding number	930	933	934	94	7	938	945
Motor Data								
1 Assigned power rating	W	6.0	6.0	6.0	6.0	6.0	6.0	6.0
2 Nominal voltage	Volt	3.0	7.2	9.0	12.0	12.0	12.0	15.0
3 No load speed	rpm	5080	9270	9460	10700	8120	7770	8460
4 Stall torque	mNm	20.9	42.5	45.7	51.7	2.7	35.1	44.4
5 Speed/torque gradient	rpm/mNm	260	225	213	211	194	227	194
6 No load current	mA	114	101	83	73	50	47	42
7 Starting current	mA	3960	5910	5160	4920	3090	2440	2680
8 Terminal resistance	Ohm	0.757	1.22	1.74	2.11	2.88	1.82	5.60
9 Max. permissible speed	rpm	11000	11000	10000	11000	10000	11000	11000
10 Max. continuous current	mA	1500	1500	1440	1220	312	300	300
11 Max. continuous torque	mNm	7.92	10.8	12.7	12.8	13.4	12.4	13.4
12 Max. power output at nominal voltage	mW	2460	9620	10800	13900	8770	6920	9590
13 Max. efficiency	%	64	73	75	76	75	74	76
14 Torque constant	mNm/A	5.28	7.19	8.85	10.5	13.8	14.4	16.6
15 Speed constant	rpm/V	1810	1330	1080	909	691	664	576
16 Mechanical time constant	ms	29	22	20	19	18	18	18
17 Rotor inertia	gcm ²	10.8	9.23	9.07	8.68	9.07	7.76	8.84
18 Terminal inductance	mH	0.07	0.12	0.18	0.26	0.45	0.48	0.64
19 Thermal resistance housing-ambient	K/W	17	17	17	17	17	17	17
20 Thermal resistance rotor-housing	K/W	2.4	2.4	2.4	2.4	2.4	2.4	2.4
21 Thermal time constant winding	s	7	6	6	6	5	6	6

Stall current?


Bearing limitation

Motor Spec Sheet

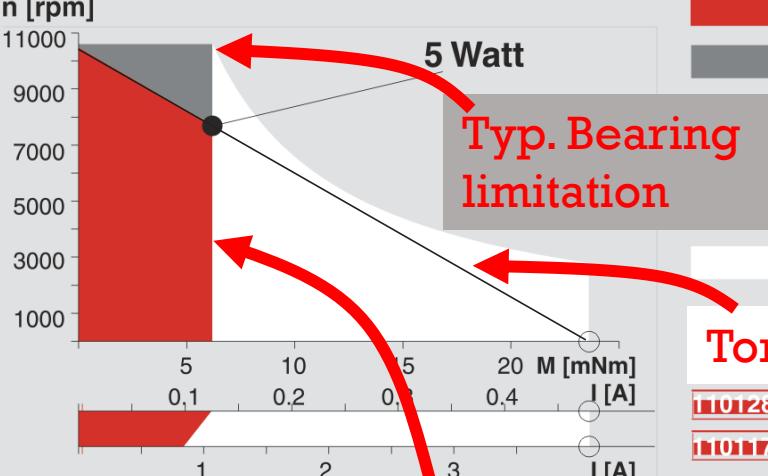Operating Ranges	Comments	Example from page 113
 <p>The graph plots speed (n) in rpm against torque (M) in mNm and current (I) in A. The red shaded area represents the recommended operating range. The grey shaded area represents continuous operation. The outer boundaries of these areas are labeled 'Typ. Bearing limitation'. The inner boundary is labeled 'Typ. Thermal limitation'. A point on the curve is marked with a black dot and labeled '5 Watt'.</p> <p>Typ. Thermal limitation</p> <p>Speed (n), torque (M), current (I): The outer edges of the values depicted represent limits for continuous and short term motor operation. Values listed in the tables (lines 3, 4, 6, 7, 12 and 13) are valid for operation at nominal voltage (line 2). These are therefore values which are only reached when operating the motor at higher voltages</p>	<p>Recommended operating range</p> <p>Continuous operation In observation of above listed thermal resistances (lines 19 and 20) the maximum permissible rotor temperature will be reached during continuous operation at 25°C ambient. = Thermal limit</p> <p>Short term operation The motor may be briefly overloaded (recurring).</p> <p>Torque Speed Curve</p> <p>110128 Motor with high resistance winding (Line 8) 110117 Motor with low resistance winding (Line 8)</p> <ul style="list-style-type: none"> ● Assigned Power Rating P_{2T} (W) (Line 1) ○ Starting current I_A at nominal voltage (Line 7) as well as related stall torque <p>M_H (mNm) (Line 4) $I_A = \frac{U}{R} \cdot 10^3$ (mA)</p> <p>110128 Winding number with the related current curve at the appropriate torque.</p>	

Motors provided for Lab 4

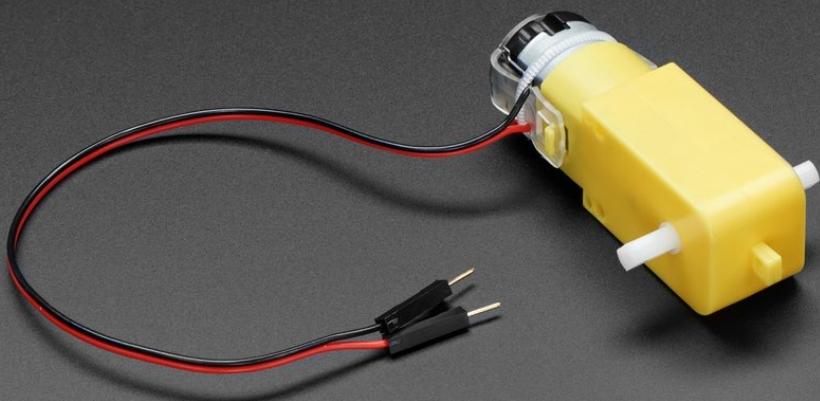
- <https://www.adafruit.com/product/3777>



- Rated Voltage: 3~6V
- Continuous No-Load Current: 150mA
- Min. Operating Speed (3V): 90 RPM
- Min. Operating Speed (6V): 200 RPM
- Stall Torque (3V): 0.4kg.cm
- Stall Torque (6V): 0.8kg.cm

03


Driving DC Motors

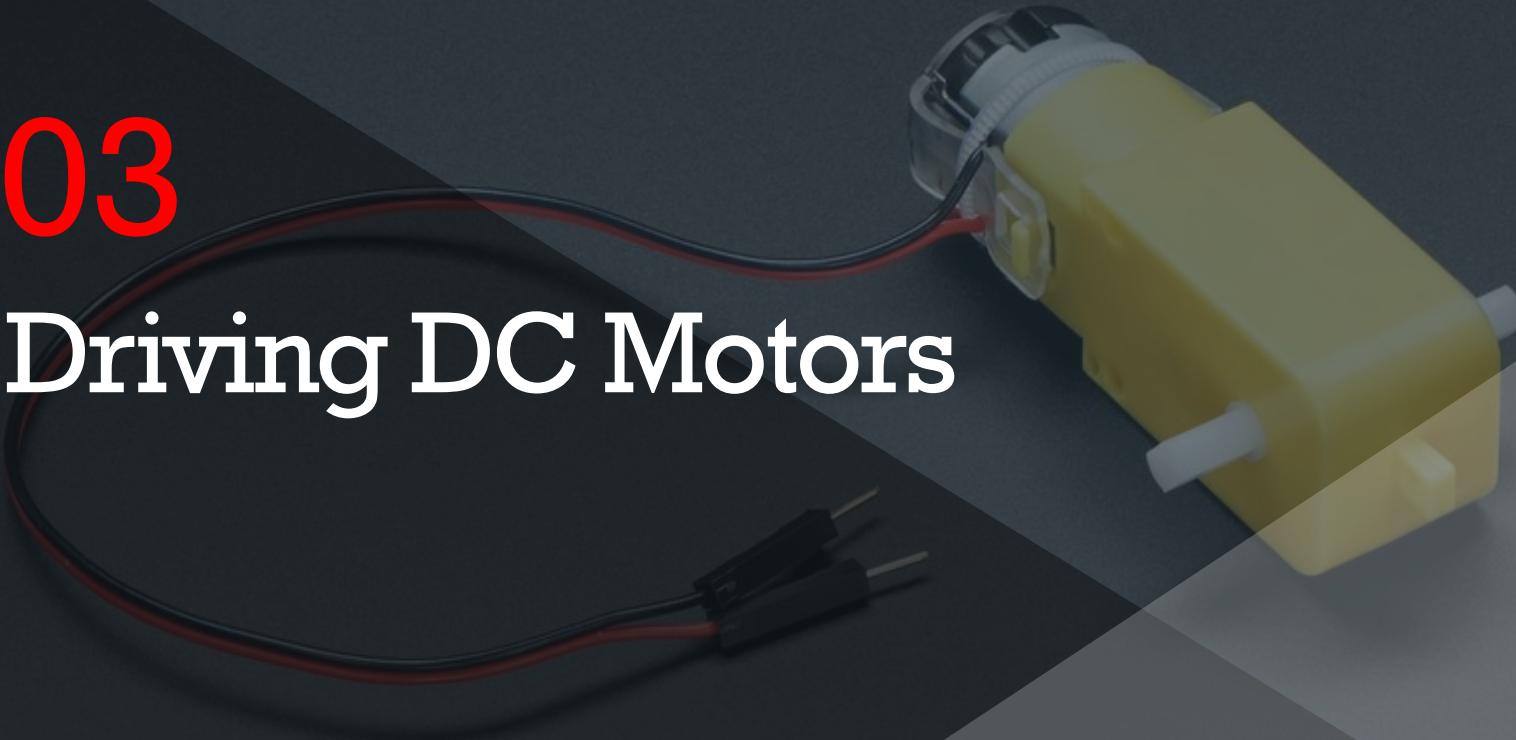

Driving a motor

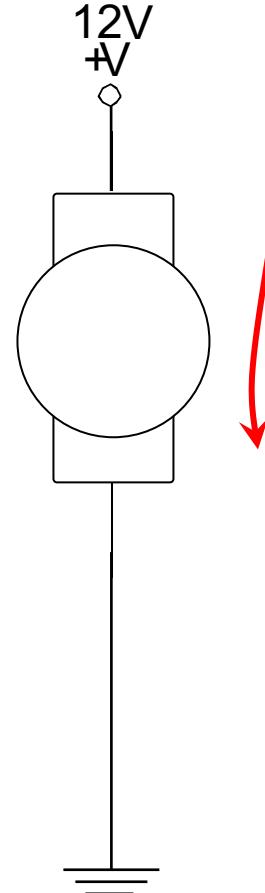Q7: To calculate how much current will flow:

- In general, what does it depend on?
- Worst case, what does it depend on?
- Can my driver (e.g. transistor) handle that much current?



Motors may require large currents

- The yellow motors for Lab 4 ~1.5 Amps @ 5V stall
- Motors in typ. MEAM510: 1 to 6 Amps @ stall
- Motors in typ. quadrotor 5 to 30 Amps @ stall
- Motors in typ. electric car 100's of Amps


Pololu part #
1516
1124
2368
2367
2365
2364
992



GM Lab Options for Driving Large Currents

- ULN2003 Seven Darlington Array ~0.5A
- TIP31C NPN Transistor 3A
- TIP102 NPN Darlington 8A
- IRLB8721 N-channel MOSFET 25A
- IRF9520 P-Channel MOSFET ~6.8A
- FQP8P10 P-Channel MOSFET 4A
- IRF630 N-Channel MOSFET 5.9A
- SN754410 H-bridge driver 1A


Switching directions

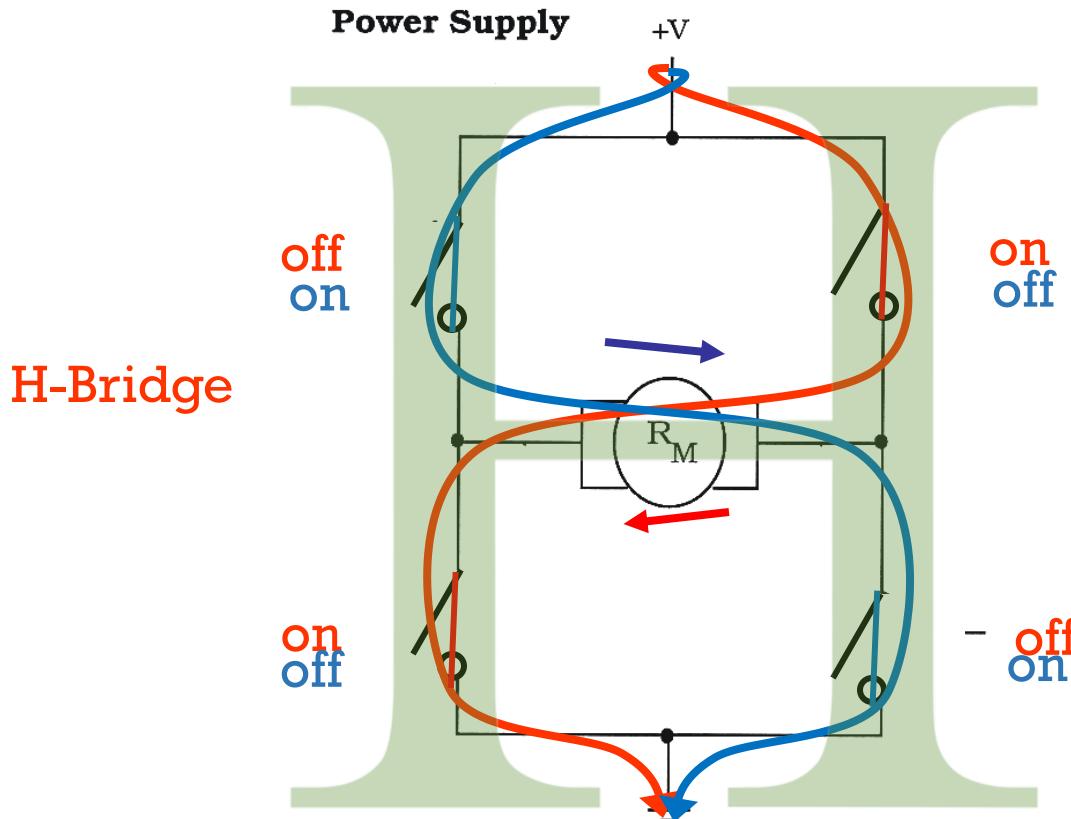


Other Switch Options

No power from supply, but
Current flows from back EMF
Acts as a brake

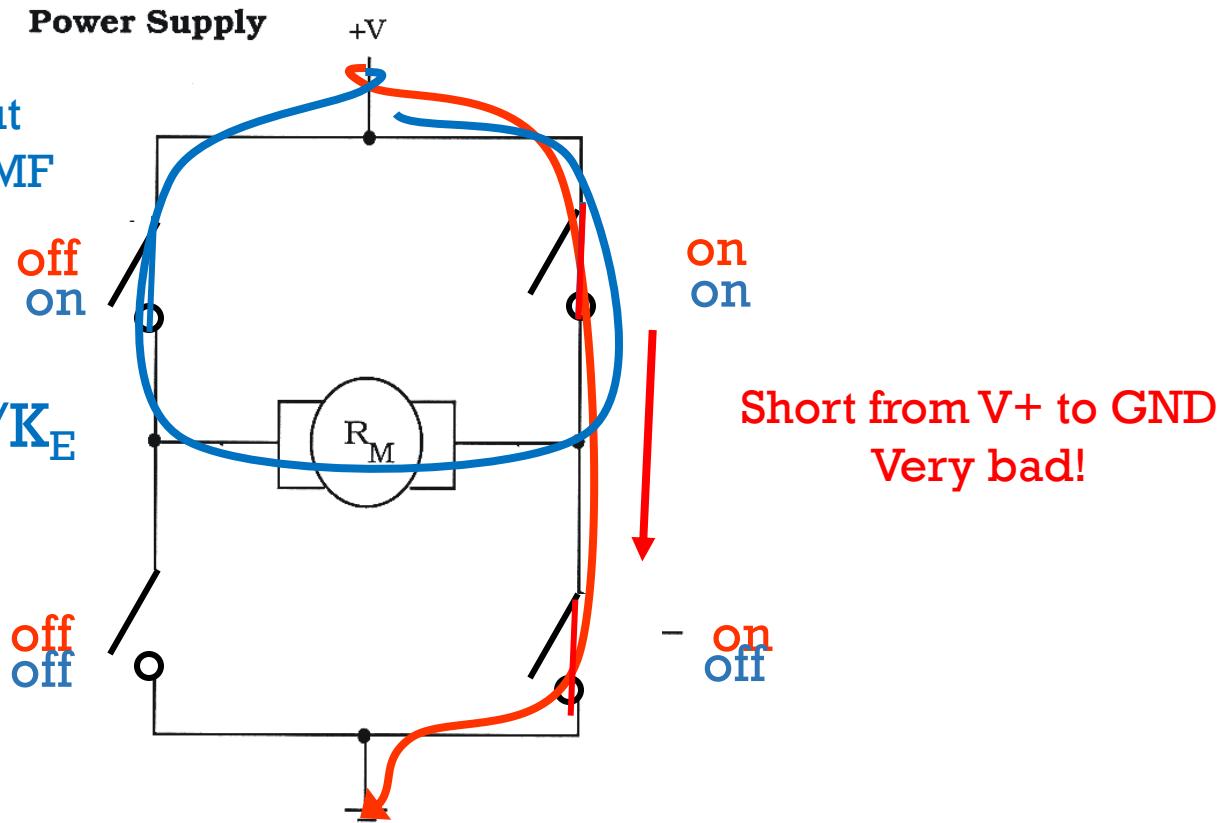
$$\omega = - \frac{R}{K_T K_E} \tau + \frac{V}{K_E}$$
$$\tau = -\omega \frac{K_T K_E}{R}$$




Half H-Bridge

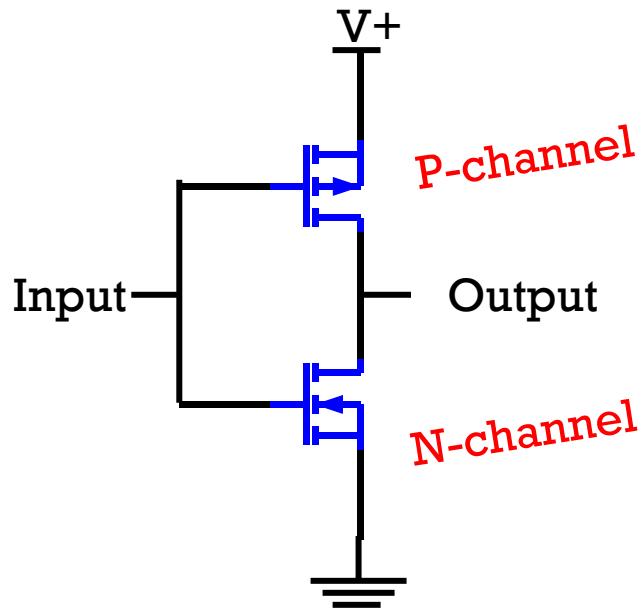

Rough schematic

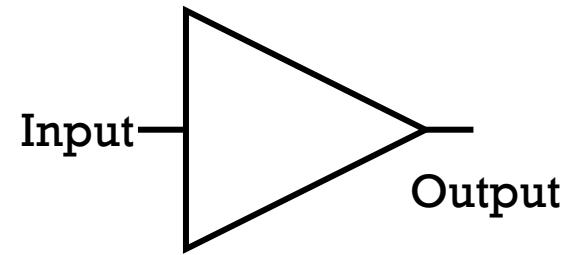

Half-bridge Symbol

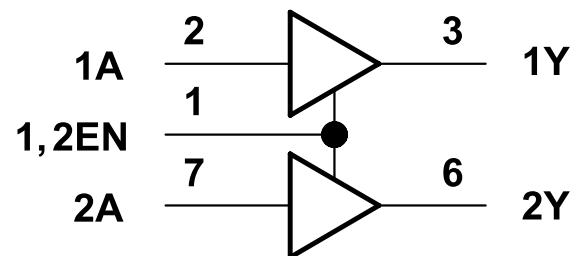


Typ H-bridge Schematic

Recall



Effect of Large Inductance

Circuit simulation package


$$v(t) = L \frac{di(t)}{dt}$$

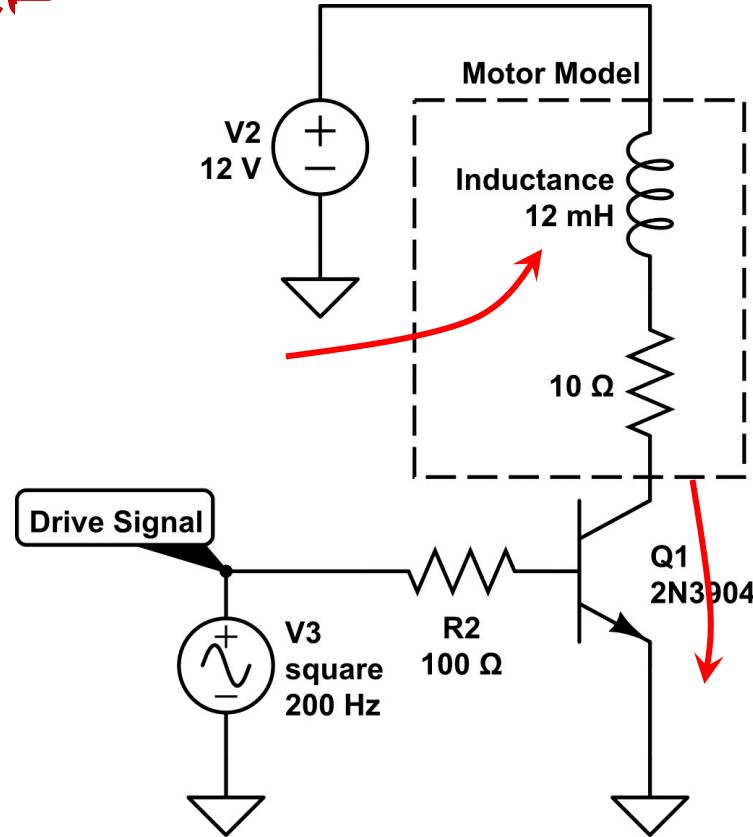

Collector Voltage

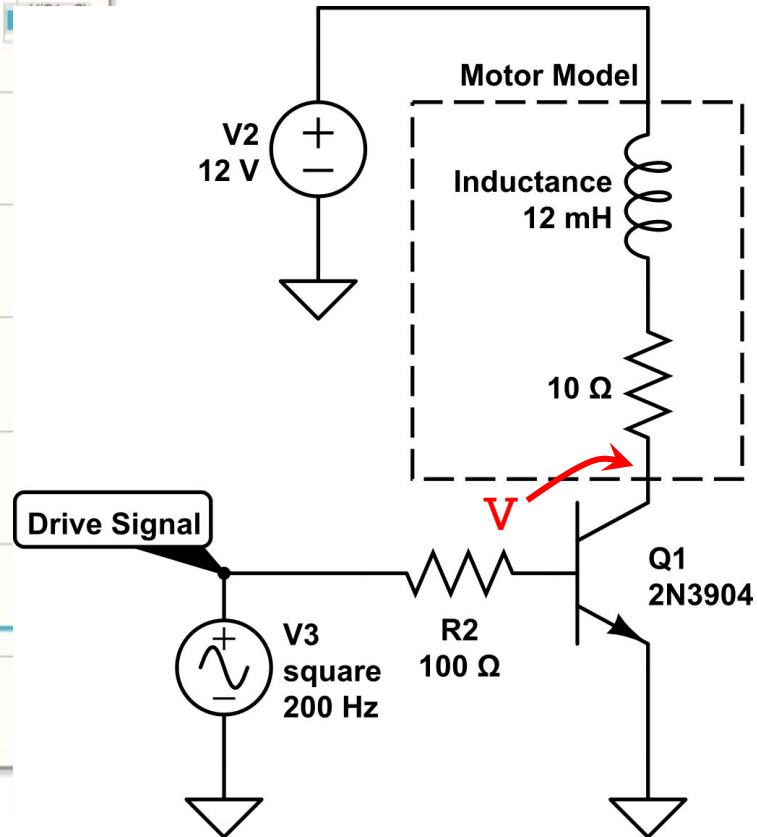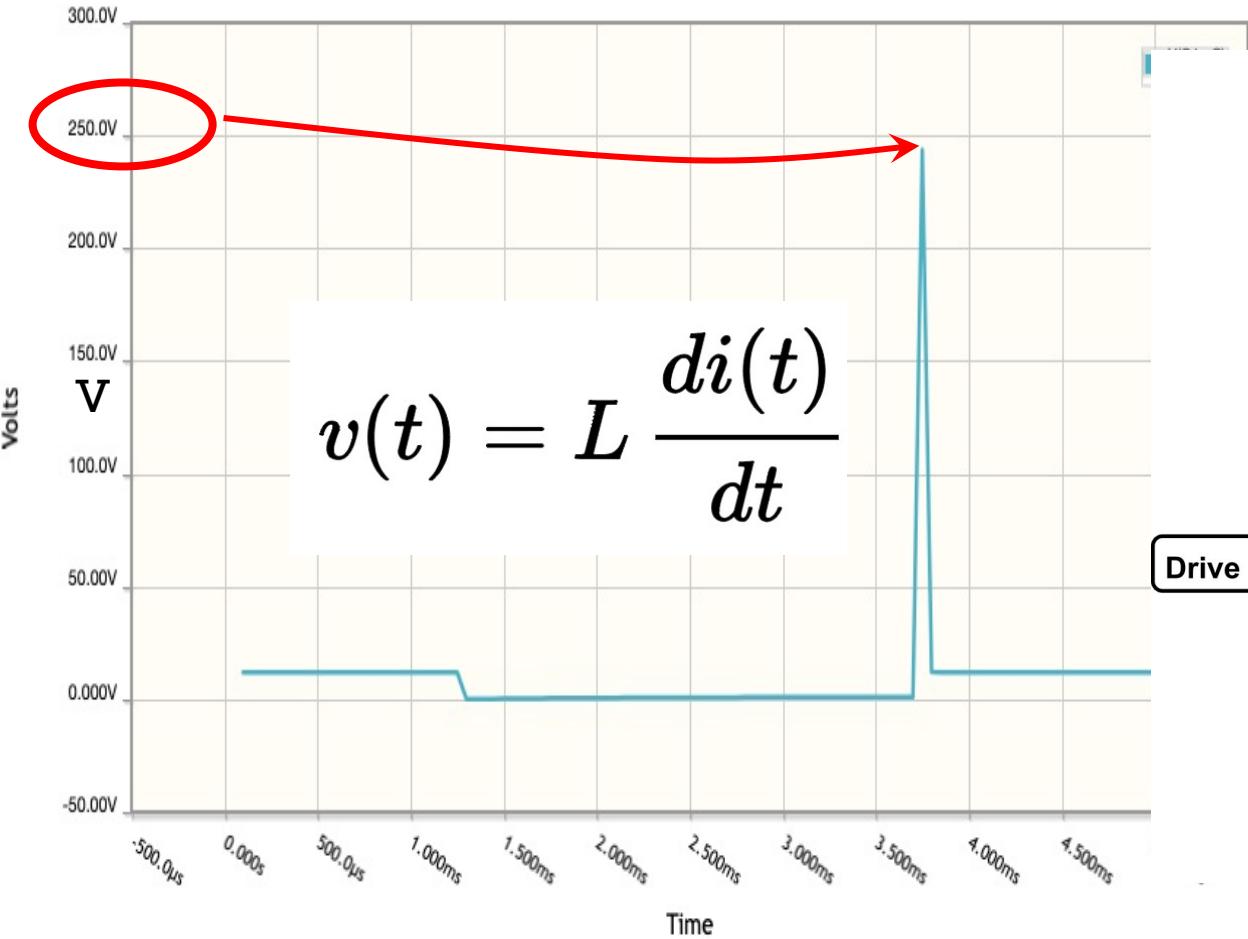

Recall Large inductance

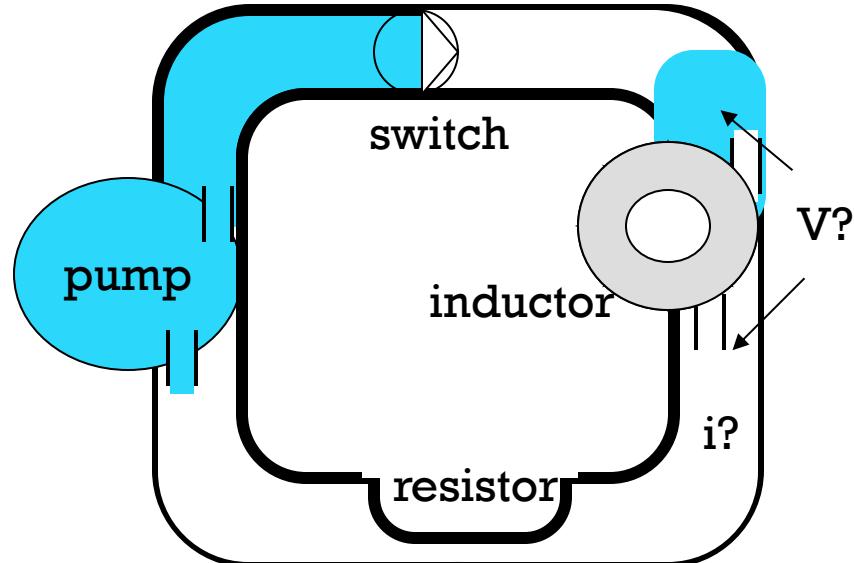

$L i$ similar to mv , momentum

Initial state, switch is off

no voltage across inductor
no current in inductor

Switch turns on

hi voltage seen on one side
no current in inductor

Steady state

voltage equal on both sides
current in inductor


Switch turns off

hi voltage on other side
no current in inductor

Steady state

voltage equal on both (0)
no current in inductor

Large inductance with clamping diode

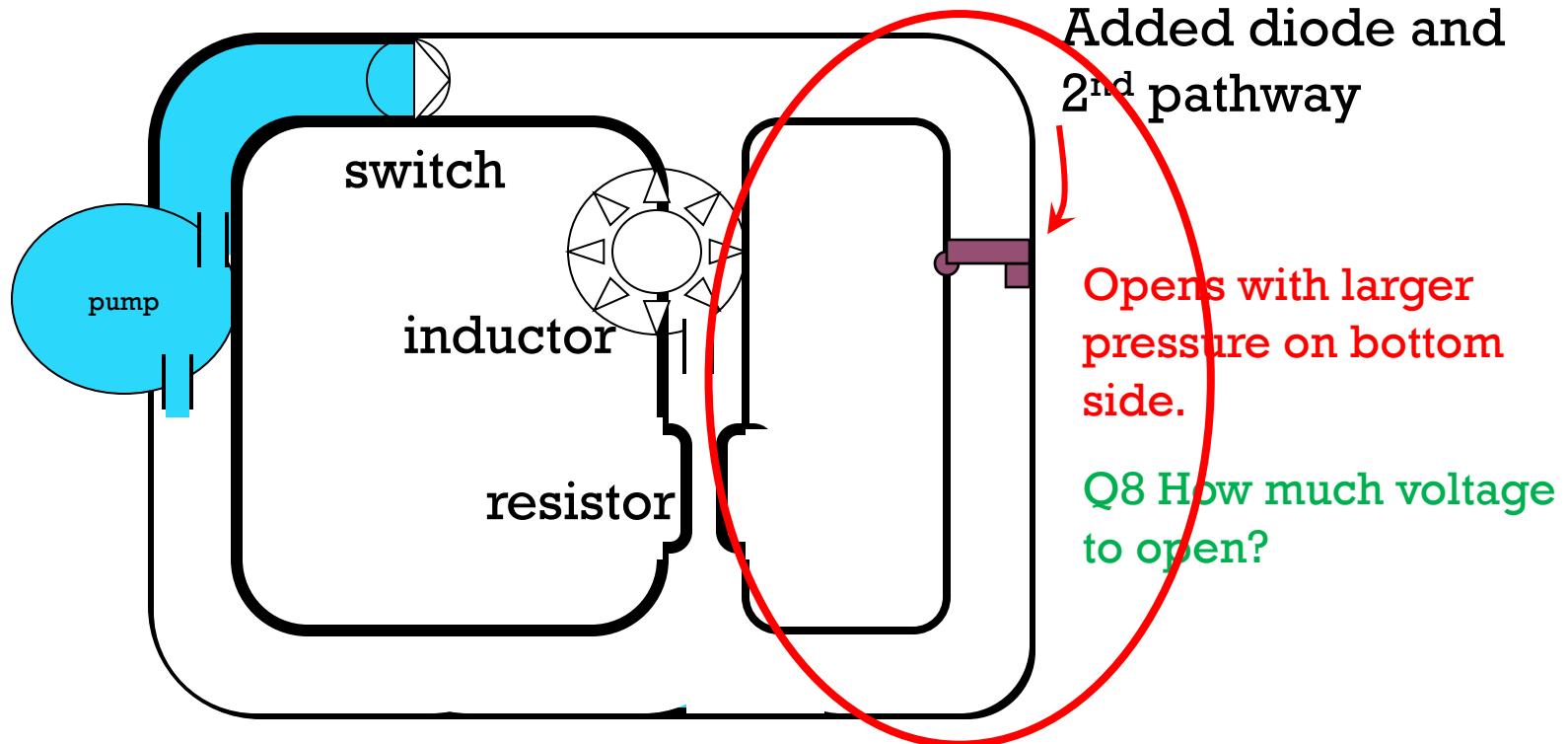

Snubber Diode


AKA Flyback Diode

AKA Clamp Diode



AKA Suppression Diode

AKA Commutation Diode



AKA Free Wheeling Diode

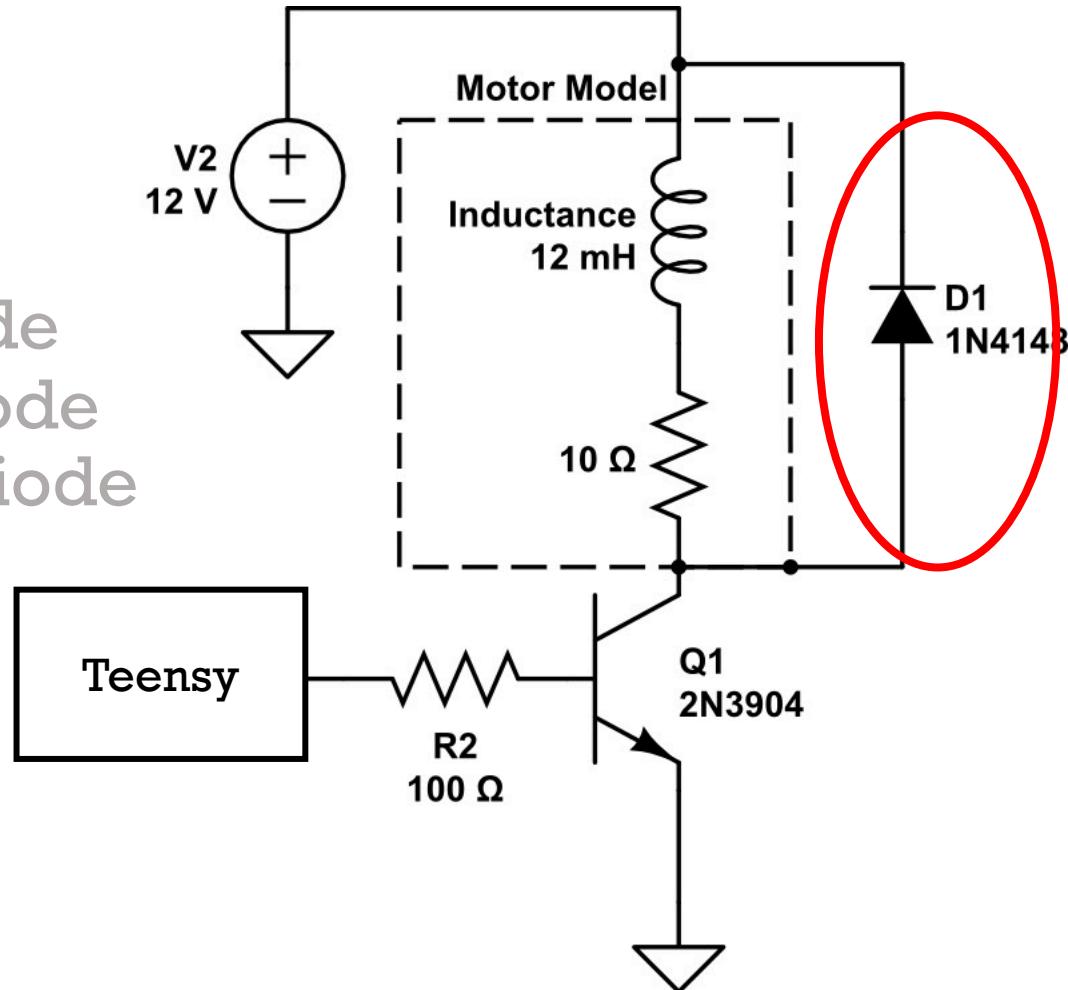


Collector Voltage with Diode Snubber

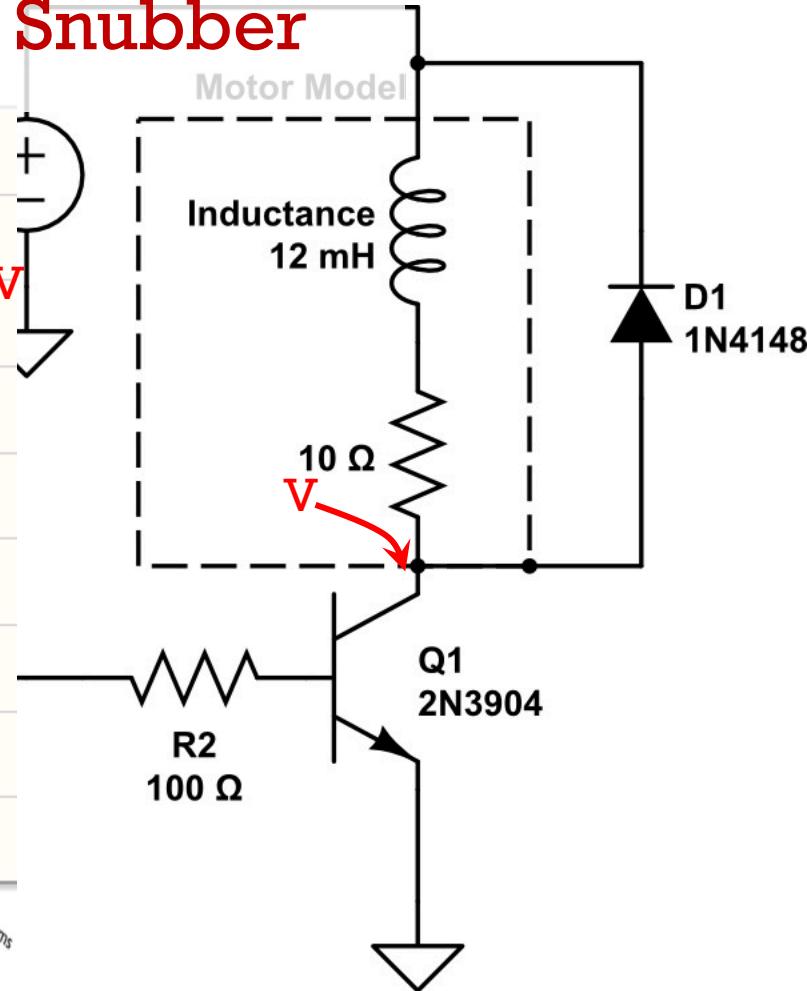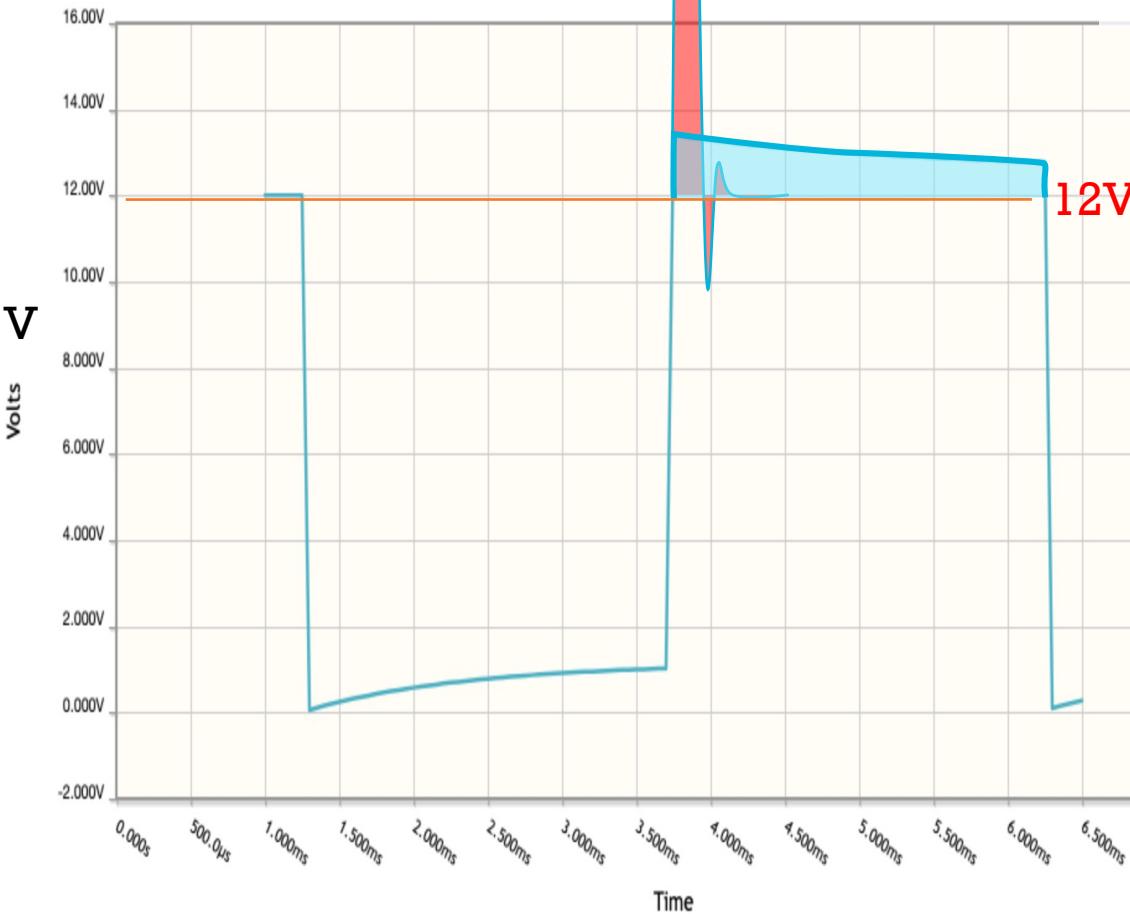

Inductor Current with Diode Snubber

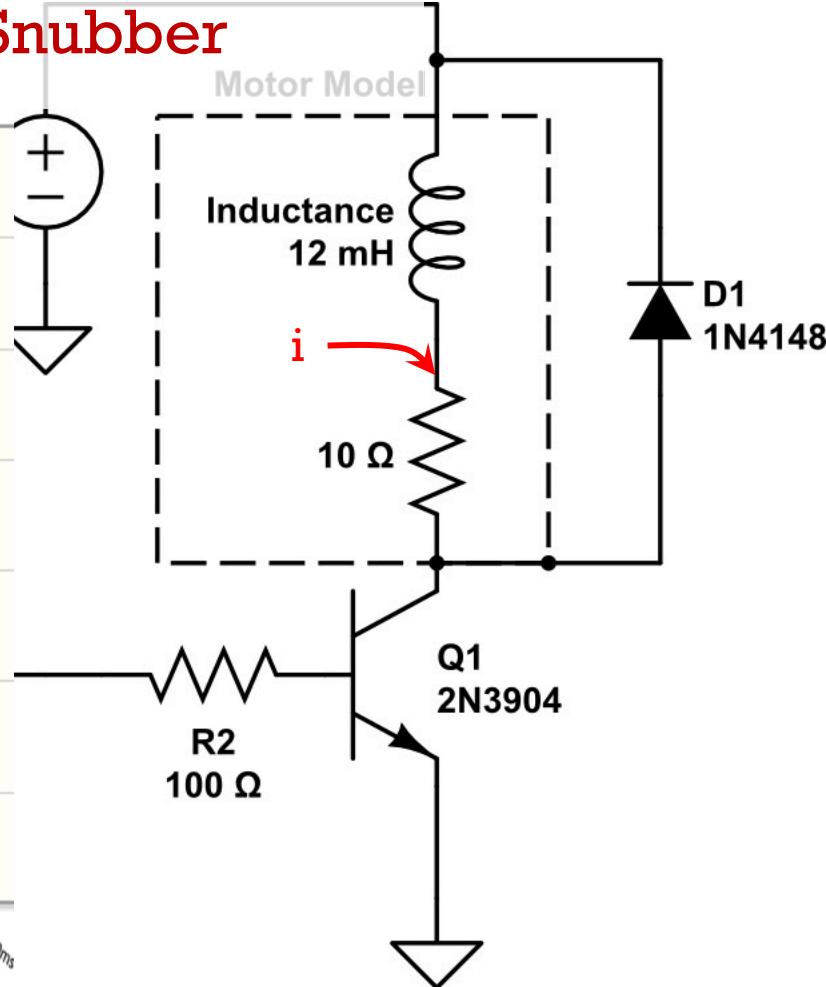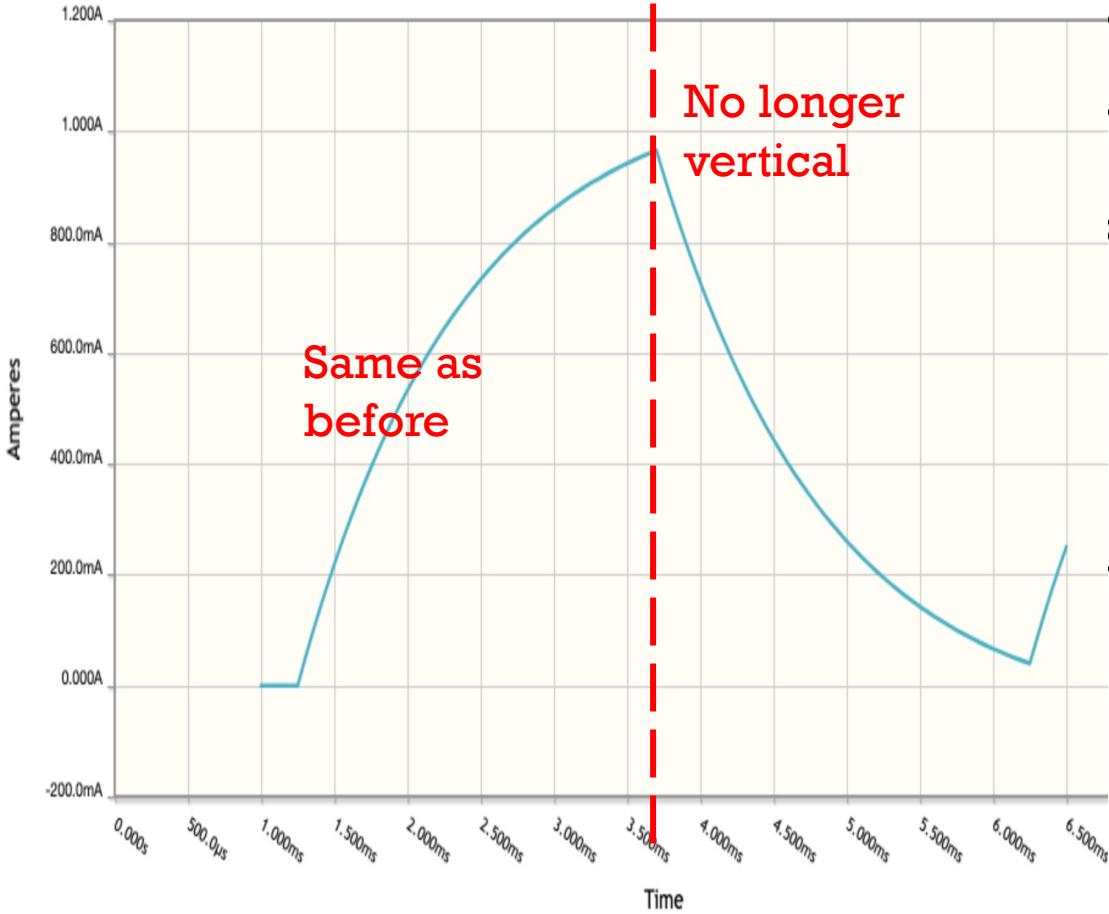


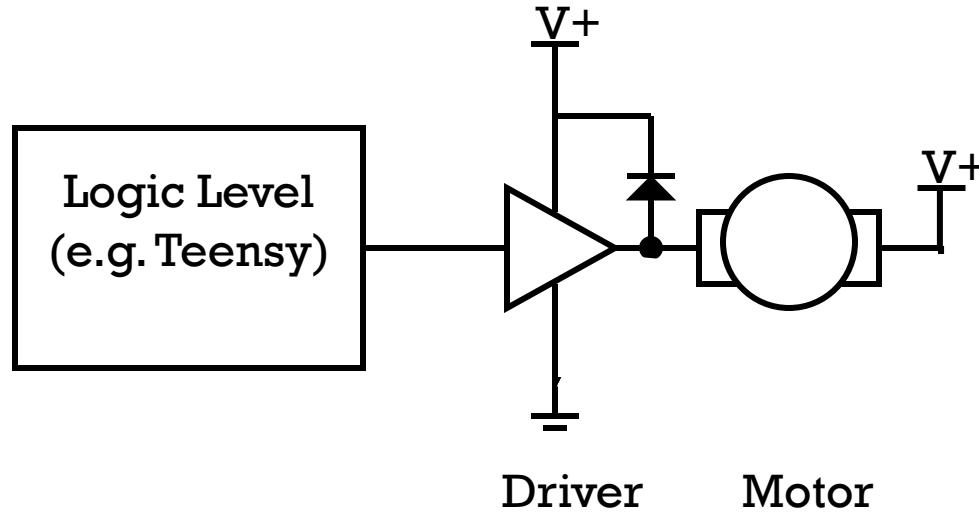So how do we drive a motor with Logic output?




Q9: Draw a snubber diode for the protecting against a negative spike

Two half-bridges w/clamping diodes

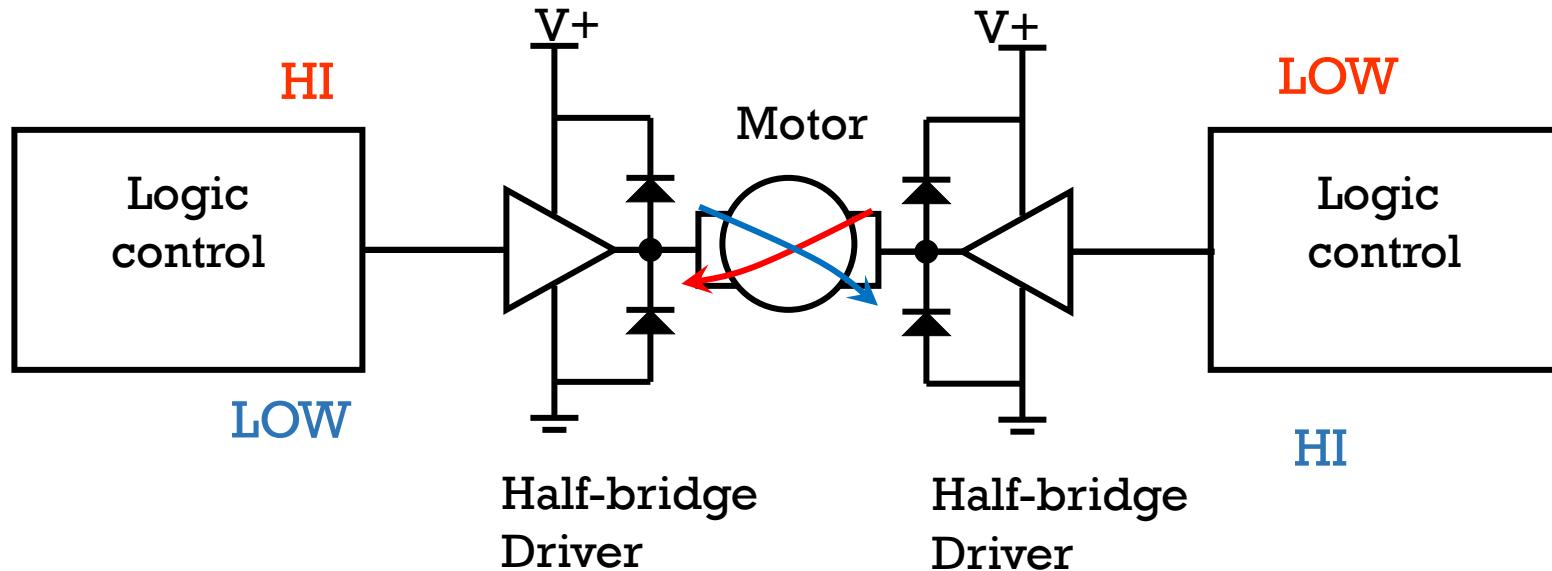


H-Bridge in ministore SN754410

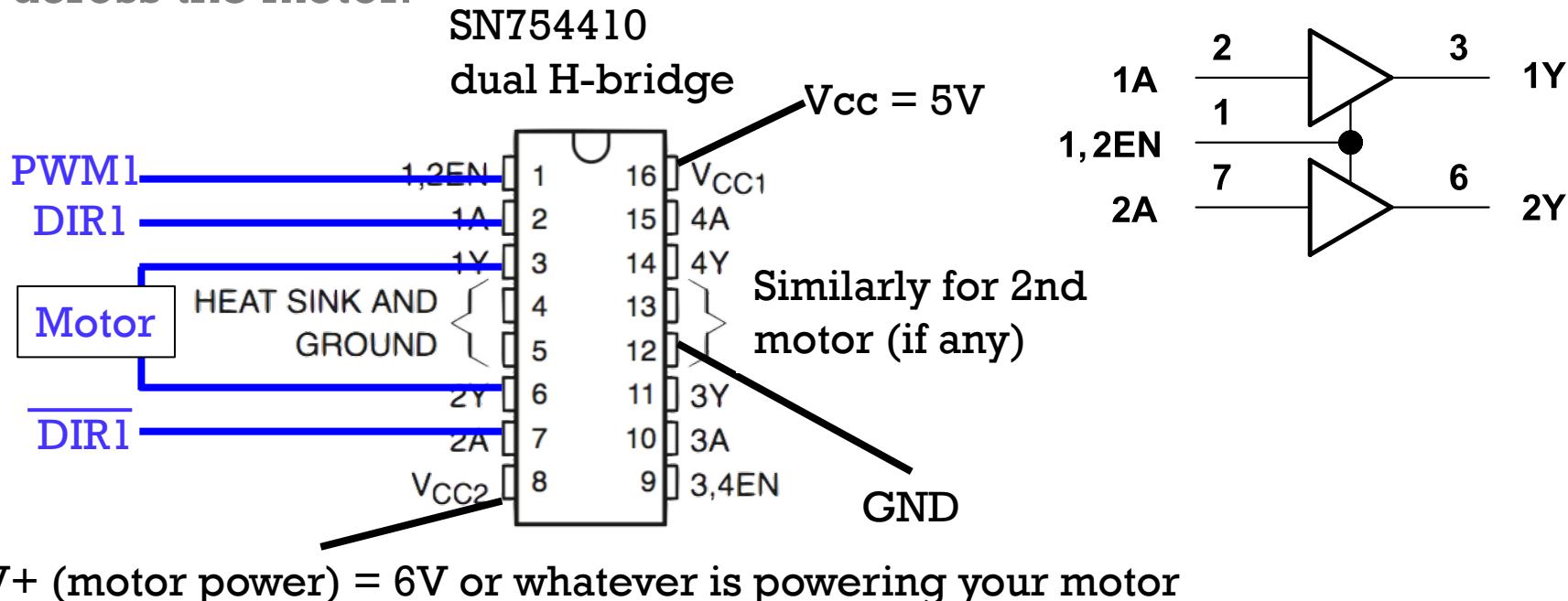- When using the h-bridge to switch directions on a motor in the circuit below, it will be equivalent to swapping 6V and ground across the motor.




SN754410 example

Motor full on forward

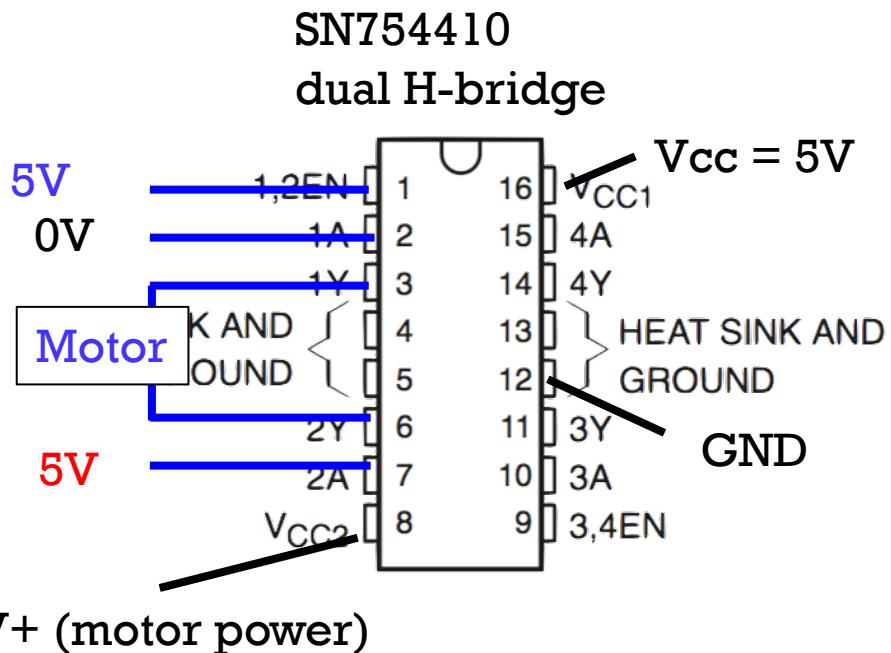


Motor full on backward

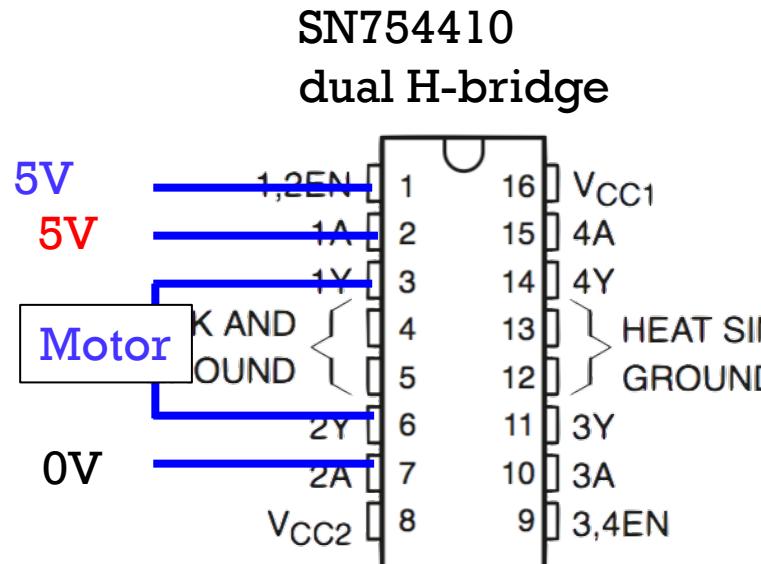


SN754410 example

Motor half on forward


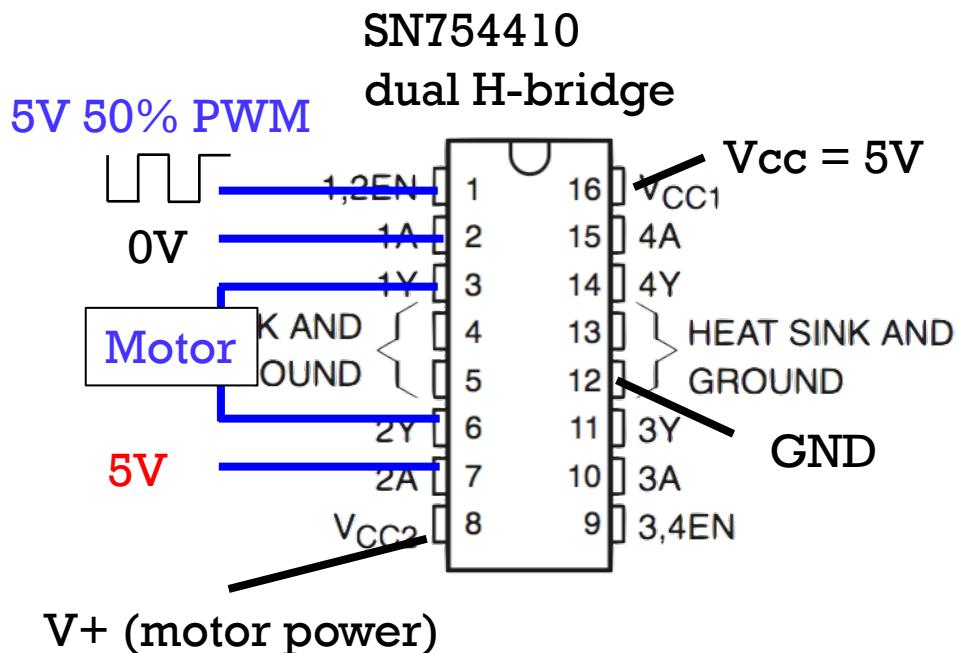


Motor half on backward

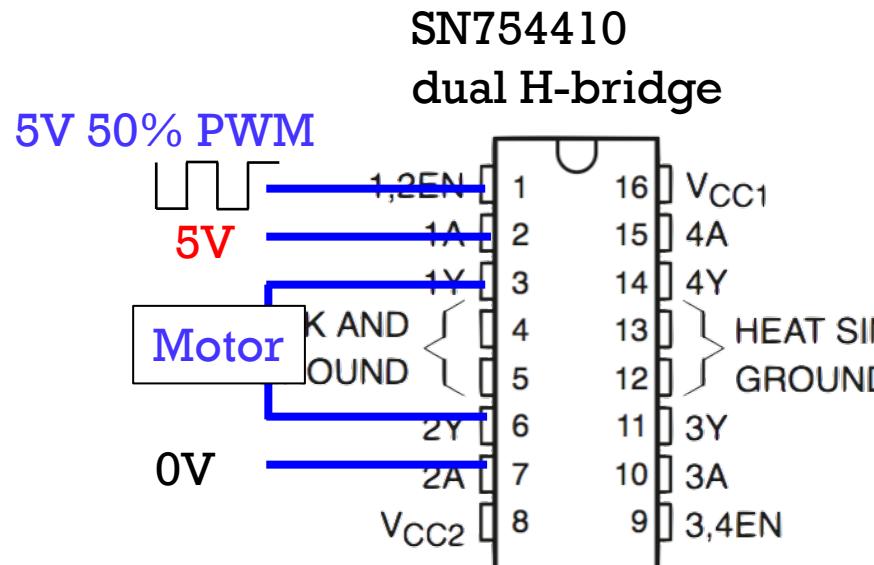


SN754410 output stage w/diode clamps

From SN754410 Datasheet:

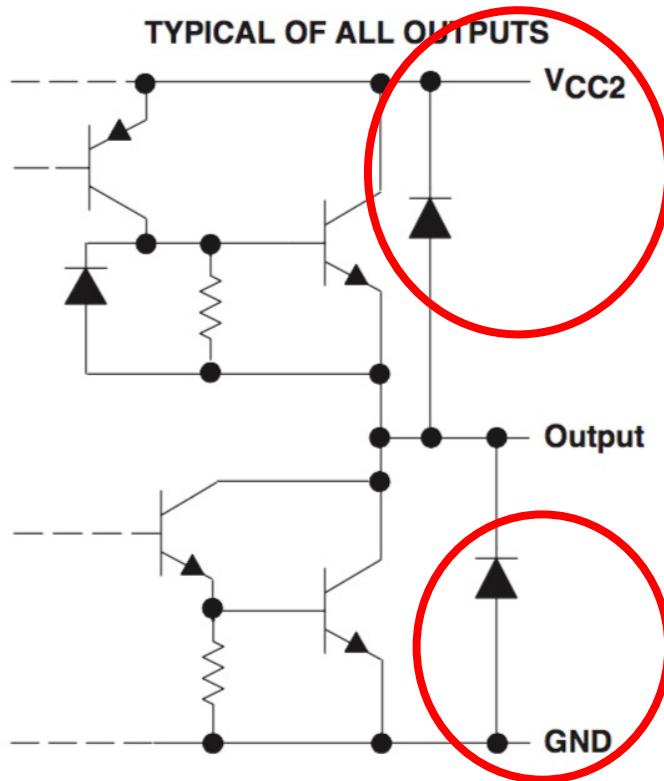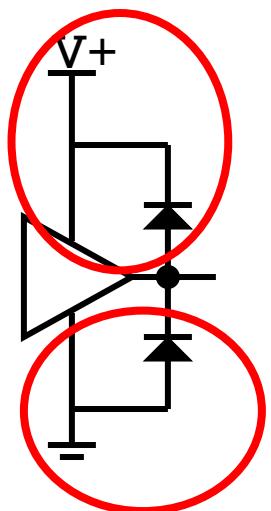


MOSFETs Body Diode

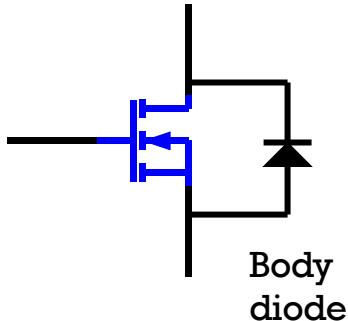- Most FETS (MOSFETs) have an inherent diode called the *body diode*
- Turns out to be convenient for inductive protection.



From SN754410 Datasheet:

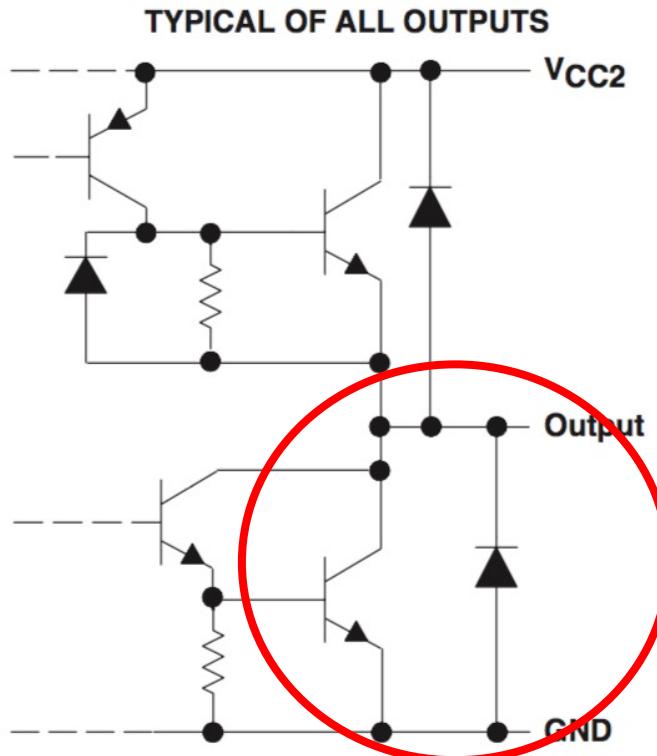

Caveat with SN754410

SN754410 QUADRUPLE HALF-H DRIVER

SLRS007B – NOVEMBER 1986 – REVISED NOVEMBER 1995


electrical characteristics over recommended ranges of supply voltage and free-air temperature (unless otherwise noted)

PARAMETER		TEST CONDITIONS	MIN	TYP†	MAX	UNIT
V_{IK}	Input clamp voltage	$I_I = -12 \text{ mA}$		-0.9	-1.5	V
V_{OH}	High-level output voltage	$I_{OH} = -0.5 \text{ A}$	$V_{CC2}-1.5$	$V_{CC2}-1.1$		V
		$I_{OH} = -1 \text{ A}$	$V_{CC2}-2$			
		$I_{OH} = -1 \text{ A}, T_J = 25^\circ\text{C}$	$V_{CC2}-1.8$	$V_{CC2}-1.4$		
V_{OL}	Low-level output voltage	$I_{OL} = 0.5 \text{ A}$		1	1.4	V
		$I_{OL} = 1 \text{ A}$		2		
		$I_{OL} = 1 \text{ A}, T_J = 25^\circ\text{C}$		1.2	1.8	



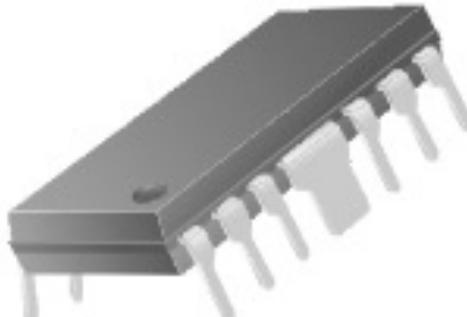
Q10: What if you were driving a motor with 5V, what is the worst case scenario for motor performance (i.e., smallest voltage across the motor?)

FAN8100


- Obsolete chip from Rochester Electronics LLC (sells large min qty obsolete stock for cheap...)
- Has better V_{OH} . Better current driving 1.5A ea channel
- Datasheet available on Canvas -> files-> Resources
- Caveat: double wide ground pins are used as heatsink fins (won't fit in protoboard) you need to solder or clip on to ground.



Double pole double throw switch

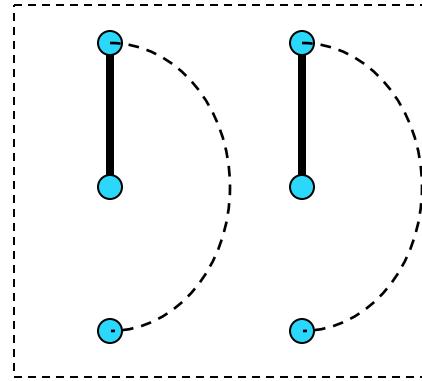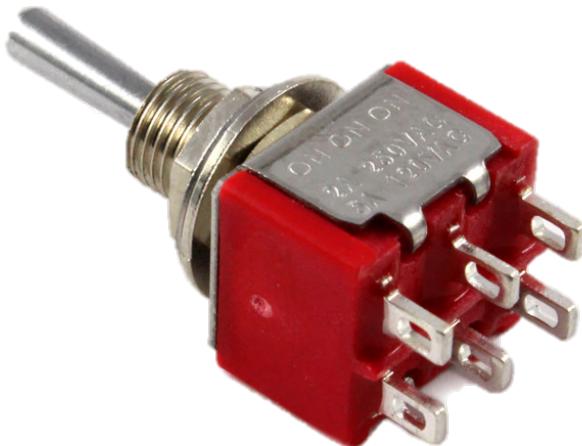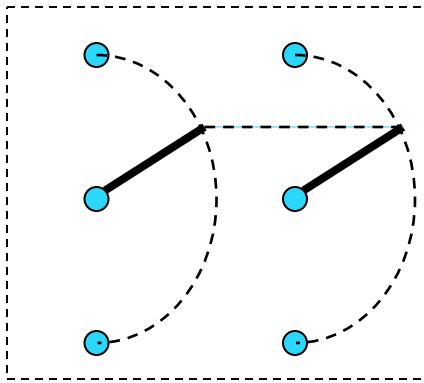


Switch
up

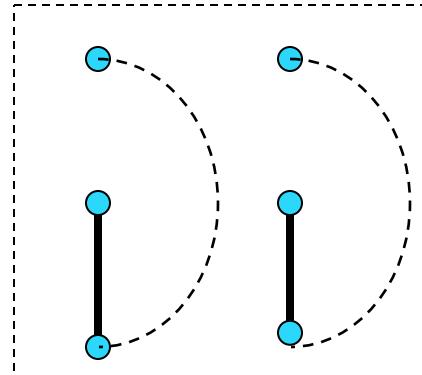

Switch
down

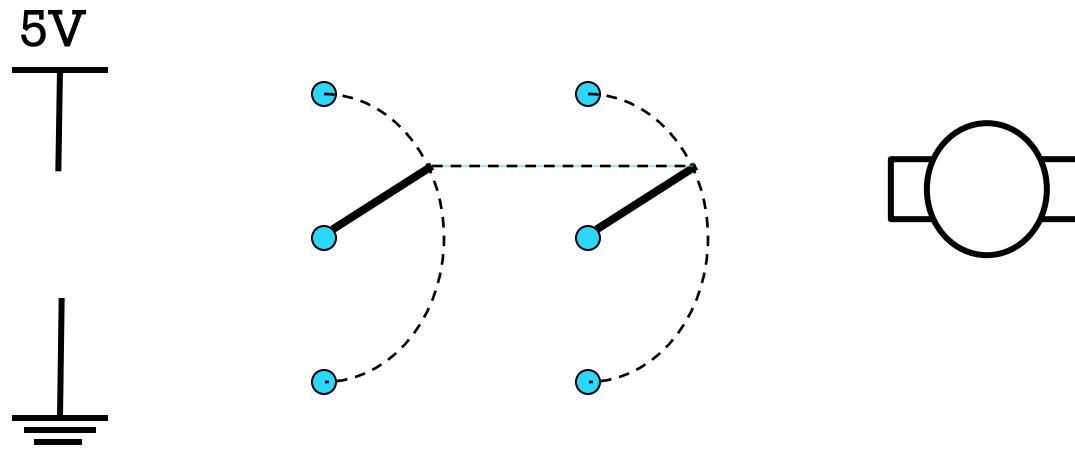Double pole double throw switch as h-bridge




Q8: Connect power ground and motor leads to the 6 leads of a DPDT connections to form an h-bridge

Summary

- Motors are more energy efficient towards higher speeds
- Motors have maximum power at half max torque.
- Large currents require special drivers.
- Driving motors and solenoids can lead to large voltage spikes.
- Snubber diodes protect from these spikes.
- H-Bridges can be used to drive current bi-directionally.
- MOSFETs are the trend for drivers. BJT's are on the way out.

Motor Exercise – Choosing motor for a design

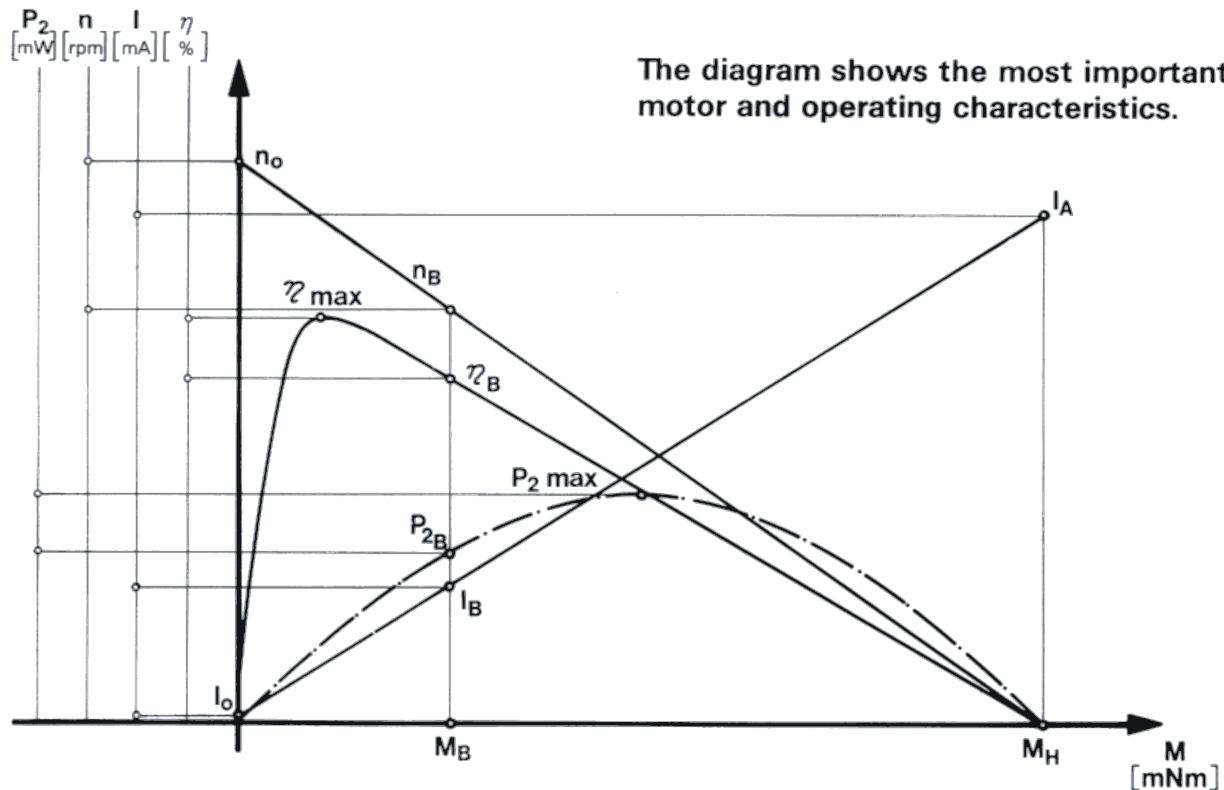- Often you motor specs include specific points (stall torque, no-load speed etc.) but will need to know torque @ some speed or other design point.



Motor exercise

You are handed a motor. The only documentation that you can find shows that the motor chosen has $K_t = 9.33 \text{ in.-oz./A}$ and produces 2.8 in.-oz. at stall when driven at 12V. The design requires that the motor deliver 0.4 in.-oz. at 1500 rpm. The motor was supposed to be driven from a 12V supply. Your boss has asked you:

- a) How can I find out how much current the motor will draw at stall ?
- b) What is K_e ?
- c) How can I find the coil resistance ?
- d) Will the design meet the requirements for torque at the given speed? If not, what changes could you suggest?
- e) Estimate the current required when running at the design point.

You may assume that there are no internal losses within the motor.

for reference: $K_T = 1.3524K_E [\text{oz-in/A} ; \text{V/krpm}]$

Answer in Chat

Answer how you feel about each topic below with:

1. I don't understand this topic at all
 2. I don't know now, but know what to do to get by
 3. I understand some, but expect to get the rest later
 4. I understand completely already
-
- A. Transistors (BJT / MOSFET)
 - B. Choosing Motors
 - C. Driving Motors with H-bridges