

Lecture 07

Comparators

Rotary Encoders

Agenda

- 00. Teensy USB-print
- 01. Comparators
- 02. Rotary Shaft Encoders
- 03. Resistor Colors


Misc. stuff

- Check off for Labs. If you are sick (or don't feel well) check off can be done via Zoom. Make arrangements with TAs.
- Lab 3 will involve laser cutting. You need to be trained.
 1. Use CAD system to create DWG files
 2. Watch video
 3. Take quiz
 4. Go to RPL for staff training – sign up info for MEAM510 will be announced on piazza.

<https://meamlabs.seas.upenn.edu/rapid-prototyping-lab/training/>

Lab 2

- 60Hz or 120Hz

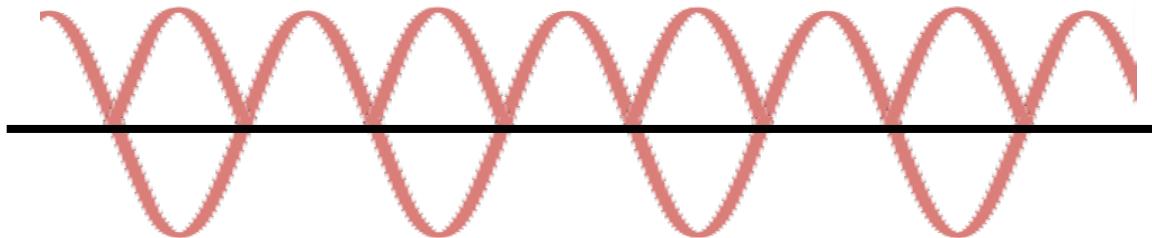

- Dealing with analog values on Teensy (LVTTL logic levels)
 - Above 1.9V is considered logic high $V_{IH} = 1.9V$
 - Below 0.9V is considered logic low $V_{IL} = 0.9V$

Print statements are slow

```
#include "teensy_general.h"
#include "t_usb.h"


#define PRINTNUM(x) m_usb_tx_uint(x); m_usb_tx_char(10); m_usb_tx_char(13)

int main(){
    m_usb_init(); // init USB for print statements
    set(PORTC,7); // turn on pull up on PC7

    for (int i=0; i<100;i++)  {
        teensy_wait(100);
        PRINTNUM(i);
        PRINTNUM(bit_is_set(PINC,7)); // print state of PC7
    }


    m_usb_tx_string("ended\n");
}
```

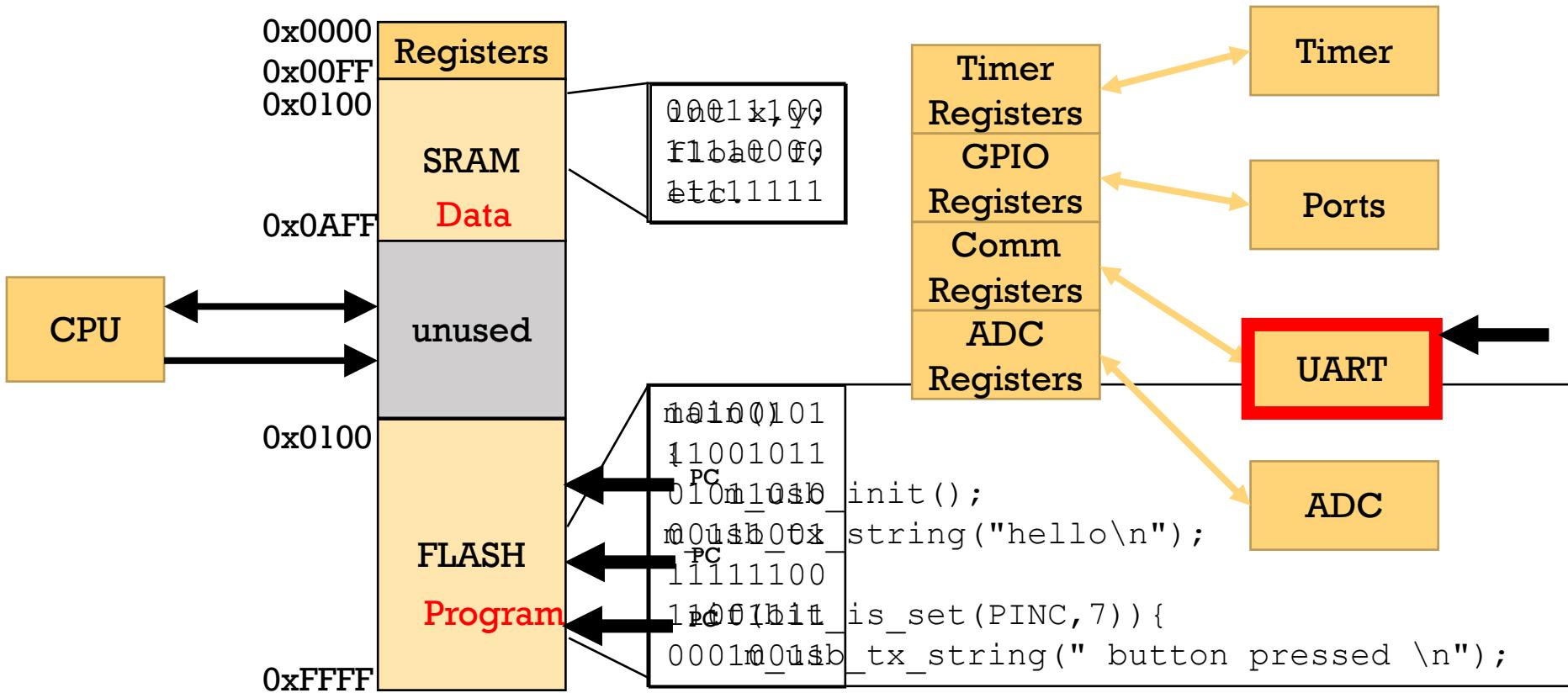Peripherals run concurrent with main code



01

Comparators

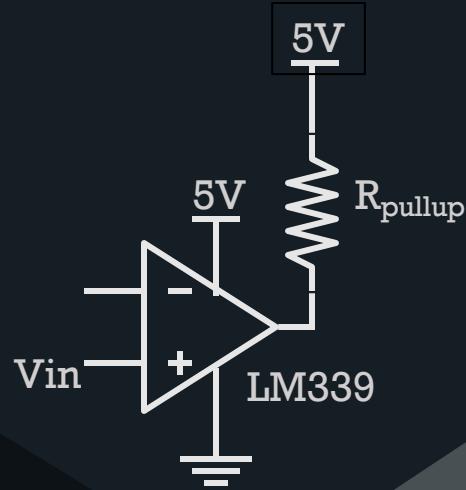


Comparator

Looks like an opamp,
but it's a comparator


Acts like an opamp
but designed for driving
output to a rail not linearity.

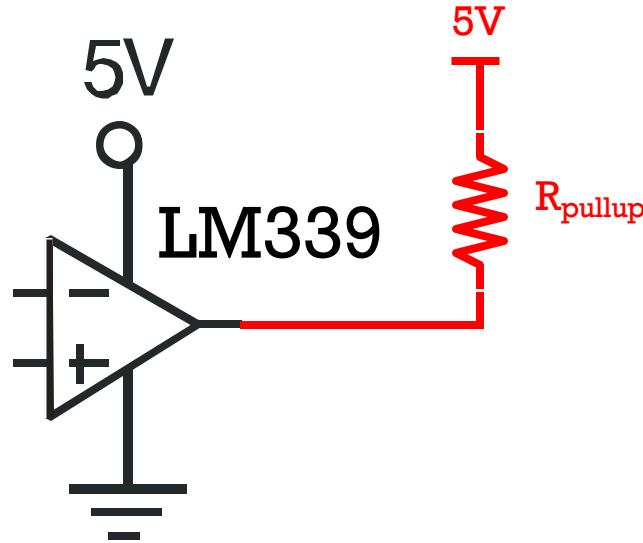Compares the two inputs
swings output to negative
rail or pulled up voltage.




Output is often
“open collector” or “open drain.”
(need pull-up resistor)


Two states of open collector comparator

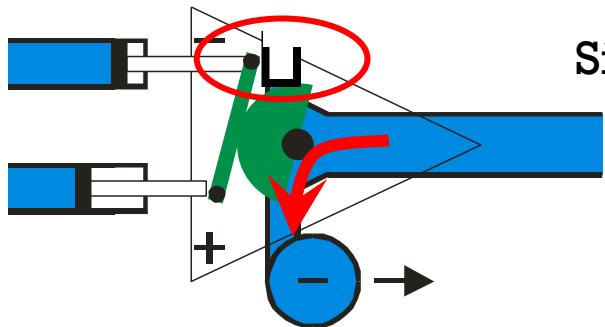

Sinking current

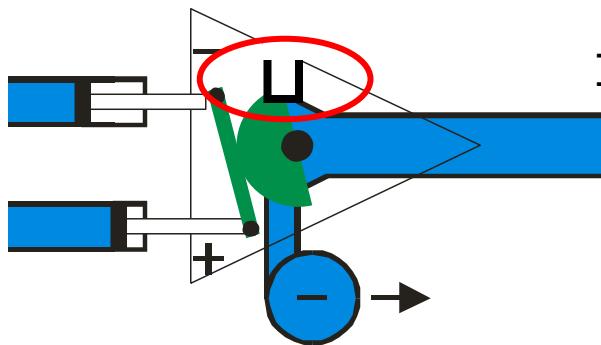

No flow

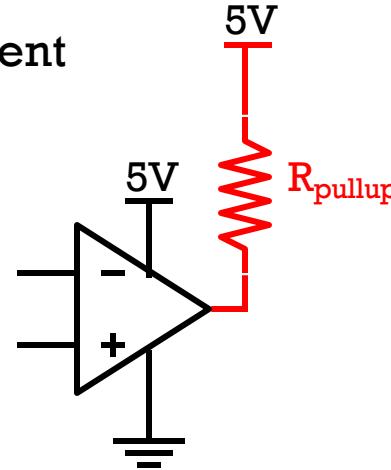


Output is "floating"

High impedance state

How do you use a comparator?

R1 and R2 are a voltage divider setting a reference voltage

| Input | Output |
|-------------|-------------|
| $V_+ < V_-$ | driven LOW |
| $V_+ > V_-$ | pulled HIGH |

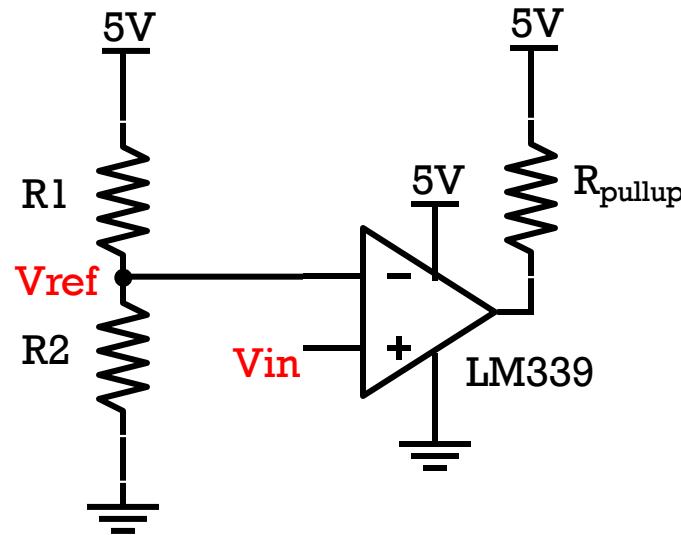


Non-inverting

What would this do?

R1 and R2 are a voltage divider setting a reference voltage

| Input | Output |
|-------------|-------------|
| $V_+ < V_-$ | driven LOW |
| $V_+ > V_-$ | pulled HIGH |

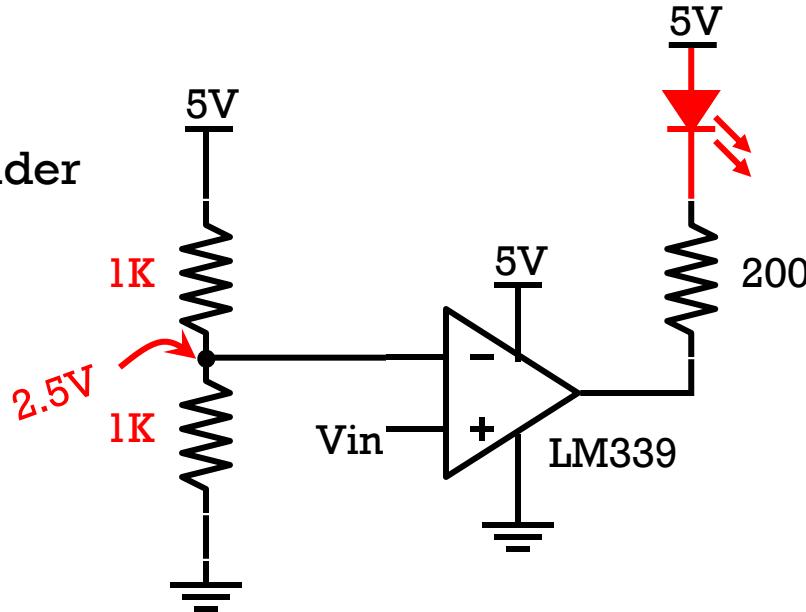


Non-inverting

Q1: in chat: What happens to the LED if Vin is 1.5V?

What would this do?


R1 and R2 are a voltage divider
setting a reference voltage

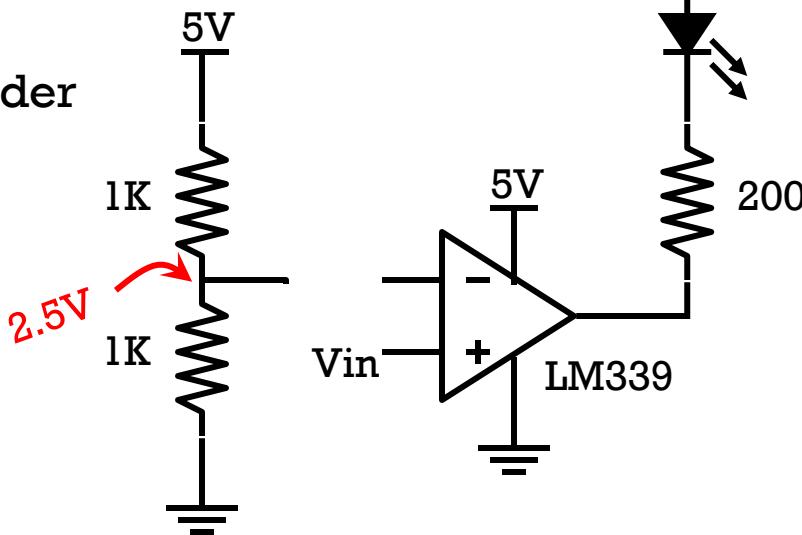If $V_{in} < 2.5V$? LED on
If $V_{in} > 2.5V$? LED off



Inverting
configuration

How does this circuit behave?

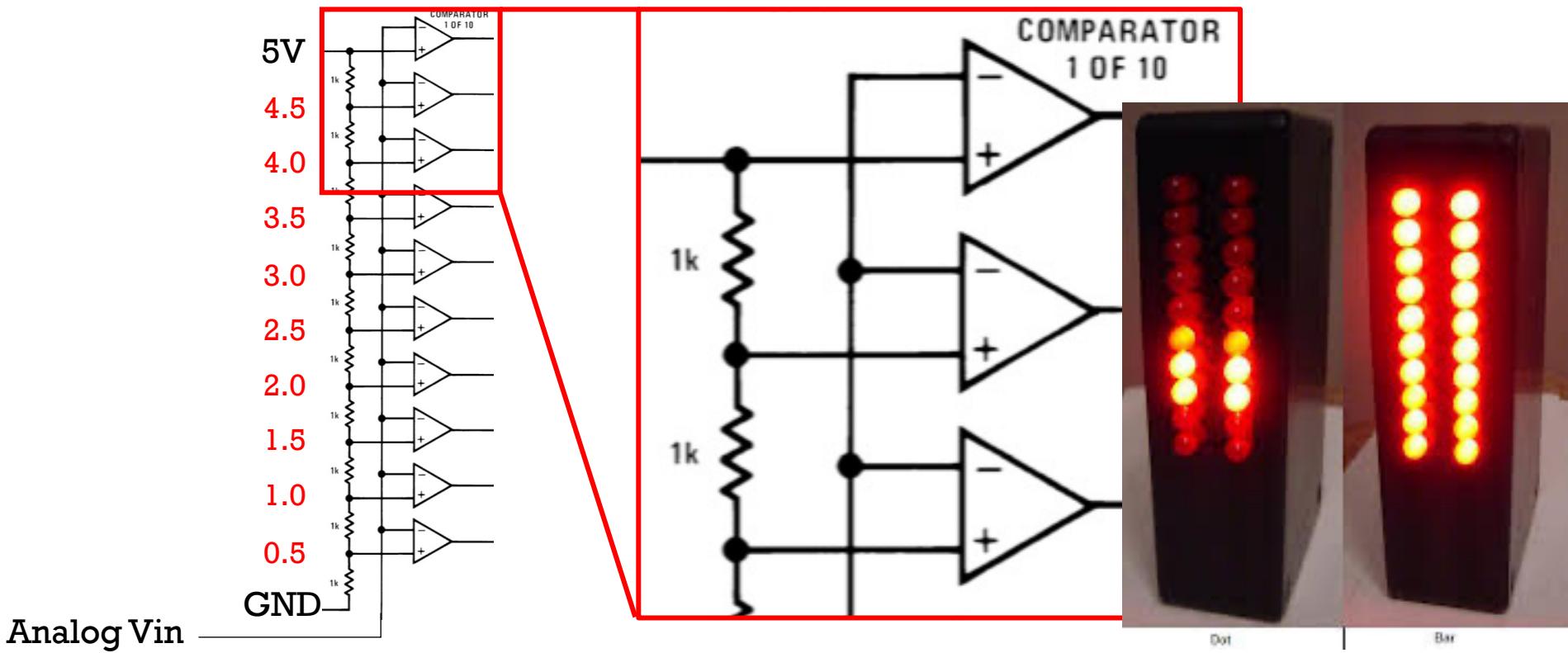


LM339

- Driving LED's with LM339A? What do we need to know?

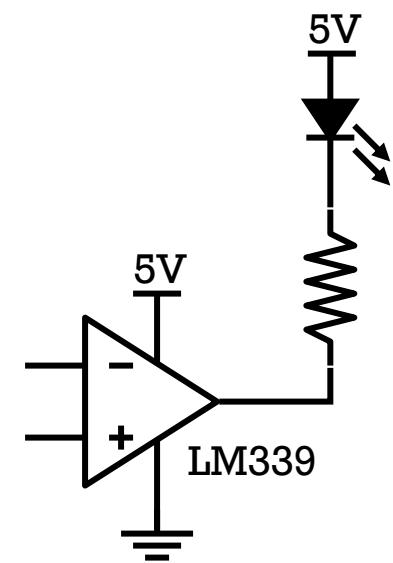Q2: Draw and hold: Circle the important value on this spec sheet.

Electrical Characteristics for LMx39 and LMx39A (continued)

at specified free-air temperature, $V_{CC} = 5$ V (unless otherwise noted)



| PARAMETER | TEST CONDITIONS ⁽¹⁾ | T_A ⁽²⁾ | LM239 LM339 | | | LM239A LM339A | | | UNIT |
|--|--------------------------------|----------------------|----------------|-----|-----|------------------|-----|---------|------|
| | | | MIN | TYP | MAX | MIN | TYP | MAX | |
| I_{OH} High-level output current | $V_{ID} = 1$ V | $V_{OH} = 5$ V | 25°C | 0.1 | 50 | 0.1 | 50 | nA | |
| | | $V_{OH} = 30$ V | Full range | 1 | | 1 | | μ A | |
| V_{OL} Low-level output voltage | $V_{ID} = -1$ V, | $I_{OL} = 4$ mA | 25°C | 150 | 400 | 150 | 400 | mV | |
| | | Full range | | 700 | | 700 | | | |
| I_{OL} Low-level output current | $V_{ID} = -1$ V, | $V_{OL} = 1.5$ V | 25°C | 6 | 16 | 6 | 16 | mA | |
| I_{cc} Supply current (four comparators) | $V_O = 2.5$ V, No load | 25°C | 0.8 | 2 | | 0.8 | 2 | mA | |

When would you use a comparator?

- Converting analog to digital. Most digital input are high impedance (e.g. draw much less than LED $<< 1\text{mA}$)
- You need to set an input analog threshold for a digital signal.

Q3: in chat: Can you use this in Lab 2 ? Which part?



Versus Op amp with very high gain?

- When you need fast signals (input or output in μs)
- When you want to tie many outputs together (wired OR)
- When you have large voltage swing output requirements.
- Op amps designed for negative feedback, not railed output, may have stability issues (e.g., MCP6044)

Ola


Comparators Hysteresis

Hysteresis like Schmidt trigger

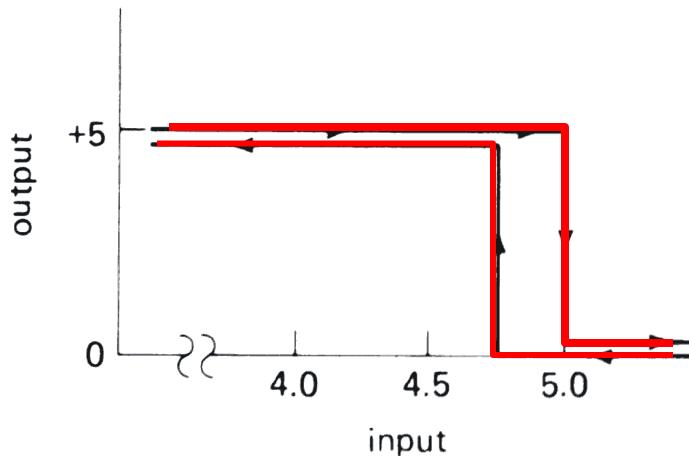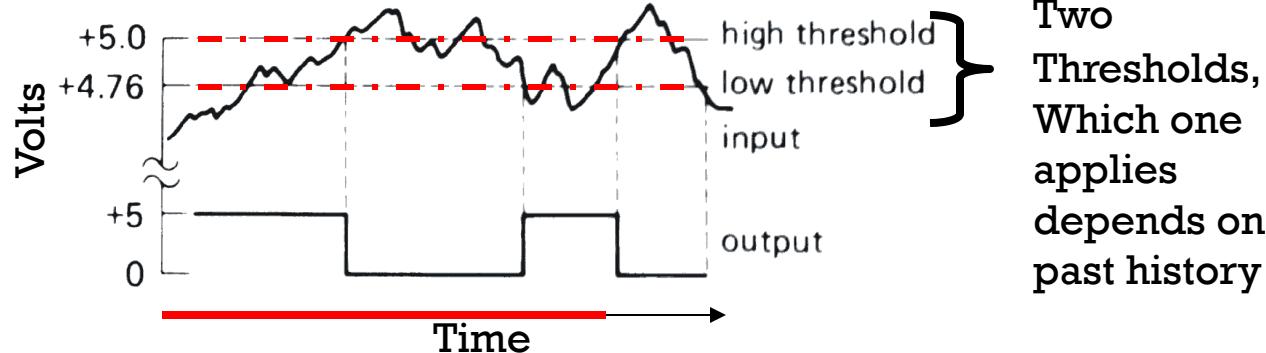


How do you add hysteresis?

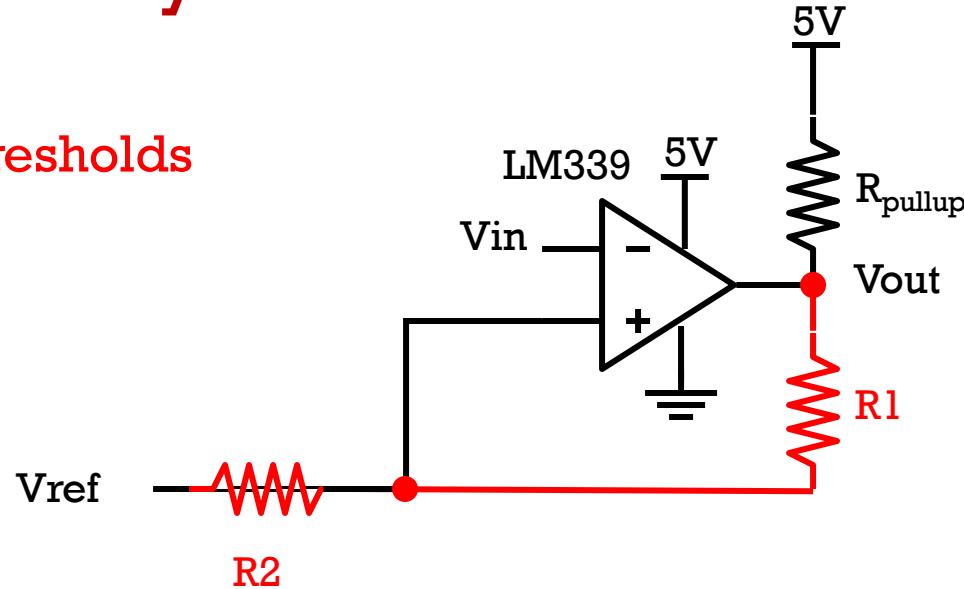Two states of V_{out} gives
mechanism to have 2 thresholds




Hysteresis is about $V_{out} R_2/R_1$

V_{REF} with voltage dividers

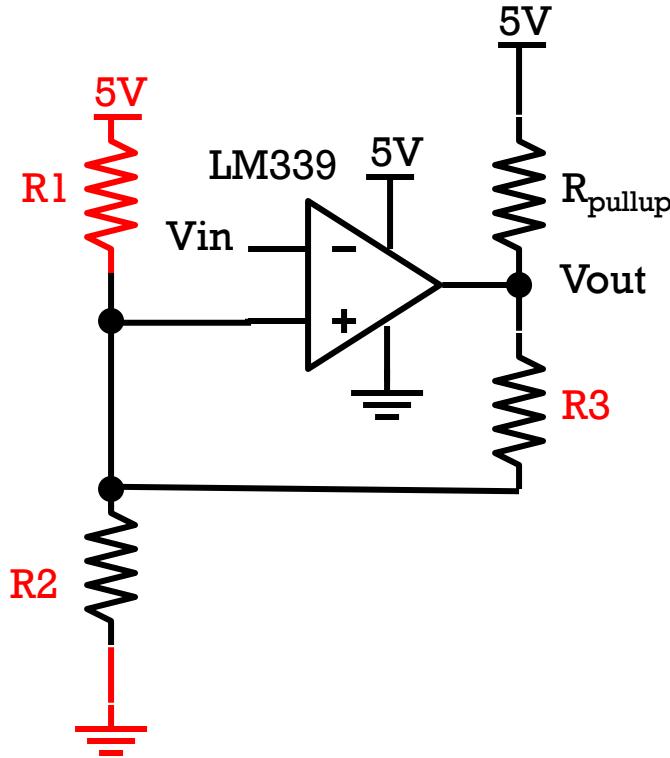


V_{REF} with voltage dividers

V_{ref}

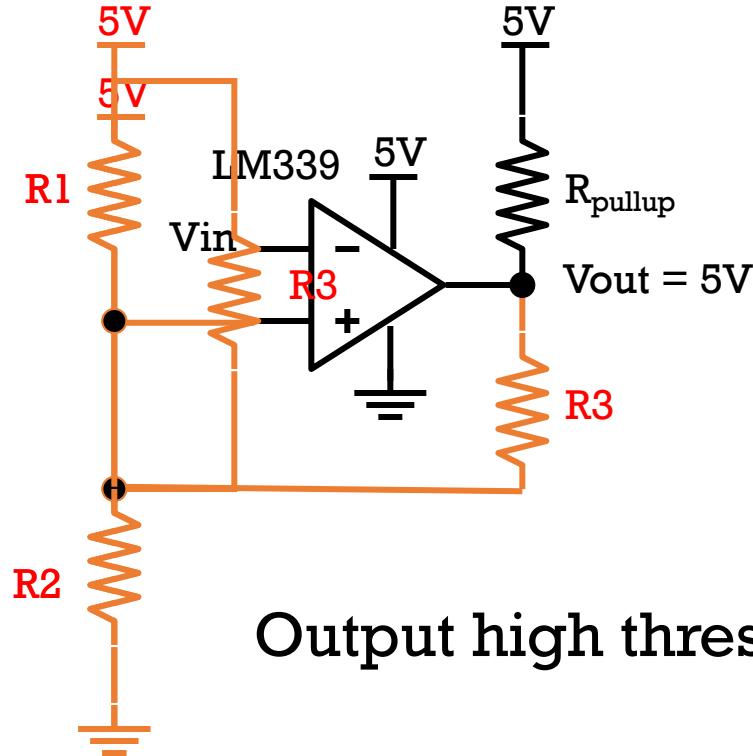

Output high threshold

V_{REF} with voltage dividers

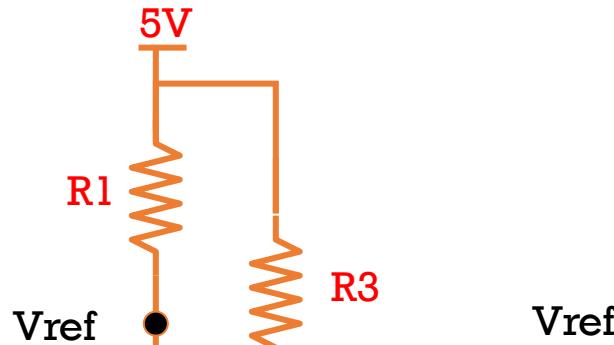

V_{ref}


R_2

5V

R_3

V_{ref}

Output high

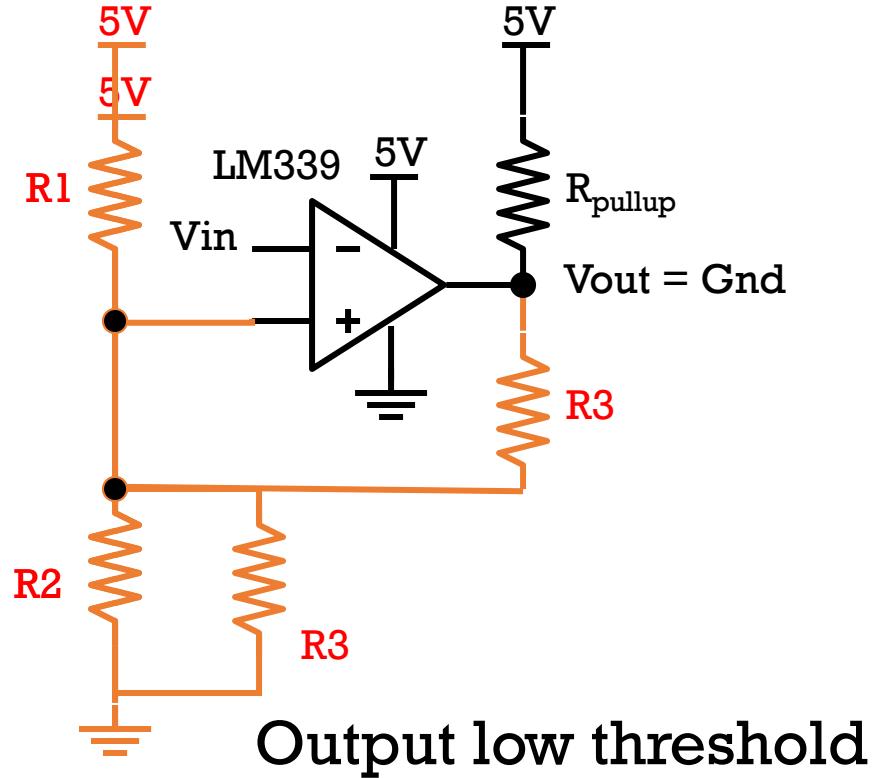

5V

5V

LM339

V_{in}

5V

5V

R_{pullup}


$V_{out} = Gnd$

R_2


R_3

Output low threshold

What are the two thresholds?

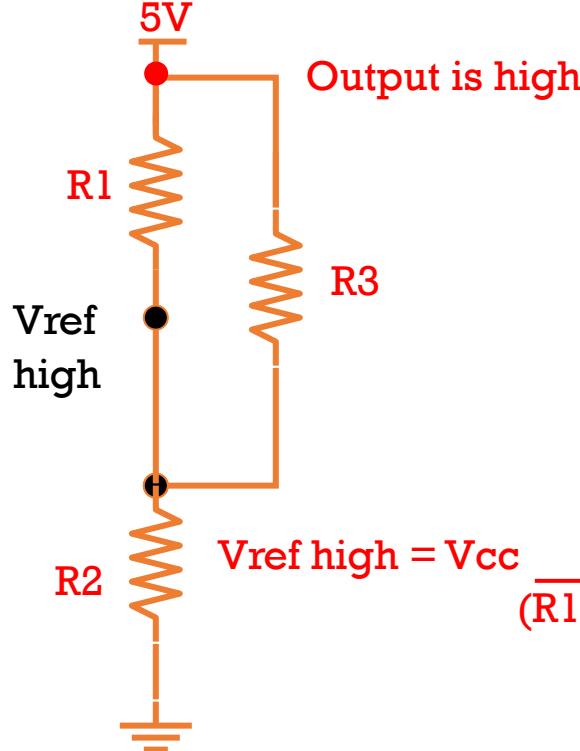

Output high

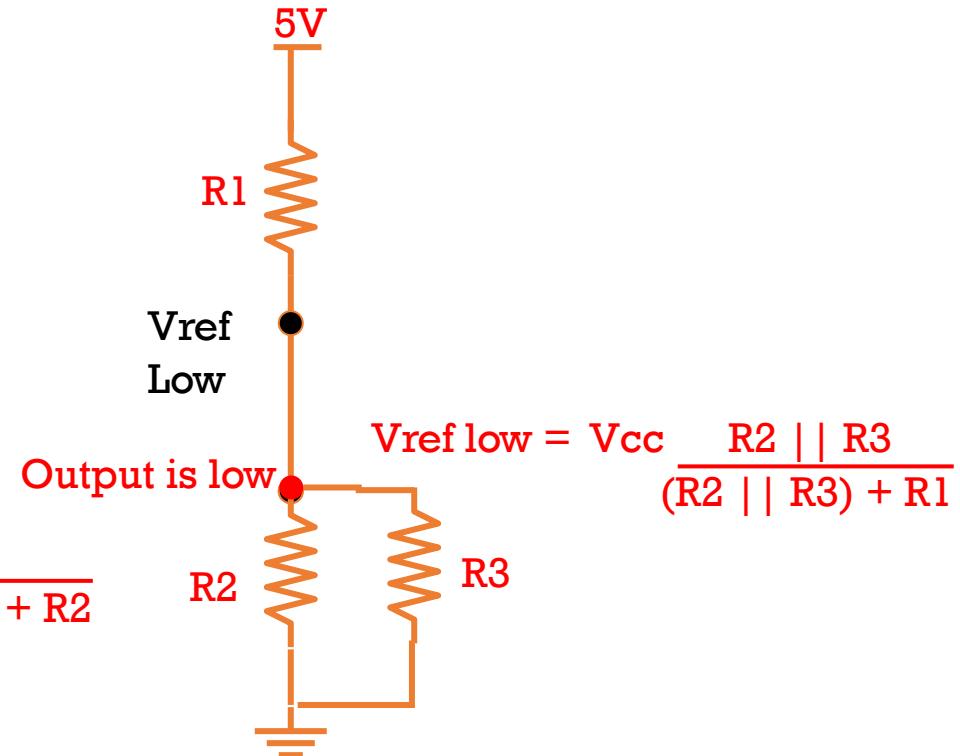

Output low threshold

Inverting Comparator Design Procedure

1) $R_{\text{pullup}} \ll R_{\text{load}}$


2) $R_3 \gg R_{\text{pullup}}$

3) Choose thresholds

$$\Delta V = V_{\text{ref high}} - V_{\text{ref low}}$$

4) $R_1 = \frac{R_3 (\Delta V)}{V_{\text{ref low}}}$

5) $R_2 = \frac{R_1 || R_3}{(V_{\text{cc}}/V_{\text{ref high}}) - 1}$

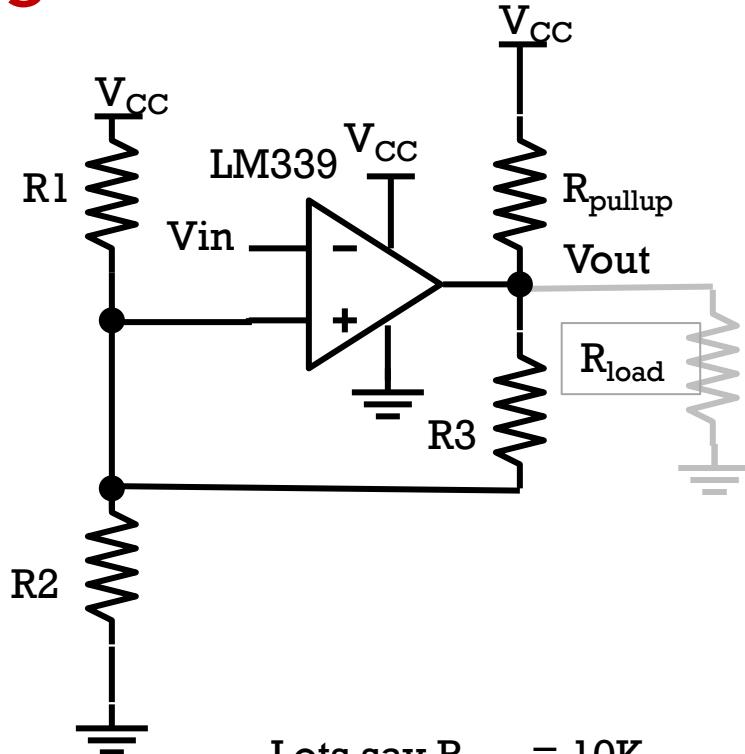

Lets say $R_{\text{load}} = 10K$
Start with $R_{\text{pullup}} = 1K$,
 $R_3 = 1.0M$

Example comparator with hysteresis


- Conditions: V_{CC} = 5V; Impedance is for CMOS input (R_{load} ~ 10K)
- Choose V_{ref} high = 2V, V_{ref} low = 1V.
- Choose pullup of 1kΩ
- Choose R₃ = 100kΩ

4) $R_1 = 100\text{K}\Omega \Delta V / V_{\text{ref low}}$

R₁ = 100KΩ

5) $R_2 = \frac{100\text{K}\Omega || 100\text{K}\Omega}{(5\text{V}/2\text{V}) - 1} = \frac{50\text{K}\Omega}{1.5}$

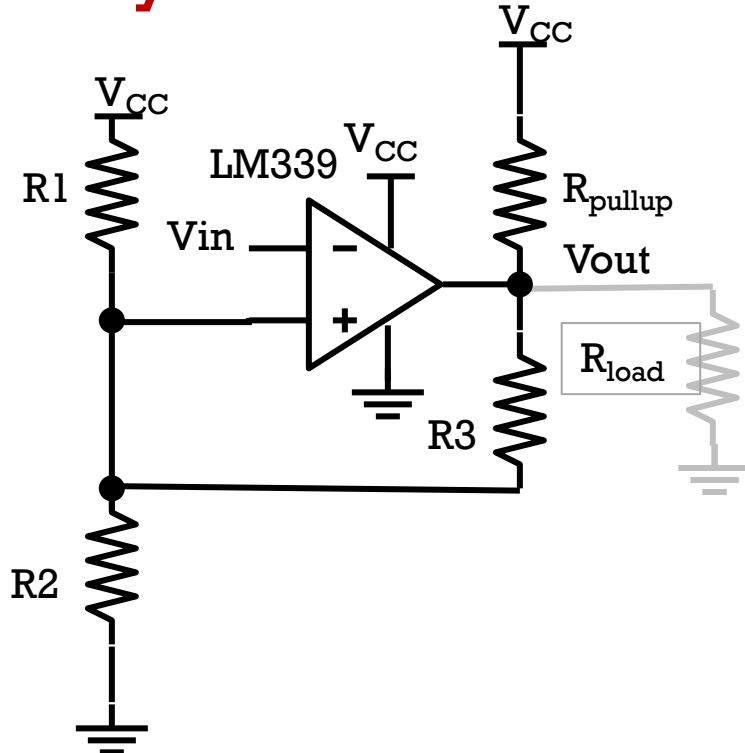
R₂ = 33KΩ Q4: What is R₁ if we change V_{ref high} = 1.1V;






Comparators vs opamp summary

- High gain difference amp - Like an opamp
- Comparators need pullup, opamps don't
- Op amps not designed to be at rails (only subset of opamps are rail-to-rail)
- The **TLV272** is rail-to-rail and could theoretically be used as comparator even with hysteresis
- **LM393** and **LM339** available in GM lab (LM393 is dual, LM339 is quad)

opamp symbol

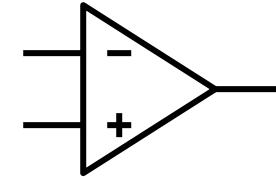

comparator symbol

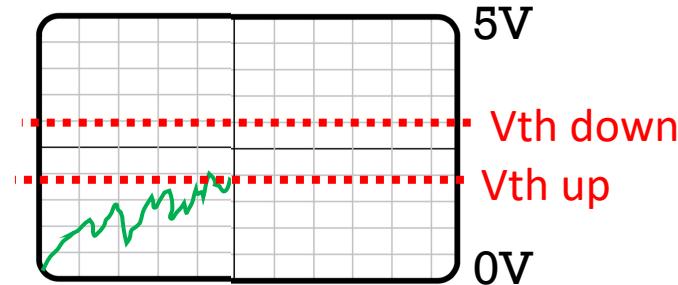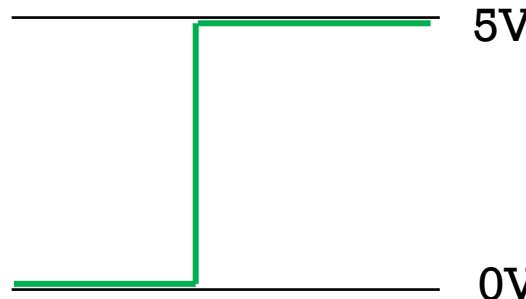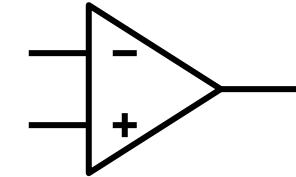

02



Rotary Position Encoders

Optical Shaft Encoders




<https://www.adafruit.com/product/3782>

<https://www.adafruit.com/product/3985>

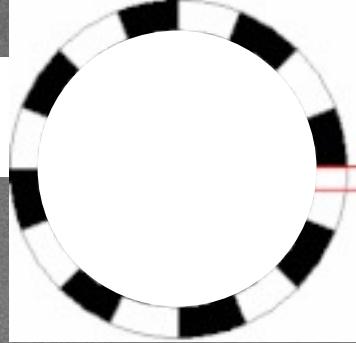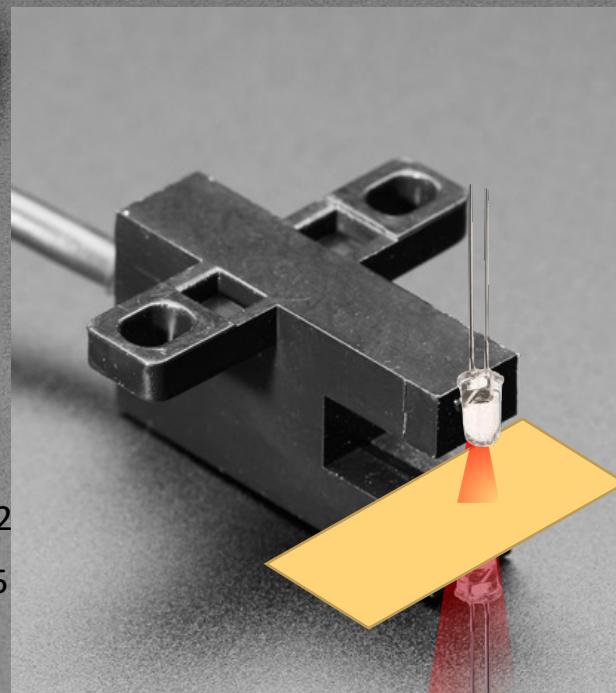

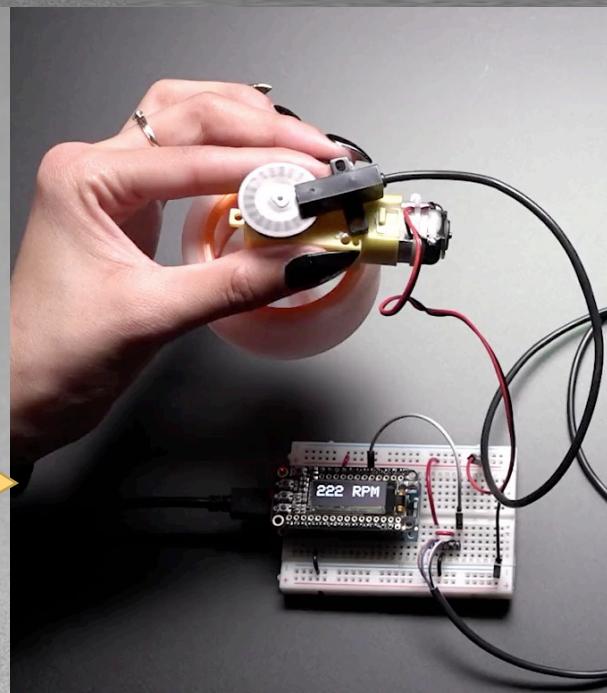
https://en.wikipedia.org/wiki/Rotary_encoder





Quadrature

1

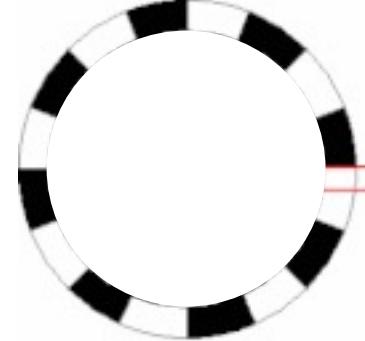Q5: What is the sequence of logic level values for A for every rising edge of B as the time moves to the right CW?



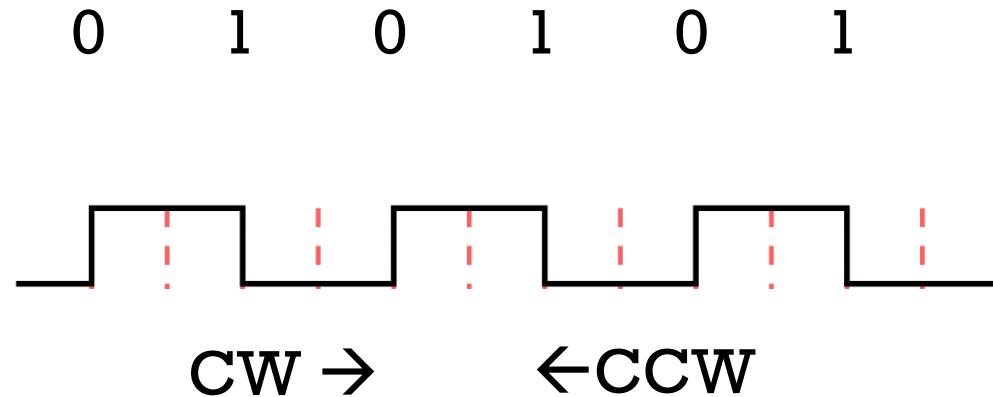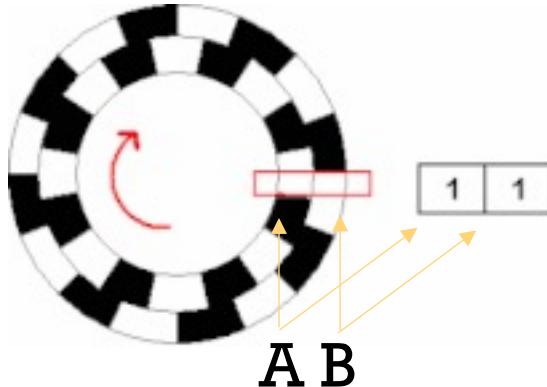- With one square wave, we cannot tell the direction the wheel spins
- With two square waves 90° phase shifted, we can!




Quadrature intuition

Channel A



Channel B

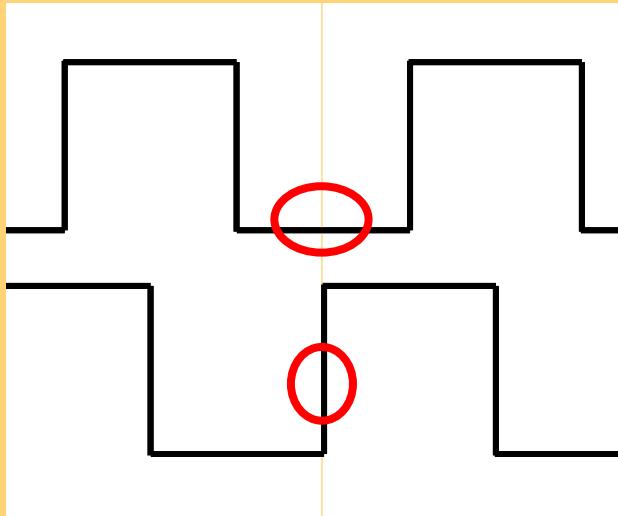


Channel A is
low on rising
edge of B when
moving **left**

Quadrature intuition

Channel A




Channel B

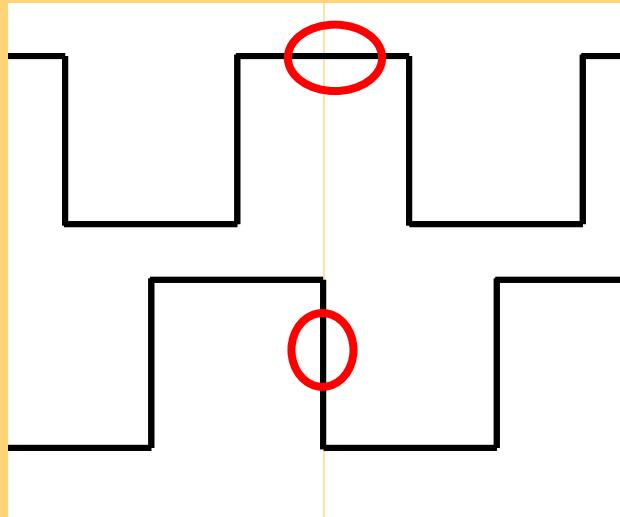

Channel A is
high on rising
edge of B when
moving **right**

So what would code look like?


- **Position Sensing** – for incremental encoder
 - Periodically poll the state of A and B lines (need to do this faster than the highest expected frequency – e.g. 100RPM and resolution of $1024 = 102,400/60 = 1706$ Hz). Polling digital lines can easily be done at >10kHz.
 - If there is a transition, then see which phase you are in. Can actually get 4x resolution by distinguishing between phases.
- Following phase transitions
 - More immune to bounces

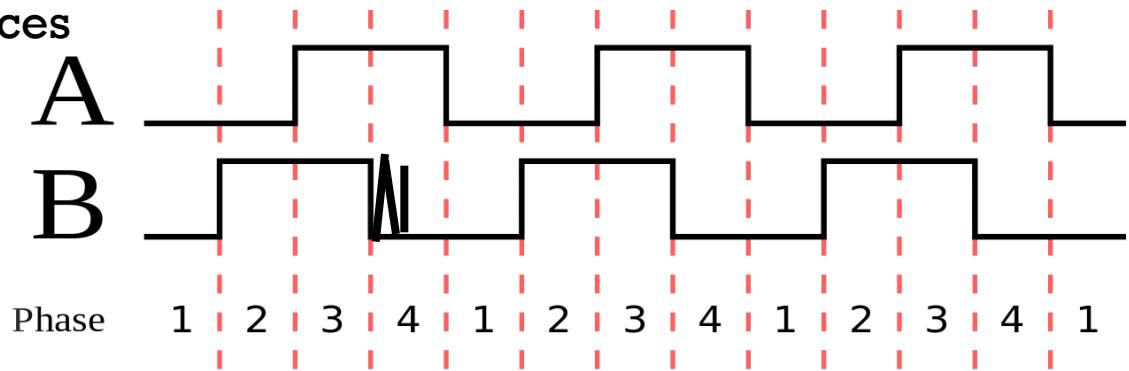

So what would code look like?


- **Velocity Sensing** – for incremental encoder
 - Can monitor position and difference based on timing.
 - Works well for fast velocities. Works poorly for slow velocities.
 - Instead use a timer to measure the pulse width. This can be done with interrupts to update a variable that stores the current velocity.
 - Need to handle the 0 velocity case as separate

Timer period

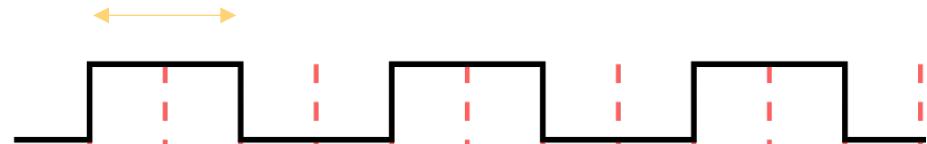


Absolute Encoders

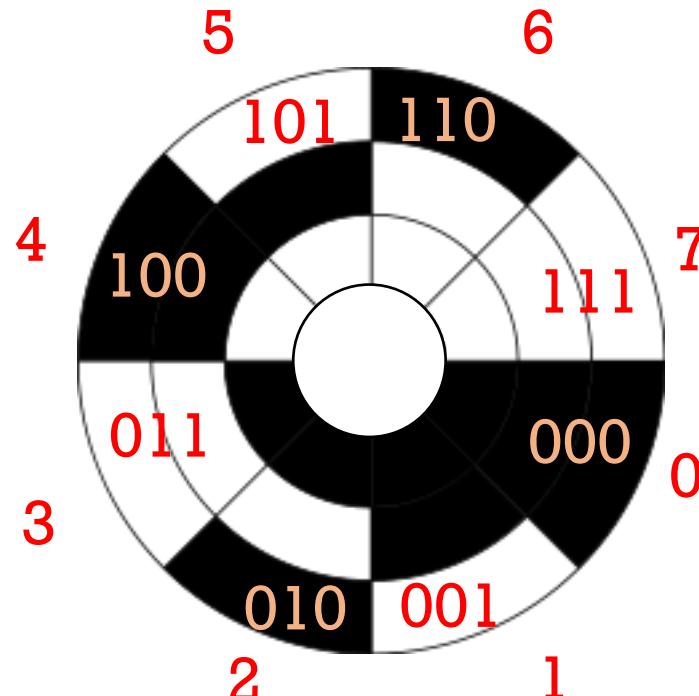- Absolute encoders divide up the circle into unique codes for each sector.




Absolute Encoder
Binary encoding

Absolute Encoders

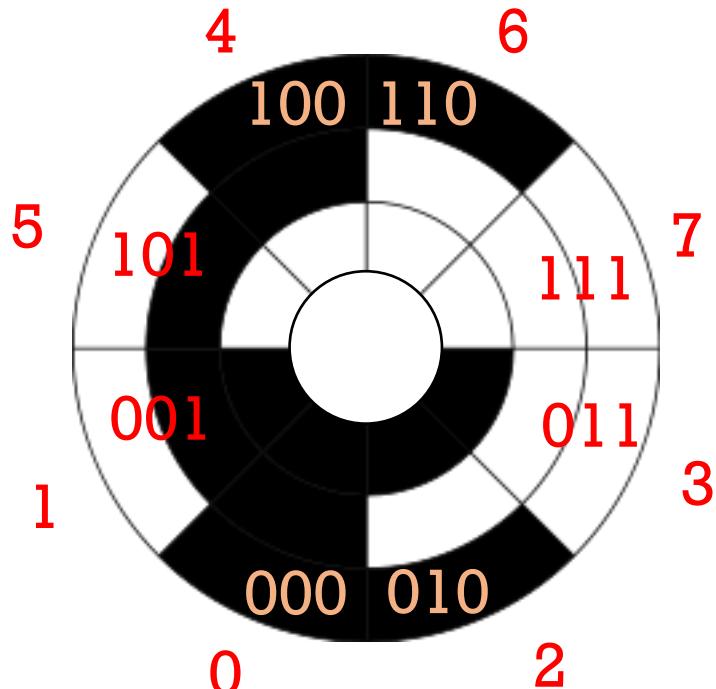


Absolute Encoder
Gray encoding

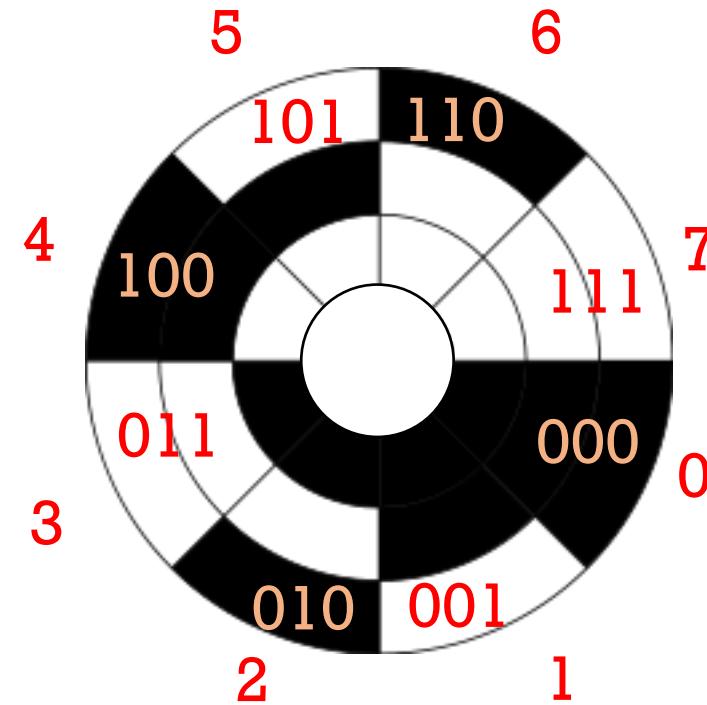

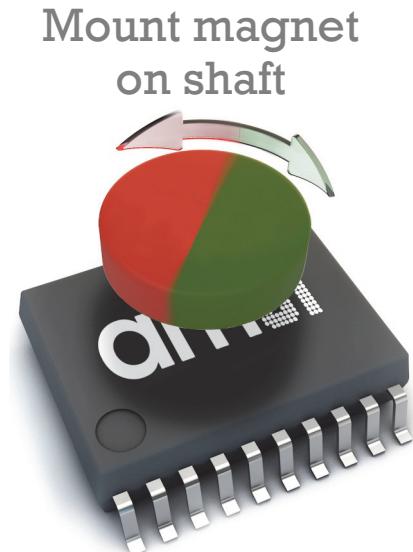Q6: What is a feature of this new pattern that is different and why might it be useful?

Other rotary sensors

- Encoders
 - Absolute
 - Incremental
- Analog
 - Potentiometer
 - Synchro
 - Resolver



8.5 bit Magnetic encoders
[AS5030-ATST](#) ~\$6 on digikey



Absolute Encoder
Gray encoding

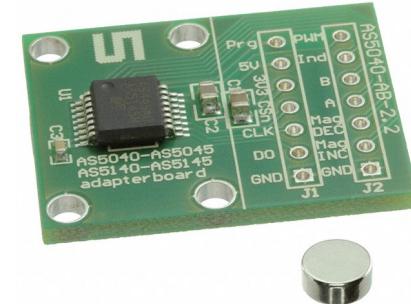
Example encoders



Mechanical Encoder
CPR: ~ 5 to 20
Cost: ~\$1
Vendor: Bournes



Optical Shaft Encoder
CPR: ~500 to 4000
Cost: ~\$30-100
Vendor: Avago/Broadcom



Magnetic Encoder
CPR: ~300-2000
Cost: ~\$8
Vendor: AMS

Rotary Shaft Encoders

Pros

- Robust to noise
- Quick to read
- Easy to make low res version
- Non contact (high life span)
- Very commonly used in industry

Cons

- Limited resolution
- Requires monitoring or losing position
- Expensive to make high res
- Sensitive to dust, impact.

Summary

- Comparators can be used to output digital logic from analog thresholds to drive logic inputs.
- Positive feedback resistors can add hysteresis
- Rotary encoders can provide a robust digital signal for the angular position of a shaft.

03

Resistor Colors (a dumb story)


Sorting resistors



Resistor Colors



Resistor Colors

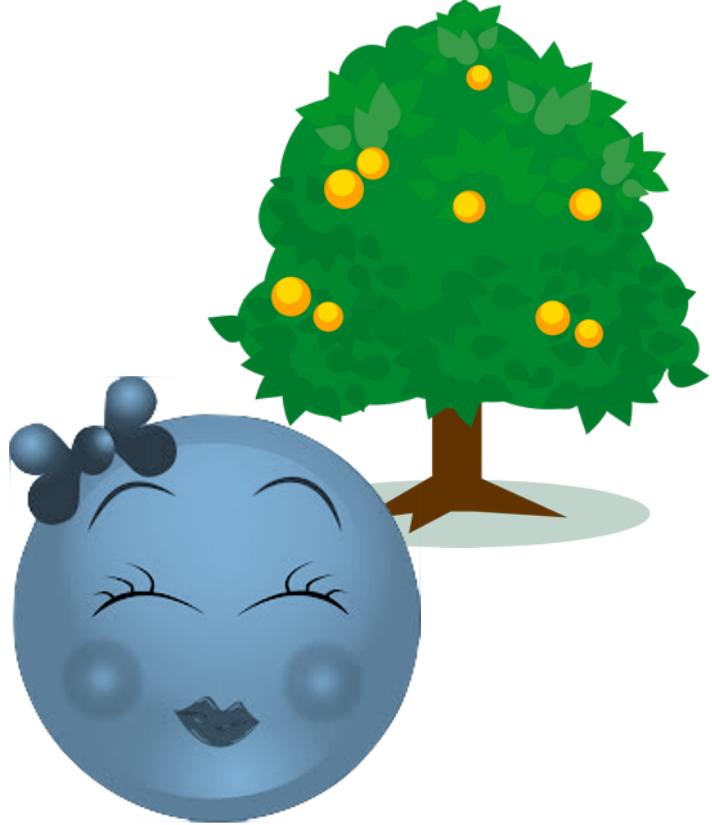

Resistor Colors



Resistor Colors



Resistor colors

- What number is?

- grey
- yellow
- red
- orange
- green

- What color is

- six
- zero
- nine
- one
- seven

- What number is?

- white
- blue
- brown
- black
- violet

- What color is

- four
- two
- five
- three
- eight


Quiz Question

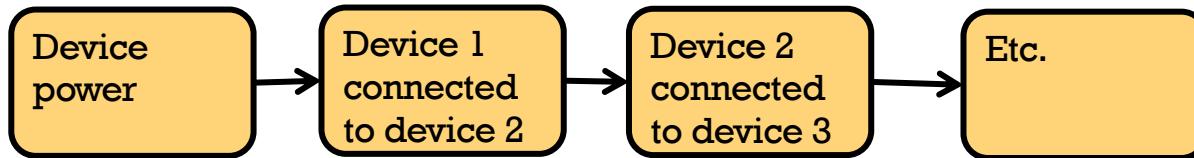- Q8: What value is this resistor?



Debugging Electronics

- Hardware and Software piece - need to check both
- Break your system apart into pieces
 - viewed as linked via inputs and outputs
 - Ideally a chain of parts with 1 output from one part going to 1 input in the next part.



- Check known voltage at each part starting with power and ground.

Debugging Code

- If you feel you need help with C or programming in general.
<https://www.onlinegdb.com/>
- Has an online debugger that lets you track the flow of code.
- Note: ATmega specific things won't work (PORTD, Timers etc.)
- Looking into setting it up so we can actually debug ATmega code (e.g. put includes and fake stubs so things can compile).

Answer in CHAT

Answer how you feel about each topic below with:

1. I don't understand this topic at all
2. I don't know now, but know what to do to get by
3. I understand some, but expect to get the rest later
4. I understand completely already

A. OpAmps

B. Comparators

C. Rotary encoders